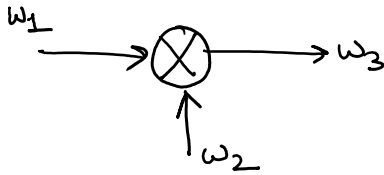


ECE 513-Lecture 23

Tuesday, November 6, 2018 9:27 AM

Mixer :

Look at the HW4
Solutions for
Midterm Exam




* A mixer is 3port circuit that employs nonlinear or time varying 'device' in order to perform frequency translation in RF systems.

↳ if the time varying element is an R or g (switch)
↳ resistive or passive


↳ time varying transconductance (g_m) → Active Mixer
↳ transistors


* Image reject mixers → require 90° phase shifters and in-phase power combiners or splitters.

UpConversion Mixer

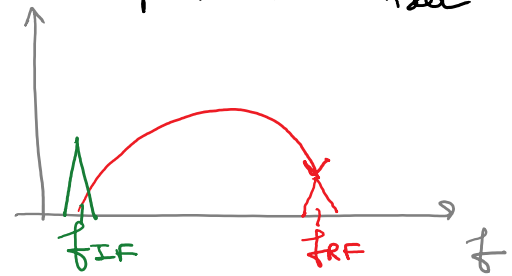

DownConversion Mixer

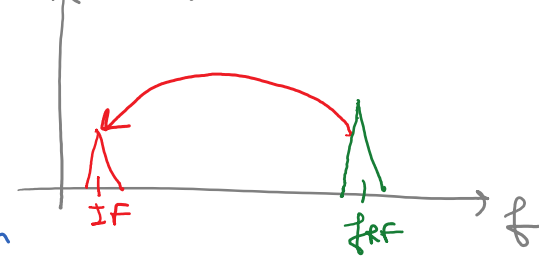

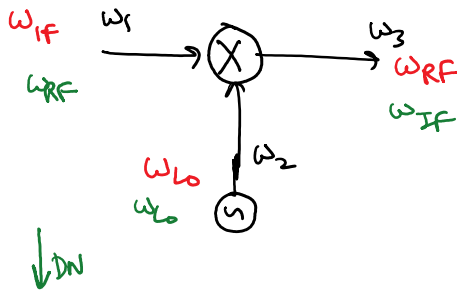

Ideal mixer behavior:

$$A \cos(\omega_1 t) \cdot B \cos(\omega_2 t) = \frac{AB}{2} [\cos(\omega_1 - \omega_2)t + \cos(\omega_1 + \omega_2)t]$$

Filtered out

→ only half of the output signal is retained, and the other half is filtered out.

→ half of the output power is lost (3dB loss)



* In practice, the mixer (or multiplier) is implemented with a non-linear element such as a diode or transistor or with switches.

→ a large number of harmonics as well as undesired products of the input signals (intermodulation)

→ To eliminate unwanted harmonics, filters are placed to select only the frequency of interest.


A side.

lossy component $\Rightarrow$ loss L dB

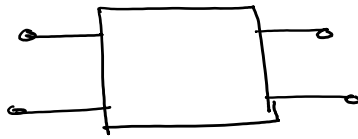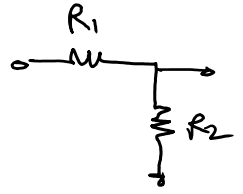


$$NF = L \Big|_{\text{dB}}$$

Razavi RF book

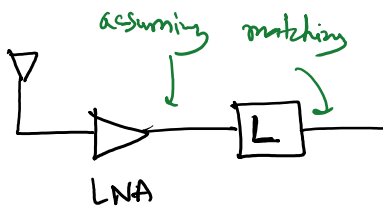

linear quantity, not dB

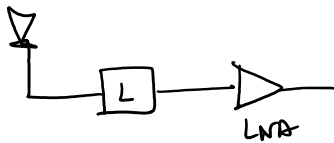
$$F = F_{\text{LNA}} + \frac{(L-1)}{G_{\text{LNA}}}$$



$$F = L + \frac{F_{\text{LNA}} - 1}{1/L}$$

Down conversion Mixer

Tuesday, November 6, 2018 9:51 AM

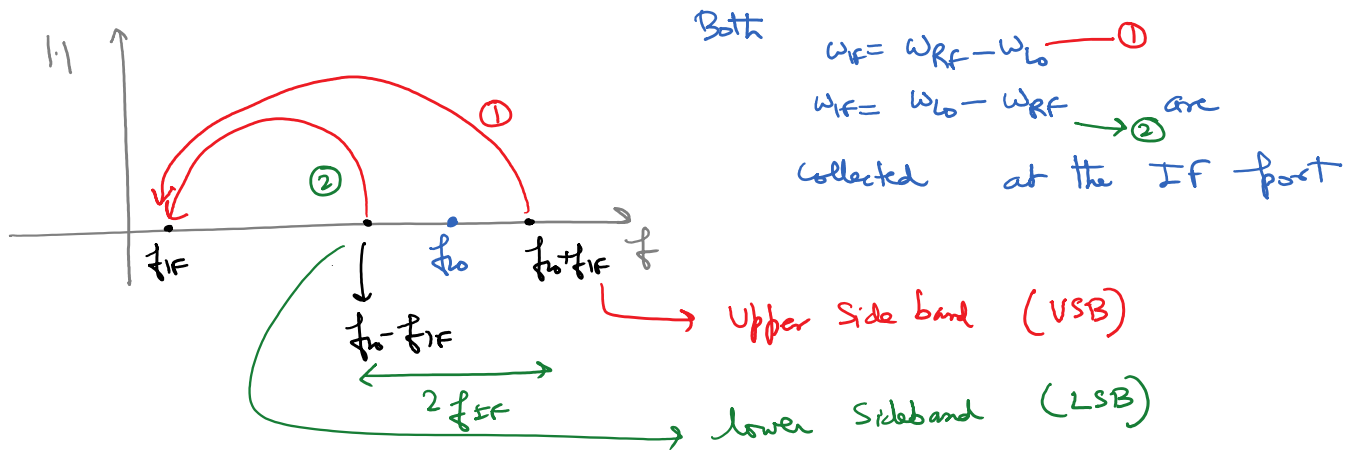

* One of them is RF and other is IM frequency.

↳ The choice of USB or LSB for RF frequency depends upon system design considerations



* Also, two LO frequencies are possible for a given RF and IF frequency combination



$$\omega_{IF} = \omega_{LO} - \omega_{RF}$$

$$\text{or } \omega_{IF} = \omega_{RF} - \omega_{LO}$$

↳ The best choice for LO frequency is determined by practical design constraints

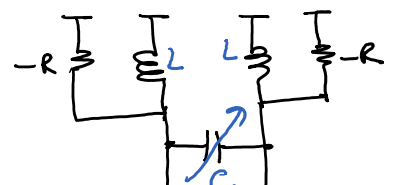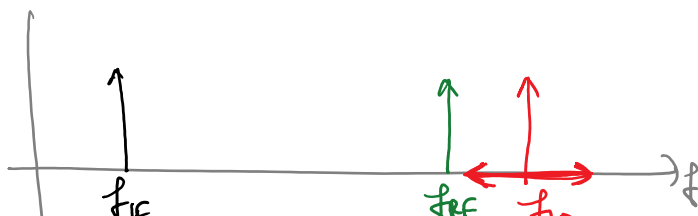↳ e.g. USB LO ($\omega_{LO} > \omega_{RF}$) is often preferred because it requires a VCO with a smaller tuning ratio for a given range of RF frequencies.



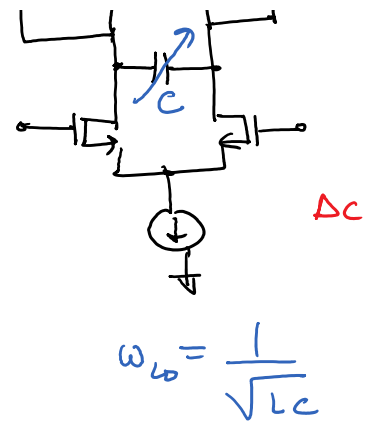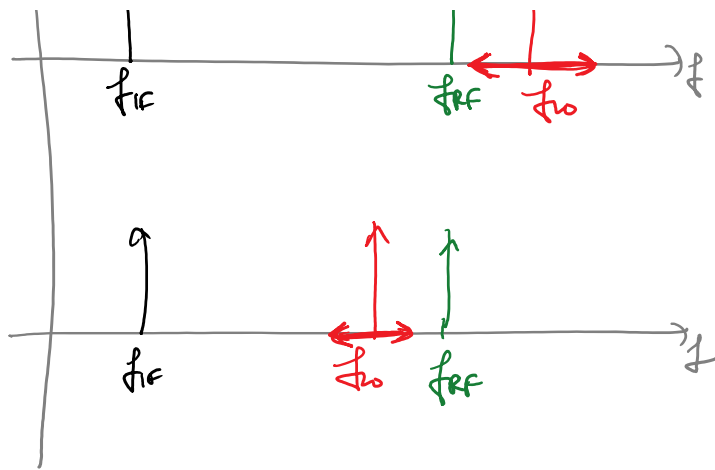

* In mmWave RX, higher L_O (frequency divider) are difficult to implement
 $\rightarrow$ LSP L_O .

Ex 9.1:

5.2 GHz WLAN

$f_{RF} = 5.2 \text{ GHz}$ and $f_{IF} = 1 \text{ GHz}$.


① Select $f_{LO} = f_{RF} - f_{IF} = 4.2 \text{ GHz}$

$\rightarrow f_{IM} = f_{LO} - f_{IF} = 3.2 \text{ GHz}$

② Select $f_{LO} = f_{RF} + f_{IF} = 6.2 \text{ GHz}$

$\rightarrow f_{IM} = f_{LO} + f_{IF} = 7.2 \text{ GHz}$



$\rightarrow$ Think!

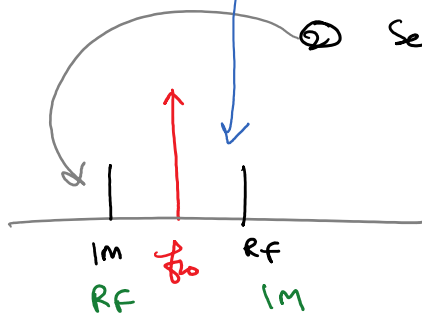



$f_{LO} = \frac{f_{RF} + f_{IM}}{2}$

Switch based Commutating Mixer

Tuesday, November 6, 2018 10:10 AM

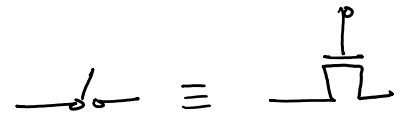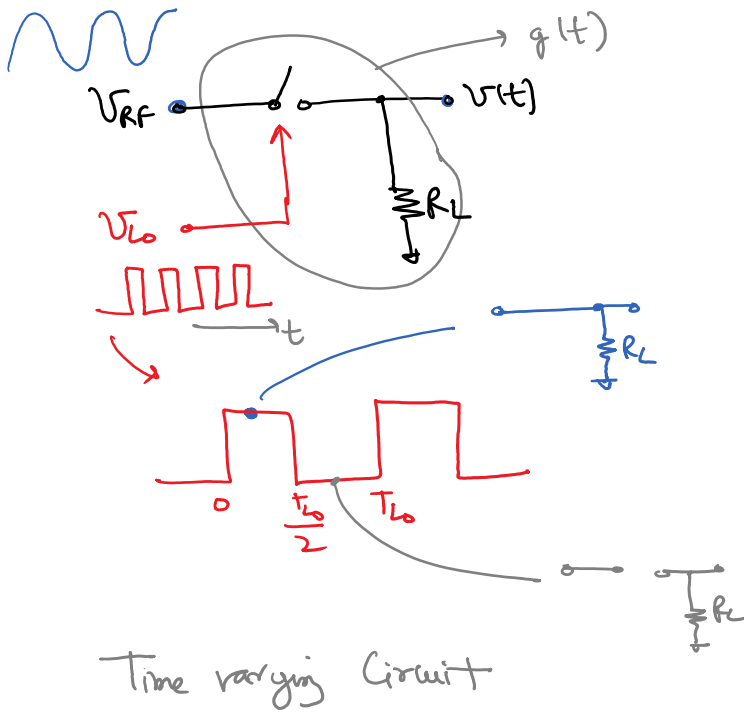

* Why use square waves for V_{LO} ?

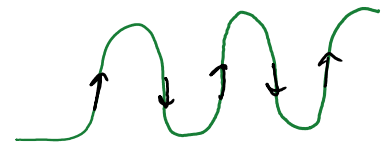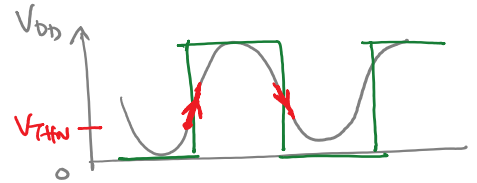

* rather have sharp edges at the transitions


* Assume ideal switch ($R_{on}=0 \leftarrow R_{off}=\infty$)

* The normalized ^{time-varying} conductance of the switch in series with R_L can be given by

$$g(t) = \begin{cases} 0 & \text{when switch is open} \\ 1/R_L & \text{when switch is closed} \end{cases}$$

$$= \frac{1}{R_L} \text{rect}\left(\frac{t}{T_{LO}}\right)$$


Expand as Fourier Series

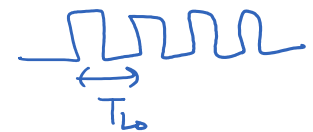

$$\Rightarrow g(t) = \underbrace{\frac{1}{2R_L}}_{a_0} + \sum_{n=1}^{\infty} \underbrace{\left(\frac{2}{n\pi R_L} \sin\left(\frac{n\pi}{2}\right) \right)}_{a_n} \cos(n\omega_{LO}t)$$

Fourier series of $\text{rect}(\cdot)$ wave terms

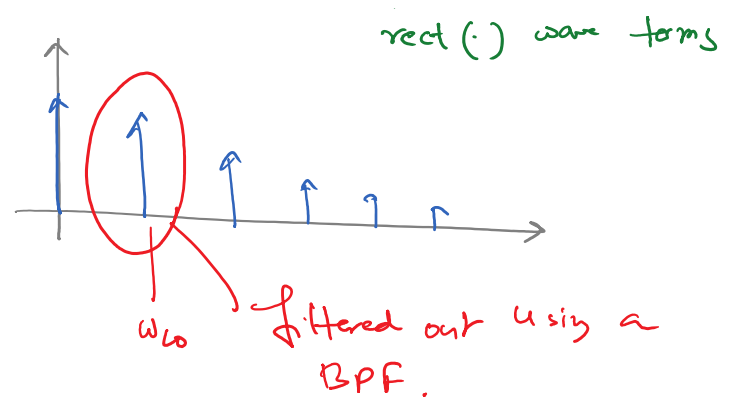↓
Average is due to
on/off switch with
50% duty cycle





$$V_{RF}(t) = V_{RF} \cos(\omega_{RF} t)$$

$$\begin{aligned} i(t) &= g(t) \cdot V_{RF}(t) = \frac{V_{RF}}{2R_L} \cos(\omega_{RF} t) + \frac{V_{RF}}{R_L} \sum_{n=1}^{\infty} \frac{2}{n\pi} \sin\left(\frac{n\pi}{2}\right) \cos(n\omega_{LO} t) \cos(\omega_{RF} t) \\ &= \frac{V_{RF}}{2R_L} \cos(\omega_{RF} t) + \frac{V_{RF}}{R_L} \sum_{n=1}^{\infty} \frac{1}{n\pi} \sin\left(\frac{n\pi}{2}\right) \left[\cos((n\omega_{LO} + \omega_{RF})t) + \cos((n\omega_{LO} - \omega_{RF})t) \right] \end{aligned}$$

* After Bandpass filtering, the IF component corresponding to $n=1$ ($\omega_{IF} = \omega_{LO} - \omega_{RF}$), we obtain

$$i_{IF}(t) = \frac{V_{RF}}{\pi R_L} \cos(\omega_{IF} t)$$

* Voltage Conversion Gain

$$A_v = \frac{V_{IF}}{V_{RF}} = \frac{I_{IF} \cdot R_L}{V_{RF}} = \frac{\frac{V_{RF}}{\pi} \cdot \frac{R_L}{R_L}}{V_{RF}} = \boxed{\frac{1}{\pi}}$$



* maximum possible conversion gain of a single-sided switch mixer = $\frac{1}{\pi}$

* In reality the non-zero switch resistance needs to be accounted for

$$A_v = \frac{1}{\pi} - \frac{R_L}{R_L + r_{sw}}$$

Mixer
Time varying device
Non-Linear Device

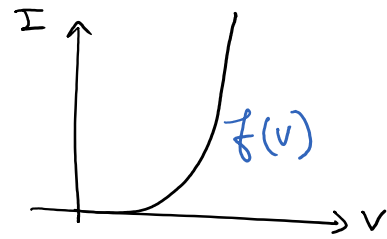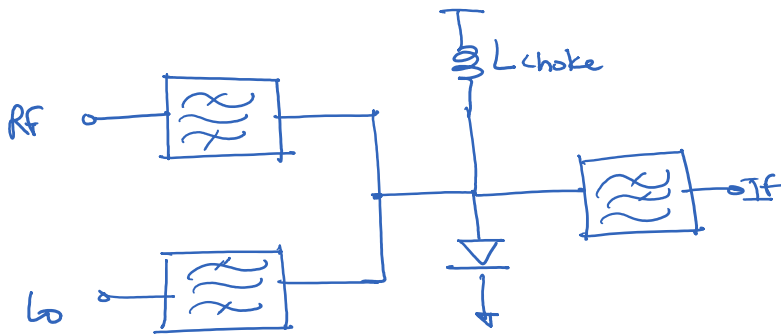- diodes
- BJTs, HBTs
- MOSFETs in their square law region




$$f(V_{RF} + V_{LO})$$

$$f(x) = f(x_0) + f'(x_0)(x-x_0) + \frac{f''(x_0)}{2!}(x-x_0)^2 + \dots$$

$$(V_{RF} + V_{LO})^2 = V_{RF}^2 + V_{LO}^2 + 2V_{RF}V_{LO}$$

FET multiplier

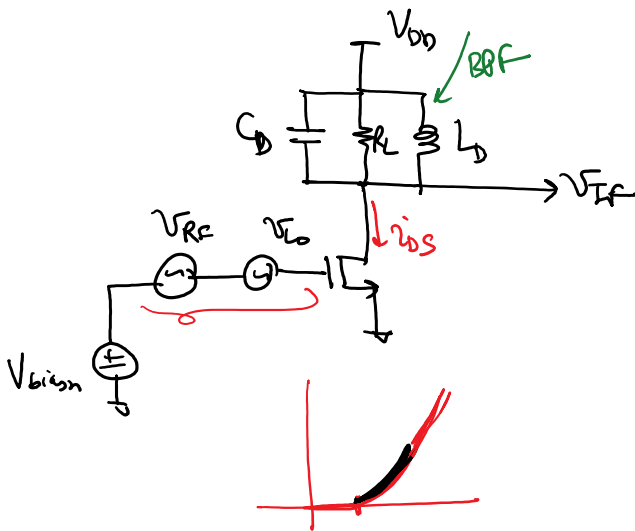

$$V_{IF} = \frac{\beta}{2} V_{LO} V_{RF}$$

in 11

$$k_B \epsilon_0 \frac{\omega}{L}$$

$$i_{DS}(t) = \frac{\beta}{2} [V_{LO} \cos(\omega_{LO} t) + V_{RF} \cos(\omega_{RF} t) - V_{THN}]^2$$

$$= \beta V_{LO} V_{RF} \cos(\omega_{LO} t) \cos(\omega_{RF} t) + \frac{\beta}{2} V_{LO}^2 \cos^2(\omega_{LO} t) + \frac{\beta}{2} V_{RF}^2 \cos^2(\omega_{RF} t) + \frac{\beta}{2} V_{THN}^2$$

$$- \beta V_{THN} V_{LO} \cos(\omega_{LO} t) - \beta V_{THN} V_{RF} \cos(\omega_{RF} t)$$

filter should allow $\omega_{LO} - \omega_{RF}$
and reject $\omega_{LO} + \omega_{RF}$
 ω_{LO}
 ω_{RF}

$$V_{IF} = \frac{K}{2} V_{LO} V_{RF}$$

WFF

→ Voltage
conversion gain

$$A_z = \frac{V_{IF}}{V_{RF}} = \frac{\beta}{2} R_L V_{LO}$$

→ depends upon V_{LO}
(Amplitude of the LO
Signal)

& second derivative of
MOSFET I-V
characteristics.