
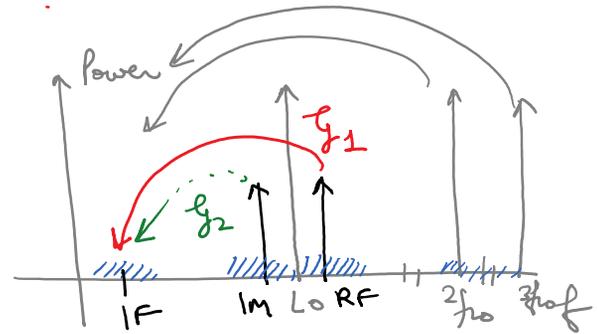


ECE 513- Lecture 24


Thursday, November 8, 2018 9:28 AM

Modeling Mixer as a Three-port Device:

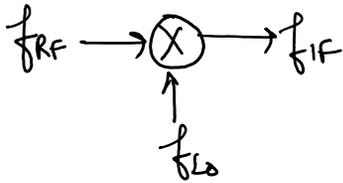

$$g_c = \frac{V_{IM}}{V_{RF}} = \begin{cases} \frac{\beta}{2} R_L V_{LO} & \text{for FET Mixer} \\ \frac{1}{\pi} & \text{for passive switch-based mixer} \end{cases}$$

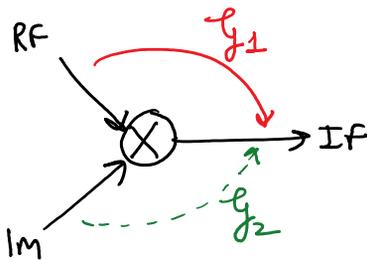a Simplistic model where we treat large LO signal as a "DC bias voltage"



↳ crude model that ignores other responses besides the RF and IM frequencies that are downconverted to the IF port

x The mixer can now be modeled by a three-port Y, S or Z matrix

S-matrix

$$\begin{bmatrix} b_{RF} \\ b_{IF} \\ b_{IM} \end{bmatrix} = \begin{bmatrix} s_{11} & s_{12} & s_{13} \\ s_{12} & s_{22} & s_{23} \\ s_{13} & s_{23} & s_{33} \end{bmatrix} \begin{bmatrix} a_{RF} \\ a_{IF} \\ a_{IM} \end{bmatrix}$$

If the mixer is matched at all ports (no reflection), then

$$\begin{bmatrix} 0 & s_{12} & s_{13} \end{bmatrix}$$

$$S = \begin{bmatrix} 0 & S_{12} & S_{13} \\ S_{12} & 0 & S_{23} \\ S_{13} & S_{23} & 0 \end{bmatrix}$$

* In an upconverter $\gamma_1 = |S_{12}|^2$ and $\gamma_2 = |S_{13}|^2$ are the power conversion gains from IF to RF and IF to IM

* Ideally, there should be no conversion from IM to RF
 $\Rightarrow S_{13} = 0$

Mixer Noise:

Thursday, November 8, 2018 9:45 AM

* Concern in downconverters, not upconverters


* Can be difficult to model mixer noise

because we have infinite number of responses from

$$(n f_0 \pm m f_{RF}) \text{ to } f_{IF}$$

↳ show up at IF as spurs and add to noise floor (if not filtered out)

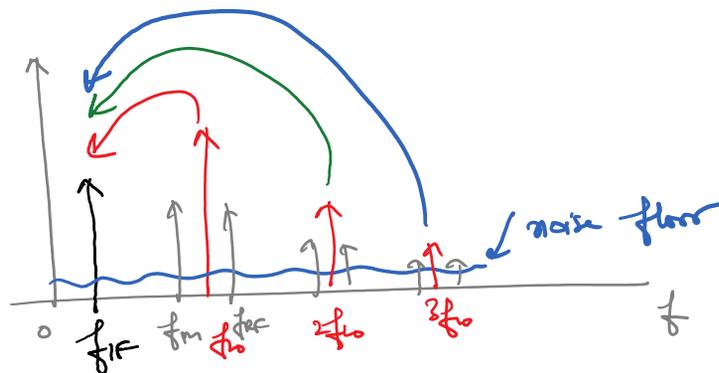* In narrowband^{Rx}, most of the noise sources are filtered out, but in broadband RX more than the two responses ($R\& + I\&$) can contribute to noise at IF.



* PSS
↳ harmonic balance (HB)

* In general, for broadband mixers, the output noise consists of noise generated within the mixer, as well as the noise of the terminations (Z_s or Z_L) at each response, downconverted to IF frequency.

(noise temperature $4kTR_s$)

$$T_{out} = T_m + \sum_{n=1}^{\infty} g_n \cdot T_s$$


termination noise temp ($Z_L = 50\Omega$)

conversion gain at the n-th response

output noise produced at the mixer only due to the internal noise sources in the mixer.


* We employ three-port mode
 ↳ assume that the L_o port doesn't contribute to noise at IF.

Mixer Single-side band (SSB) noise temp

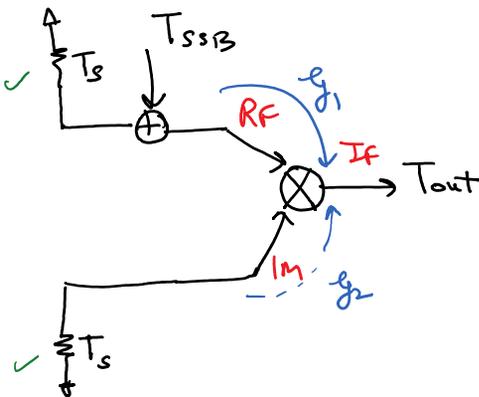

↳ All noise generated inside the mixer is referred to the RF part only.

Mixer Double-side band (DSB) noise temp

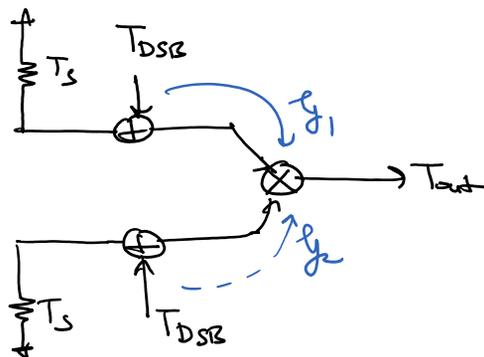

↳ mixer noise is referred to both RF and IM parts.

Output noise temp:

$$T_{out} = (T_s + T_{SSB})g_1 + T_s \cdot g_2$$

from here we derive


$$\underline{T_{SSB}} = \frac{T_{out} - T_s(g_1 + g_2)}{g_2} = \frac{T_{out}}{g_2} - T_s \left(1 + \frac{g_2}{g_1}\right) \rightarrow \textcircled{1}$$

Similarly,

$$T_{DSB} = \frac{T_{out}}{g_1 + g_2} - T_s \rightarrow \textcircled{2}$$

↳ more useful for automotive RADARs where information in both RF and IM band is processed.

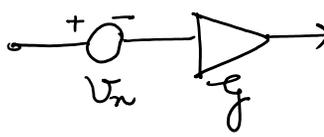* Circuit Noise is always referred to the input to take gain out of the comparison



$$\overline{V_{out}^2} = g \cdot \overline{V_n^2}$$

$$= |A_v|^2 \overline{V_n^2}$$

reput $\overline{V_n^2} = \frac{\overline{V_{out}^2}}{|A_v|^2}$

Noise Figure :

Thursday, November 8, 2018 10:10 AM

Total ^{available} noise at the mixer output

$$N_o = kTof (g_1 + g_2) + N_a$$

* Assuming that the signals at RF and IM frequencies have the same amplitude, V_{RF} ,

$$V_{iDSB} = V_{RF} \cos(\underbrace{\omega_{LO} - \omega_{RF}}_{IM} t) + V_{RF} \cos(\underbrace{\omega_{LO} + \omega_{RF}}_{RF} t)$$

* After downconversion of both RF and IM bands to IF, the output power at IF port is

$$S_{oIF} = (G_1 + G_2) \frac{V_{RF}^2}{2}$$

Using the SNR ratio definition of noise factor

$$F_{DSB} = \frac{SNR_{iDSB}}{SNR_o} = \frac{V_{RF}^2 [(G_1 + G_2) kTof + N_a]}{(G_1 + G_2) V_{RF}^2 kTof} = 1 + \frac{N_a}{kTof (G_1 + G_2)}$$

$$F_{SSB} = \frac{SNR_{iSSB}}{SNR_o} = \frac{V_{RF}^2 [(G_1 + G_2) kTof + N_a]}{G_1 \cdot V_{RF}^2 \cdot kTof} = \left(1 + \frac{G_1}{G_2}\right) \left[1 + \frac{N_a}{kTof (G_1 + G_2)}\right]$$

* If the mixer doesn't have an image rejection filter or an image reject topology, and if $G_1 = G_2 = 0$, then

$$NF_{SSB} = NF_{DSB} + 3dB$$

↳ In an image reject mixer, $G_2 = 0 \Rightarrow NF_{SSB} = NF_{DSB}$

* If the mixer is ideal and contributes $N_a = 0$
 then $F_{SSB} = 2 \Rightarrow \underline{\underline{3dB}}$ and equals mixer's conversion loss.

\Rightarrow NF of a lossy circuit is equal to its loss in dB.




loss = 3dB


Conversion gain:

Thursday, November 8, 2018 10:27 AM

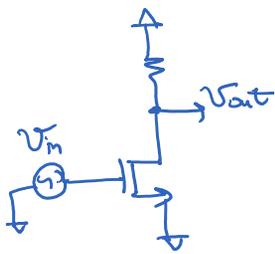* Small signal power gain from RF port to IF port (DN)
IF → RF (UP)



$$A_v = -g_m R_D$$

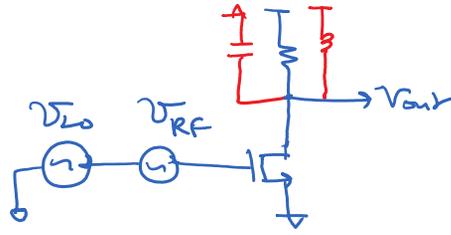

$$\omega_{IF} = \omega_{LO} - \omega_{RF}$$

~~$\omega_{LO} + \omega_{RF}$~~ filtered out

$$|G| = \frac{V_{out}}{V_{RF}} \leq \frac{1}{2} g_m R_D$$


* Conversion gain of a mixer will always be smaller than the gain of the corresponding amplifier realized with the same transistor topology

(Passive)
* Resistive mixers → diodes, switches → these exhibit conversion loss

* Active mixers → transistors → Gilbert's Mixer
↳ conversion gain

* Linearity:

* Isolation:

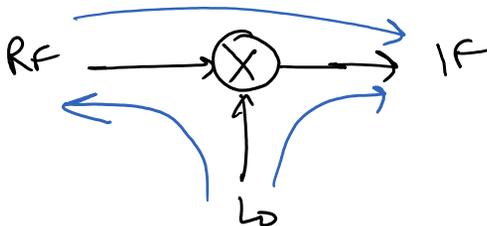


Isolation between ports → measured in dB

$$* L_0 \rightarrow IF \rightarrow IS_{L_0 \rightarrow RF}$$


$$* L_0 \rightarrow RF \rightarrow IS_{L_0 \rightarrow RF}$$

$$* IF \rightarrow L_0 \rightarrow IS_{F \rightarrow L_0}$$

Single-balanced


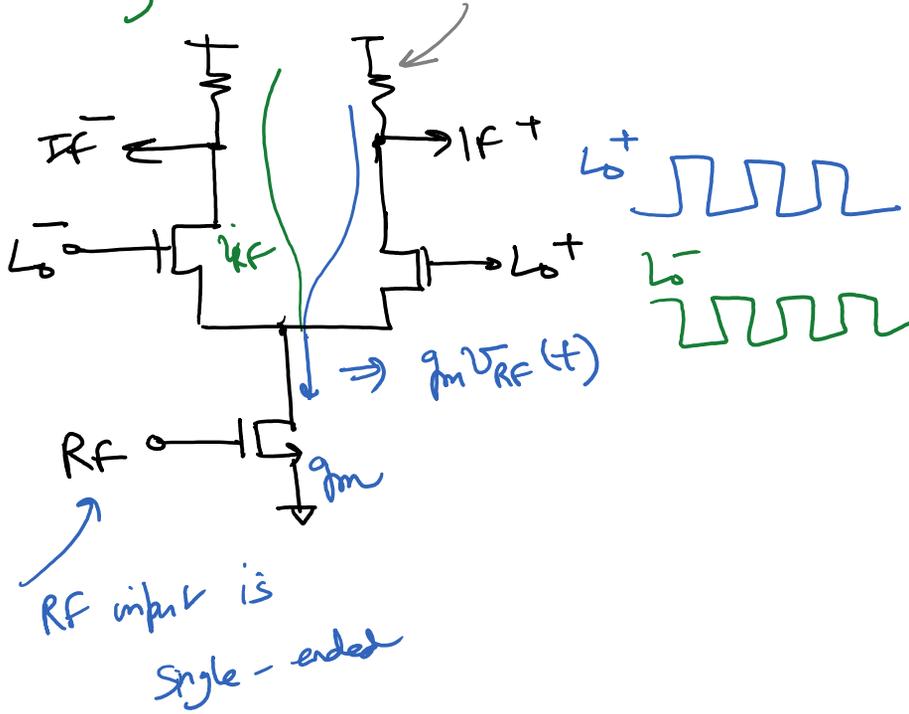


Double-balanced

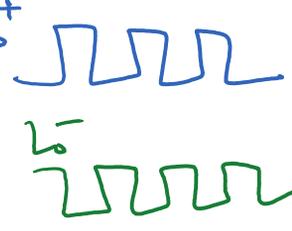

Double-Balanced Gilbert Cell Mixer Topology (Active Mixer)

Thursday, November 8, 2018 10:37 AM

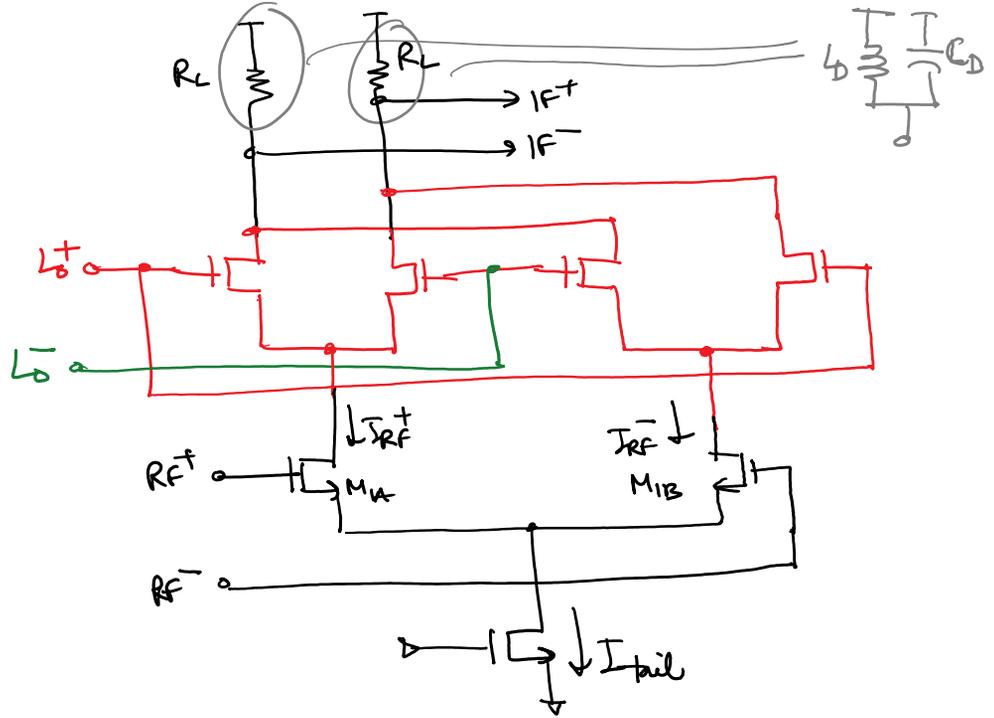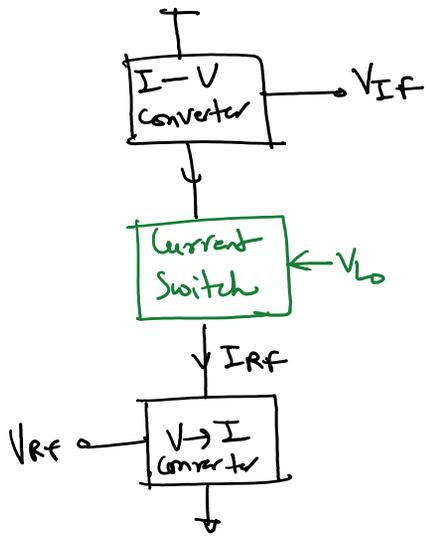

$$g_c = \frac{2}{\pi} g_{m1} R_L$$

passive mixer $\frac{g_c}{1/\pi}$
 Double-balanced " " $\frac{2}{\pi}$

$$\frac{2}{\pi} \times g_{m1} R_L$$