

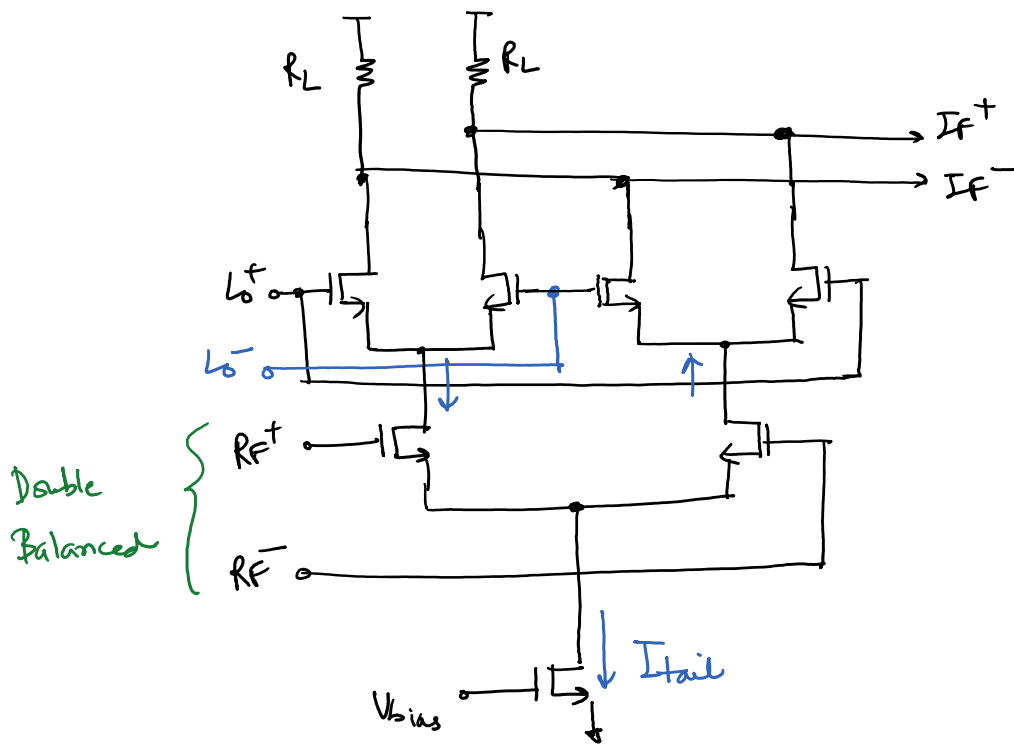


ECE 513- Lecture 25

Thursday, November 15, 2018 9:30 AM

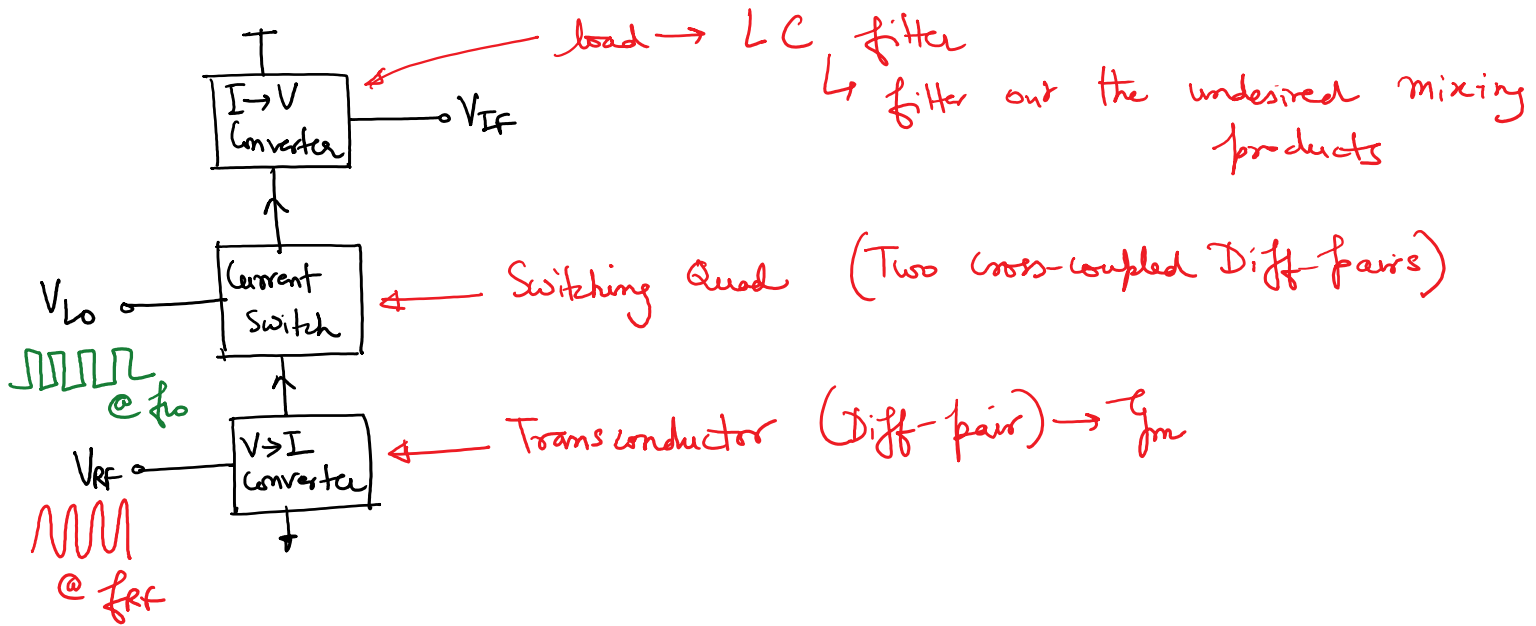Double-balanced Gilbert Cell Mixer Topology



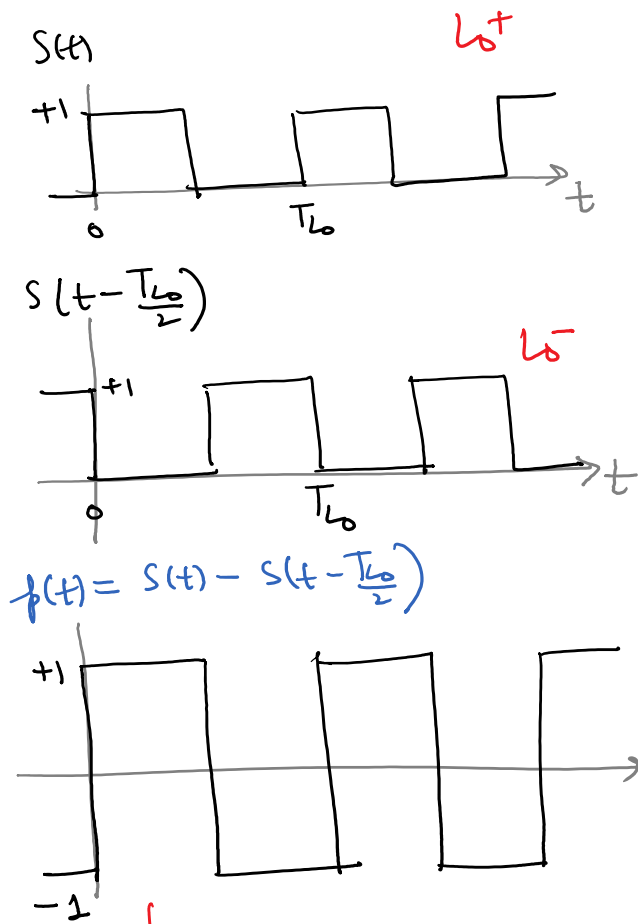

Fourier expansion


↳ fundamental amplitude = $\frac{4}{\pi}$

$$V_{out}(t) = I_{RF}(t) \cdot R_L \cdot \frac{4}{\pi} \cos(\omega_{Lo}t) + \dots \text{higher harmonic terms}$$

↳ $g_m V_{RF} \cos(\omega_{RF}t)$

After multiplication & filtering of the $\omega_{Lo} + \omega_{RF}$ term
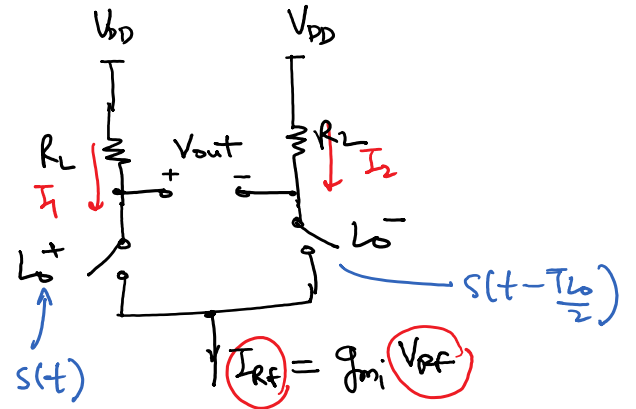
$$\Rightarrow V_{IF}(t) = \frac{2}{\pi} g_m R_L \cdot V_{RF} \cos((\omega_{RF} - \omega_{Lo})t)$$



$$I_1 = I_{RF} \cdot S(t)$$

$$I_2 = I_{RF} \cdot S(t - \frac{T_{Lo}}{2})$$




$$\begin{aligned} V_{out} &= (V_{DD} - I_1 R_L) - (V_{DD} - I_2 R_L) \\ &= I_{RF} \cdot R_L \cdot [S(t - \frac{T_{Lo}}{2}) - S(t)] \end{aligned}$$

$$\Rightarrow V_{out}(t) = I_{RF} \cdot R_L \cdot f(t)$$

↳ L_o waveform
waveform that toggles between $+1$ and -1

voltage Conversion gain

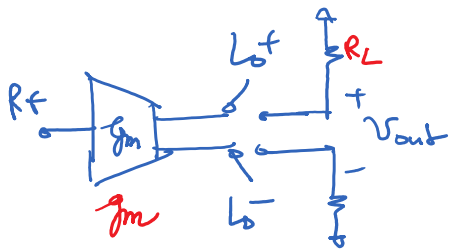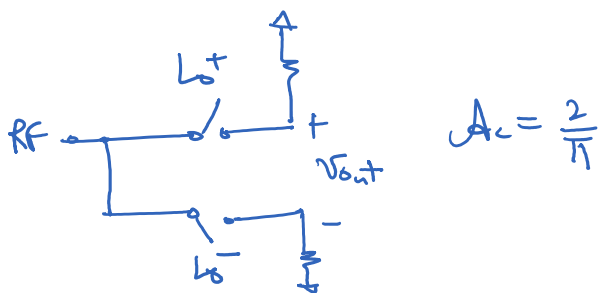
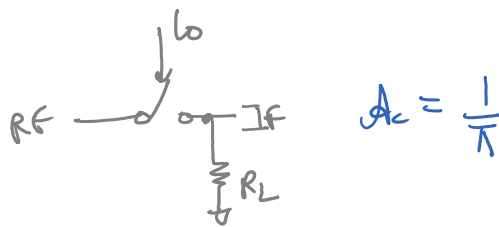
$$A_c = \frac{V_{IFPK}}{V_{RFpk}} = \frac{2}{\pi} g_{m1} R_L$$





Gilbert Mixer

for increasing mixer linearity.

Source degeneration

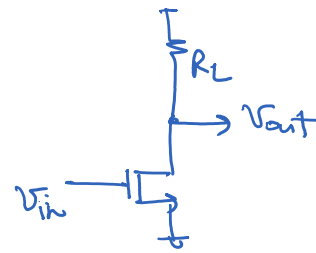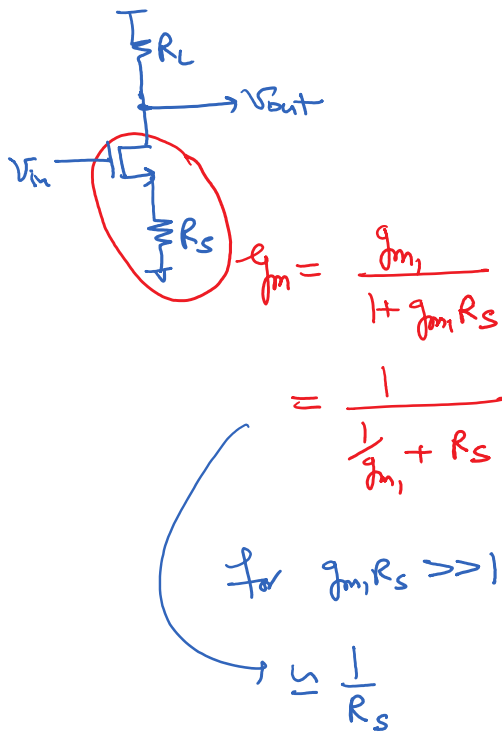



$$A_v = g_{m1}R_L$$

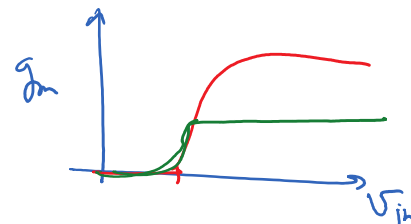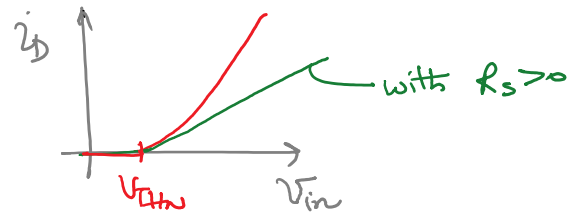


* Effective g_m drops but its a 'more linear' response

* Use Source degeneration in the mixer to trade conversion gain with linearity.

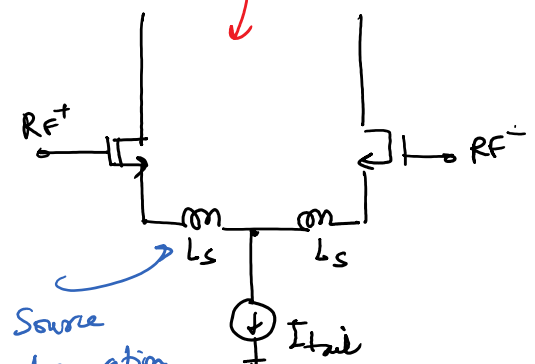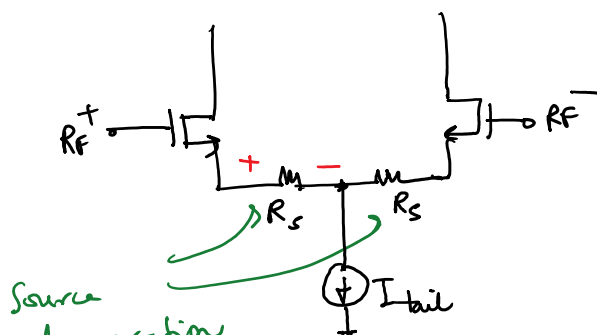Goal for voltage headroom
frequency dependent



Source degeneration

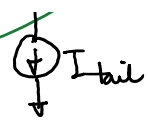

Source degeneration inductors for linearity.





Can be part of the input match similar to the LNA.



g_m will be $\frac{g_{m1}}{1 + j\omega_{RF} L_S g_{m1}}$

* Similar to the matched LNA power gain, we can derive the power gain of the mixer that is matched at the RF port to Z_{in} & at the IF port to R_L
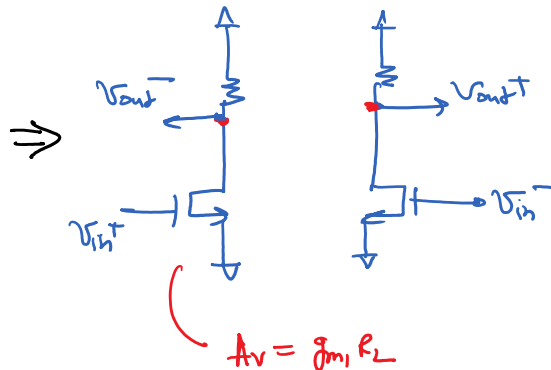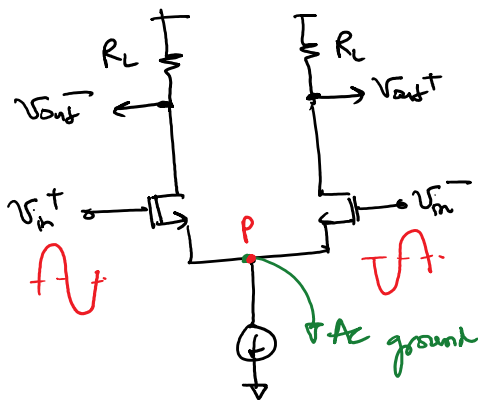
$$G_{pmax} = \frac{1}{2\pi} \frac{f_{TGH}^2}{f_{RF}^2} \cdot \frac{R_L}{Z_{in}}$$



Differential Half Circuits

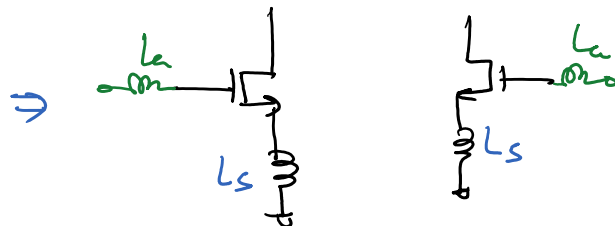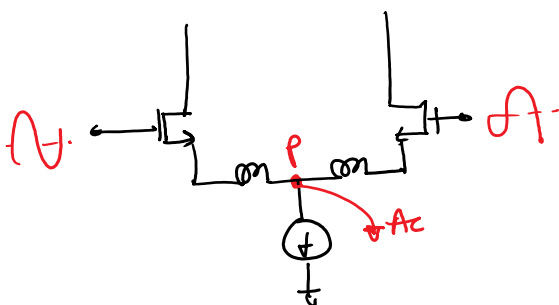

linearity.

* Read Example 9.8 from the Book




* Downconversion Mixer at 5GHz RF frequency, $f_{IF} = 1\text{GHz}$.

$$f_o = 4\text{GHz} \Rightarrow f_{IM} = 3\text{GHz}$$

1) Low-noise transconductors, linear


2) mixing quad

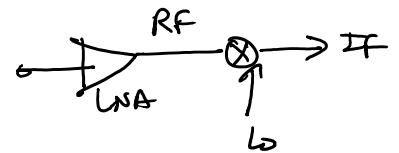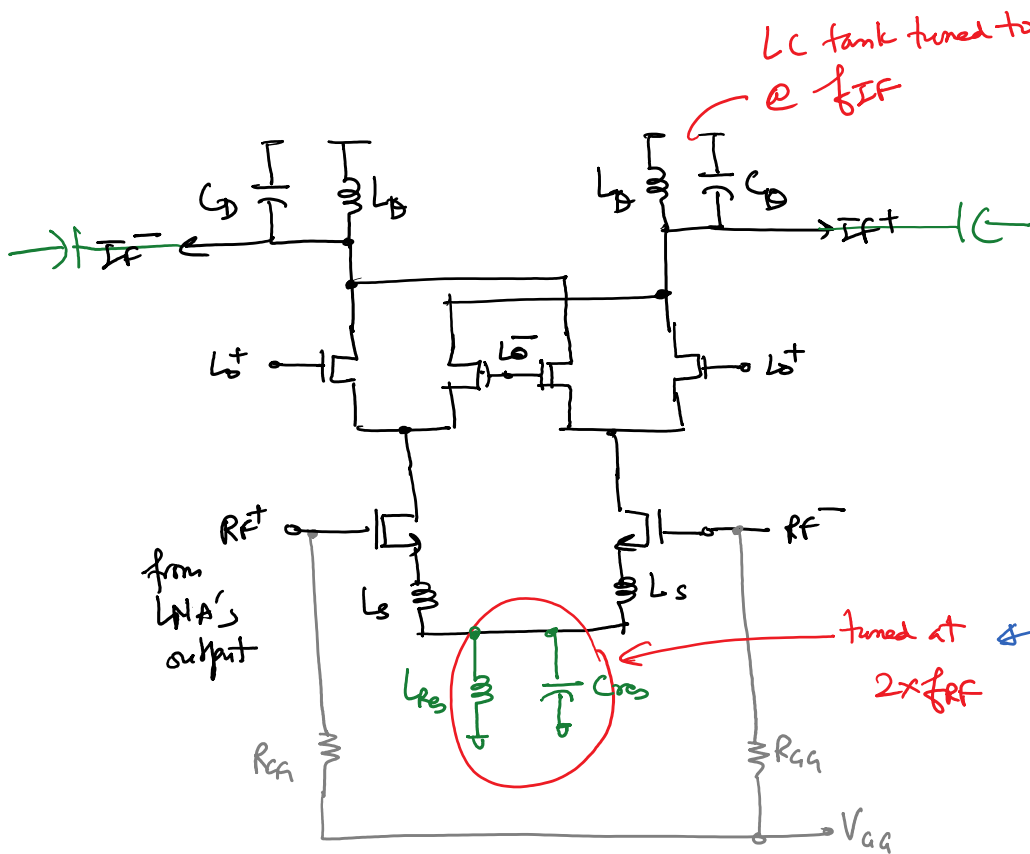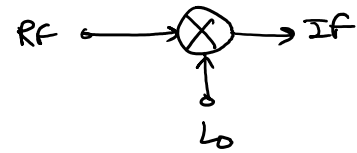3) an L_o or RF trap (a bandreject filter centered at RF frequency) at the IF input




better common-mode rejection at even order harmonics of f_{RF}

Differential half circuit

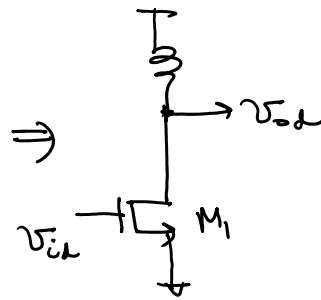

Common-Mode Half Circuit

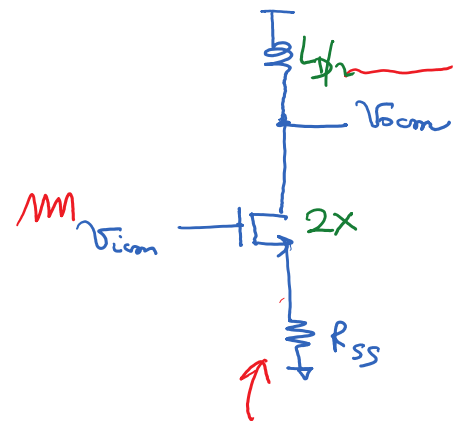


for $R_{SS} \rightarrow \infty$

$\Rightarrow$ common-mode gain $\rightarrow 0$

$\Rightarrow$ common-mode rejection


At high frequencies

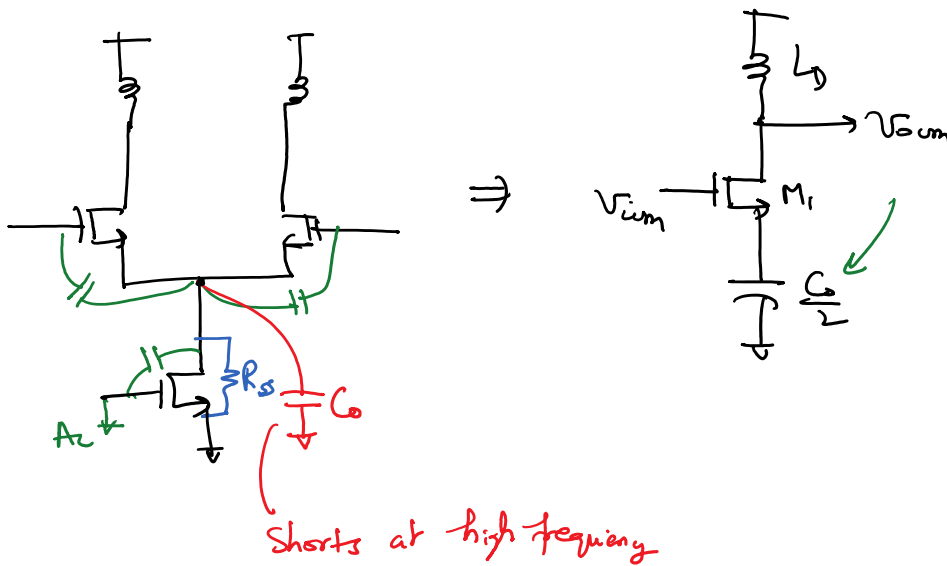

output impedance of the current source

$$Z_{ocs} = \frac{r_o}{1 + s r_o C} = \frac{r_o}{1 + s/\omega_z}$$

$$\omega_z = \frac{1}{r_o C}$$

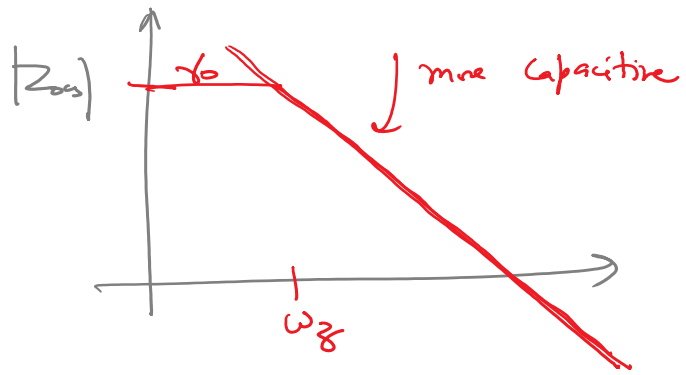

* In 65nm CMOS

$$f_z = 17.7 \text{ GHz}$$

* Degrades CM rejection at high frequencies

↳ even-order harmonics of RF (as well as ω_0) will show up at the mixer output.

* Solutions to improve CM-rejection

