

ECE 513 - Lecture 29.



Tuesday, December 4, 2018 1:56 PM

Class-B

→ conduction angle $\theta = \pi$

* transistor conducts only half the period of fundamental frequency

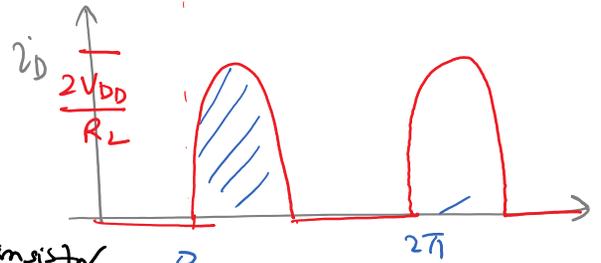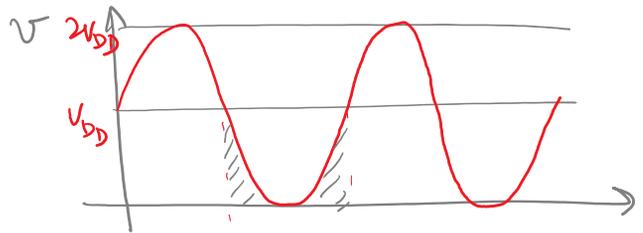↳ Bias V_{DS} such that the transistor is at the edge of cutoff sat. $\theta = \pi$



⇒ The peak current in the load is still the same as class-A ⇒ $\frac{2V_{DD}}{R}$

↳ power consumption is reduced compared to class-A PA.

* g_m & the power gain is reduced to half w.r.t class-A
↳ -6 dB

* The PA becomes non-linear

* A higher voltage swing is required for the same output power as class-A.


Average or DC current

$$\theta = \omega t$$

$$I_{DC} = -\frac{I_{max}}{2\pi} \int_{\pi}^{2\pi} \sin \theta d\theta = \frac{I_{max}}{\pi} = \frac{2V_{DD}}{\pi R_L}$$

$$\eta_{\text{drain}} = \frac{P_L}{P_c} = \frac{V_s \cdot I}{2 I_{Bz} V_{DD}} = \frac{V_{DD} \cdot \frac{I_{\text{max}}}{2}}{\frac{2 V_{DD}}{\pi} I_{\text{max}}} = \frac{\pi}{4} = 78.5\%$$

Push pull class-B PA :

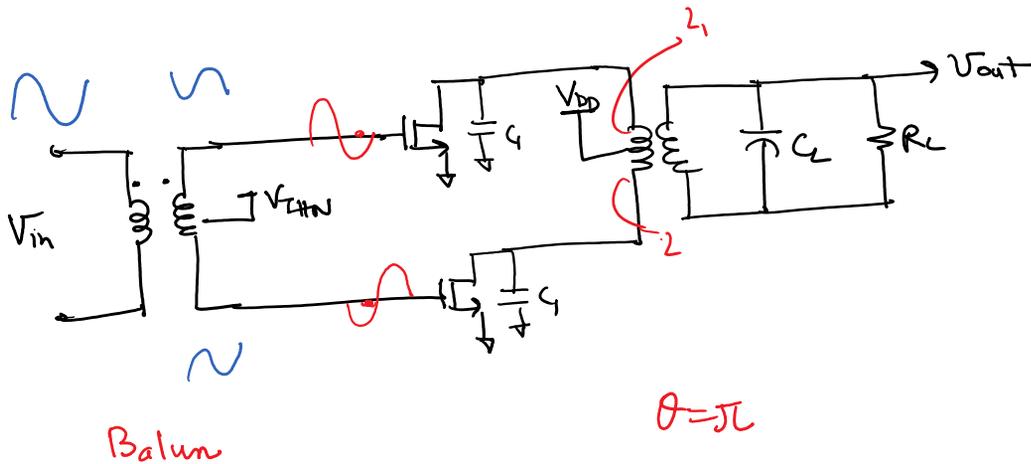

Class-C $\rightarrow \theta < \pi$

* A significant contributor to the nonlinearity of Class B stage is the C_{gs} , which varies significantly when the transistor is driven into the cutoff region.

↳ This leads to deviation from the 50% duty cycle
 ↳ degrades the overall efficiency

↳ one technique to reduce this nonlinearity is to place a short circuit at 2nd harmonic.

Class-AB :

* workhorse of the linear PA industry

↳ compromise between the efficiency of class-B and linearity of class-A operation.

$\theta > \pi$

↳ θ depends upon the biasing condition

↳ experimentally determined as a sweet spot at which the gm of a FET is $\frac{1}{2}$ of the peak-gm of the transistor.


$$i_D(t) = \begin{cases} I_{DC} + I_p \sin(\omega t), & \omega t < \frac{3\pi}{2} - \frac{\theta_{off}}{2} \\ 0, & \frac{3\pi}{2} - \frac{\theta_{off}}{2} \leq \omega t \leq \frac{3\pi}{2} + \frac{\theta_{off}}{2} \\ I_{DC} + I_p \sin(\omega t), & \omega t \geq \frac{3\pi}{2} + \frac{\theta_{off}}{2} \end{cases}$$

$\theta = \omega t$
 $\theta_{off} = 2\pi - \theta$

$$\eta_{drain} = \frac{\frac{1}{2} \frac{1 - \frac{1}{2\pi} (\theta_{off} - \sin(\theta_{off}))}{\cos(\frac{\theta_{off}}{2}) + \frac{1}{\pi} \left[\sin(\frac{\theta_{off}}{2}) - \frac{\theta_{off}}{2} \cos(\frac{\theta_{off}}{2}) \right]}{\left(\frac{V_{DS} - V_{in}}{V_{DD}} \right)}$$


Class AB is mostly used in push-pull configuration

→ T n




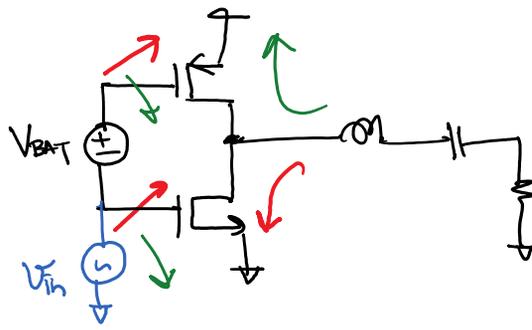


Switching PAs :

Class-D PA

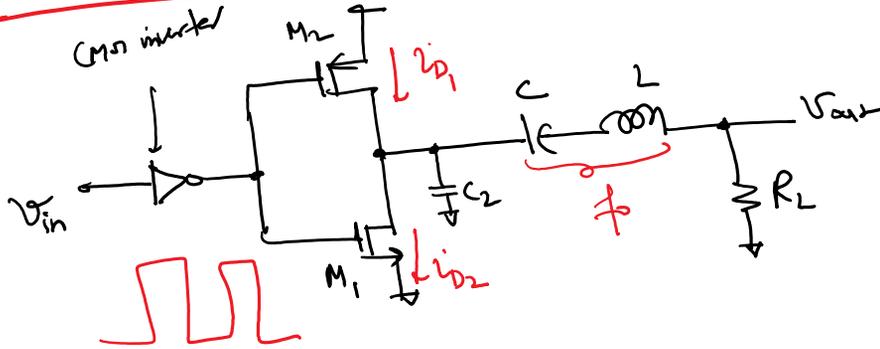

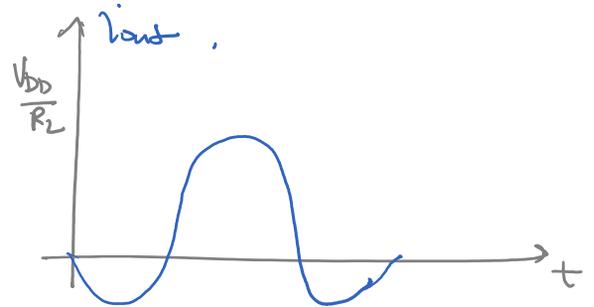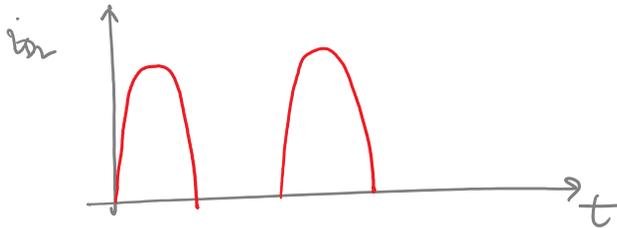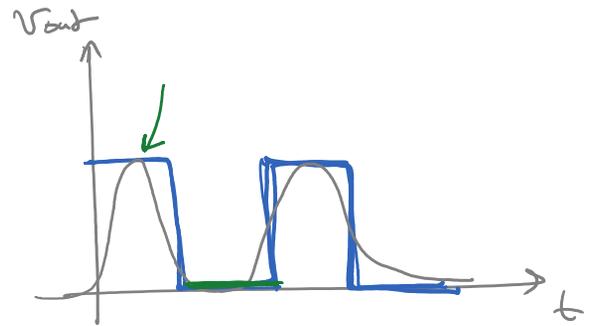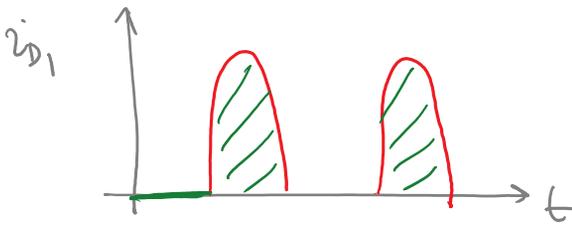Current is pulled from V_{DD} through M_2



max suitable for frequencies



$f_{RF} \ll f_T$ or f_{max}

29 THz

$f_T > 100\text{ GHz}$

60 GHz

Class-E :

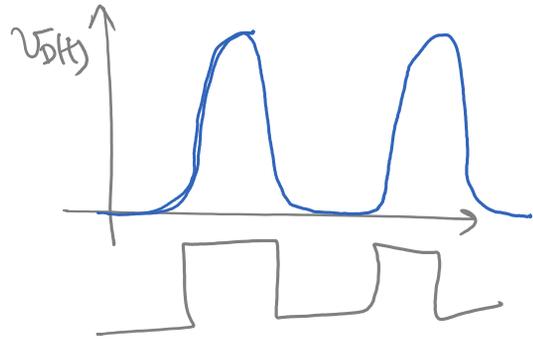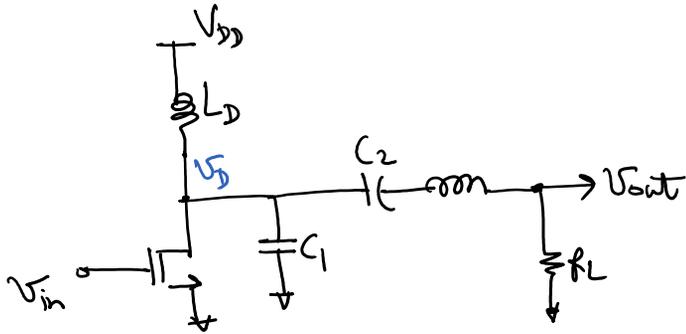


* Not only the drain switch voltage is $V_D=0$ when the current is flowing but also $\frac{dV_D(t)}{dt}=0$

↳ makes PA operation relatively insensitive to the rise time of the input signal

↳ the higher efficiency obtained is accompanied by a very strong nonlinearity

Class-F

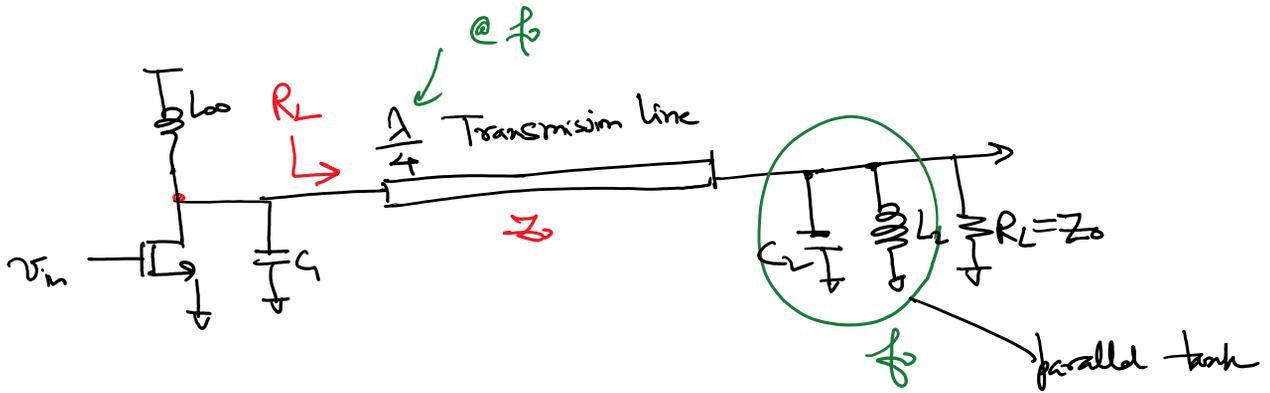

$$Z_L(f_0) = R_L$$


even harmonics $Z_L(2kf_0) = 0$

odd harmonics $Z_L((2k+1)f_0) = \infty$

* If the first three harmonics are terminated $\rightarrow 81\%$

If the first 5 harmonics are terminated $\rightarrow 95\%$ efficiency

Class F⁻¹

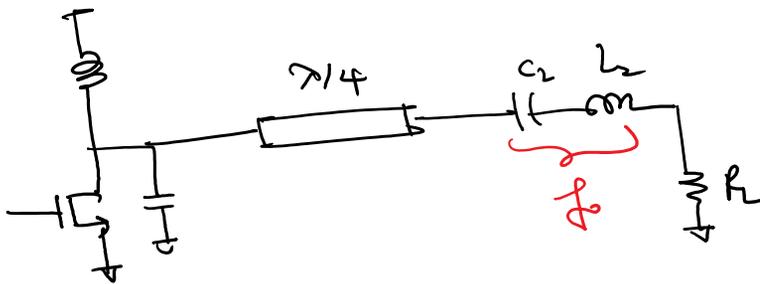

* Switch is biased at J_{FT}