
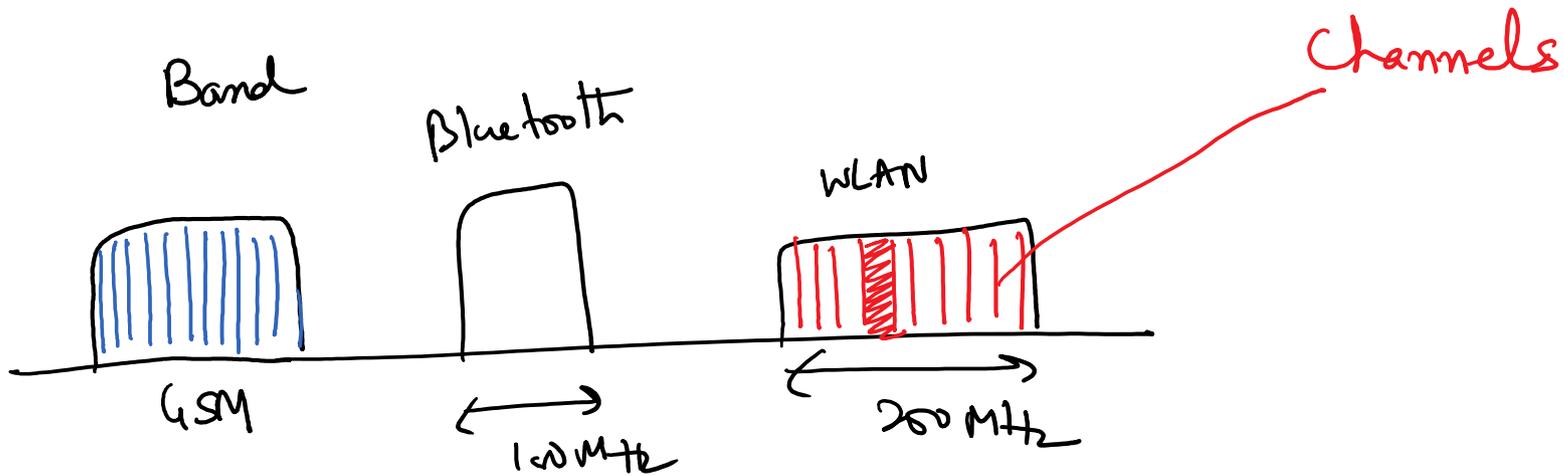




ECF 513 - Lecture 4

Thursday, August 30, 2018 9:30 AM

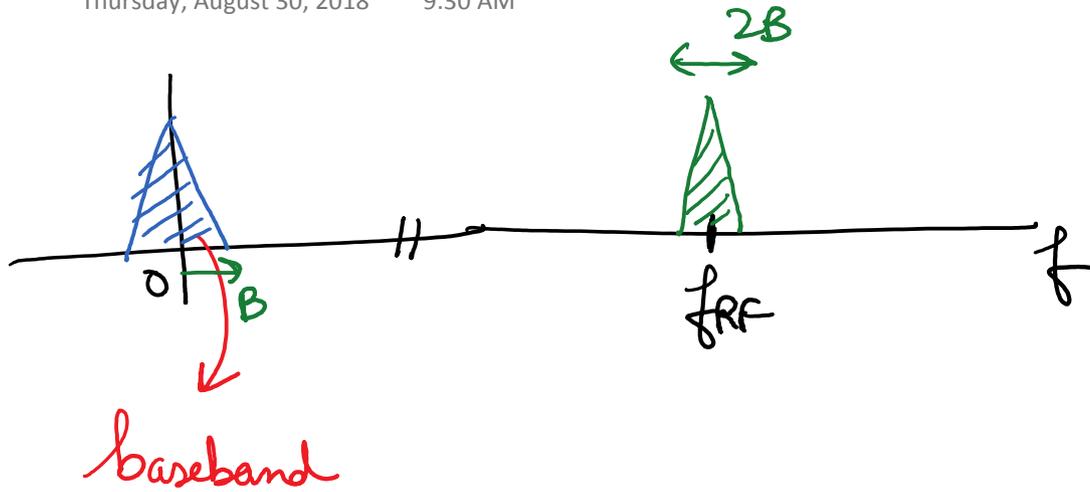

Receiver Architectures

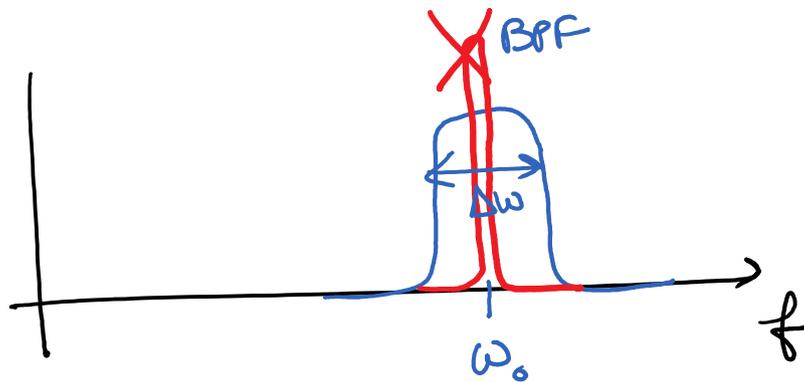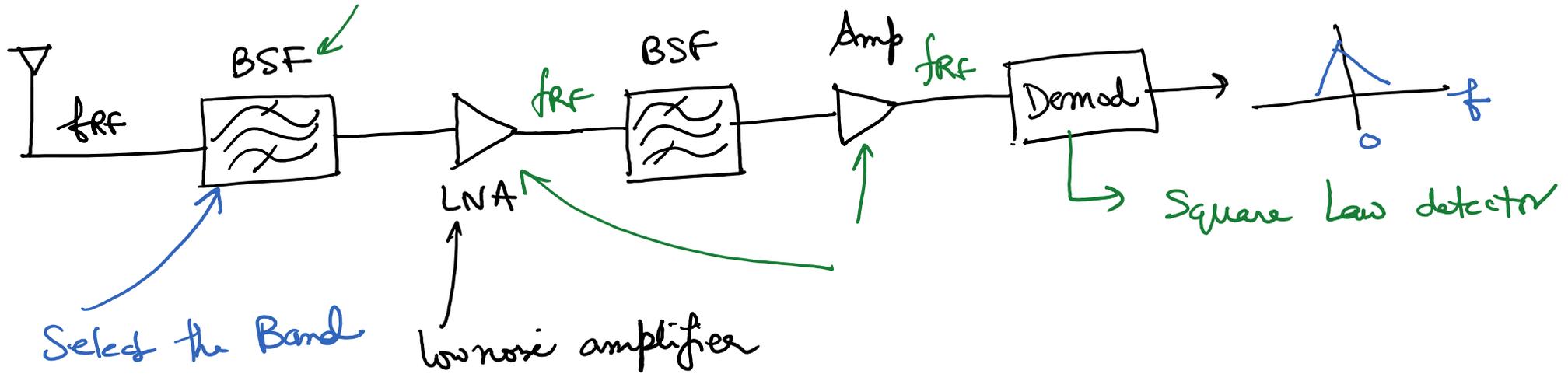① Tuned Homodyne or Direct Detection Receiver



$$Q = 2\pi \frac{\omega_0}{\Delta\omega}$$

Quality factor

$$Q < 25$$

Square Law Detector



$$S(t) = m(t) \cos \omega_c t$$

$$s(t) = S(t) = m(t) \cos \omega_c t$$

$$v(t) = m^2(t) \cos^2 \omega_c t = \frac{m^2(t)}{2} [1 + \cos(2\omega_c t)]$$

↓ LPF
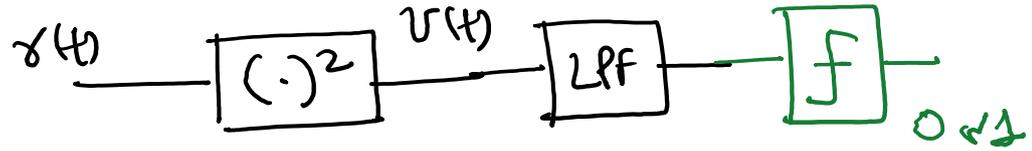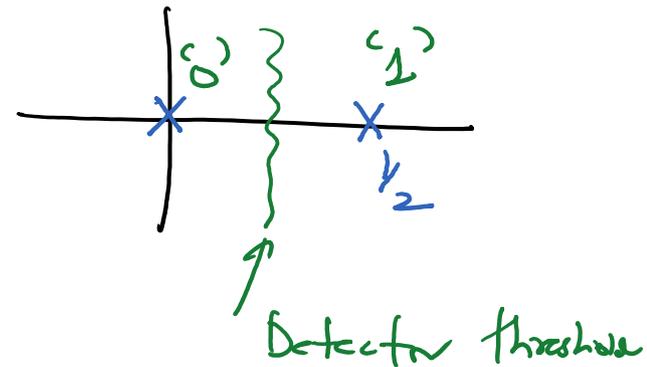
$$\frac{1}{2} m^2(t) \rightarrow \frac{1}{2} m(t)$$



high RF gain has

stability issues

* Need 50-60 dB gain at RF frequency

↳ the whole receive chain before detection should be linear


↳ channel selection is very difficult at high RF/carrier frequencies

↳ limited Q of BPF.
↳ selectivity issue.

Heterodyne Architecture

Thursday, August 30, 2018 9:54 AM

* year 1906

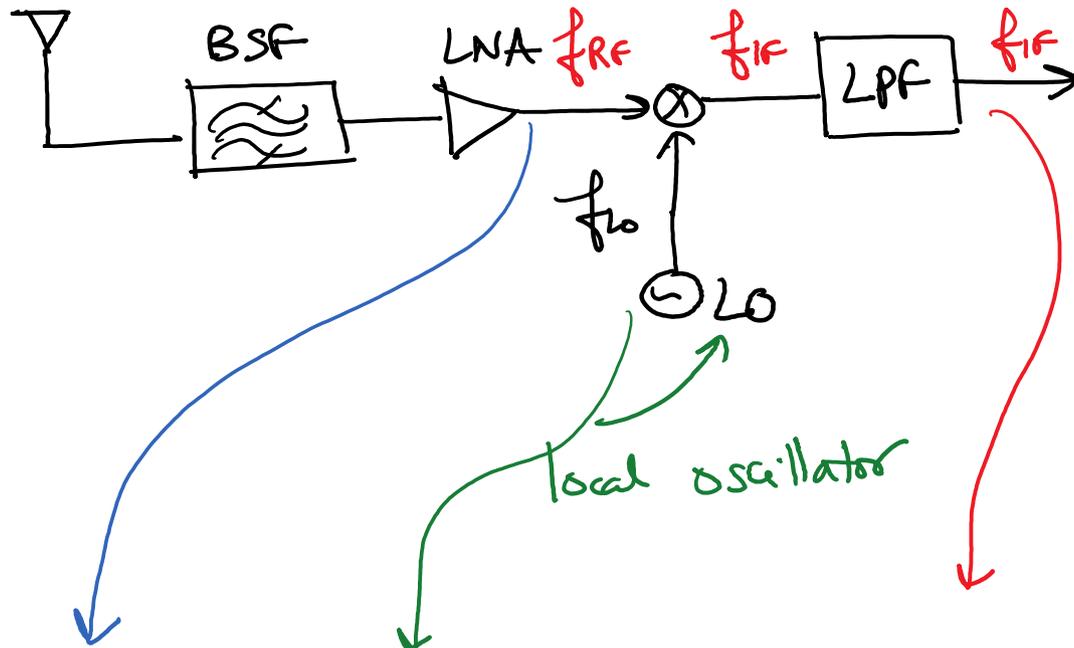

$$A \cos(\omega_{RF} t) \cdot \cos(\omega_{LO} t) = \frac{A}{2} \left[\cos((\omega_{RF} + \omega_{LO})t) + \cos((\omega_{RF} - \omega_{LO})t) \right]$$

$$\Rightarrow \frac{A}{2} \cos(\omega_{IF} t) = \frac{A}{2} \cos((\omega_{RF} - \omega_{LO})t) = \frac{A}{2} \cos((\omega_{LO} - \omega_{RF})t)$$

$$f_{IF} = f_{RF} - f_{LO} \quad \Rightarrow \quad f_{RF} = f_{IF} + f_{LO}$$

$$\left. \begin{aligned} f_{IF} &= f_{RF} - f_{LO} \\ f_{IF} &= f_{LO} - f_{RF} \end{aligned} \right\} \Rightarrow \begin{aligned} f_{RF1} &= f_{IF} + f_{LO} \\ f_{RF2} &= f_{LO} - f_{IF} \end{aligned}$$


Two possibilities for f_{RF}

Thursday, August 30, 2018 10:04 AM

$$f_{RF1} = f_{LO} + f_{IF}$$

$$f_{RF2} = f_{LO} - f_{IF}$$
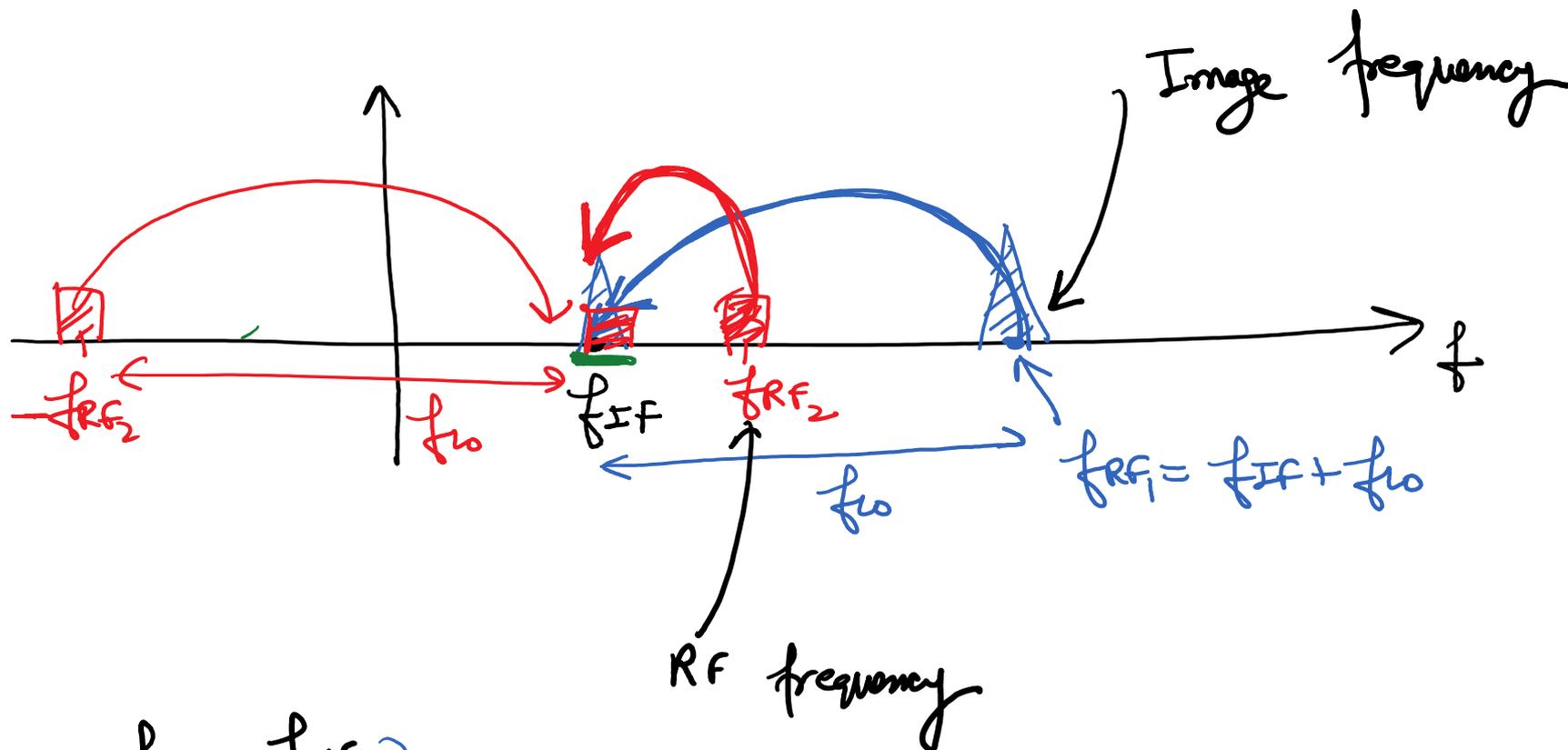
$$\cos(\omega_0 t) = \cos(2\pi f_{LO} t)$$



$$\left. \begin{aligned} f_{RF} &= f_{LO} - f_{IF} \\ f_{IM} &= f_{LO} + f_{IF} \end{aligned} \right\} \rightarrow$$

$$f_{IM} = 2f_{LO} - f_{RF}$$


$f_{LO} \quad f_{RF}$

$f_{LO} + f_{IM}$


$$f_{im} = f_{fo} + f_{if} \rightarrow$$

$$f_{im} = f_{fo} + \Delta f$$

$$f_{fo} = \frac{f_{RF} + f_{IM}}{2}$$

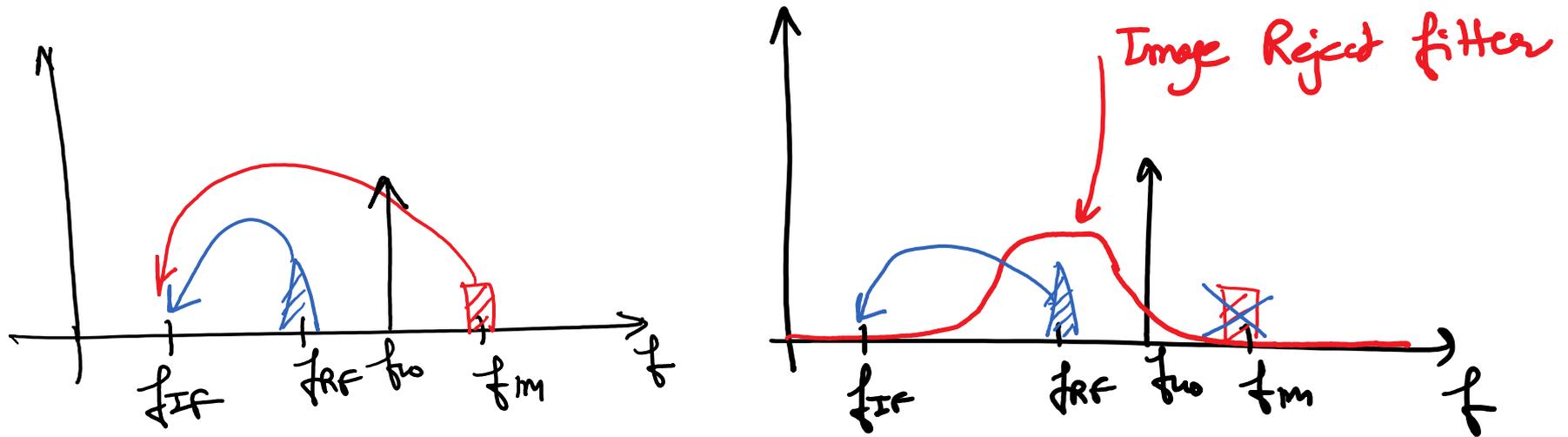

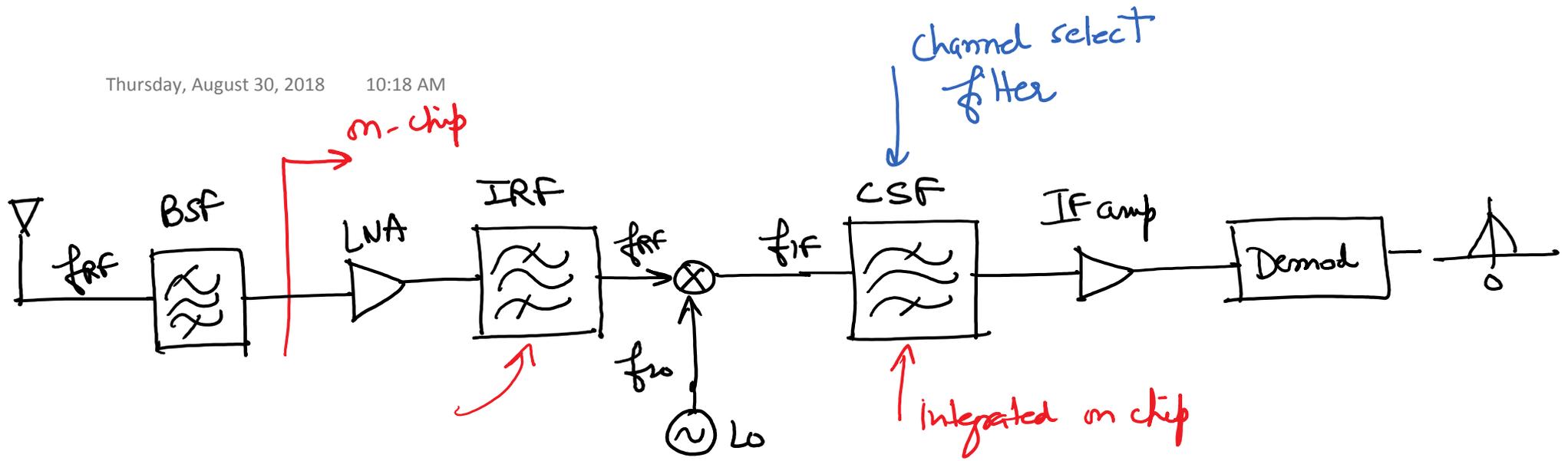- * RF frequency is translated to an intermediate frequency (f_{IF})
↳ use single or two-step downconversion
- * The image reject filter (IRF) allows the signal in the desired RF channel while attenuating the signals at the image frequency (f_{IM}).



Two Options:

- 1) Fixed f_{LO} frequency \rightarrow each RF channel is downconverted to a different IF frequency
- 2) Tunable f_{LO} frequency \rightarrow RF channel of interest is translated to a fixed IF frequency
 \hookrightarrow more common

↳ Don't need a variable CSF

ASK
FSK
PSK → QAM

After DRF the RF signal is $A(t) \cos(\omega_{RF}t + \alpha(t))$

multiplied by $\cos(\omega_{LO}t)$

at IF frequency,


$$S_{IF}(t) = A(t) \cos(\omega_{RF}t + \alpha(t)) \cdot \cos(\omega_{LO}t)$$

↓ LRF

$$\frac{A(t)}{2} \cdot \cos(\omega_{IF}t - \alpha(t))$$

↳ Both magnitude and phase are translated to IF frequency.

Dual Conversion

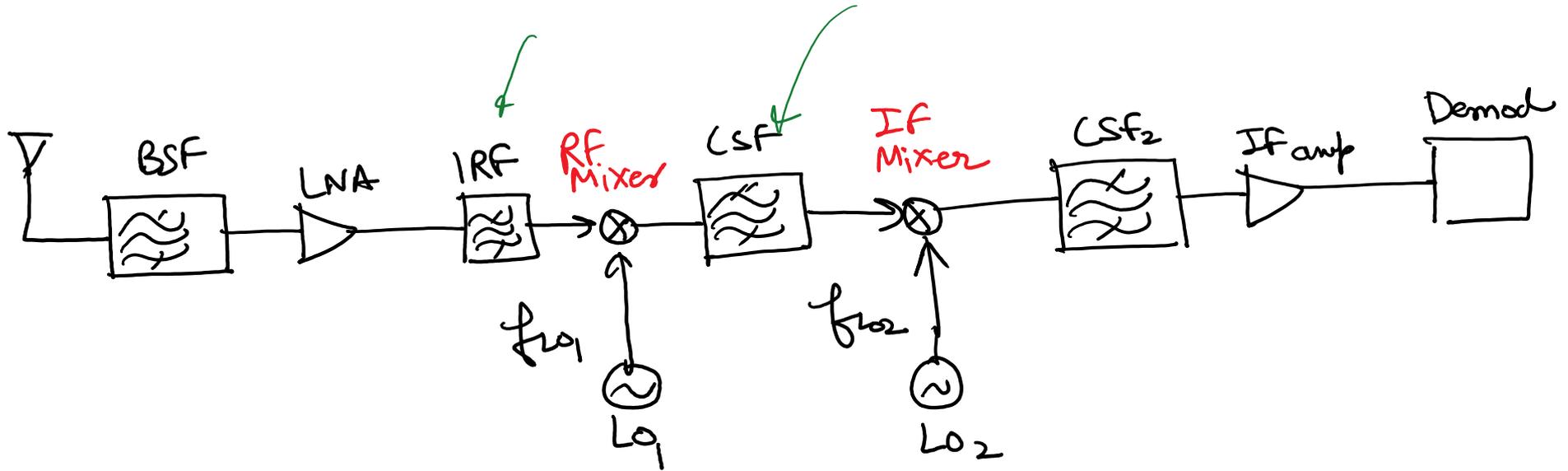


↳ Eases trade off between the IRF and CSF requirements,

Hartley Image Reject Receiver

Thursday, August 30, 2018

10:37 AM

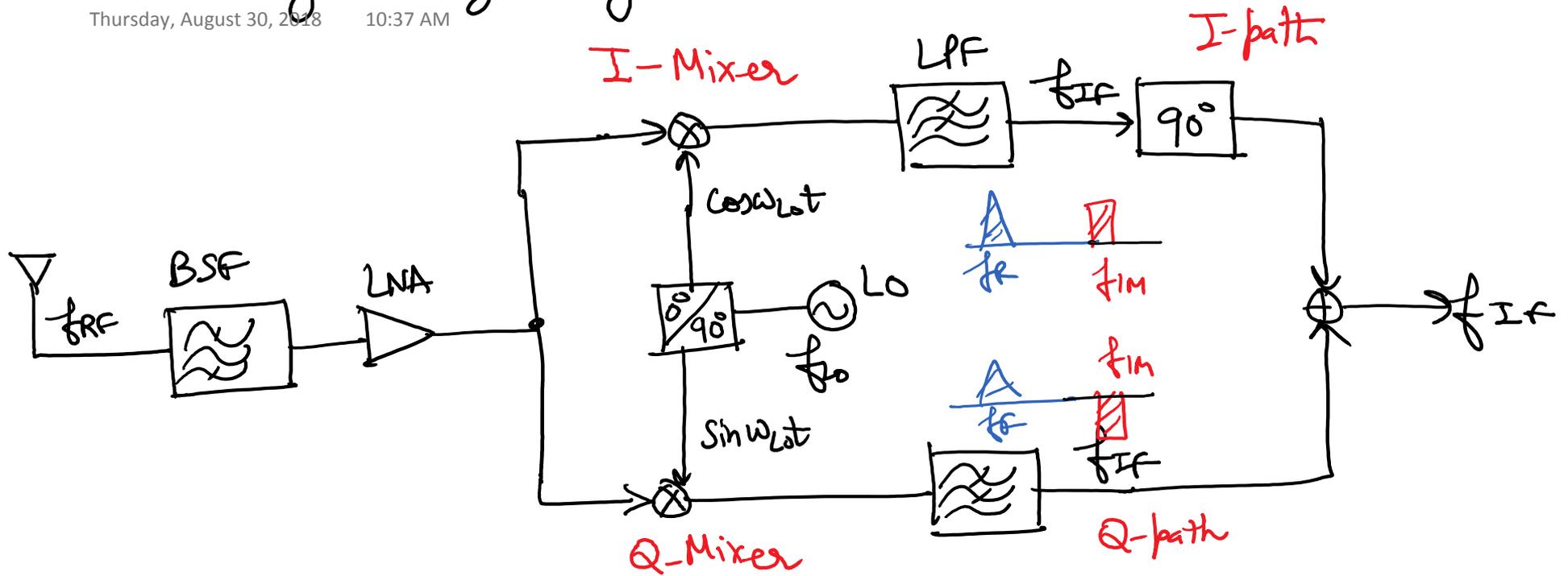

Hartley
& Weaver

Read up in the Book