


ECE 415/515 –ANALOG INTEGRATED CIRCUIT DESIGN

CS AMPLIFIER FREQUENCY RESPONSE:
POLE SPLITTING

VISHAL SAXENA
VSAXENA@UIDAHO.EDU




CS Amplifier With Input Source Impedance

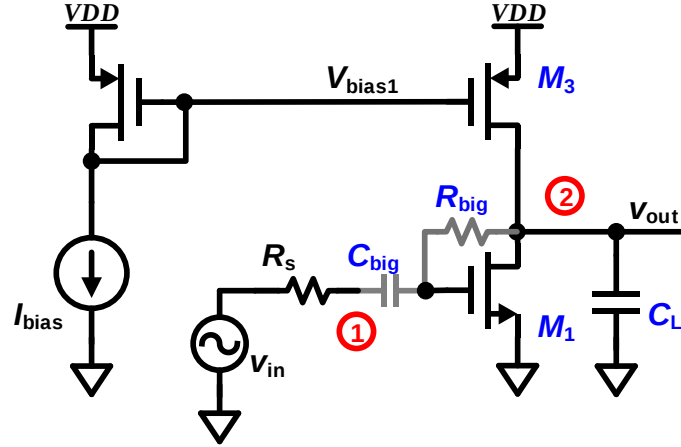


CS Amplifier With Input Source Impedance (1)

DC Picture

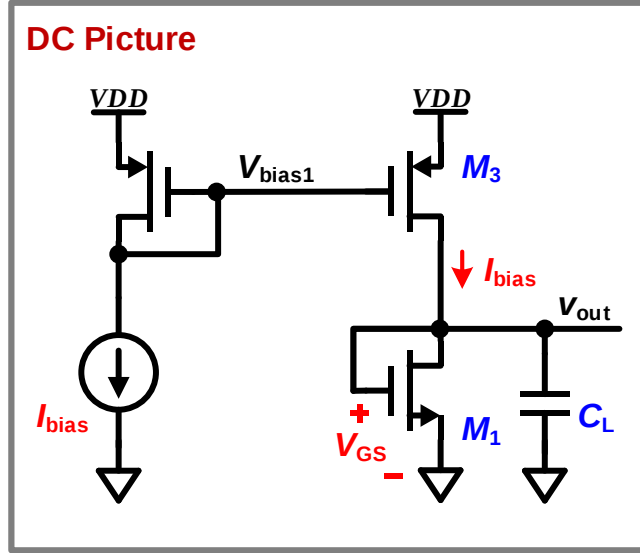

AC Picture

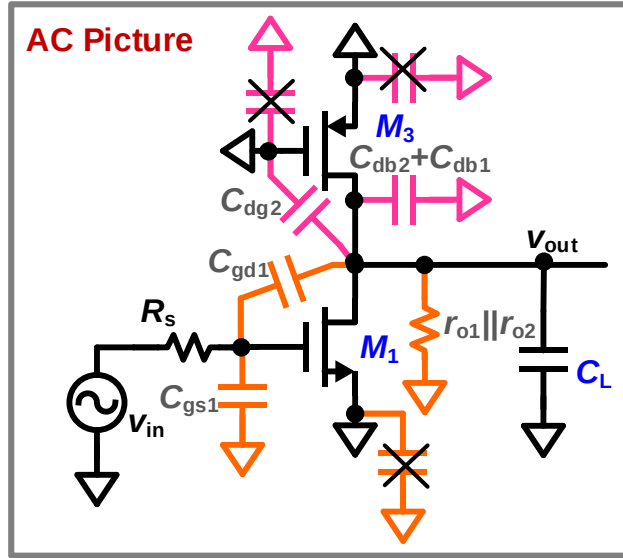

$$A_v = -g_{m1} \cdot r_{o1} || r_{o2}$$

$$C_{in} = C_{gs1}$$


$$R_o = r_{o1} || r_{o2}$$

$$C_o = C_{db1} + C_{db2} + C_{dg2} + C_L$$

$$C_c = C_{gd1}$$



CS Amplifier Analysis (1)

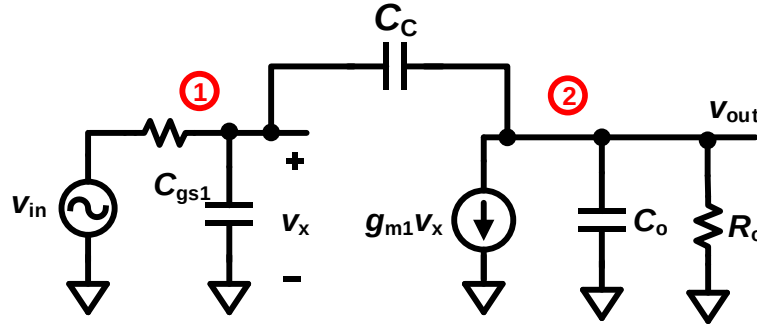

$$\frac{v_x - v_{in}}{R_s} + v_x s C_{gs1} + (v_x - v_{out}) s C_{gd1} = 0 \quad (1)$$

$$(v_x - v_{out}) s C_{gd1} + g_{m1} v_x + v_{out} (R_o^{-1} + s C_o) = 0 \quad (2)$$

$$\frac{v_{out}}{v_{in}}(s) = \frac{(s C_{gd1} - g_{m1}) R_o}{R_s R_o \xi s^2 + [R_s (1 + g_{m1} R_o) C_{gd1} + R_s C_{gs1} + R_o (C_{gd1} + C_o)] s + 1} \quad (3)$$

$$\text{where } \xi = C_{gs1} C_{gd1} + C_{gs1} C_o + C_{gd1} C_o$$



CS Amplifier Analysis: Zero

Numerator: $(sC_{gd1} - g_{m1})R_o = 0$

$$\omega_z = \frac{g_{m1}}{C_{gd1}} \quad \text{RHP zero}$$



CS Amplifier Analysis: Poles (1)

Denominator: $D(s) = \left(\frac{s}{\omega_{p1}} + 1\right) \left(\frac{s}{\omega_{p2}} + 1\right) = \frac{s^2}{\omega_{p1}\omega_{p2}} + \left(\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}}\right)s + 1$

For $|\omega_{p1}| \ll |\omega_{p2}|$

$$D(s) \approx \frac{s^2}{\omega_{p1}\omega_{p2}} + \frac{s}{\omega_{p1}} + 1 \quad (4)$$

Dominant pole by equating coefficient of 's' in Eq. (3) and (4)

$$\omega_{p1} = \frac{1}{R_s \underbrace{(1 + g_{m1} R_o) C_{gd1}}_{\text{Miller input cap}} + R_s C_{gs1} + \underbrace{R_o (C_{gd1} + C_o)}_{\text{Extra term due to the output node}}}$$

Miller input cap

Extra term due to the
output node



CS Amplifier Analysis: Poles (2)

Non-dominant pole by equating coefficient of 's²' in Eq. (3) and (4)

$$\begin{aligned}\omega_{p2} &= \frac{1}{\omega_{p1}} \cdot \frac{1}{R_s R_o \xi} \\ &= \frac{1}{\omega_{p1}} \cdot \frac{1}{R_s R_o [C_{gs1} C_{gd1} + C_{gs1} C_o + C_{gd1} C_o]} \\ &= \frac{R_s (1 + g_{m1} R_o) C_{gd1} + R_s C_{gs1} + R_o (C_{gd1} + C_o)}{R_s R_o [C_{gs1} C_{gd1} + C_{gs1} C_o + C_{gd1} C_o]}\end{aligned}$$

$$\frac{v_{out}}{v_{in}}(s) = \frac{A_v (1 - \frac{s}{\omega_z})}{\left(\frac{s}{\omega_{p1}} + 1\right) \left(\frac{s}{\omega_{p2}} + 1\right)}$$



CS Amplifier Analysis: Poles (3)

If C_{gs1} is very large: $R_s C_{gs1} \gg R_s(1 + g_{m1} R_o) C_{gd1} + R_o(C_{gd1} + C_o)$

$$\omega_{p2} = \frac{\cancel{R_s(1 + g_{m1} R_o) C_{gd1}} + R_s C_{gs1} + \cancel{R_o(C_{gd1} + C_o)}}{R_s R_o [C_{gs1} C_{gd1} + C_{gs1} C_o + C_{gd1} C_o]}$$

$$= \frac{\cancel{R_s} C_{gs1}}{\cancel{R_s} R_o [C_{gs1} C_{gd1} + C_{gs1} C_o + \cancel{C_{gd1} C_o}]}$$

$$\omega_{p2} \approx \frac{1}{R_o(C_{gd1} + C_o)}$$

Extreme case only when C_{gs1} is very large



Pole Splitting: Dominant Pole

$$\omega_{p1} = \frac{1}{R_s(1+g_{m1}R_o)C_c + R_sC_{gs1} + R_o(C_c + C_o)}$$

$$\omega_{p1}|_{C_c=0} = \frac{1}{R_sC_{gs1} + R_oC_o}$$

$$\omega_{p1}|_{C_c \gg C_{gs1}} = \frac{1}{R_s(1+g_{m1}R_o)C_c + R_o(C_c + C_o)}$$



Pole Splitting: Non-Dominant Pole

$$\omega_{p2} = \frac{R_s(1+g_{m1}R_o)C_c + R_sC_{gs1} + R_o(C_c + C_o)}{R_sR_o[C_{gs1}C_c + C_{gs1}C_o + C_cC_o]}$$

$$\omega_{p2}|_{C_c=0} = \frac{R_sC_{gs1} + R_oC_o}{R_sR_o[C_{gs1}C_o]} \approx \frac{1}{R_sC_{gs1}} + \frac{1}{R_oC_o} \approx \boxed{\frac{1}{R_oC_o}}$$

$$\omega_{p2}|_{C_c \gg C_{gs1}} \approx \frac{R_s(g_{m1}R_o)C_c + R_o(C_c + C_o)}{R_sR_o[C_{gs1}C_c + C_cC_o]} \approx \frac{R_s(g_{m1}R_o)}{R_sR_o[C_{gs1} + C_o]} \approx \frac{g_{m1}}{[C_{gs1} + C_o]}$$


$$\omega_{p2}|_{C_c \gg C_{gs1}} \approx \boxed{\frac{g_{m1}}{C_o} = g_{m1}R_o \left(\frac{1}{R_oC_o} \right)}$$

Second pole pushed to higher frequency by $g_{m1}R_o$ for a large value of C_c




Pole Splitting: Non-Dominant Pole

	$C_c=0$	$C_c \approx C_o \gg C_{gs1}$
ω_{p1}	$\frac{1}{R_s C_{gs1} + R_o C_o}$	$\frac{1}{R_s (1 + A_v) C_c + R_o (C_c + C_o)}$
ω_{p2}	$\approx \frac{1}{R_o C_o}$	$\approx \frac{g_{m1}}{C_o} = g_{m1} R_o \left(\frac{1}{R_o C_o} \right)$
ω_z	$\frac{g_{m1}}{C_{gd1}}$	$\frac{g_{m1}}{C_c}$

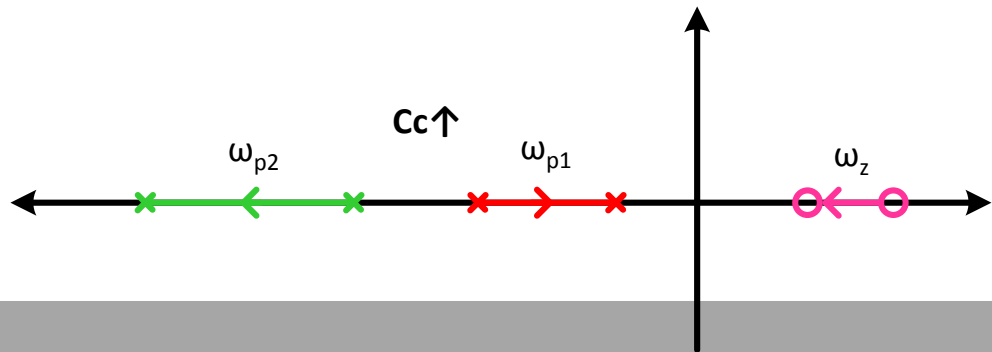

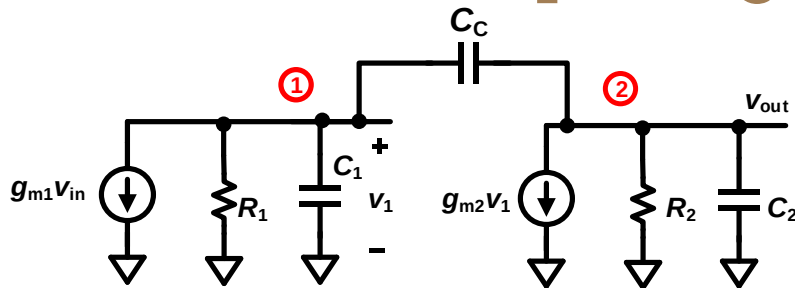Miller Compensation/Pole Splitting Summary



$$\frac{v_{out}}{v_{in}}(s) = \frac{A_v(1 - \frac{s}{\omega_z})}{(\frac{s}{\omega_{p1}} + 1)(\frac{s}{\omega_{p2}} + 1)}$$

$$A_v = g_{m1}R_1g_{m2}R_2$$

$$\omega_z = +\frac{g_{m2}}{C_c}$$

$$\omega_{un} = A_v\omega_{p1} = \frac{g_{m1}}{C_c}$$

$$\omega_{p1} = \frac{1}{R_1[C_1 + (1 + g_{m2}R_2)C_c] + R_2(C_2 + C_c)}$$

$$\approx \frac{1}{g_{m2}R_2R_1C_c}$$


$$\omega_{p2} \approx \frac{R_1(1 + g_{m2}R_2)C_c + R_1C_1 + R_2(C_c + C_2)}{R_1R_2[C_1C_c + C_2C_2 + C_cC_2]}$$

$$\approx \frac{g_{m2}C_c}{C_1C_c + C_2C_2 + C_cC_2} \propto \frac{g_{m2}}{C_2}$$



Pole Splitting Simulation (1)
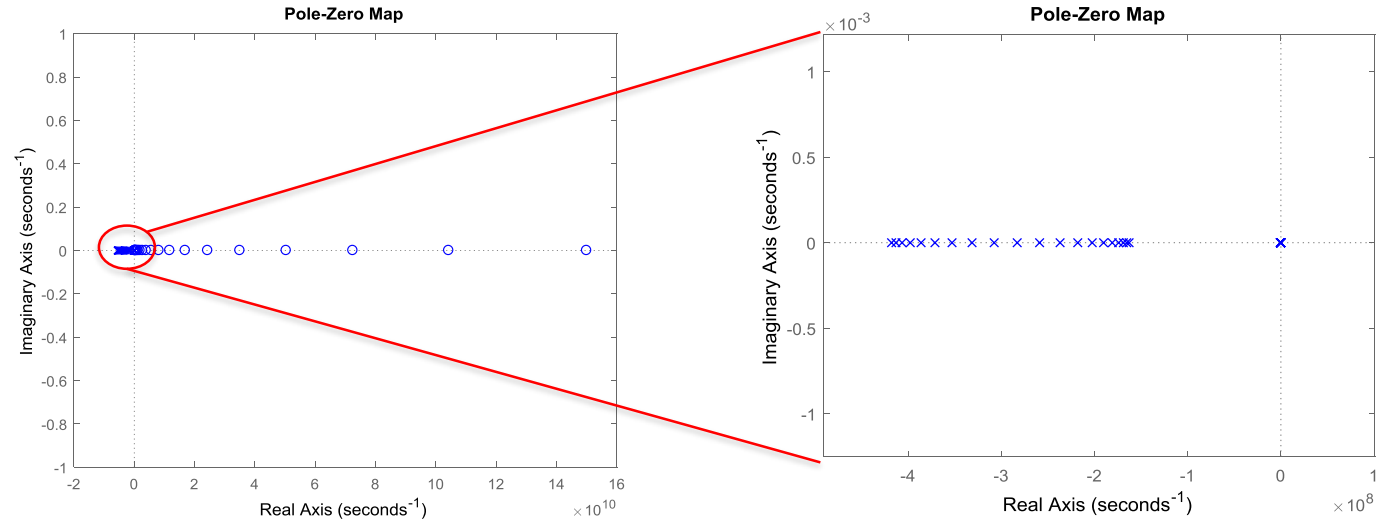
```
Rs = 100e3;  
gm1=1/Rs; gm2=150e-6;  
R1 = Rs; R2=2.22e6;  
C1=23.3*fF; C2=1*pF;
```





See Matlab file [CommonSourcePoleSplitting.m](#)



Pole Splitting Simulation (2)
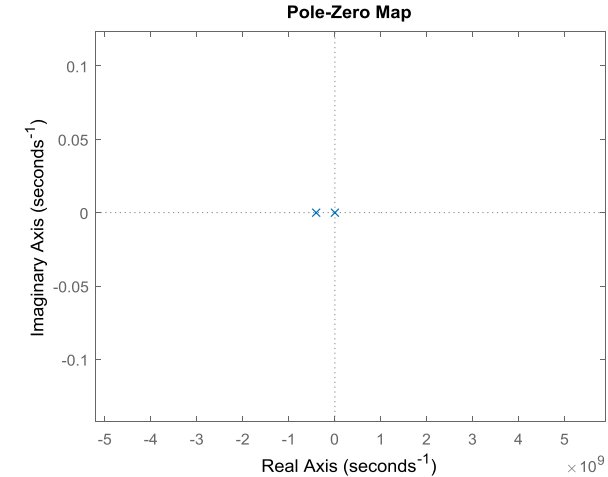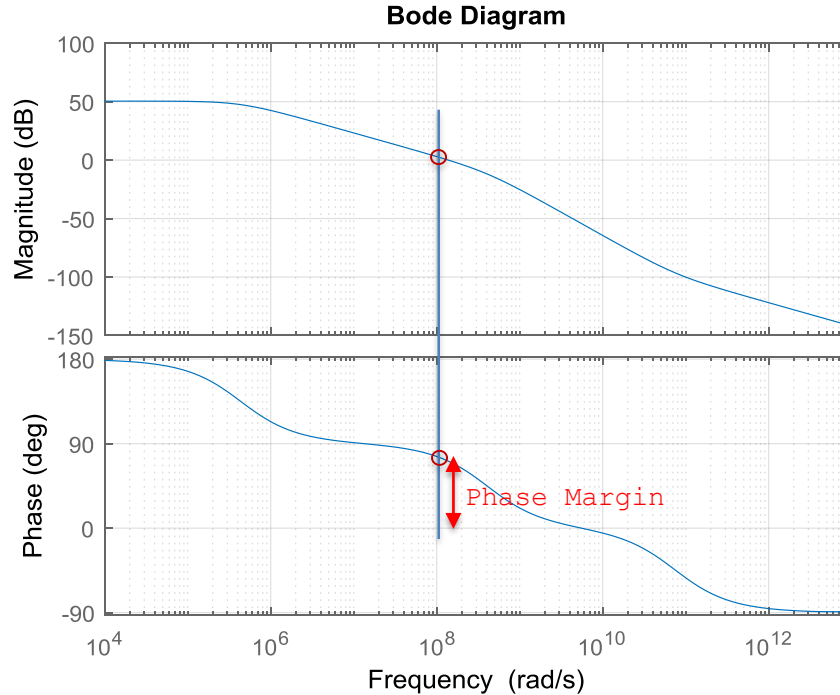
```
Rs = 100e3;  
gm1=1/Rs;  
gm2=150e-6;  
R1 = Rs;  
R2=2.22e6;  
C1=23.3*fF;  
C2=1*pF;  
Cc= 2*fF;
```





See Matlab file [CommonSourceFreqResp1.m](#)



Pole Splitting Simulation (2)

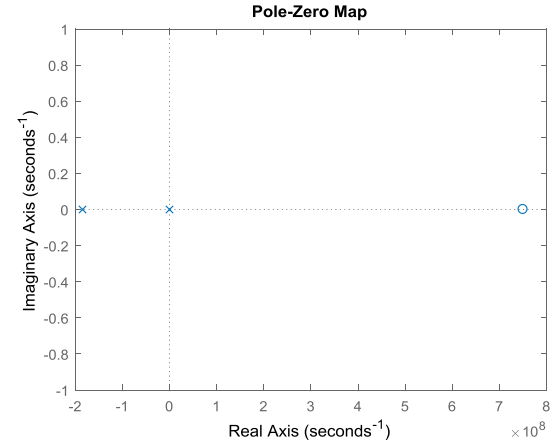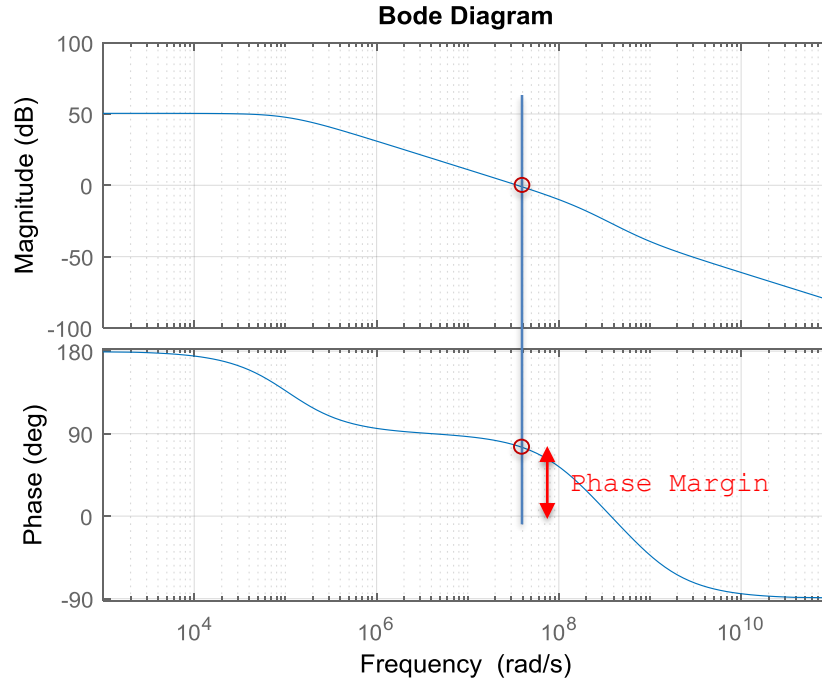
```
Rs = 100e3;  
gm1=1/Rs;  
gm2=150e-6;  
R1 = Rs;  
R2=2.22e6;  
C1=23.3*fF;  
C2=1*pF;  
Cc=200*fF;
```



See Matlab file [CommonSourceFreqResp1.m](#)



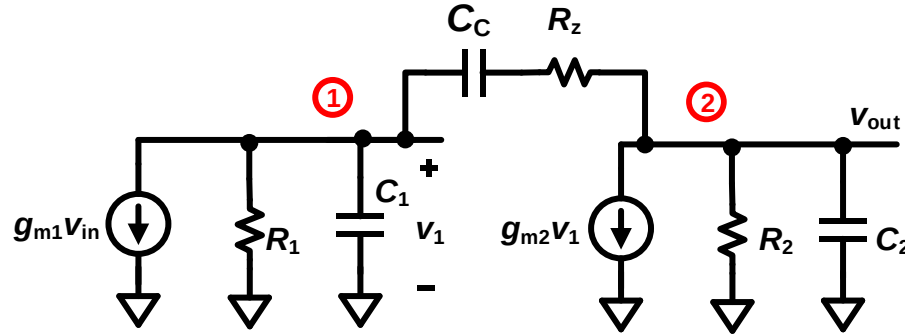Miller Compensation with Zero-Nulling Resistance



$$\omega_z = \frac{1}{C_c \left(\frac{1}{g_{m2}} - R_z \right)}$$



$$\omega_z \rightarrow \infty, R_z = \frac{1}{g_{m2}}$$

- Standard Miller compensation technique with zero nulling-R
- The RHP zero is pushed out to infinity
- Additional parasitic pole added at a higher frequency



Two-Stage Amplifier Simulation

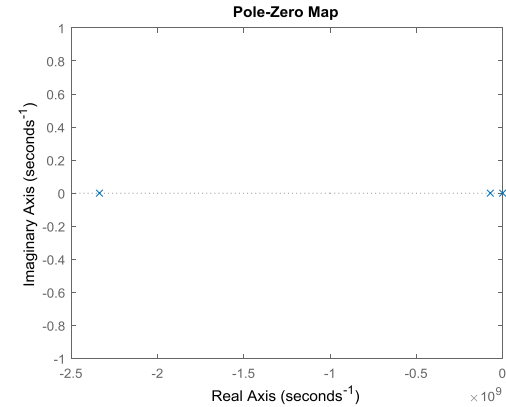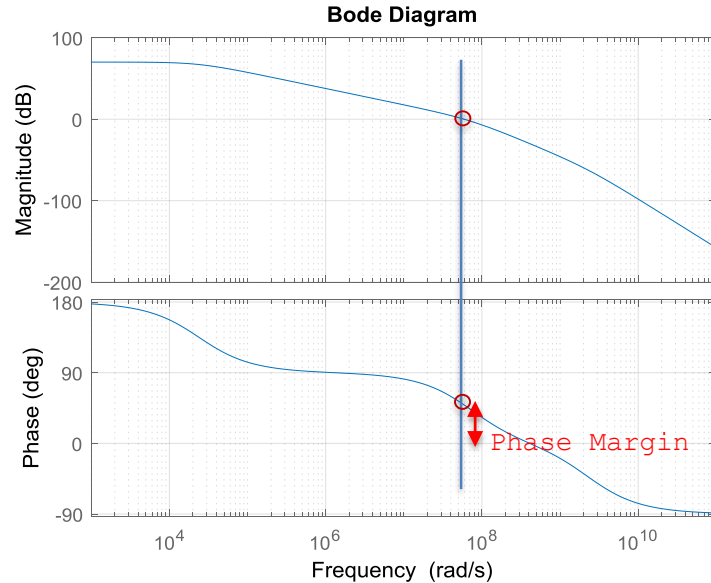$gm1=20e-6$;
 $gm2=80e-6$;
 $R1 = 4e6$; $R2=0.5e6$;
 $C1=40*fF$; $C2=1*pF$;
 $Cc=250*fF$;
 $Rz=12.5e3$;



See Matlab file TwoStageFreqResp1.m

