

ECE 5/415 Analog Integrated Circuit Design

Sample Midterm 1

Oct 10, 2017

Name: _____

Closed Book, Closed Notes, Closed Computer.
Show your steps clearly to get credit.
State clearly any assumptions made.
This exam has 6 questions, for a total of 100 points.

Use the following transistor parameters for problems in this exam. $V_{DD} = 5\text{V}$ and scale factor of $1\mu\text{m}$.

Parameter	NMOS	PMOS
$V_{THN,P}$	0.8 V	0.9 V
$KP_{n,p}$	$120 \frac{\mu\text{A}}{\text{V}^2}$	$40 \frac{\mu\text{A}}{\text{V}^2}$
$\lambda_{n,p}$	0.01 V^{-1}	0.0125 V^{-1}


1. Answer the following parts:

(a) (5 points) For an NMOS, sketch g_m vs V_{GS} plot. On this plot, label the g_m corresponding to a fixed gate overdrive voltage V_{ov} .

(b) (5 points) Sketch g_m as a function of current (I_D) when the W/L ratio is constant.


- (c) (5 points) Explain the temperature behavior of an NMOS transistor using I_D vs V_{GS} curves.

 - (d) (5 points) Find the small-signal gain of this amplifier in terms of small-signal parameters g_{m1} , r_{o1} , g_{m2} , r_{o2} of the transistors.




2. (10 points) Define the transition frequency (f_T) for an NMOS and derive an expression for f_T . How does f_T depends on the channel length (L) and the gate overdrive voltage (V_{ov})?

 3. (a) (5 points) Sketch the circuit(s) used to generate references V_{bias1} and V_{bias2} from a beta-multiplier reference (BMR).




- (b) (5 points) Derive an exact expression for the output resistance of the cascode current source seen above.

 4. (20 points) Calculate all the DC voltages and currents in the circuit shown below.




 5. Consider the beta multiplier reference (BMR) circuit shown in the figure below.



- (10 points) Derive expressions for I_{ref} , V_{GS1} and g_{m1} . Note that M2 is K times wider than M1.
- (5 points) Draw the schematic for a start-up circuit for this BMR.
- (5 points) Modify this circuit to make it suitable for short-channel design.

 6. Consider the regulated drain current mirror shown below.



- (a) (3 points) Assign the positive and negative terminals on the amplifier to ensure overall negative feedback.
- (b) (7 points) Label all the nodes in the circuits in terms of $V_{DS,sat}$ and V_{THN} . What is the allowable range for the voltage V_o ?
- (c) (10 points) Derive an expression for the output resistance of this current mirror.

- (d) (0 points) **Bonus:** Sketch the PMOS and wide-swing version of this circuit.