

ECE 5/415 Analog Integrated Circuit Design

Sample Midterm 1

Oct 10, 2017

Name: _____

Key

Closed Book, Closed Notes, Closed Computer.

Show your steps clearly to get credit.

State clearly any assumptions made.


This exam has 6 questions, for a total of 100 points.

Use the following transistor parameters for problems in this exam. $V_{DD} = 5V$ and scale factor of $1\mu m$.

Parameter	NMOS	PMOS
$V_{THN,P}$	0.8 V	0.9 V
$KP_{n,p}$	$120 \frac{\mu A}{V^2}$	$40 \frac{\mu A}{V^2}$
$\lambda_{n,p}$	$0.01 V^{-1}$	$0.0125 V^{-1}$


1. Answer the following parts:

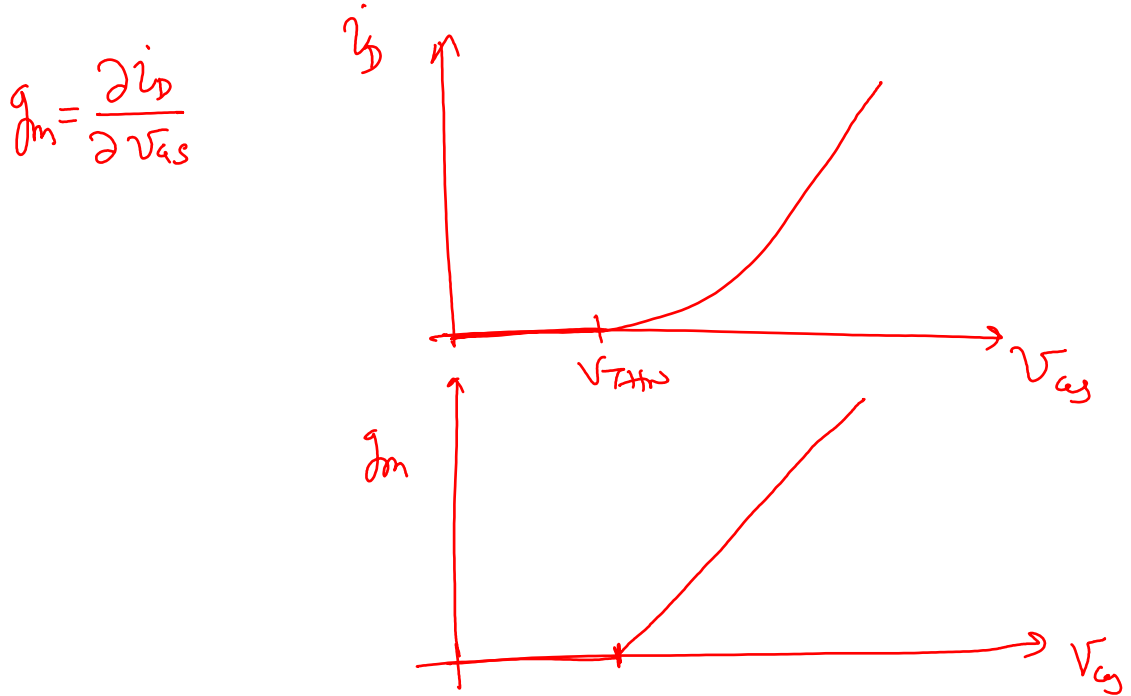- (a) (5 points) For an NMOS, sketch g_m vs V_{GS} plot. On this plot, label the g_m corresponding to a fixed gate overdrive voltage V_{ov} .




- (b) (5 points) Sketch g_m as a function of current (I_D) when the W/L ratio is constant.

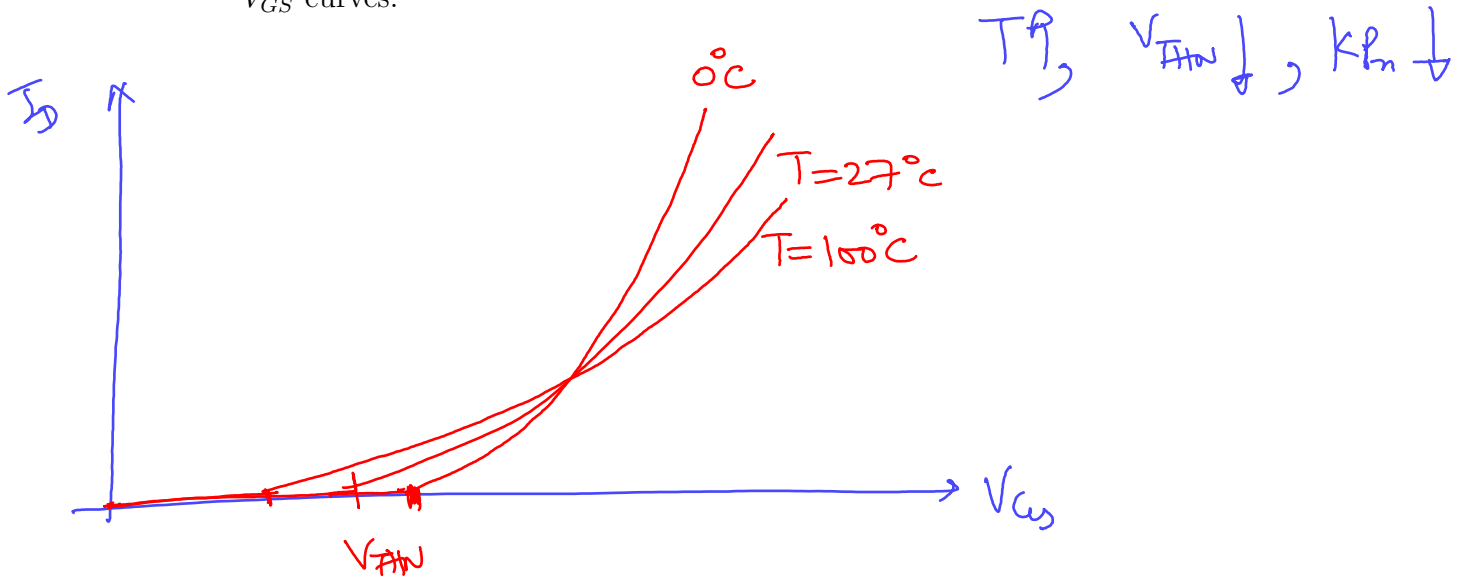- (c) (5 points) Explain the temperature behavior of an NMOS transistor using I_D vs V_{GS} curves.




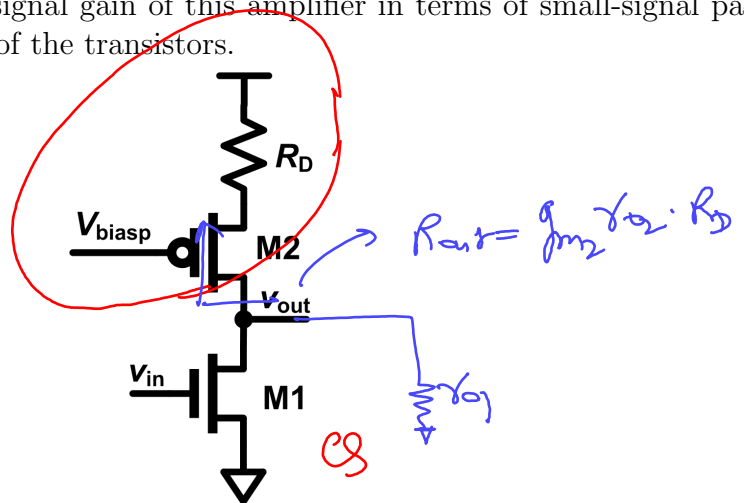- (d) (5 points) Find the small-signal gain of this amplifier in terms of small-signal parameters g_{m1} , r_{o1} , g_{m2} , r_{o2} of the transistors.



$$A_v = -g_{m1} [r_{o1} \parallel (g_{m2} r_{o2} R_D)]$$

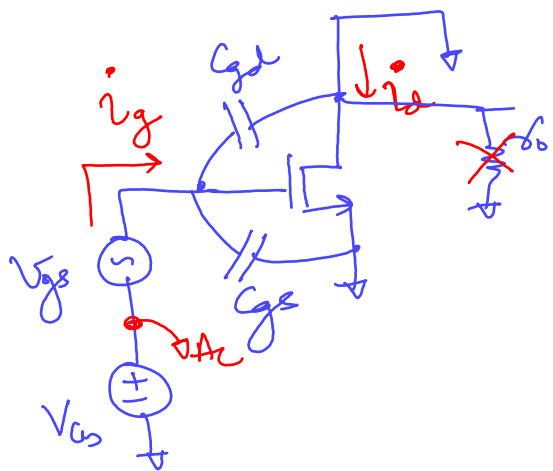2. (10 points) Define the transition frequency (f_T) for an NMOS and derive an expression for f_T . How does f_T depend on the channel length (L) and the gate overdrive voltage (V_{ov})?



$$@ f = f_T \quad \left| \frac{i_d}{i_g} \right| = 1$$

$$i_g = \frac{v_{gs}}{\frac{1}{s(C_{gs} + C_{gd})}}} = s(C_{gs} + C_{gd})v_{gs} \rightarrow (1)$$

$$i_d = g_m v_{gs} \rightarrow (2)$$

$$\frac{i_d}{i_g} = \frac{g_m v_{gs}}{s(C_{gs} + C_{gd})v_{gs}}$$


$$\left| \frac{i_d}{i_g} \right| = 1 \Rightarrow \frac{g_m}{2\pi f_T (C_{gs} + C_{gd})} = 1$$

$$f_T = \frac{g_m}{2\pi (C_{gs} + C_{gd})} \approx \frac{g_m}{2\pi C_{gs}}$$



$$f_T \propto \frac{V_{ov}}{L^2} \quad \text{for long-channel}$$

$$\propto \frac{V_{ov}}{L} \quad \text{for short-channel}$$

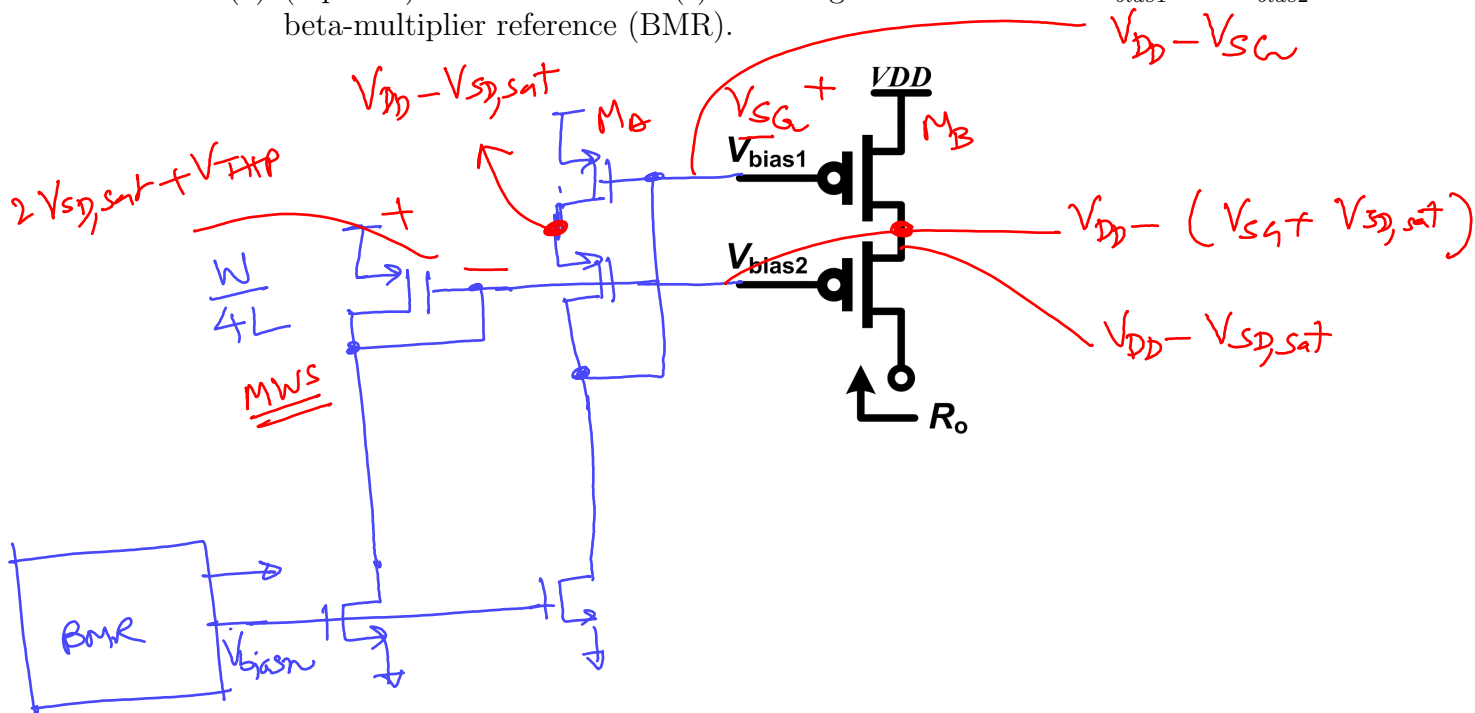3. (a) (5 points) Sketch the circuit(s) used to generate references V_{bias1} and V_{bias2} from a beta-multiplier reference (BMR).



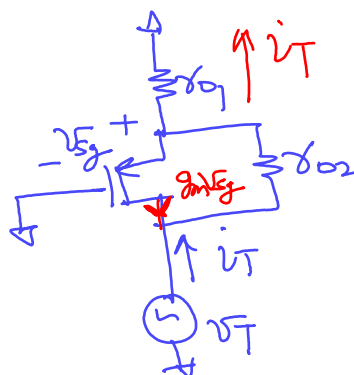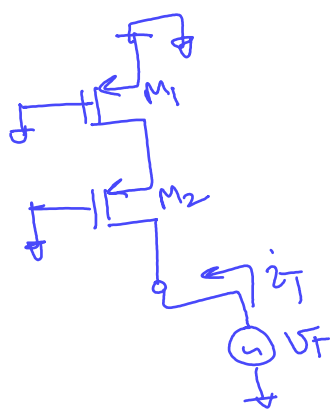- (b) (5 points) Derive an exact expression for the output resistance of the cascode current source seen above.




$$V_{sg} = + i_T r_{o1}$$

$$V_T = (i_T + g_{m2} V_{sg}) r_{o2} + i_T r_{o1}$$

$$= i_T [r_{o2} + g_{m2} r_{o2} r_{o1} + r_{o1}] \Rightarrow$$

$$R_{out} = \frac{V_T}{i_T} = g_{m2} r_{o2} r_{o1} + r_{o1} + r_{o2}$$

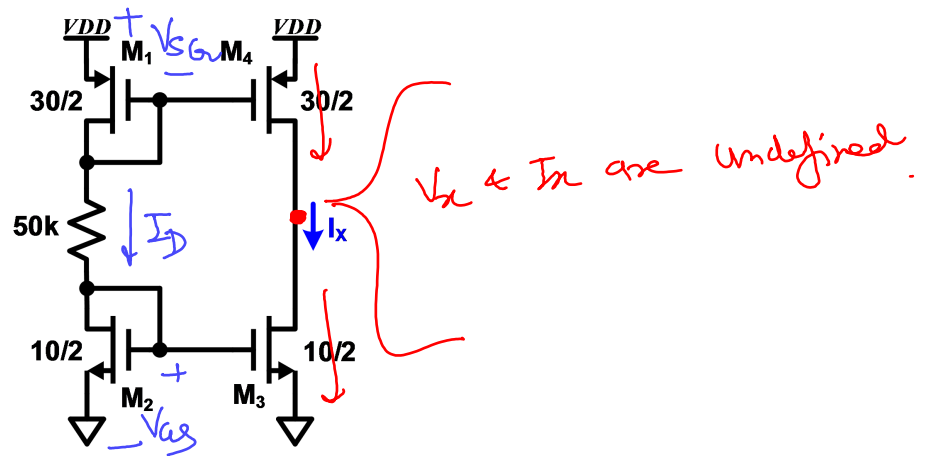4. (20 points) Calculate all the DC voltages and currents in the circuit shown below.



$$V_{DD} = V_{SG} + V_{AS} + I_D R$$

$$= \sqrt{\frac{2I_D}{\beta_P}} + |V_{THP}| + \sqrt{\frac{2I_D}{\beta_N}} + |V_{THN}| + I_D R$$

$$\Rightarrow I_D R + \sqrt{I_D} \left(\sqrt{\frac{2}{\beta_P}} + \sqrt{\frac{2}{\beta_N}} \right) - (V_{DD} - V_{THN} - |V_{THP}|) = 0$$

$$\text{Let } x = \sqrt{I_D}$$


$$x^2 R + x \left(\sqrt{\frac{2}{\beta_P}} + \sqrt{\frac{2}{\beta_N}} \right) - (V_{DD} - V_{THN} - |V_{THP}|) = 0$$

$$\text{Solve for } x = ?$$



$$I_D = ?$$

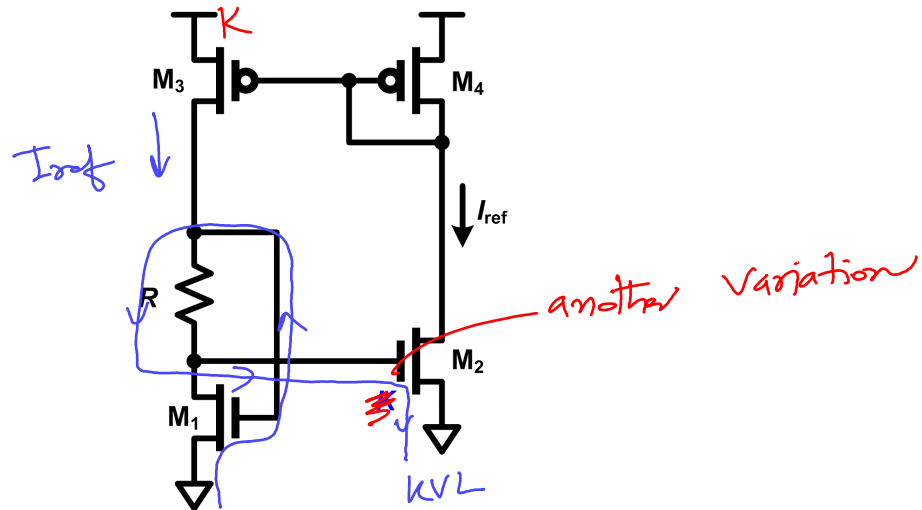5. Consider the beta multiplier reference (BMR) circuit shown in the figure below.



- (10 points) Derive expressions for I_{ref} , V_{GS1} and g_{m1} . Note that M2 is K times wider than M1.
- (5 points) Draw the schematic for a start-up circuit for this BMR.
- (5 points) Modify this circuit to make it suitable for short-channel design.


$$V_{GS1} - I_{ref} R = V_{GS2}$$

$$\sqrt{\frac{2I_{ref}}{\beta}} + \cancel{V_{TH1}} - I_{ref} R = \sqrt{\frac{2I_{ref}}{K\beta}} + \cancel{V_{TH2}}$$


$$\Rightarrow \sqrt{\frac{2I_{ref}}{\beta}} \left(1 - \frac{1}{\sqrt{K}}\right) = I_{ref} R$$

$$\Rightarrow I_{ref} = \begin{cases} 0 \\ \frac{2}{\beta R^2} \left(1 - \frac{1}{\sqrt{K}}\right)^2 \end{cases}$$

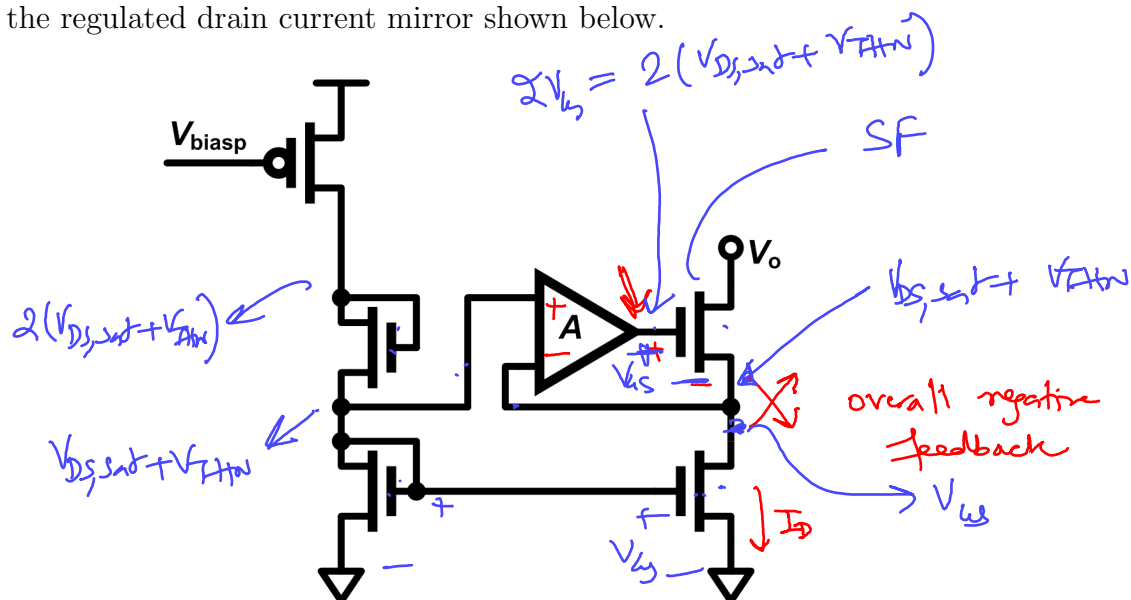6. Consider the regulated drain current mirror shown below.



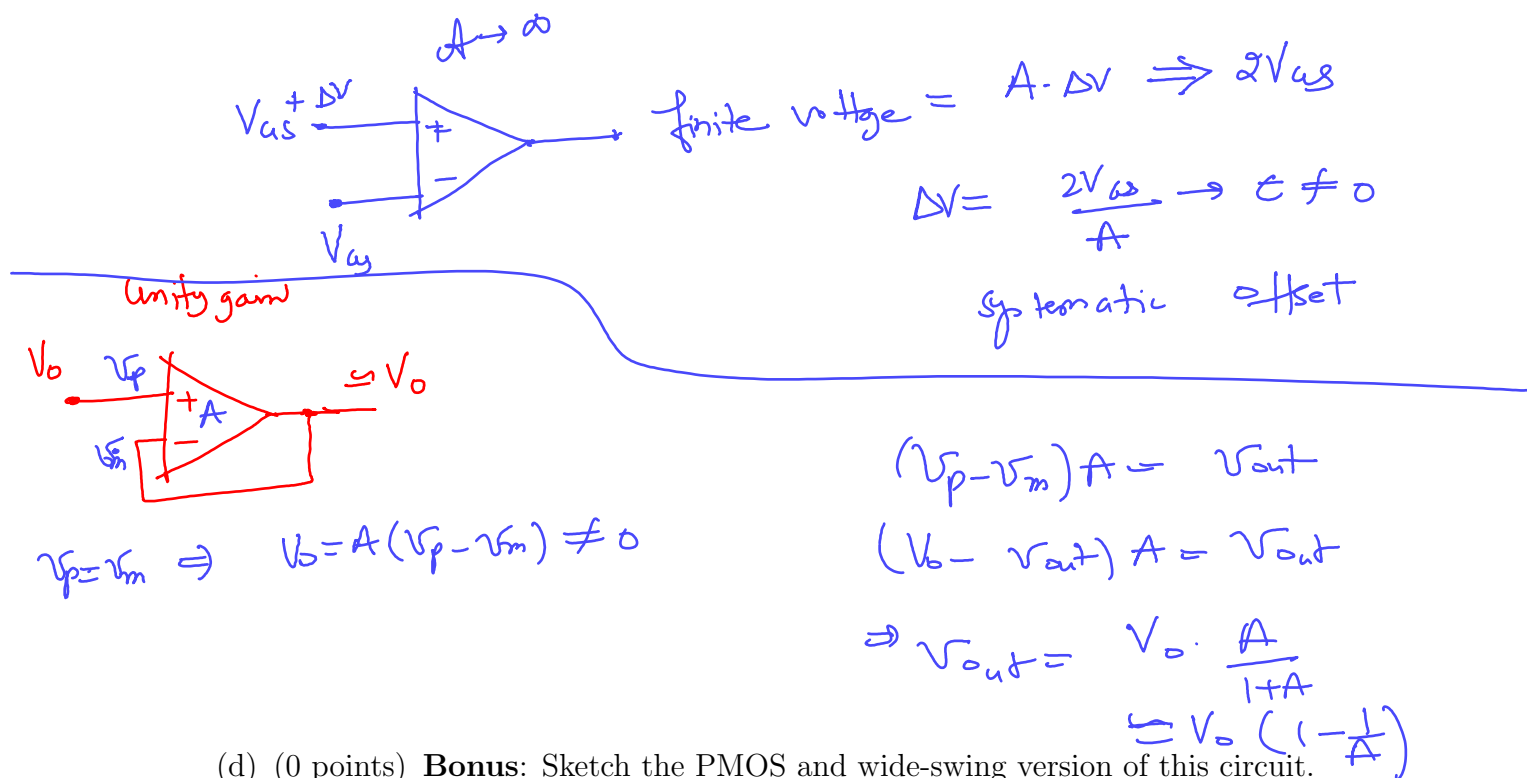- (3 points) Assign the positive and negative terminals on the amplifier to ensure overall negative feedback.
- (7 points) Label all the nodes in the circuits in terms of $V_{DS,sat}$ and V_{THN} . What is the allowable range for the voltage V_o ?
- (10 points) Derive an expression for the output resistance of this current mirror.



(d) (0 points) **Bonus:** Sketch the PMOS and wide-swing version of this circuit.

$$R_{out} = g_{m2} r_{o2} A r_{o1} + r_{o1} + r_{o2} \approx g_{m2} r_{o2}^2 A$$