# ECE 415/515 –ANALOG INTEGRATED CIRCUIT DESIGN

SHORT CHANNEL BIASING

#### VISHAL SAXENA VSAXENA@UIDAHO.EDU



© Vishal Saxena



### LONG-CHANNEL CMOS, $L_{MIN}$ =1UM

 Table 9.1 Typical parameters for analog design using the *long-channel* CMOS process discussed in this book. Note that the parameters may change with temperature or drain-to-source voltage (e.g., Fig. 9.24).

<i>Long</i> -channel MOSFET parameters for general analog design <i>VDD</i> = 5 V and a scale factor of <b>1</b> μ <b>m</b> ( <i>scale</i> = 1e–6)			
Parameter	NMOS	PMOS	Comments
Bias current, $I_D$	20 µA	20 µA	Approximate
W/L	10/2	30/2	Selected based on $I_{D}$ and $V_{{\it DS}, {\it sat}}$
$V_{\rm DS,sat}$ and $V_{\rm SD,sat}$	250 mV	250 mV	For sizes listed
$V_{\rm GS}$ and $V_{\rm SG}$	1.05 V	1.15 V	No body effect
$V_{T\!H\!N}{\rm and}V_{T\!H\!P}$	800 mV	900 mV	Typical
$\partial V_{THN,P} / \partial T$	$-1 \text{ mV/C}^{\circ}$	$-1.4 \text{ mV/C}^{\circ}$	Change with temperature
$KP_n$ and $KP_p$	$120 \ \mu A/V^2$	$40 \ \mu A/V^2$	$t_{ox} = 200 \text{ Å}$
$C'_{ox} = \varepsilon_{ox}/t_{ox}$	$1.75 f \mathrm{F/\mu m^2}$	$1.75f\mathrm{F/\mu m^2}$	$C_{ox} = C'_{ox}WL \cdot (scale)^2$
$C_{oxp}$ and $C_{oxp}$	35 <i>f</i> F	105 <i>f</i> F	PMOS is three times wider
$C_{\scriptscriptstyle gsn} \text{ and } C_{\scriptscriptstyle sgp}$	23.3 <i>f</i> F	70 <i>f</i> F	$C_{gs} = \frac{2}{3}C_{ox}$
$C_{\mathit{gdn}} \text{ and } C_{\mathit{dgp}}$	2fF	6 <i>f</i> F	$C_{gd} = CGDO \cdot W \cdot scale$
$g_{mn}$ and $g_{mp}$	150 μA/V	150 μA/V	At $I_D = 20 \ \mu A$
$r_{on}$ and $r_{op}$	5 ΜΩ	$4 \mathrm{M}\Omega$	Approximate at $I_D = 20 \ \mu A$
$g_{mn}r_{on}$ and $g_{mp}r_{op}$	750 V/V	600 V/V	Open circuit gain
$\lambda_n$ and $\lambda_p$	0.01 V <sup>-1</sup>	0.0125 V <sup>-1</sup>	At <i>L</i> = 2
$f_{Tn}$ and $f_{Tp}$	900 MHz	300 MHz	For $L = 2$ , $f_T$ goes up if $L = 1$

fldaho

Figures from CMOS Circuit Design, Layout, and Simulation, Copyright Wiley-IEEE, CMOSedu.com



### SHORT-CHANNEL CMOS, $L_{MIN}$ =50NM

Short-channel MOSFET parameters for general analog design VDD = 1 V and a scale factor of 50 nm (scale = 50e-9) Parameter NMOS PMOS Comments Approximate, see Fig. 9.31 Bias current, ID 10 uA 10 uA W/L50/2100/2Selected based on  $I_D$  and  $V_{av}$  $5\mu m/100nm$ Actual W/L 2.5µm/100nm  $L_{min}$  is 50 nm  $V_{DS,sat}$  and  $V_{SD,sat}$ 50 mV50 mVHowever, see Fig. 9.32 and the associated discussion Vom and Vov 70 mV70 mV $V_{GS}$  and  $V_{SG}$ 350 mV350 mVNo body effect 280 mV280 mV Typical V<sub>THN</sub> and V<sub>THP</sub>  $\partial V_{THNP} / \partial T$  $-0.6 \text{ mV/C}^{\circ}$ - 0.6 mV/C° Change with temperature  $110 \ge 10^3 \text{ m/s}$  $90 \ge 10^3 \text{ m/s}$ From the BSIM4 model  $v_{sam}$  and  $v_{sam}$ 14 Å 14 Å Tunnel gate current, 5 A/cm<sup>2</sup> t<sub>ar</sub>  $C'_{ox} = \varepsilon_{ox}/t_{ox}$  $25 f F/\mu m^2$  $25 f F/\mu m^2$  $C_{ox} = C'_{ox}WL \cdot (scale)^2$ PMOS is two times wider  $C_{oxp}$  and  $C_{oxp}$ 6.25 f F 12.5 f F  $C_{gs} = \frac{2}{3}C_{ox}$ C\_m and C\_sep 4.17 fF 8.34 fF  $C_{gd} = CGDO \cdot W \cdot scale$ 1.56 f F 3.7*f* F  $C_{adm}$  and  $C_{dem}$  $150 \ \mu A/V$  $g_{mn}$  and  $g_{mp}$ 150 µA/V At  $I_D = 10 \ \mu A$ 167 kΩ 333 kΩ Approximate at  $I_D = 10 \ \mu A$ ron and rov 25 V/V 50 V/V !!Open circuit gain!! gmmron and gmprov  $0.6 V^{-1}$  $0.3 V^{-1}$ L = 2 $\lambda_n$  and  $\lambda_n$  $f_{T_n}$  and  $f_{T_n}$ 6000 MHz 3000 MHz Approximate at L = 2

 
 Table 9.2 Typical parameters for analog design using the *short-channel* CMOS process discussed in this book. These parameters are valid only for the device sizes and currents listed.

Figures from CMOS Circuit Design, Layout, and Simulation, Copyright Wiley-IEEE, CMOSedu.com



#### © Vishal Saxena

# BMR CIRCUIT IN 1UM CMOS

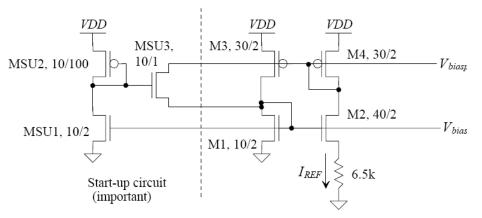


Figure 20.15 Beta-multiplier reference for biasing in the long-channel process described in Table 9.1.

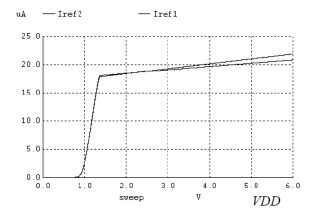


Figure 20.16 The reference currents through M1 and M2 in the Beta-multiplier.

Figures from CMOS Circuit Design, Layout, and Simulation, Copyright Wiley-IEEE, CMOSedu.com

Ι

© Vishal Saxena

## **50NM BMR CIRCUIT**

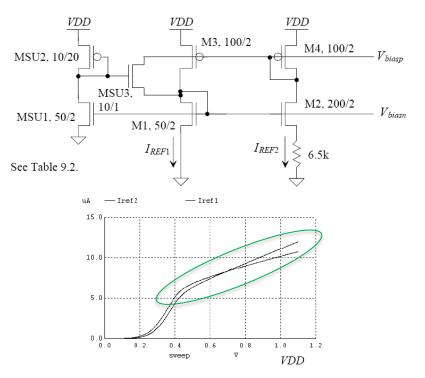


Figure 20.18 Beta-multiplier reference for short-channel design (see Table 9.2).

Figures from CMOS Circuit Design, Layout, and Simulation, Copyright Wiley-IEEE, CMOSedu.com





#### © Vishal Saxena

## SHORT-CHANNEL BMR CIRCUIT

 



Figure 20.19 Increasing the output resistance of short-channel MOSFETs using feedback. The result, for the Beta-multiplier circuit, is better power supply sensitivity.

Figures from CMOS Circuit Design, Layout, and Simulation, Copyright Wiley-IEEE, CMOSedu.com

][

C Vishal Saxena

## **CASCODE CURRENT SOURCES**

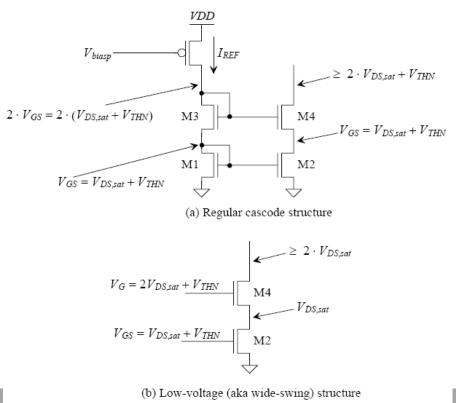


Figures from CMOS Circuit Design, Layout, and Simulation, Copyright Wiley-IEEE, CMOSedu.com



Figure 20.31 DC voltages in (a) a cascode current mirror and in (b) a low-voltage cascode.



## WIDE-SWING CASCODE CURRENT SOURCES

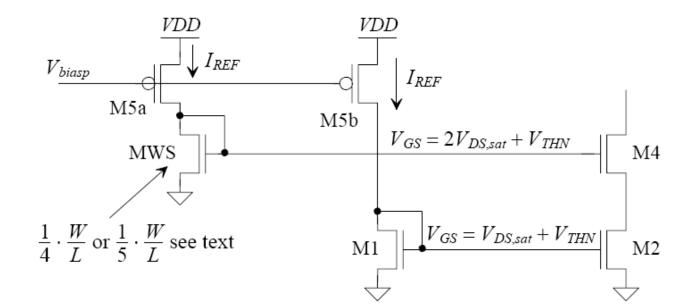


Figures from CMOS Circuit Design, Layout, and Simulation, Copyright Wiley-IEEE, CMOSedu.com

Figure 20.32 Generating a bias voltage for M4.



© Vishal Saxena

## WIDE-SWING CASCODE CURRENT SOURCES

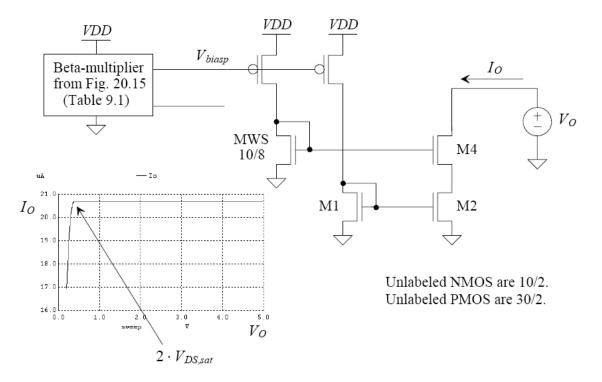

Figures from CMOS Circuit Design, Layout, and Simulation, Copyright Wiley-IEEE, CMOSedu.com


Figure 20.33 Wide-swing cascode current source in the long-channel process.

© Vishal Saxena

College of Engineering

<u>Oniversity or idaho</u>

### LONG-CHANNEL BIAS CIRCUITS

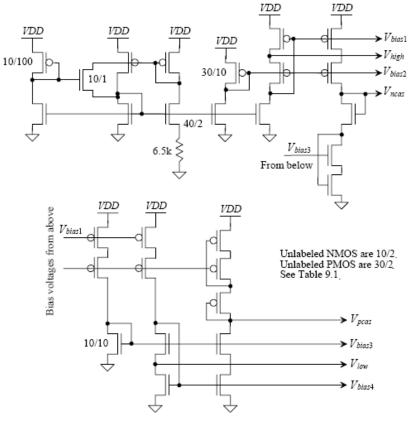

Figures from CMOS Circuit Design, Layout, and Simulation, Copyright Wiley-IEEE, CMOSedu.com




/ishal S

Figure 20.43 General biasing circuit for long-channel CMOS design using the data in Table 9.1

yof Idaho

#### SHORT-CHANNEL BIAS CIRCUITS

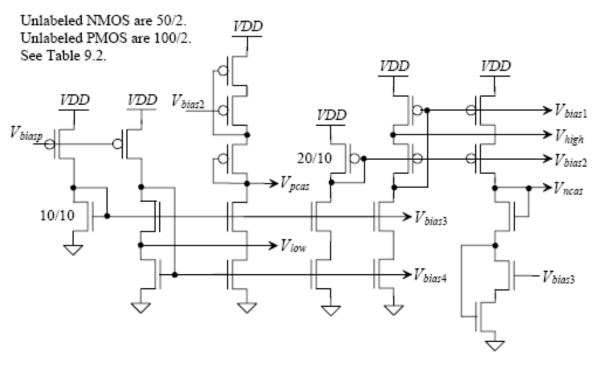


Figures from CMOS Circuit Design, Layout, and Simulation, Copyright Wiley-IEEE, CMOSedu.com

Figure 20.47 General biasing circuit for short-channel design using the data in Table 9.2.

#### © Vishal Saxena

College of Engineering

### **USING BIAS REFERENCES**

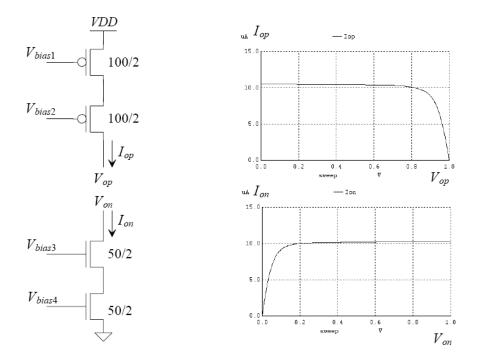

Figures from CMOS Circuit Design, Layout, and Simulation, Copyright Wiley-IEEE, CMOSedu.com

Bias voltages come from Fig. 20.47 (short-channel parameters in Table 9.2).

Figure 20.48 Cascode current sources operating in a short-channel process.

#### © Vishal Saxena