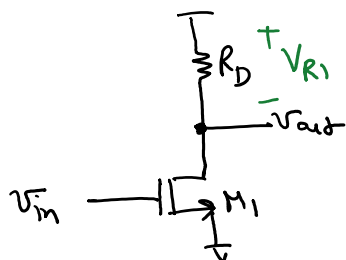


ECE 515 - Lecture 10

Tuesday, September 25, 2018 10:58 AM



$$\begin{aligned}
 A_v = \frac{v_{out}}{v_{in}} &\Rightarrow -g_{m1} R_D \\
 &= -\sqrt{2\mu_n \frac{W}{L} \cdot I_D} \cdot \left(\frac{V_{RD}}{I_D} \right) \\
 &= -\sqrt{2\mu_n \frac{W}{L}} \cdot \frac{V_{RD}}{\sqrt{I_D}}
 \end{aligned}$$

$$|A_v| \uparrow \Rightarrow$$



$$\frac{W}{L} \uparrow \Rightarrow \text{large device cap} \propto \sqrt{W/L}$$

$$V_{RD} \uparrow \Rightarrow R_D \uparrow \Rightarrow \text{lower swings for } V_{DS}$$


$$I_D \downarrow \Rightarrow \text{lower speed}$$

$$V_{RD} = I_D \cdot R_D$$

Use current mirror loads

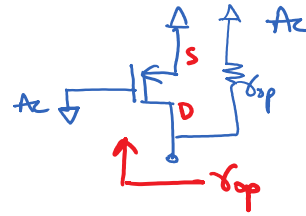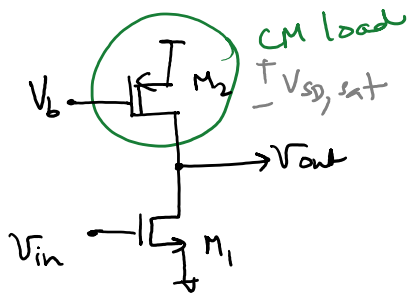

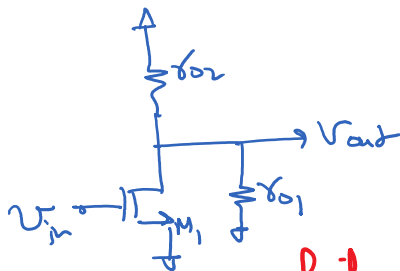output impedance value is no longer coupled with the voltage drop across the load!



higher gain!

$$\Rightarrow A_v = \frac{V_{out}}{V_{in}} = -g_{m1} \cdot (r_{O1} \parallel r_{O2})$$



$$\approx -\frac{g_{m1} r_{O1}}{2}$$

if $r_{O1} = r_{O2} = r_O$


Max gain

CS Stage with Current-source load

Tuesday, September 25, 2018 11:16 AM

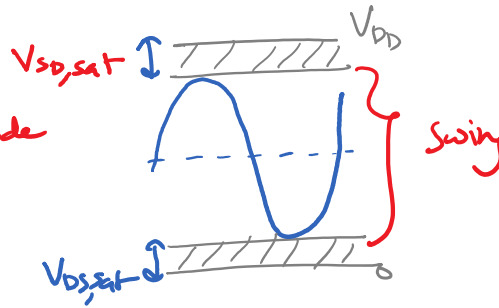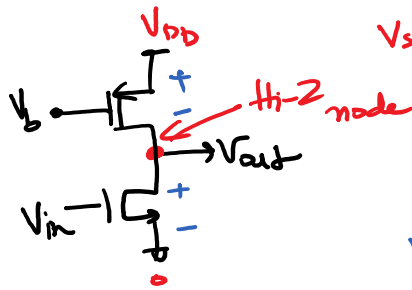



large output swings!

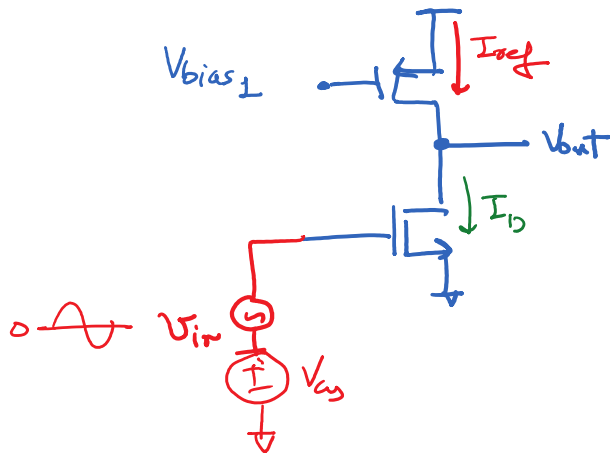


Two current sources trying to set drain bias level

Need to bias the CS stage properly.

DC picture

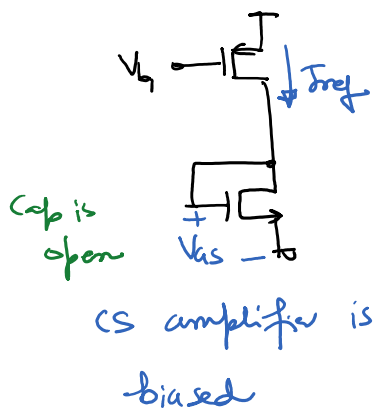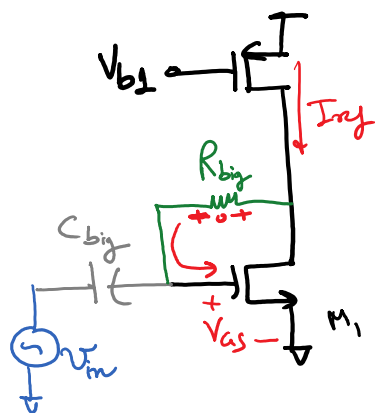




Ac picture

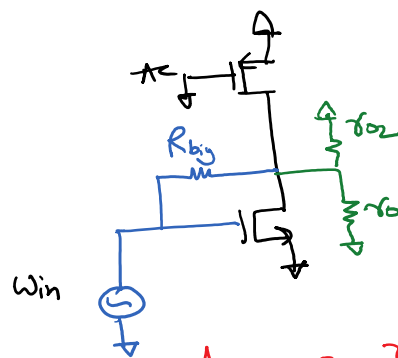

$$A_v = -g_{m1} (r_{o1} \parallel r_{o2} \parallel R_{big})$$

$$\approx -g_{m1} (r_{o1} \parallel r_{o2})$$

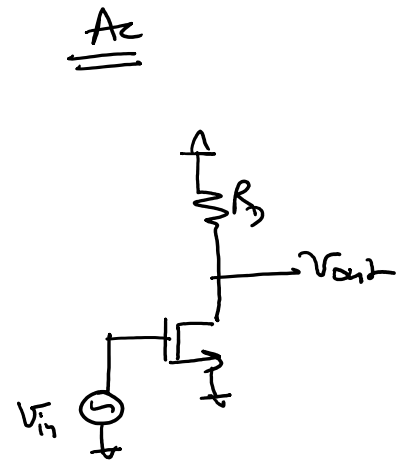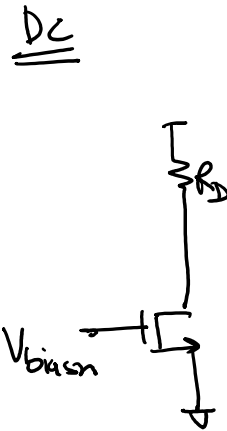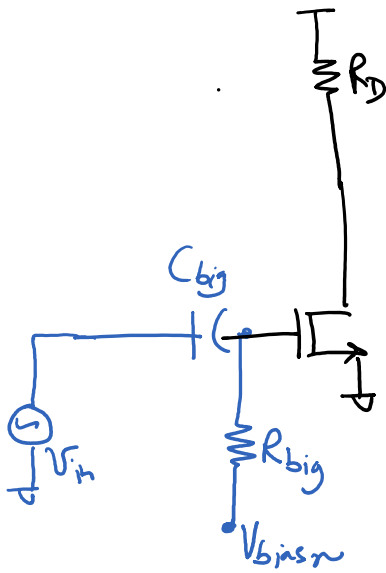
$$\omega_{in} \Rightarrow \omega_x = \frac{1}{R_{big} C_{big}}$$



$$\omega_{in} \gg \omega_x$$

$$\omega_{in} > 10 \cdot \omega_x = \frac{10}{R_{big} C_{big}}$$


Solution

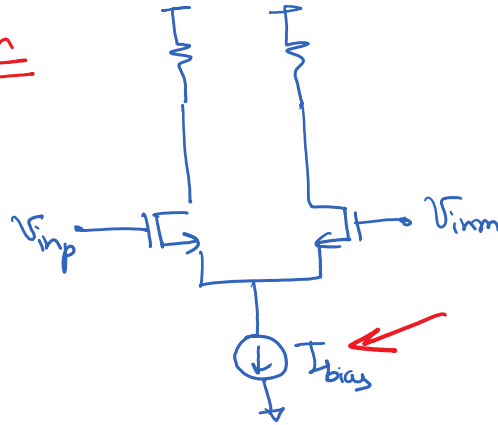

Diff pair input solves
biasing problems
↳ we'll see later in!

Diode Connected Load:

Low-Z node

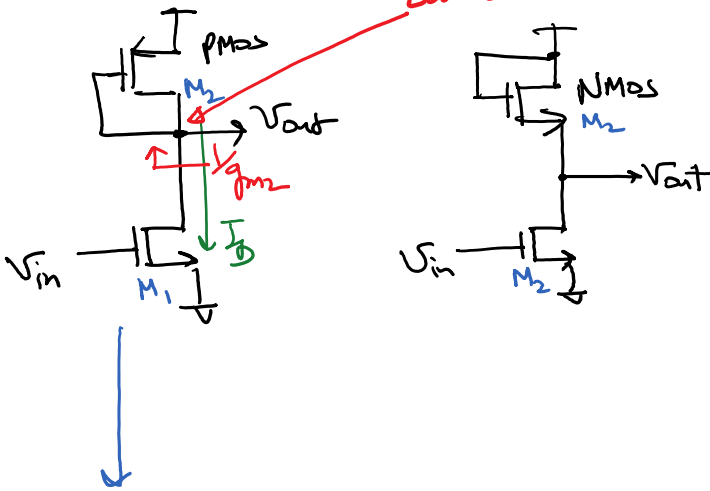


$$A_v = -g_{m1} \cdot \left(\frac{1}{g_{m2}} \parallel r_{o1} \right)$$


$$\approx -\frac{g_{m1}}{g_{m2}}$$

$$= -\frac{\sqrt{2k_{pn} \cdot (W/L)_1 I_D}}{\sqrt{2k_{pp} \cdot (W/L)_2 I_D}} = -\sqrt{\frac{k_{pn}(W/L)_1}{k_{pp}(W/L)_2}}$$


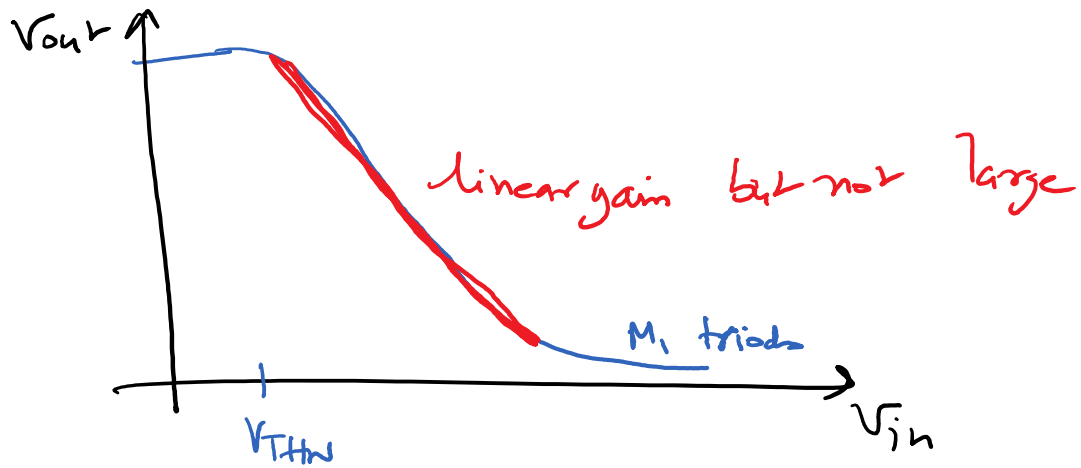
can't get large gains :'
 \rightarrow linear gain



Body effect

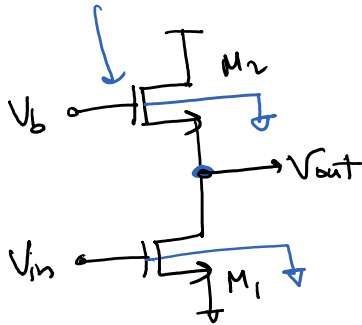

Considering the body-effect

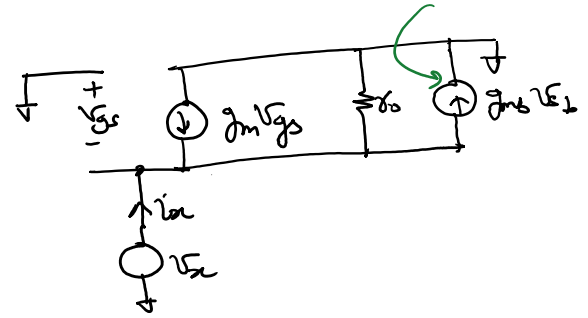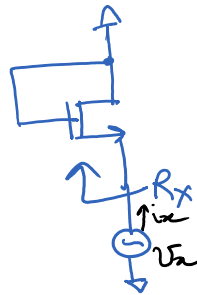

$$(g_m + g_{mb})V_x + \frac{V_x}{R_L} = i_{ix}$$

$$\Rightarrow R_x = \frac{V_x}{i_{ix}} = \frac{1}{g_m + g_{mb} + \frac{1}{R_L}}$$

lower impedance due to body effect $\leq \frac{1}{g_m + g_{mb}} = \frac{1}{g_m(1+\eta)}$

$$g_{mb} = \eta g_m$$



$$\eta < 1$$

$$A_v = -g_{m1} \cdot \frac{1}{g_{m2} + g_{mb2}}$$

$$= -\frac{g_{m1}}{g_{m2}} \cdot \frac{1}{1+\eta}$$

$$= -\sqrt{\frac{(W/L)_1}{(W/L)_2}} \cdot \frac{1}{1+\eta} \quad \leftarrow \text{lower gain due to body-effect}$$

Triode MOSFET as load

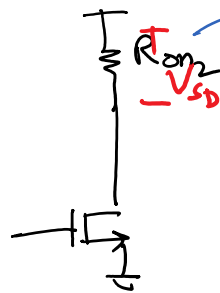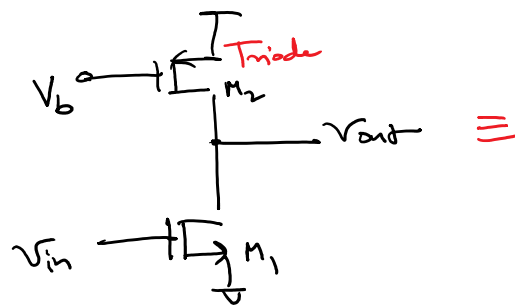


$$K_p \left(\frac{W}{L} \right)_2 (V_{DD} - V_b - |V_{thp}| - V_{SD})$$

non linear resistor
 ↳ distortion
 non linear term when not in deep Triode


CS with Source Degeneration

Tuesday, September 25, 2018 11:52 AM

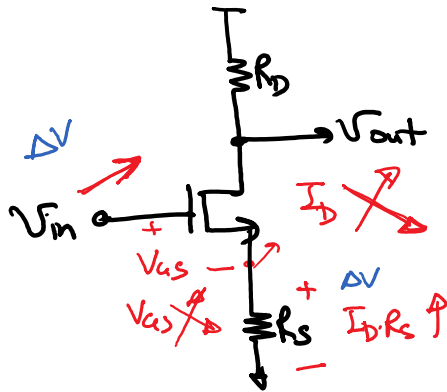

Negative feedback
more linear relationship between
 I_D & V_{in}

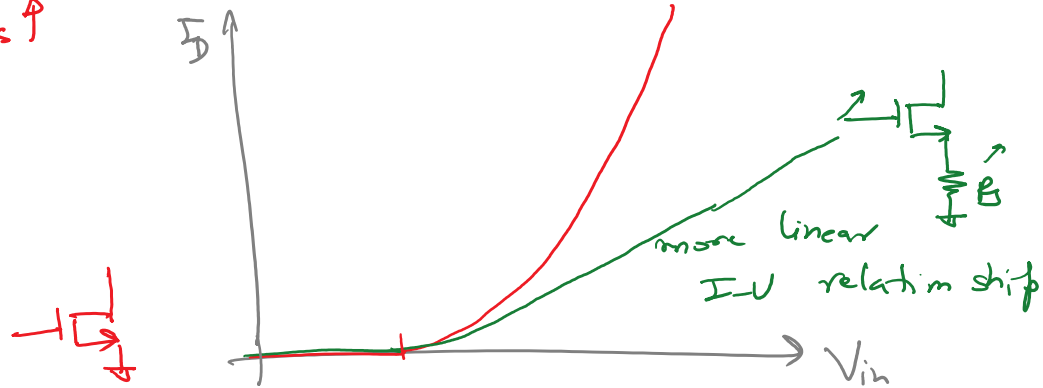→ most of the change in V_{in} is
dropped across R_s .




Application: Linear amplifier stages.

VGA → variable gain amplifier is R_s is programmable

Simplified Analysis ($\lambda=0, g_{mb}=0$)

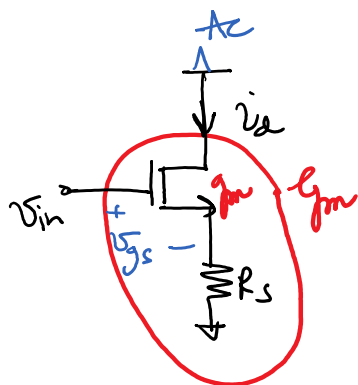channel length mod and body-effect are ignored



$$v_{gs} = v_{in} - v_o R_s \rightarrow ①$$

$$v_o = g_m v_{gs} \rightarrow ② \Leftarrow r_o \rightarrow \infty$$

① & ② combined

$$v_o = g_m (v_{in} - v_o R_s)$$

$$\Rightarrow v_o (1 + g_m R_s) = g_m v_{in}$$

$$\Rightarrow \frac{v_o}{v_{in}} = \boxed{\frac{g_m}{1 + g_m R_s} = g_m}$$

effective trans conductance of CS+SD

$$G_m = \frac{g_m}{1 + g_m R_s} = \frac{1}{\frac{1}{g_m} + R_s} \longrightarrow \approx \frac{1}{R_s} \text{ for } R_s \gg \frac{1}{g_m}$$

$\Rightarrow g_m R_s \gg 1$

* as R_s increases, G_m becomes a weak function of g_m .

↑
can think of as
loop gain



↳ drain current is a linearized function of input voltage

- (+) higher linearity
- (-) lower gain
- (-) higher noise


with $\lambda \neq 0, \gamma \neq 0$

$$g_m = \frac{g_{m0}}{R_s + [1 + (g_m + g_{m0})R_s]r_o}$$

← Razavi

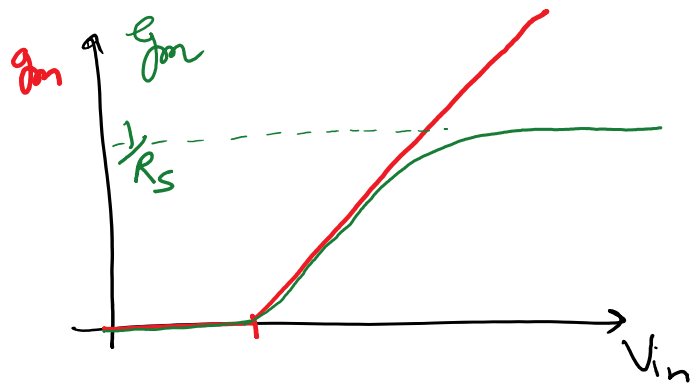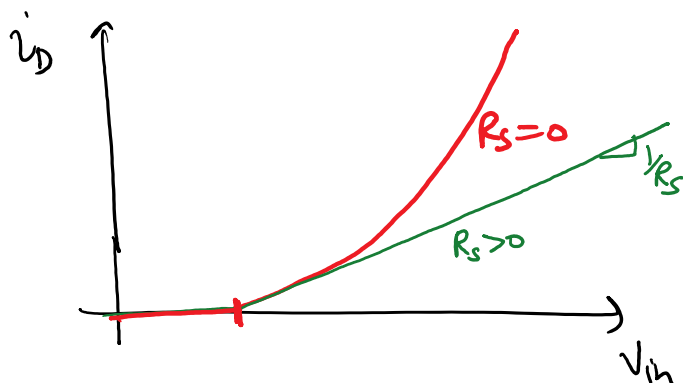

Example:

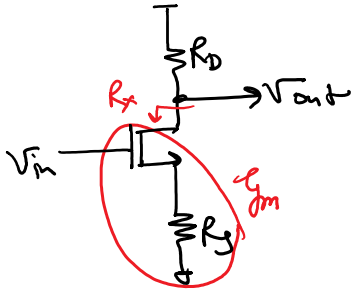


$$A_v = -g_m \cdot R_D \parallel R_x$$

$$= -\frac{g_m}{1 + g_m R_s} \cdot (R_D \parallel R_x)$$

$$= -\frac{g_m R_D}{1 + g_m R_s} = -\frac{R_D}{\frac{1}{g_m} + R_s} \approx -\frac{R_D}{R_s} \quad \text{for } g_m R_s \gg 1$$


$\therefore R_x \gg R_D$

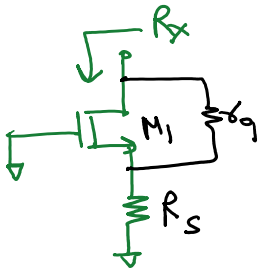

$$R_x = g_{m1} r_{o1} R_s + r_{o1} + R_s$$

$$\approx g_{m1} r_{o1} R_s \ll R_x$$

See Cascode output resistance derivation

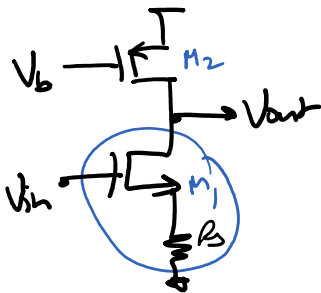

$$A_v = -g_{m2} \cdot r_{o2} \parallel (g_{m1} r_{o1} R_s) \approx -g_{m2} r_{o2}$$

$$= -\frac{g_{m2} r_{o2}}{1 + g_{m1} R_s}$$