
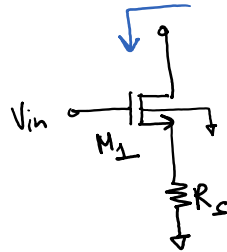


# ECE 511 - Lecture 11

Thursday, September 27, 2018 11:06 AM


Razavi Book

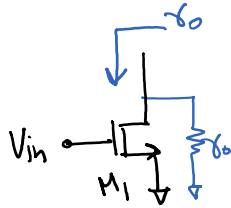

$$R_{out} = [1 + (g_m + g_{mb1}) R_s] r_{o1}$$

$$\approx g_{m1} r_{o1} R_s$$

$M_2$  has body-effect

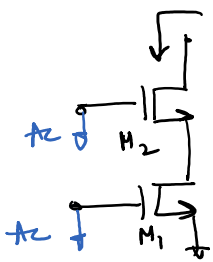



$$R_{out} \approx g_{m2} r_{o2} \cdot r_{o1}$$

~~$$R_{out} = r_{o1} + r_{o2}$$~~

# Source Follower (Common Drain Amplifier)

Thursday, September 27, 2018



11:12 AM

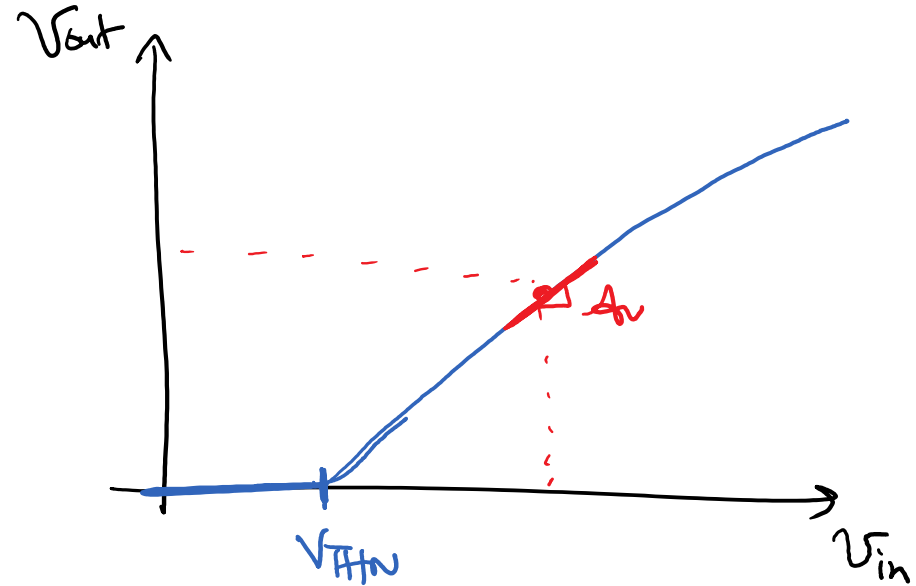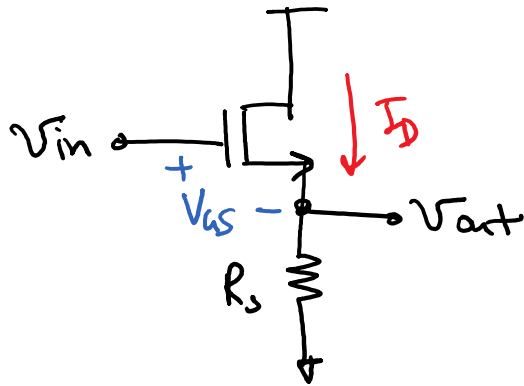

$$V_{out} = V_{in} - V_{GS}$$

→ level shift

Small signal gain:

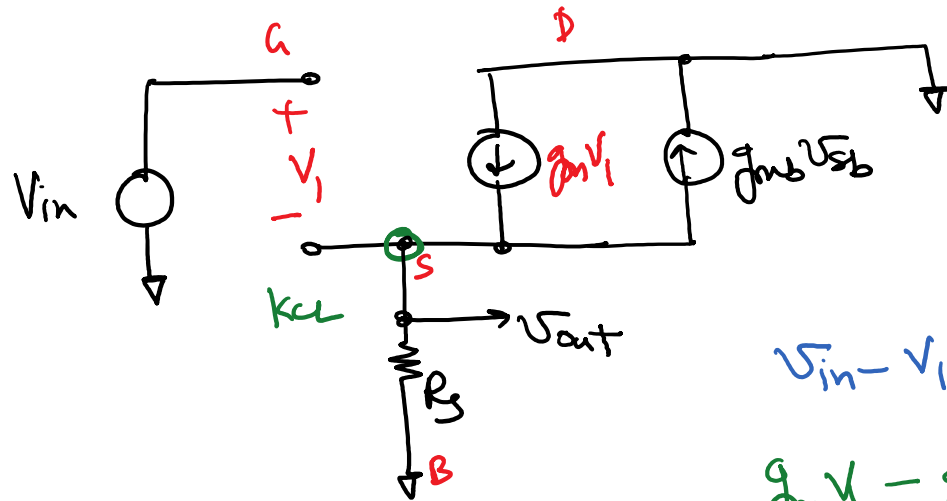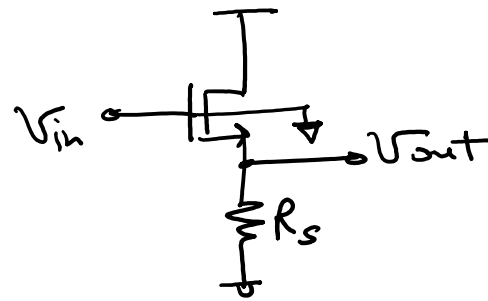

$$V_{sb} = V_{out}$$

$$V_{in} - V_1 = V_{out} \rightarrow \textcircled{1}$$

$$g_m V_1 - g_{m_b} V_{out} = \frac{V_{out}}{R_s} \rightarrow \textcircled{2}$$

$$\Rightarrow g_m (V_{in} - V_{out}) - g_{m_b} V_{out} = \frac{V_{out}}{R_s}$$


$$\Rightarrow V_{out} \left[ (g_m + g_{m_b}) + \frac{1}{R_s} \right] = g_m V_{in}$$

$$A_v = \frac{V_{out}}{V_{in}} = \frac{g_m R_s}{1 + (g_m + g_{m_b}) R_s}$$



$$A_v = \frac{v_{out}}{v_{in}} = \frac{v_{in}}{1 + (g_m + g_{mb})R_s}$$


$$A_v = \frac{g_{mR_S}}{1 + (\eta + 1)g_{mR_S}} = \frac{1}{(\eta + 1) + \frac{1}{g_{mR_S}}} \approx \frac{1}{\eta + 1} \quad \text{if } g_{mR_S} \gg 1$$

$$\Rightarrow A_v < 1$$

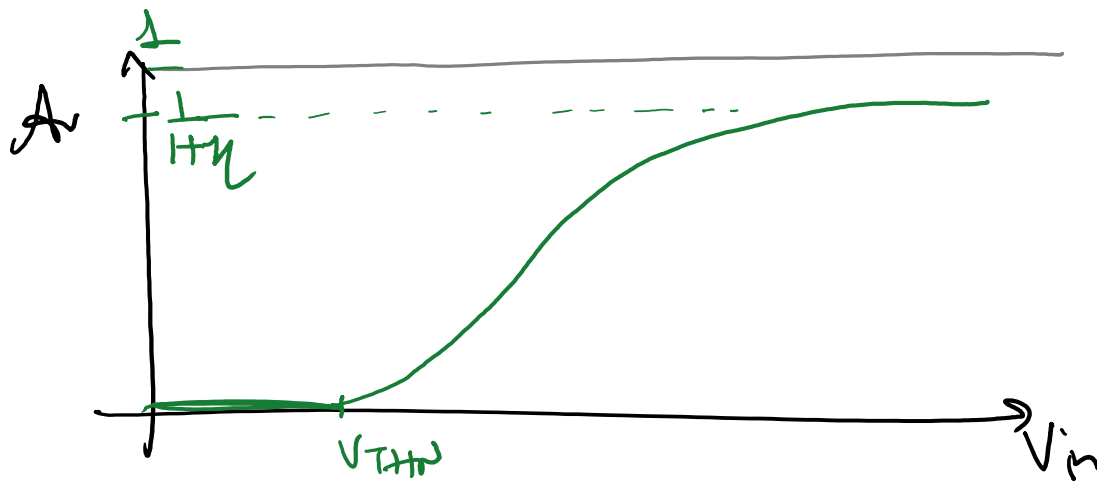

Thursday, September 27, 2018 11:25 AM

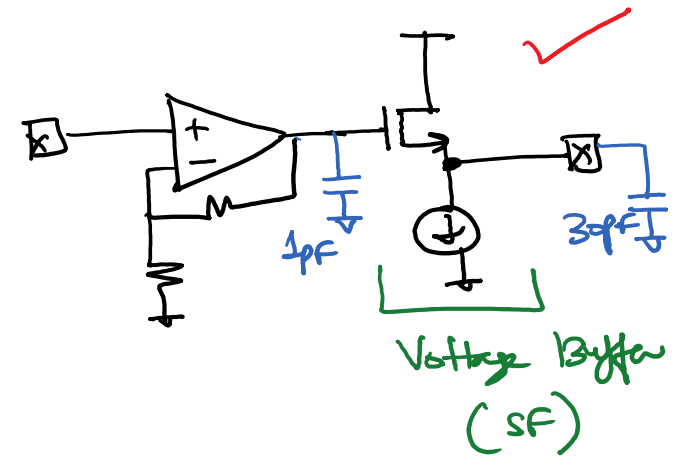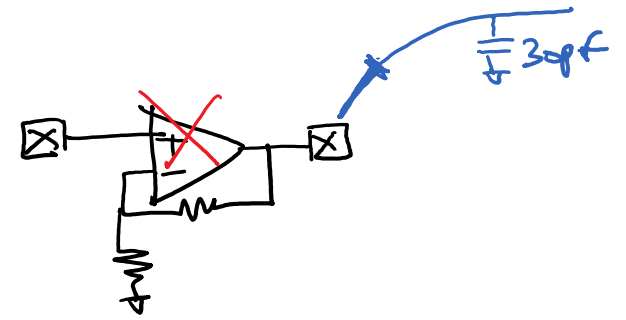

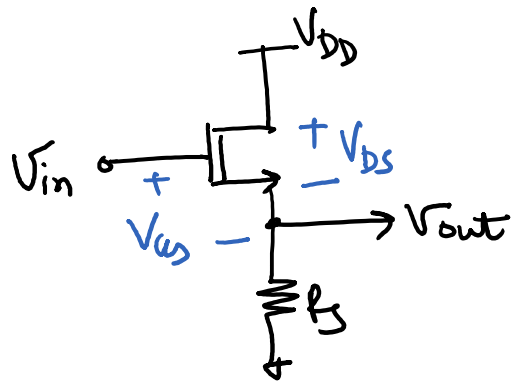

$$\begin{aligned}
 V_{DS} &= V_{DD} - V_{out} \\
 &= V_{DD} - (V_{in} - V_{as}) \\
 &= V_{DD} - V_{in} + V_{as} \rightarrow \textcircled{1}
 \end{aligned}$$


for SAT:  $V_{DS} > V_{DS,sat}$

$$V_{DD} - V_{in} + \cancel{V_{as}} > \cancel{V_{as}} - V_{THN}$$


$$V_{DD} - V_{in} > -V_{THN}$$

$$\Rightarrow V_{in} \leq V_{DD} + V_{THN}$$




$M_1$  never triodes!

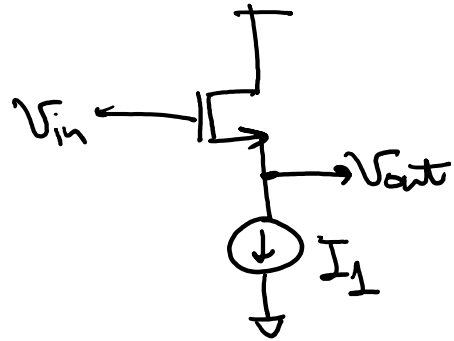

NMOS SF


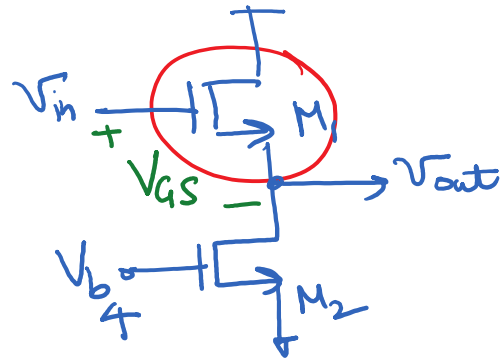


PMOS SF

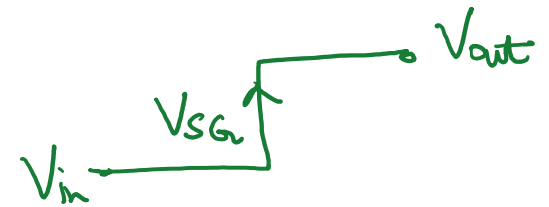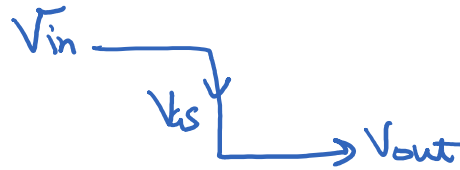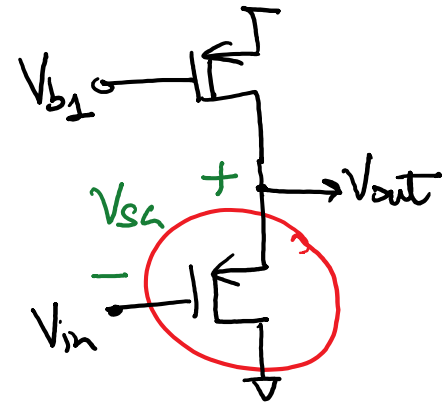

Level shifter



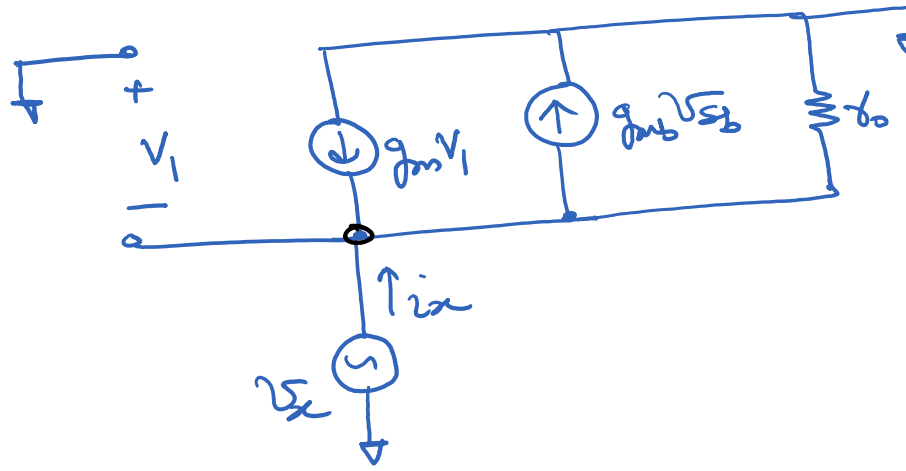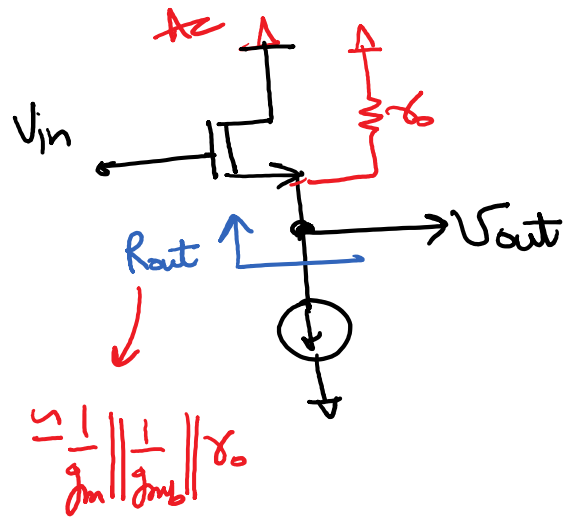


KCL:



$$i_x - g_m V_x - g_{m_b} V_x + \frac{V_x}{r_o} = 0$$

$$R_{out} = \frac{1}{g_m + g_{m_b} + r_o^{-1}} = \frac{1}{g_m} \parallel \frac{1}{g_{m_b}} \parallel r_o \approx \frac{1}{g_m}$$


resistance looking into the source

\* low-impedance output

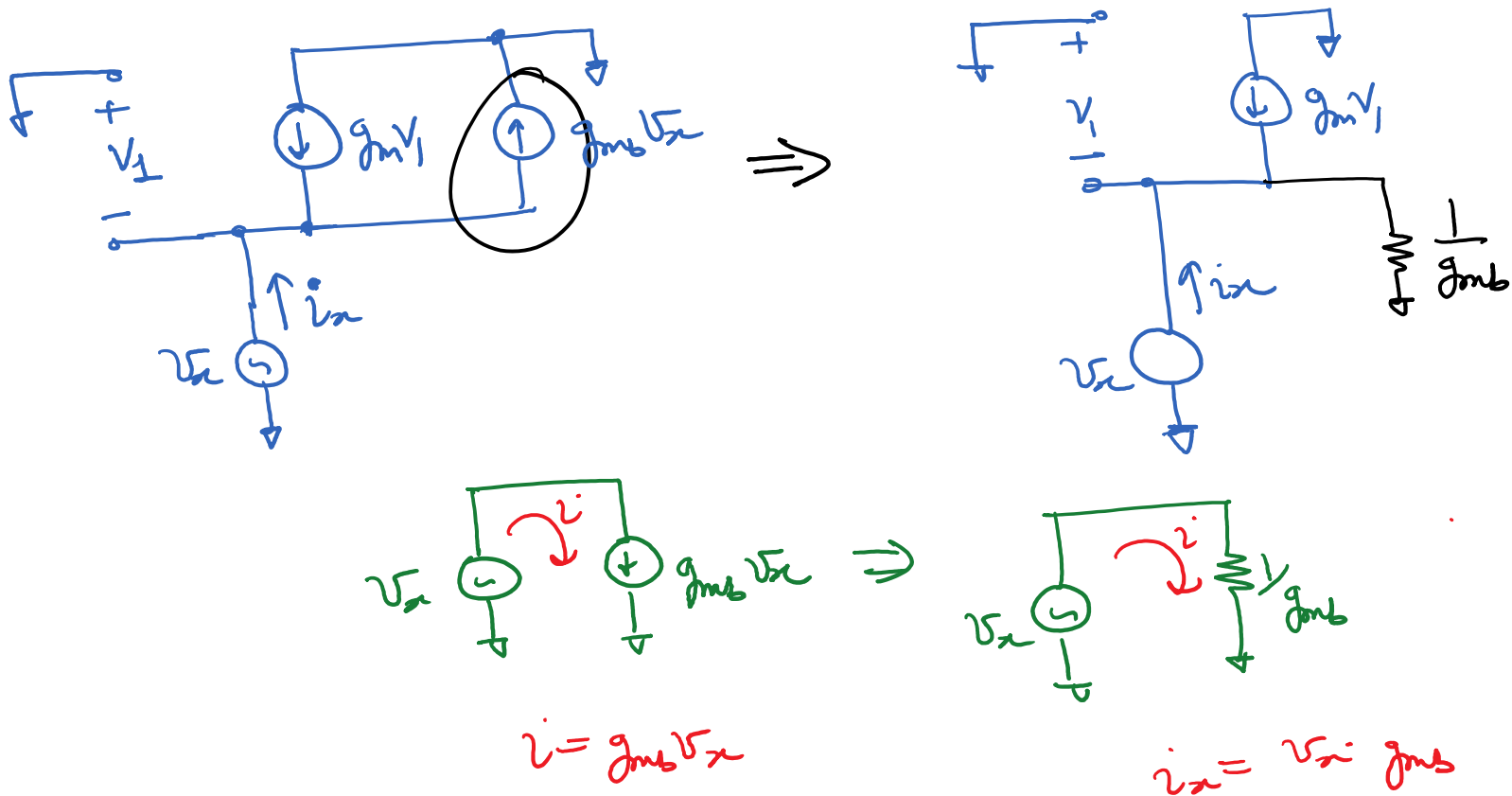


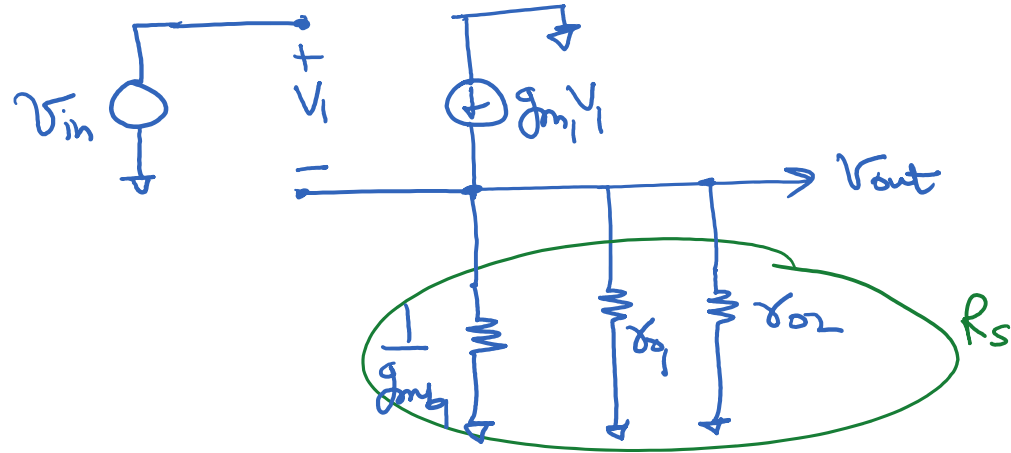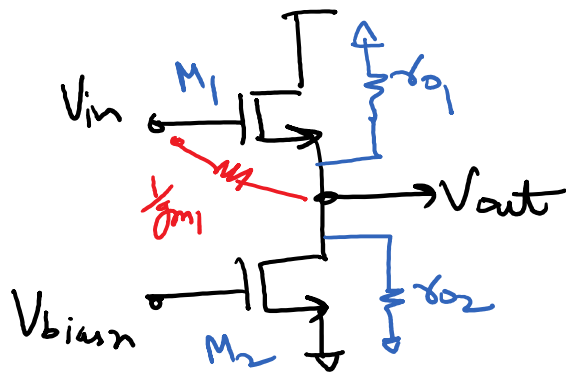
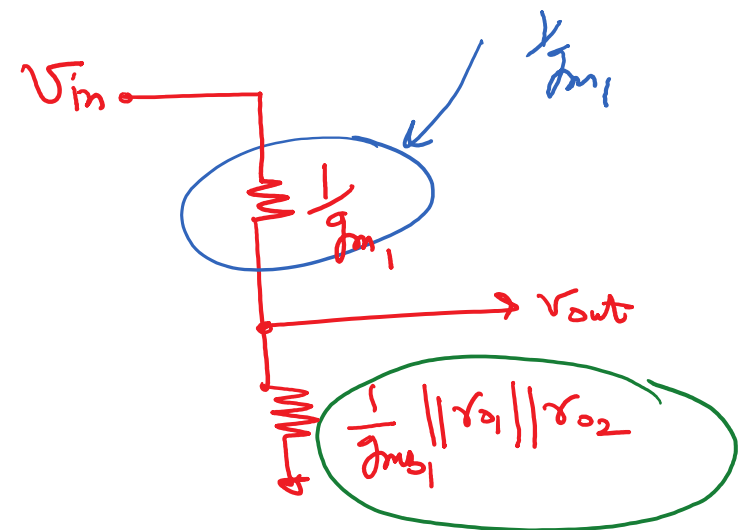
$$\frac{V_{out}}{V_{in}} = \frac{\frac{1}{g_{m2}} \parallel r_{o1} \parallel r_{o2}}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}} \parallel r_{o1} \parallel r_{o2}}$$



Resistance connected to the source


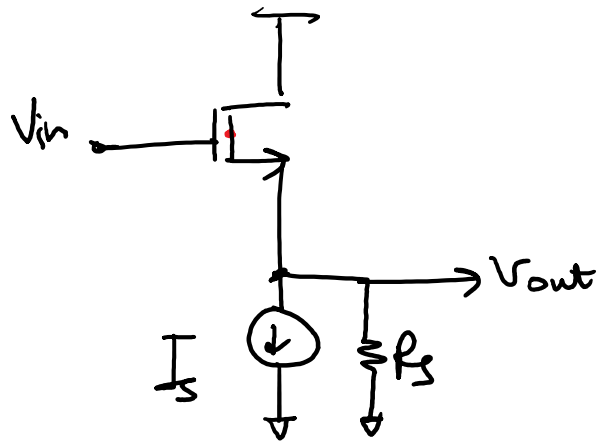


$$A_v = \frac{R_S \parallel \frac{1}{g_{m2}} \parallel r_{o1}}{\frac{1}{g_{m1}} + R_S \parallel \frac{1}{g_{m2}} \parallel r_{o1}}$$

ignoring  $g_{m2}$  we would have gotten

$$A_v = \frac{R_S \parallel r_{o1}}{\frac{1}{g_{m1}} + R_S \parallel r_{o1}}$$

X

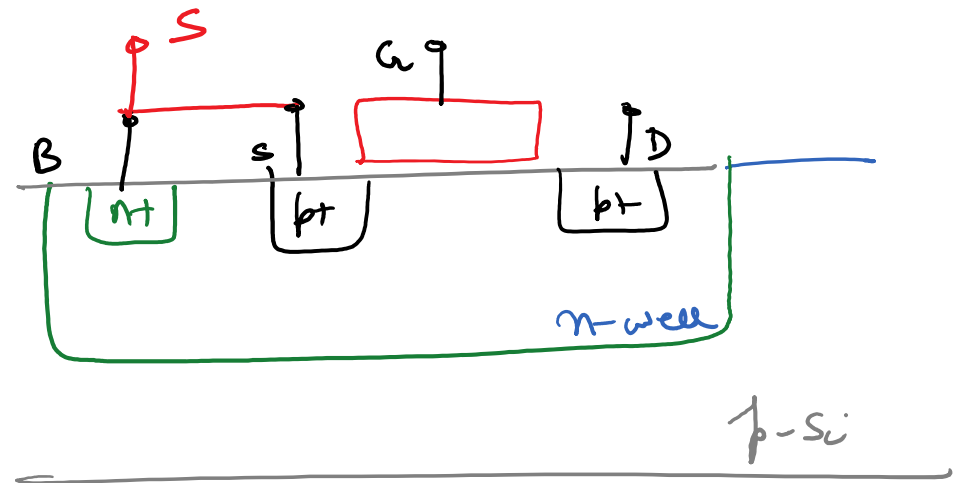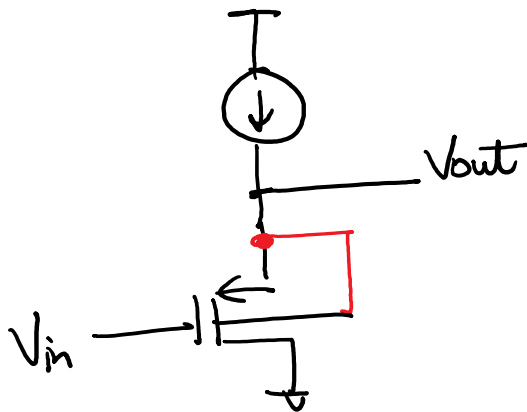


MOSFET offers flexibility of eliminating body effect

# Voltage amplifier

Thursday, September 27, 2018

11:56 AM

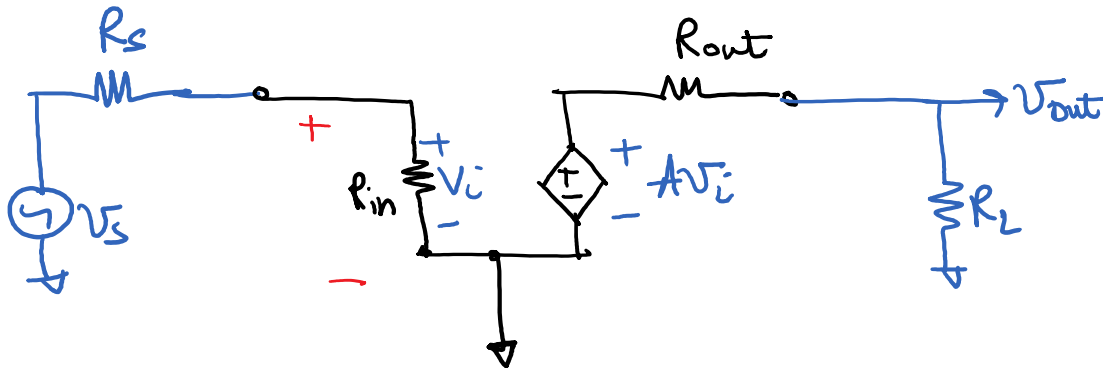

$$V_{out} \approx A V_i$$


$$R_{in} \rightarrow \infty$$

$$R_{out} \rightarrow 0$$

$$V_i = V_s$$

$$SF \rightarrow R_{out} \approx \frac{1}{g_m} \Rightarrow \text{low-}Z \text{ output}$$

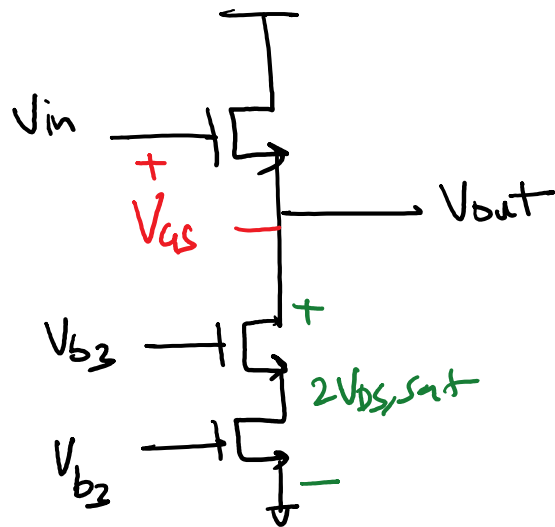most of the voltage is transferred to the load




Issue with SF as a buffer

DC level shift

⇒ limited input swing

$$V_{in} > V_{gs} + 2V_{DS,sat}$$

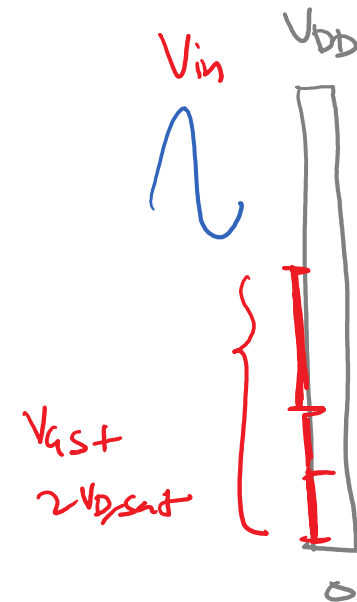

⇒ reduced V<sub>OV</sub> headroom

