
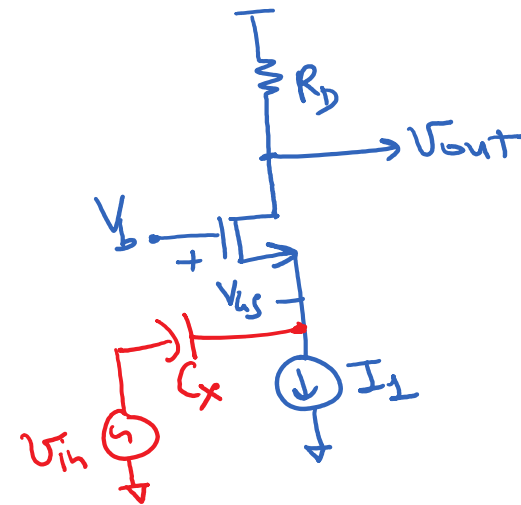
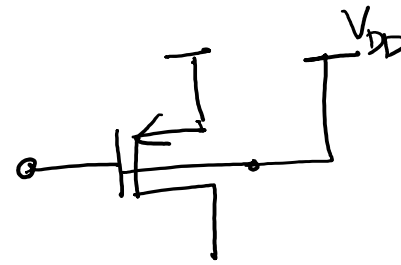


# ECE S11 - Lecture 12



Tuesday, October 2, 2018

11:01 AM

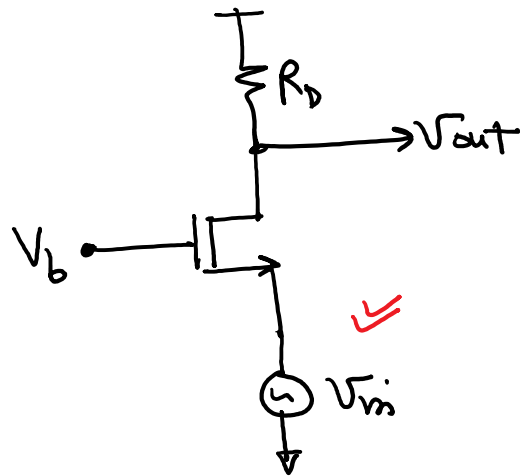



# ECE S11- Lecture 12

Tuesday, October 2, 2018 11:09 AM

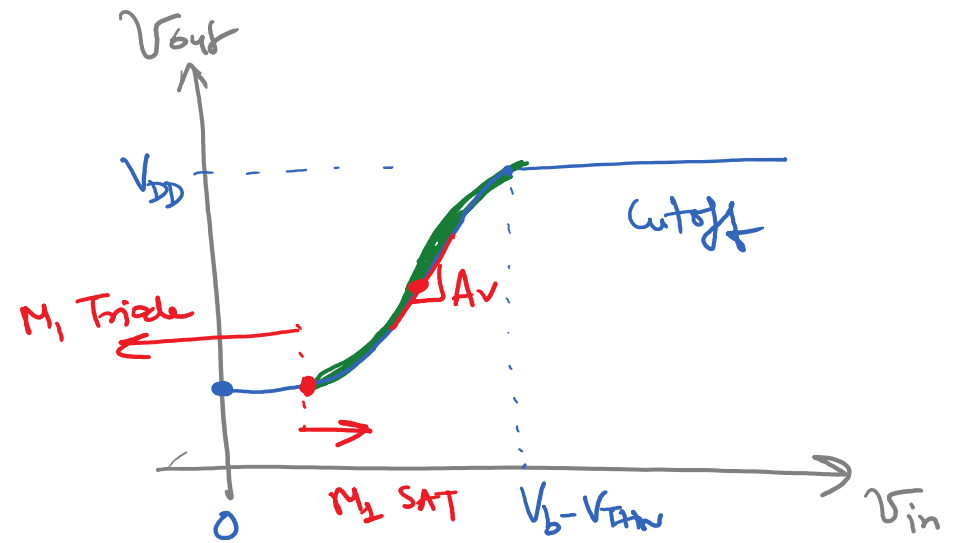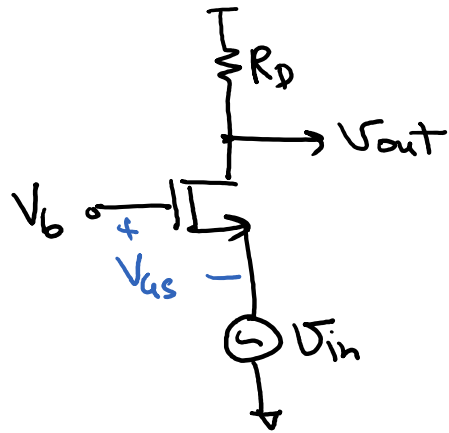

# Small signal analysis:

Tuesday, October 2, 2018 11:14 AM

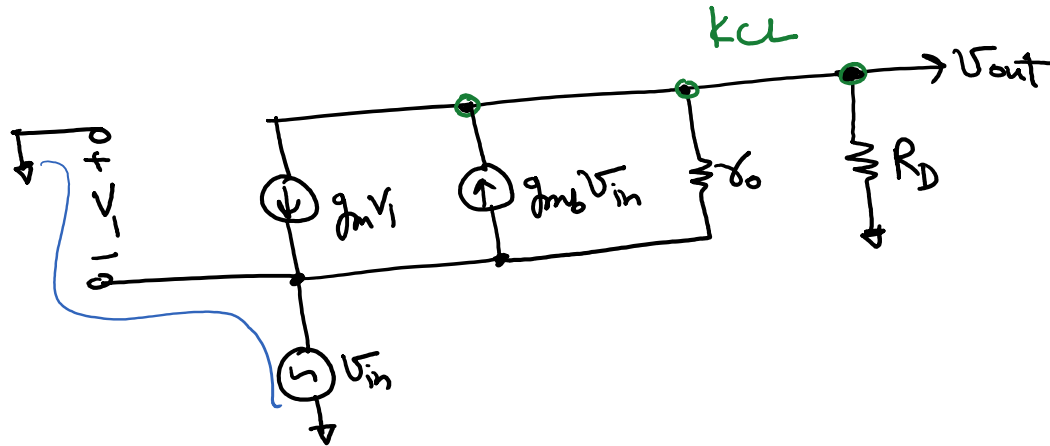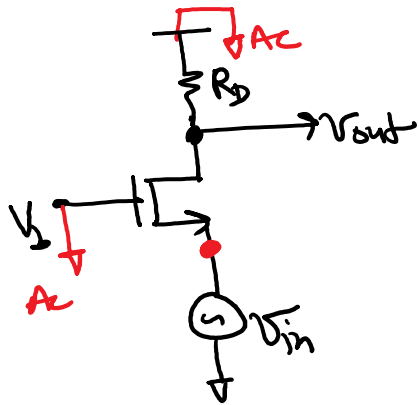

$$V_1 = -V_{in} \rightarrow \textcircled{1}$$

$$-g_m V_1 + g_{mb} V_{in} - \frac{(V_{out} - V_{in})}{r_o} - \frac{V_{out}}{R_D} = 0$$

$$\Rightarrow V_{in} \left[ \frac{1}{r_o} + (g_m + g_{mb}) \right] = \frac{V_{out}}{r_o \parallel R_D}$$

$$\Rightarrow A_v = \frac{V_{out}}{V_{in}} = \frac{(g_m + g_{mb}) \cancel{r_o} + \cancel{1}}{\cancel{R_D} + \cancel{r_o}} \cdot R_D$$

$$A_v = +(\eta + 1)g_m R_D$$


$$g_{mb} = \eta g_m$$

$$\therefore r_o \gg R_D$$

$$g_m r_o \gg 1$$


# ECE 511 - Lecture 12

Tuesday, October 2, 2018 11:20 AM

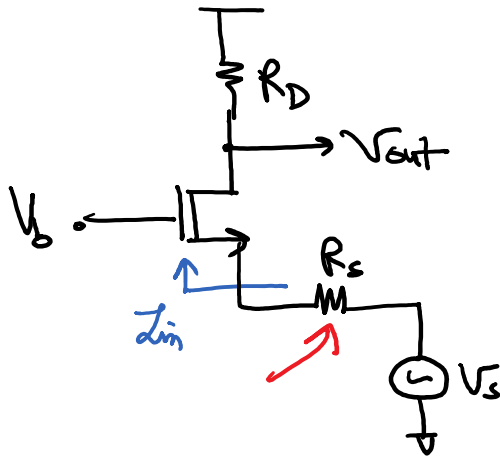


$$A_v = \frac{V_{out}}{V_{in}} = \frac{(g_m + g_{mb})r_o + 1}{r_o + (g_m + g_{mb})r_o R_S + R_S + R_D} \cdot R_D$$

See Razavi Book for details

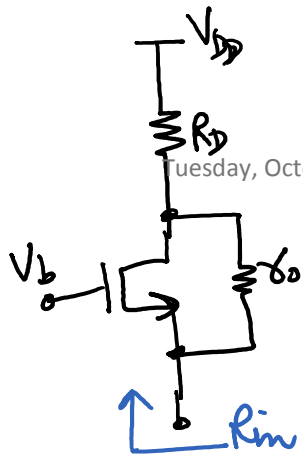

Tuesday, October 2, 2018 11:23 AM

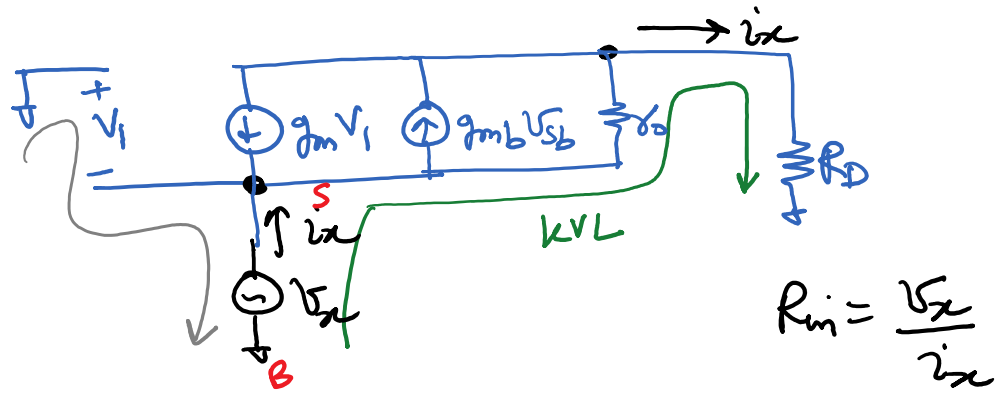

$$R_{in} = \frac{V_x}{i_x}$$

$$\Rightarrow V_1 = -V_x \quad \text{①}$$

Current thru  $\gamma_0 \Rightarrow i_x + g_m V_1 - g_{mb} V_x = i_{\gamma_0}$

$$\Rightarrow i_{\gamma_0} = i_x - (g_m + g_{mb}) V_x \quad \text{②}$$

\* Adding up voltages across  $\gamma_0$  and  $R_D$ .

$$V_x = R_D i_x + \gamma_0 \cdot i_{\gamma_0} = R_D i_x + i_x \gamma_0 - (g_m + g_{mb}) \gamma_0 V_x$$


$$\Rightarrow V_x [1 + (g_m + g_{mb}) \gamma_0] = (R_D + \gamma_0) i_x$$

$$\Rightarrow R_{in} = \frac{V_x}{i_x} = \frac{R_D + \gamma_0}{1 + (g_m + g_{mb}) \gamma_0} = \boxed{\frac{R_D}{(g_m + g_{mb}) \gamma_0} + \frac{1}{(g_m + g_{mb})}} \quad \text{Rin}$$

$$R_{in} \approx \frac{R_D}{(g_m + g_{m_b})r_o} + \frac{1}{(g_m + g_{m_b})}$$

Case A:  $R_D = 0$

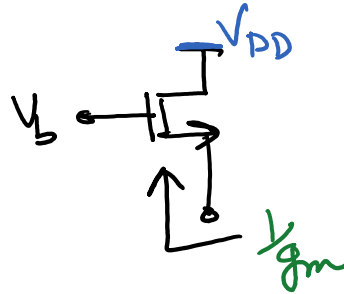
$$R_{in} = \frac{1}{g_m + g_{m_b}} \approx \frac{1}{g_m}$$



Case B:

$$R_D \leq r_o$$
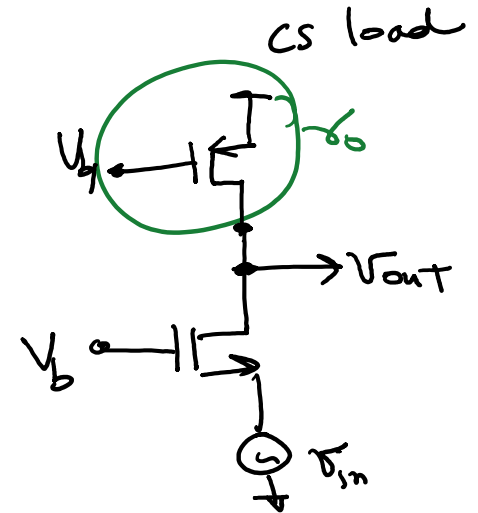
$$R_{in} = \frac{2}{(g_m + g_{m_b})} \approx \frac{1}{g_m}$$



Case C:  $R_D = g_m r_o^2$

$$R_{in} = \frac{g_m r_o^2}{(g_m + g_{m_b})r_o} + \frac{1}{(g_m + g_{m_b})}$$

$$\approx r_o$$

PMOS Cascode current source load

$$\therefore r_o \gg \frac{1}{g_m}$$



# Case D

Tuesday, October 2, 2018

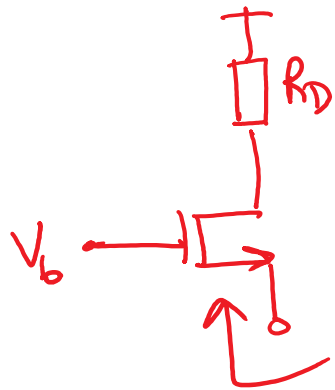
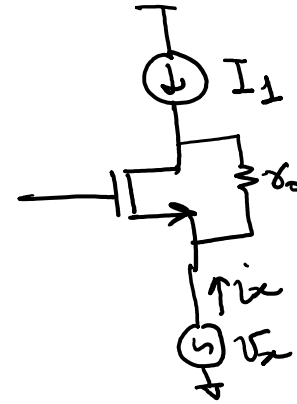
11:38 AM

$$R_D \rightarrow \infty$$

$$R_{in} = \frac{R_D}{(g_m + g_{m_b}) r_o} \rightarrow \infty$$



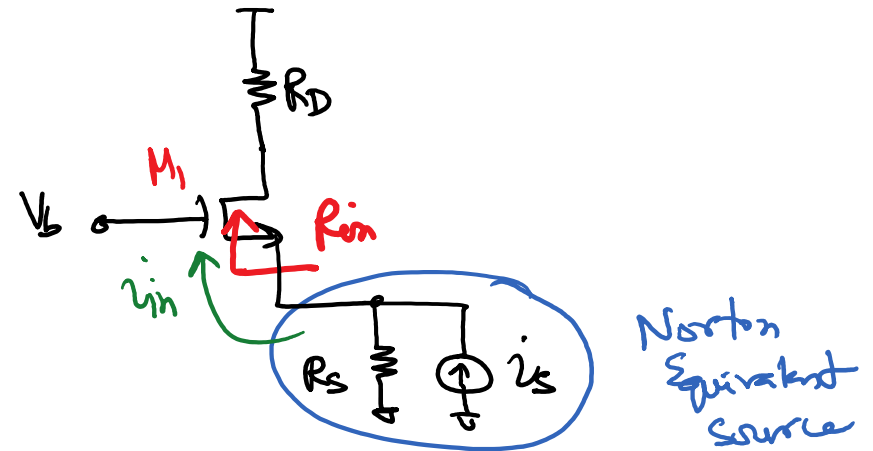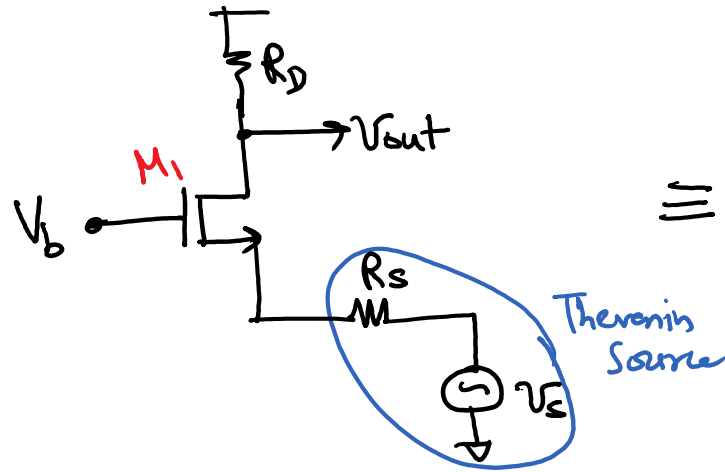$R_{in}$  is  $\approx 1/g_m$  in only special cases  
 $R_D \leq r_o$



$i_s$  is current divided between  $R_s$  and  $R_{in}$

$$v_{in} = i_s \cdot \left( \frac{R_s}{R_{in} + R_s} \right)$$

for most of the current to enter  $M_2$

$$\Rightarrow R_{in} \rightarrow 0$$

if  $R_D \leq r_o \Rightarrow$  current division between  $g_m$  &  $R_s$

T.L. + Impedance is low  $\Rightarrow$  CG is rather a better current



amplifier than a voltage amplifier


# Summary :

Tuesday, October 2, 2018 11:47 AM

Amplifier	Gain	$Z_{in}$	$Z_{out}$	Application
CS	Large	$\infty$	Moderate ( $r_o$ )	Voltage Amplifier
CS + SD	Moderate	$\infty$	High ( $g_m r_o R_s$ )	Linear Voltage Amplifier
CD / SF	low $< 1$	$\infty$	Low ( $1/g_m$ )	Voltage Buffer
CG	Large	Low	Moderate/High ( $r_o$ )	Current buffer or amplifier

# Cascode Amplifier:

Tuesday, October 2, 2018 11:52 AM

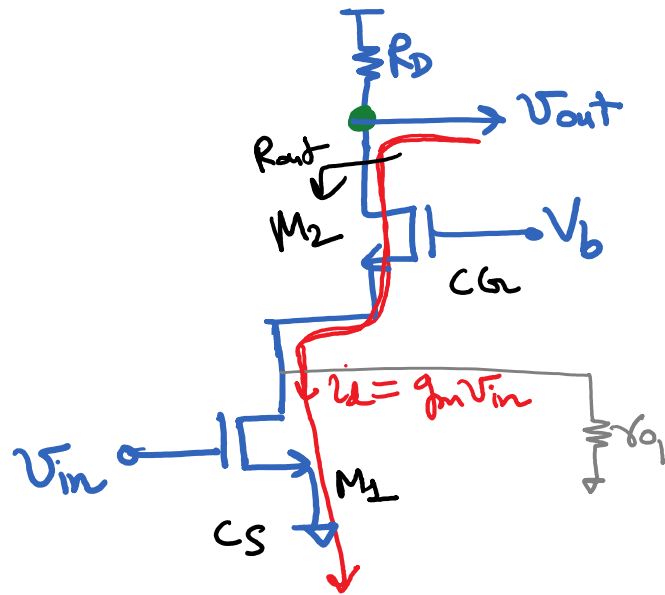

$$R_D \leq r_o$$

$i_d$  sees current division  
between  $\frac{1}{g_{m2}}$  &  $r_{o1}$

Lets say most of  $i_d$   
goes into  $M_2$   
 $\Rightarrow \frac{1}{g_{m2}} \ll r_{o1}$

$$R_{out} = g_{m2} r_{o2} r_{o1}$$

$$V_{out} = -i_d (R_D \parallel R_{out}) = -g_m V_{in} (R_D \parallel R_{out})$$

$$A_v = (-g_m) R_{out} = - (g_m r_o)^2$$

$\downarrow$   
 $(g_m r_o^2)$

\* Need a better analysis method

$$\text{if } R_D \rightarrow \infty$$

Lemma: In a linear circuit voltage gain  $= -g_m R_{out}$

Tuesday, October 2, 2018 11:59 AM

where




$g_m \Rightarrow$  transconductance of the circuit when the output is shorted to ground (output short circuit transconductance)

$R_{out} \Rightarrow$  output resistance of the circuit when the input is set to zero.

\* See the proof in Razavi Book

Example:  $C_s$

Tuesday, October 2, 2018 12:03 PM

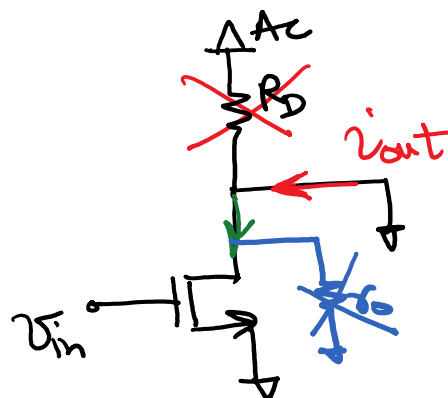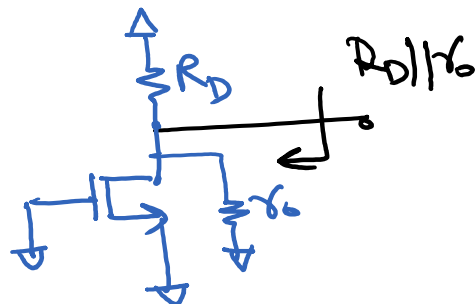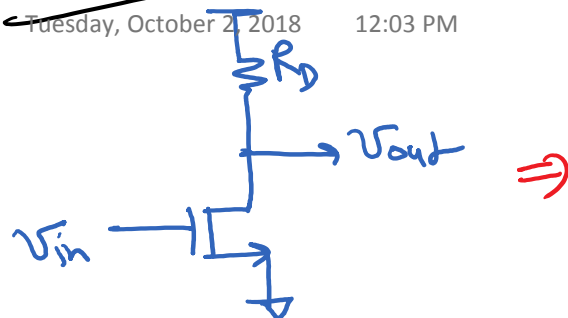

$$i_{out} = i_d = g_m V_{in}$$



$$g_m = \frac{i_{out}}{V_{in}} = g_m$$

$$A_v = -g_m R_{out}$$


$$= -g_m (R_D || r_o)$$

# ECE S11 - Lecture 12

Tuesday, October 2, 2018 12:05 PM

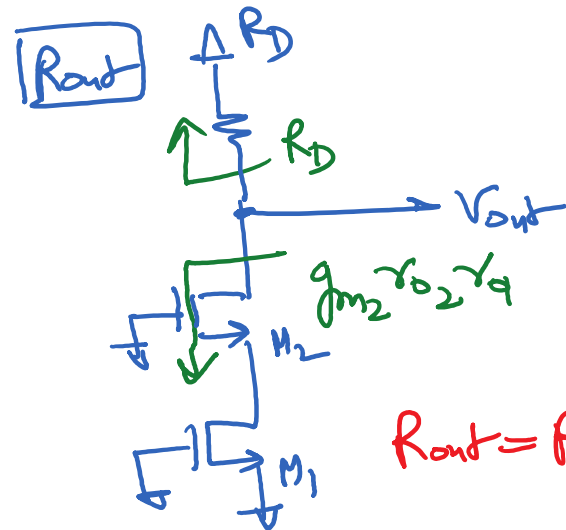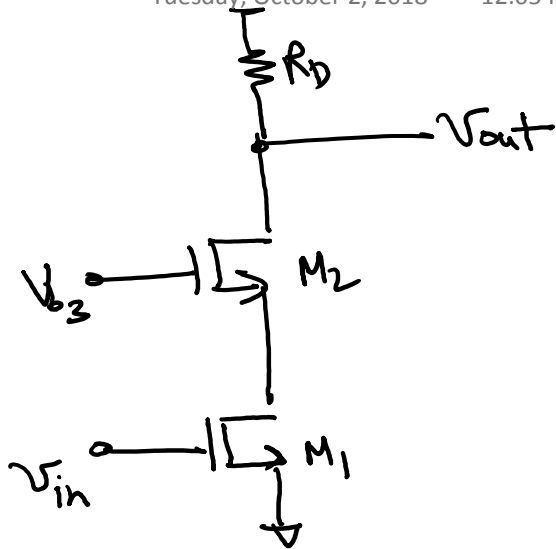
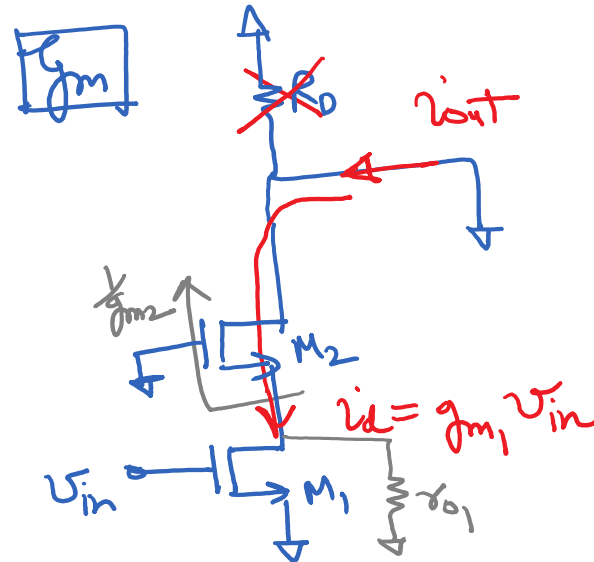
$$R_{out} = R_D \parallel (g_{m2} r_{o2} r_{o1})$$



$$i_{out} = i_d = g_{m1} V_{in}$$

$$\Rightarrow g_m = g_{m1}$$


$$A_v = -g_m R_{out} = -g_{m1} R_D \parallel (g_{m2} r_{o2} r_{o1})$$

$$\approx -g_{m1} R_D$$

Approximation :

$$\frac{1}{g_{m2}} \ll r_{o1}$$

\* M2 acts as a current buffer

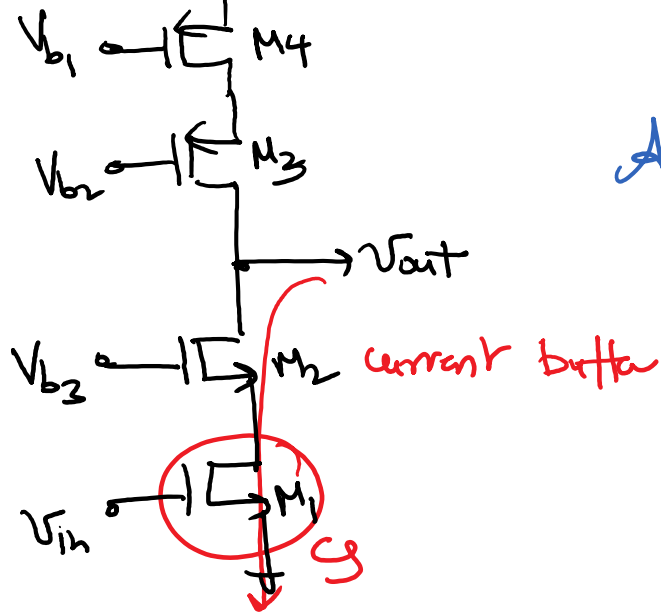

$$A_v = -g_{m1} R_{out}$$

$\downarrow g_{m1}$ 
 $\downarrow R_{pce0} \parallel R_{nca3}$

$$= g_{m1} \delta_3 \delta_4$$

$$= g_{m1} \delta_3 \delta_4$$

$$= g_{m1} \delta_3 \delta_4$$

\* Biasing is not shown  
only conceptual

$$A_v = -g_{m1} \cdot [(g_{m1} \delta_n^2) \parallel (g_{mp} \delta_p^2)]$$

$$= -g_{m1} \cdot \frac{g_{m1} \delta_0^2}{2} = -\frac{(g_{m1} \delta_0)^2}{2}$$

all transistors  
have same  
 $g_{m1} \delta_0$