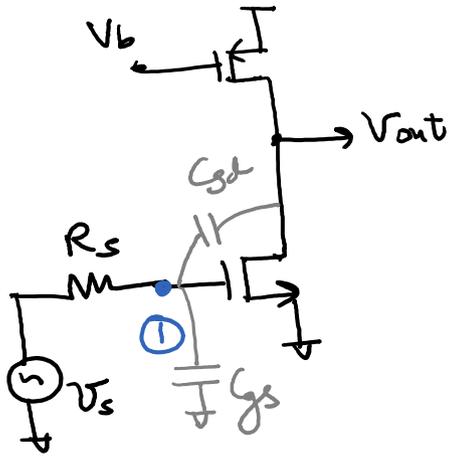


# ECE SIS- Lecture 17

Thursday, October 18, 2018 11:01 AM

$$D(s) = \frac{s^2}{\omega_{p1}\omega_{p2}} + \left(\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}}\right)s + 1$$

→ very small



$$\frac{V_{out}}{V_{in}}(s) = \frac{(sC_{gd} - g_{m1})R_o}{R_s R_o \left[ s^2 + \left[ R_s(1 + g_{m1}R_o)C_{gd} + R_s C_{gs} + R_o(C_{gd} + C_{cb}) \right] s + \xi \right]}$$

$$\xi = C_{gs}C_{gd} + C_{gs}C_o + C_{gd}C_o$$

$$\omega_{p1} \Rightarrow \text{coeff of 's'}$$

$$= \frac{1}{R_s(1 + g_{m1}R_o)C_{gd} + R_s C_{gs} + R_o(C_{gd} + C_o)}$$

2<sup>nd</sup> pole:      coeff of  $s^2$  is  $\frac{1}{\omega_{p1}\omega_{p2}}$

$$\omega_{p2} = \frac{1}{\omega_{p1}} \cdot \frac{1}{R_s R_o \xi}$$

$$\Rightarrow \omega_{p2} = \frac{1}{\omega_{p1}} \times \frac{1}{R_s R_o [C_{gs1} C_{gd1} + C_{gs1} C_o + C_{gd1} C_o]}$$

$$= \frac{R_s (1 + g_m R_o) C_{gd1} + \boxed{R_s C_{gs1}} + R_o (C_{gd1} + C_o)}{R_s R_o [C_{gs1} C_{gd1} + C_{gs1} C_o + C_{gd1} C_o]}$$

\* ~~if~~  $C_{gs1} \Rightarrow (1 + g_m R_o) C_{gd1} + \frac{R_o}{R_s} (C_{gd1} + C_o)$

$$\omega_{p2} \approx \frac{1}{R_o (C_{gd1} + C_o)}$$

← Same as  $\omega_{out}$  in the Miller approximation

Valid only when  $C_{gs1}$  dominates the response, otherwise not.

# Pole Splitting

Thursday, October 18, 2018 11:14 AM

$$\omega_z = + \frac{g_{m1}}{C_{gd1}} \quad (\text{RHP zero})$$

$$\omega_{p1} = \frac{1}{R_s [(1 + |A_v|) C_c + C_{gs1}] + R_o (C_c + C_o)}$$


$$\omega_{p2} = \frac{R_s (1 + g_{m1} R_o) C_c + R_s C_{gs1} + R_o (C_c + C_o)}{R_s R_o [C_{gs1} C_c + C_{gs1} C_o + C_c C_o]}$$

\* For  $C_c = 0$  and a large  $C_o$

$$\omega_{p1} \approx \frac{1}{R_s C_{gs1} + R_o C_o}$$

$$\omega_{p2} \approx \frac{R_s C_{gs1} + R_o C_o}{R_s R_o C_{gs1} C_o} = \frac{1}{R_o C_o} + \frac{1}{R_s C_{gs1}}$$

$$\approx \frac{1}{R_o C_o}$$

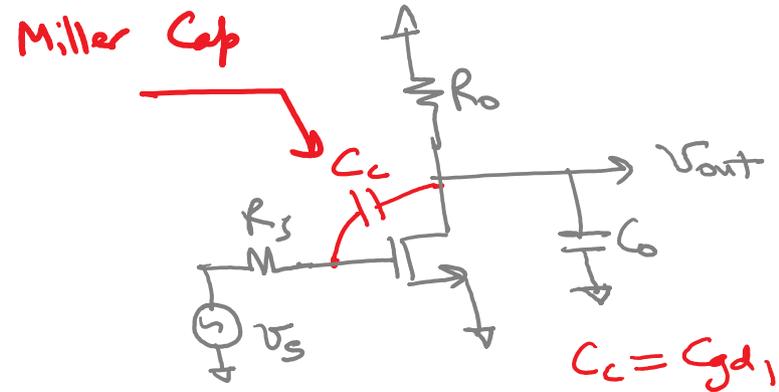

Now, increase  $C_c$

$$C_c \gg C_{gs1}$$

$$\omega_{p1} \approx \frac{1}{R_s (1 + |A_v|) C_c + R_o (C_c + C_o)}$$

$$\omega_{p2} \approx \frac{\cancel{R_s} (1 + \overbrace{g_{m1} R_o}) \cancel{C_c} + \cancel{R_o} (C_c + C_o)}{\cancel{R_s} \cancel{R_o} \cancel{C_c} [C_o + C_{gs1}]}$$

→ very small

$$\approx \frac{g_{m1}}{C_o + C_{gs1}}$$

$C_c = 0$

$C_c \rightarrow C_{gs1}$

$\omega_{p1} \approx \frac{1}{R_s C_{gs1} + R_o C_o}$

$\frac{1}{R_s(1+|A|)C_c + R_o[C_c + C_o]}$


$\omega_{p2} \approx \frac{1}{R_o C_o}$

$\approx \frac{g_{m1}}{C_c + C_{gs1}} \approx \frac{g_{m1}}{C_o} = g_{m1} R_o \left[ \frac{1}{R_o C_o} \right]$

$\omega_z \approx \frac{g_{m1}}{C_{gs1}}$


$\frac{g_{m1}}{C_c}$

"Miller Compensation"

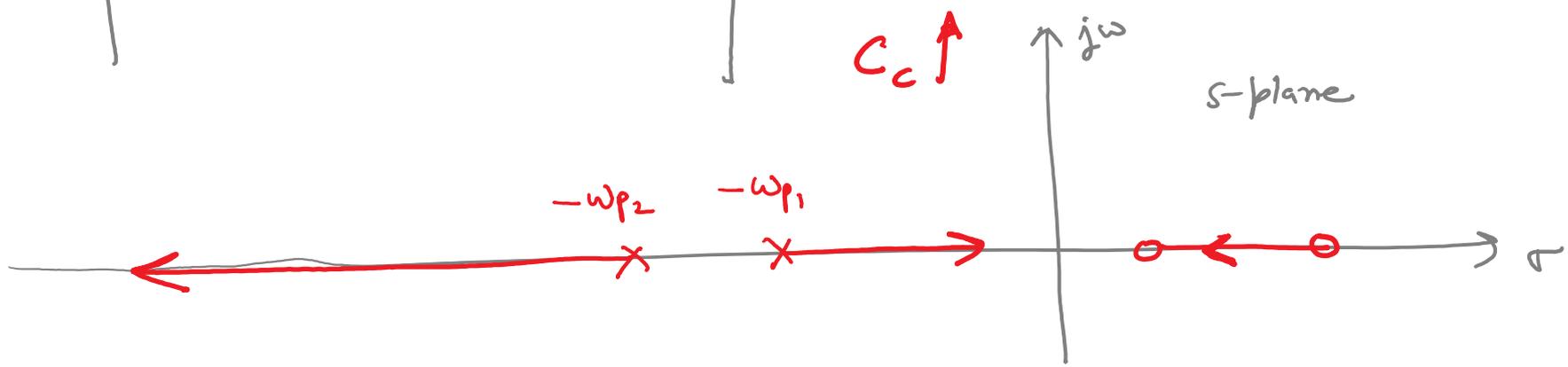

$$\omega_z = \frac{g_{m2}}{C_c}$$

## RHP zero Cancellation

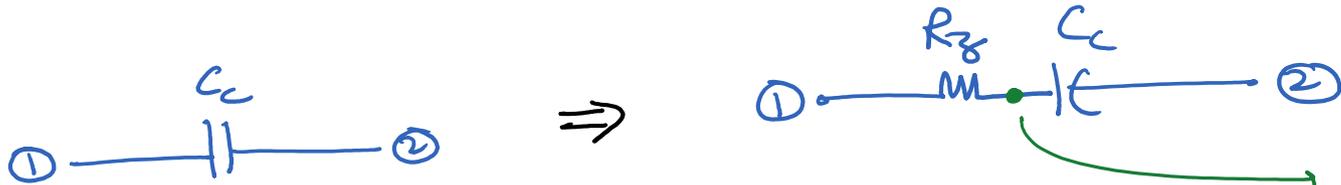

$$\omega_z = \frac{1}{C_c \left( \frac{1}{g_{m2}} - R_z \right)}$$


additional pole at very high frequencies

Set  $R_z = \frac{1}{g_{m2}} \rightarrow$  zero is pushed to  $\infty$  (it disappears)

$R_z > \frac{1}{g_{m2}} \rightarrow$  zero is pushed into the LHP

LHP zero  $\rightarrow$  add to the phase

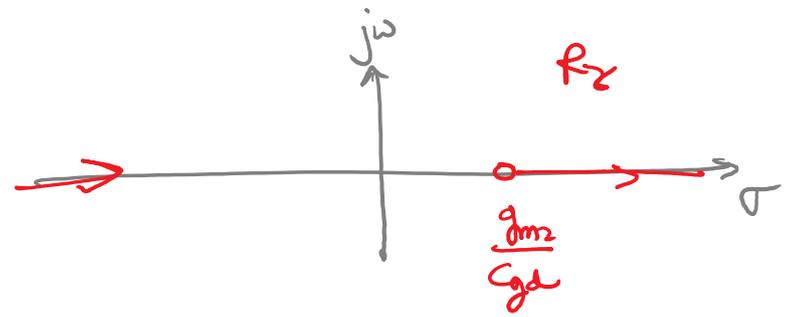
\* Typically we just use  $R_z$  for zero-cancellation.



$$A_v(s) = \frac{A_{v0} (1 - s/\omega_z)}{(1 + s/\omega_{p1})(1 + s/\omega_{p2})} = \frac{A_{v0}}{(1 + s/\omega_{p1})(1 + s/\omega_{p2})}$$

zero nulling

$\omega_{p1} \ll \omega_{p2}$

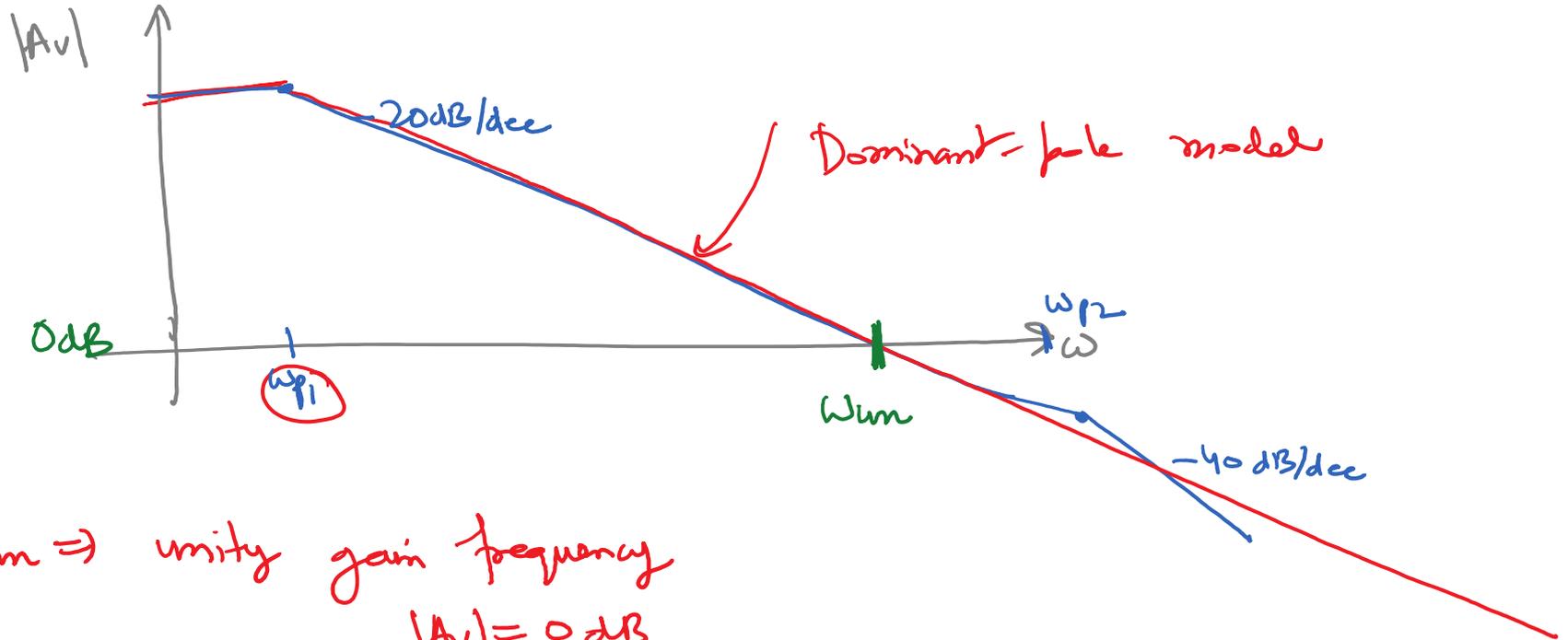

$\omega_{um} \Rightarrow$  unity gain frequency  
 $|A_v| = 0 \text{ dB}$

$\omega_{um} \Rightarrow$  depends upon  $f_T \Rightarrow$   $f_{um} \approx \frac{f_T}{20}$  Empirical number


$$\omega_{3dB} \Rightarrow \omega_{p1}$$

Dominant pole Model

$$A_v(s) = \frac{A_{v0}}{(1 + s/\omega_{p1})} \approx \frac{A_{v0}}{(1 + s/\omega_{3dB})}$$

$$A_{v0} = g_{m1} R_1 g_{m2} R_2$$
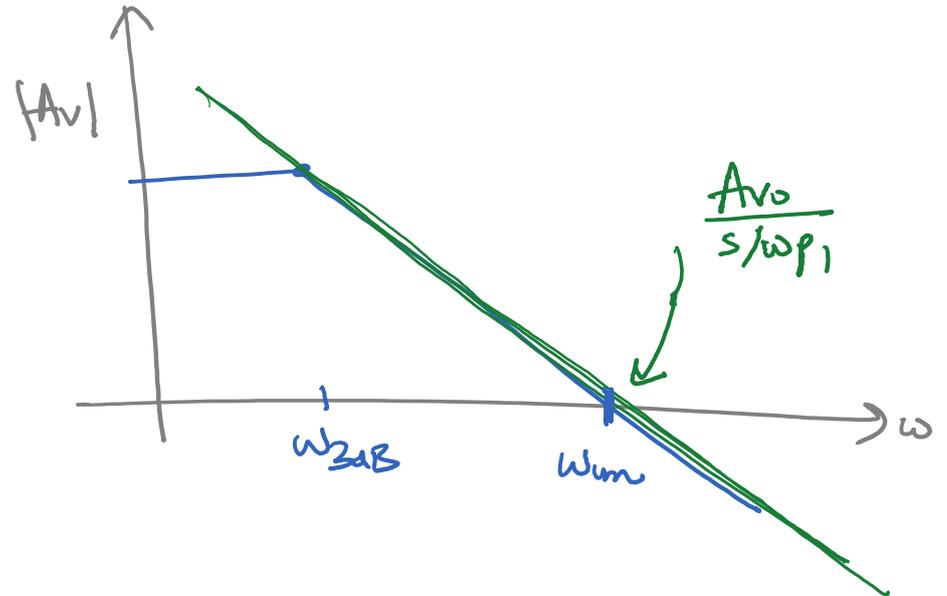
$$\omega_{3dB} = \frac{1}{g_{m2} R_2 R_1 C_c}$$



Around  $\omega \ll \omega_{um}$

$$A_v(s) \approx \frac{A_{v0}}{s/\omega_{3dB}}$$

$$A_v(s) \approx \frac{A_{v0} \omega_{3dB}}{s} \Rightarrow$$



$$A_v(j\omega_{um}) = \left| \frac{A_{v0} \omega_{3dB}}{j\omega_{um}} \right| = 1$$

$$\omega_{um} \approx A_{v0} \omega_{3dB}$$

Gain-BW ←

$$\begin{aligned} \omega_{um} &= A_{10} \cdot \omega_{2dB} \\ &= \cancel{g_{m1} R_1} \cdot \cancel{g_{m2} R_2} \cdot \frac{1}{\cancel{g_{m2} R_2} R_1 C_c} \\ &= \frac{g_{m1}}{C_c} \end{aligned}$$
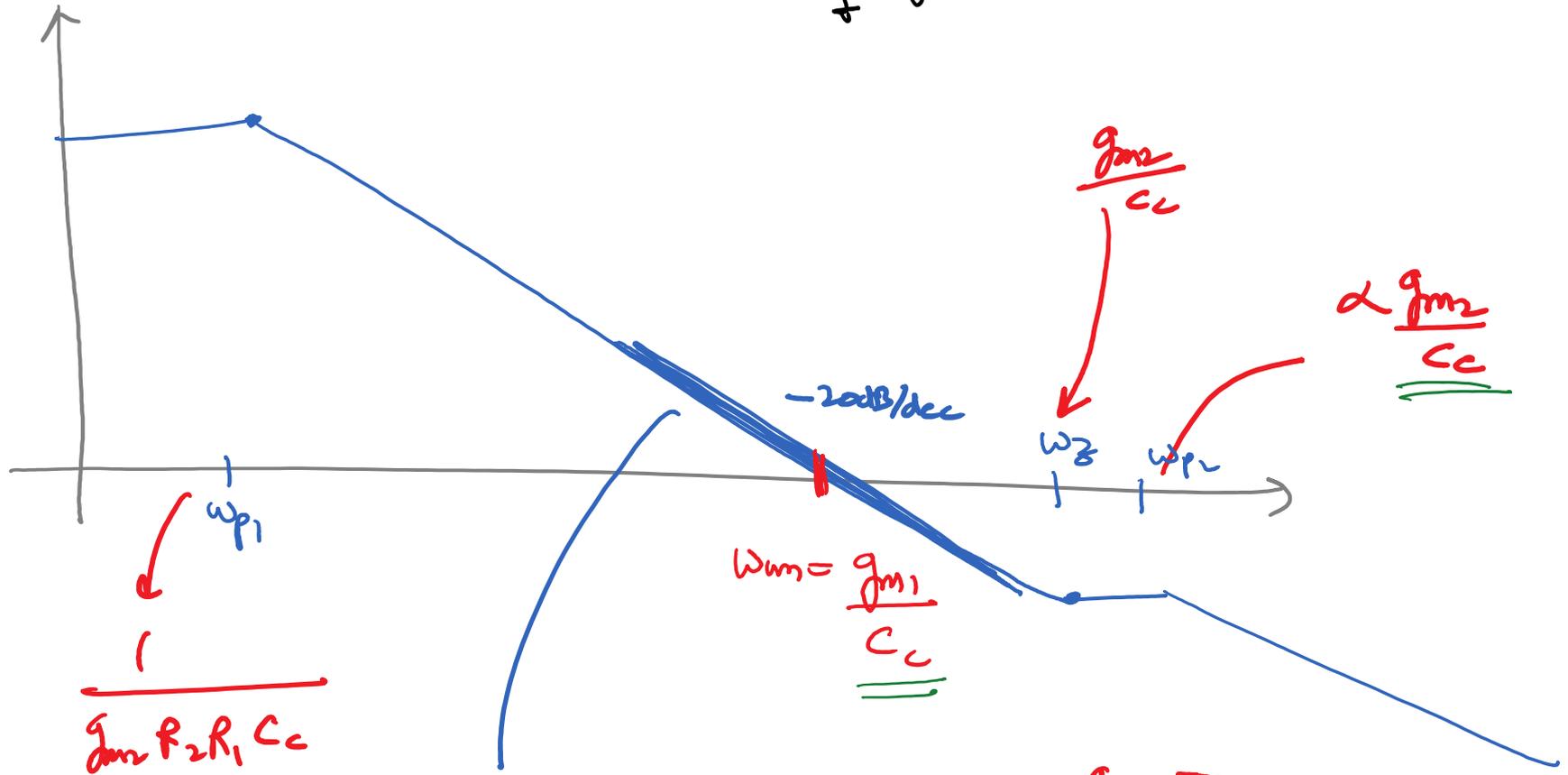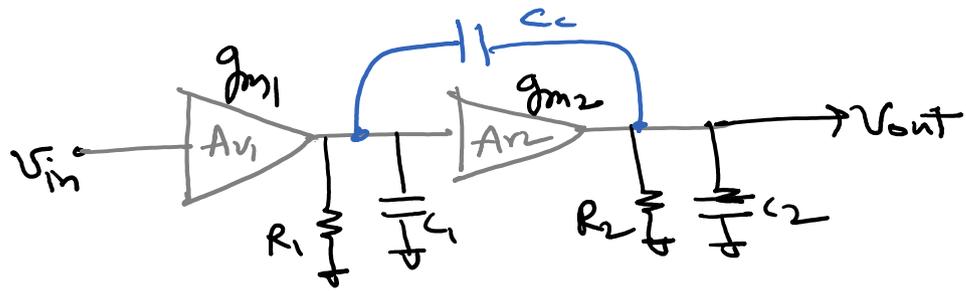
$$\boxed{\omega_{um} = \frac{g_{m1}}{C_c}}$$



$\frac{1}{g_{m2} R_2 R_1 C_c}$

$\omega_{um} = \frac{g_{m1}}{C_c}$

$\frac{g_{m2}}{C_c}$

$\propto \frac{g_{m2}}{C_c}$


\* Should look like a first order system around  $\omega \leq \omega_{um}$   $g_{m2} > g_{m1}$

\*  $C_{gd1}$  provides a feed forward path that conducts input signal to the output at high frequencies.

↳ adds to  $g_m V_i$  in opposite phase

↳ bring the phase down

↳ RHP zero

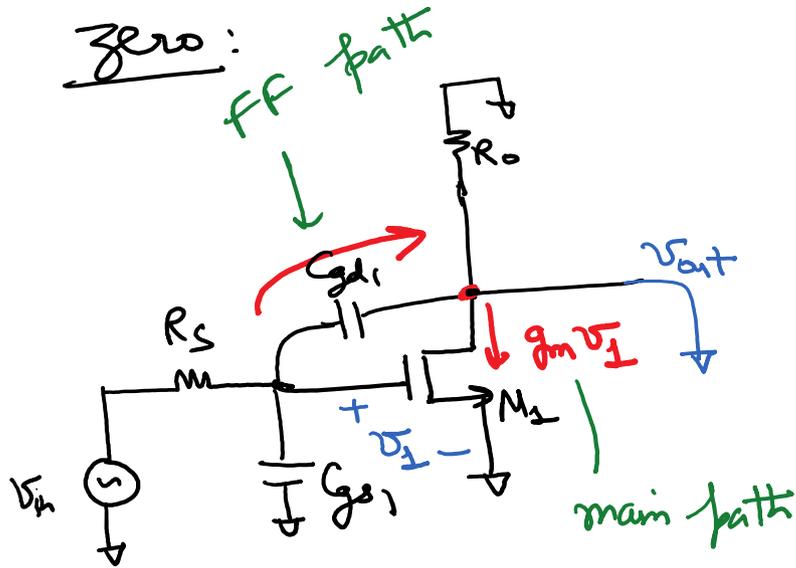

At frequency

$\omega = \omega_z \Rightarrow$  these two currents cancel each other  
 ↳ gives rise to the zero.

\* To estimate zero, output can be shorted to ground at  $S = j\omega_z$

$$\therefore V_{out}(S = j\omega_z) = 0$$

$\Rightarrow$


$$V_i \cdot C_{gd1} \cdot S_z = g_m V_i$$

$$\Rightarrow S_z = \frac{g_m}{C_{gd1}}$$

$$\Rightarrow \omega_z = \frac{g_m}{C_{gd1}}$$

# Source Follower Frequency Response:

Thursday, October 18, 2018 12:13 PM

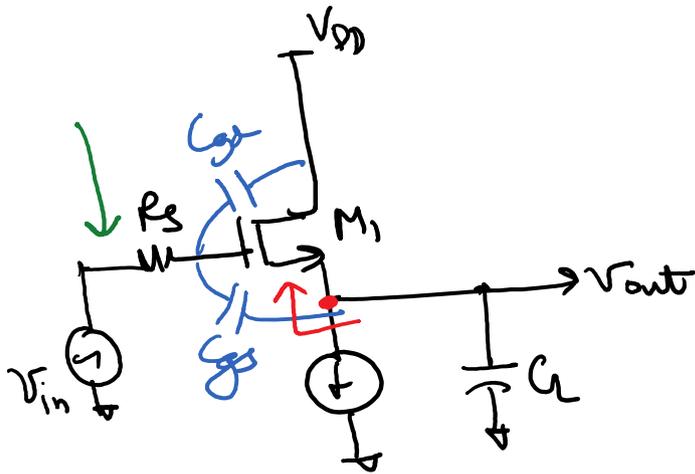

$$\frac{1}{R_C} = \frac{1}{\frac{1}{g_m} \cdot C_L} = \frac{g_m}{C_L}$$