
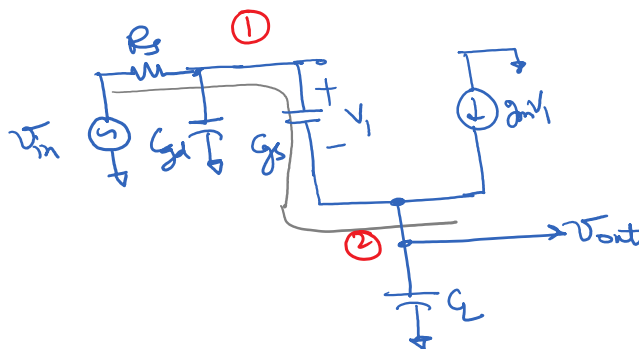


EECE 515 - Lecture 18

Tuesday, October 23, 2018 11:03 AM

SF frequency Response :

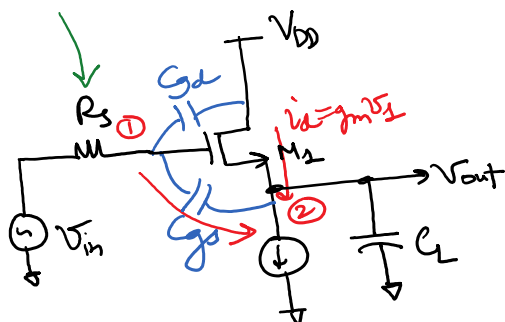$\lambda \rightarrow 0$
 $\lambda \rightarrow \infty$



KCL
@ node-2

$$V_1 s C_{gs} + g_m V_1 = V_{out} s C_L$$

$$\Rightarrow V_1 = \frac{s C_L}{g_m + s C_{gs}} \cdot V_{out}$$

* KVL beginning from V_{in}

$$V_{in} = R_s [V_1 s C_{gs} + (V_1 + V_{out}) s C_{gd}] + V_1 + V_{out}$$

Substitute V_1

$$(g_m + s C_{gs})$$

$$\frac{V_{out}}{V_{in}}(s) = \frac{(g_m + s C_{gs})}{R_s [C_{gs} C_L + C_{gs} C_{gd} + C_{gd} C_L] s^2 + [g_m R_s C_{gd} + C_L + C_{gs}] s + g_m}$$

LHP zero

$$\omega_z = -\frac{g_m}{C_{gs}}$$

\Rightarrow signal conducted by C_{gs} adds to the signal carried by the main transistor with the same polarity.

Assuming $|\omega_{p1}| \ll |\omega_{p2}|$


* Dominant pole:

$$\omega_{p1} \approx \frac{g_m}{g_m R_s C_d + C_L + C_{gs}}$$


$$= \frac{1}{R_s C_d + \frac{C_L + C_{gs}}{g_m}} = \frac{g_m}{C_L + C_{gs}} \text{ iff } R_s = 0$$

$$f_T = \frac{g_m}{C_{gs}}$$

* wideband buffers

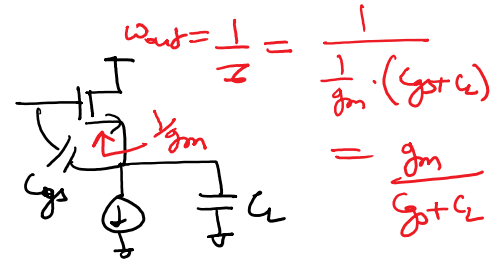


Input Impedance of SF:

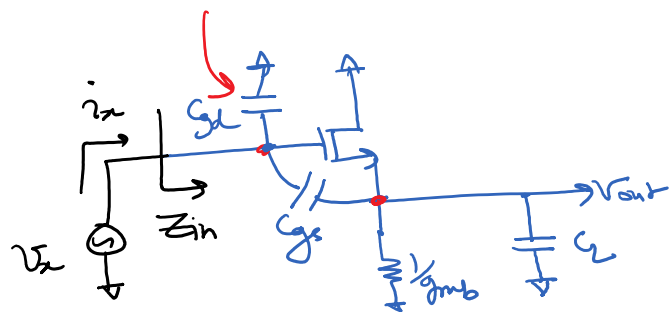

$$\bar{Z}_{in} = \underbrace{\frac{1}{sC_{gd}}}_{C_{gd}} + \underbrace{\left(1 + \frac{g_m}{sC_{gs}}\right) \frac{1}{g_{mb} + sC_L}}_{\text{modified } C_{gs}}$$

* @ low-frequencies

$$g_{mb} \gg |sC_L|$$

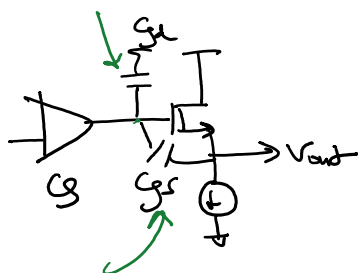

$$\Rightarrow \bar{Z}_{in1} \approx \frac{1}{sC_{gs}} \left(1 + \frac{g_m}{g_{mb}}\right) + \frac{1}{g_{mb}} = \frac{1}{\frac{sC_{gs}}{\left(1 + \frac{g_m}{g_{mb}}\right)}} + \frac{1}{g_{mb}}$$

→ input cap is only a fraction of C_{gs} .

→ loading on the driving stage is reduced

* At higher frequencies

$$g_{m0} < |sC_L|$$

$$\Rightarrow Z_{in} \approx \frac{1}{sC_g} + \frac{1}{sC_L} + \frac{g_m}{C_g C_L s^2}$$

for some $s = j\omega$

$$Z_{in} = \underbrace{\frac{1}{j\omega} \left[\frac{1}{C_g} + \frac{1}{C_L} \right]}_{\text{Capacitance}} - \underbrace{\frac{g_m}{C_g C_L \omega^2}}_{\text{Negative resistance}}$$


↳ can lead to oscillations

Output Impedance :


$$Z_{out} = \frac{sR_s C_{gs} + 1}{g_m + sC_{gs}}$$

@ low frequencies $\Rightarrow Z_{out} = \frac{1}{g_m}$

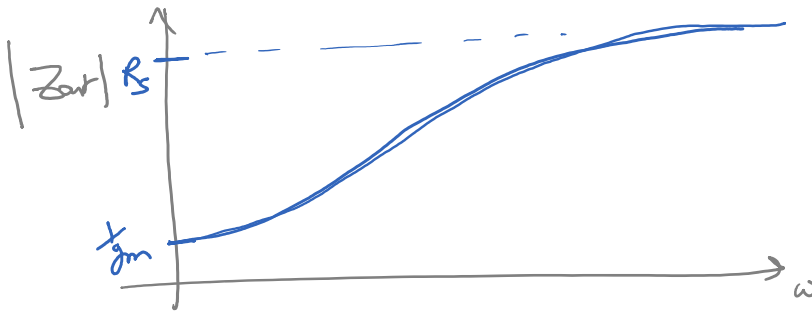@ very high $f \Rightarrow Z_{out} = R_s$



Equivalent circuit

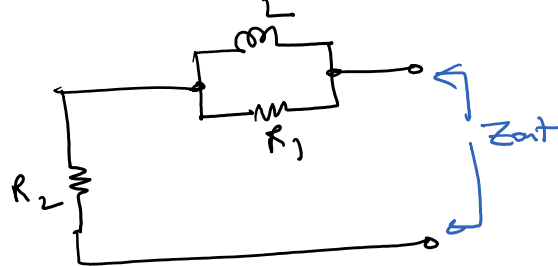

$$R_2 = \frac{1}{g_m}$$

$$R_1 = R_s - \frac{1}{g_m}$$



$$L = \frac{C_{gs}}{g_m} (R_s - \frac{1}{g_m})$$



$$L = \frac{C_{gs}}{g_m} (R_s - \frac{1}{g_m})$$

* If the SF is driven by a large R_s

$$R_s \gg \frac{1}{g_m}$$

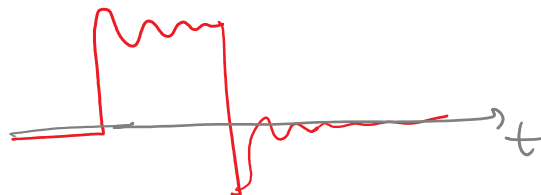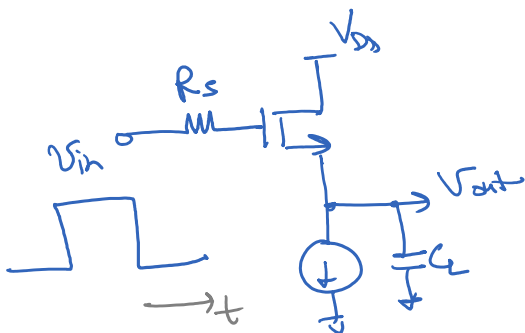
\Rightarrow Substantial inductive behavior



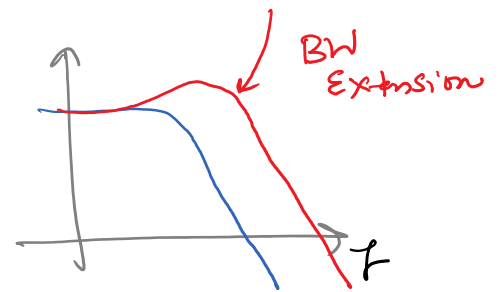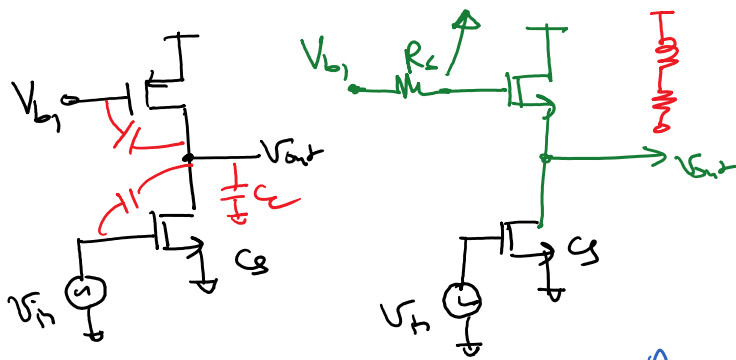


* An active inductor load for BW Extension

Common Gate Frequency Response :

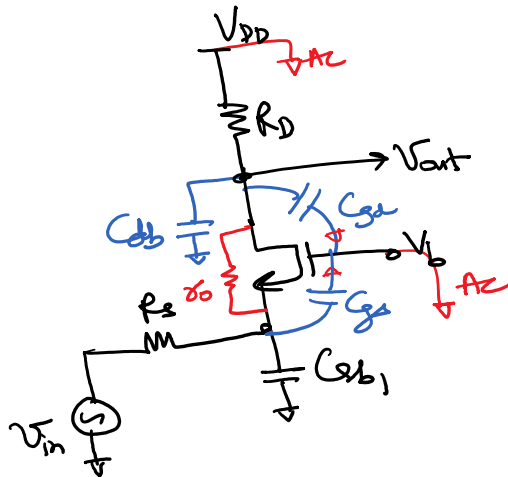

⇒

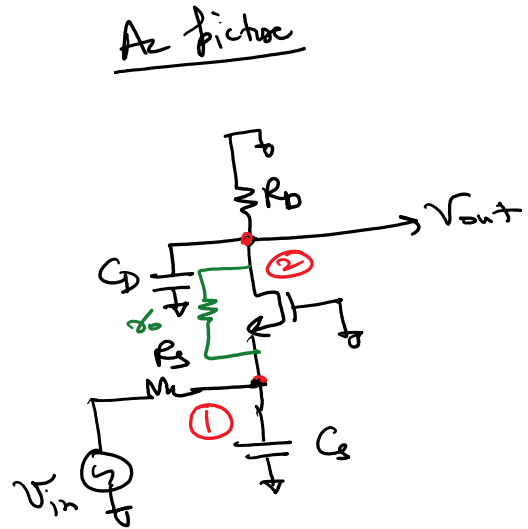

$$C_S = C_{gs1} + C_{sb1}$$

$$C_D = C_{gd1} + C_{db}$$

No Miller Cap

↳ nodes ① & ② are isolated


$$\omega_{p1} = \omega_{in} = \frac{1}{\left(R_s \parallel \frac{1}{g_m + g_{mb}} \right) C_S} \quad \hookrightarrow \quad \frac{g_m}{C_S} \rightarrow \infty \text{ if } R_s \rightarrow 0$$

$$\omega_{p2} = \omega_{out} = \frac{1}{R_D C_D} \quad \hookrightarrow \quad \frac{1}{R_D C_D}$$

only Two poles


→ no zeros
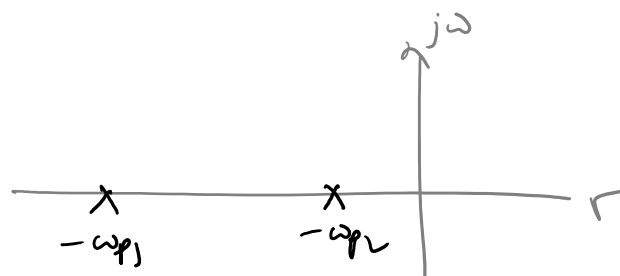
$$\Rightarrow \quad \frac{V_{out}}{V_{in}}(s) = \frac{1}{(1 + s/\omega_{p1})(1 + s/\omega_{p2})}$$



Cascode Amplifier Frequency Response :

Tuesday, October 23, 2018 11:26 AM

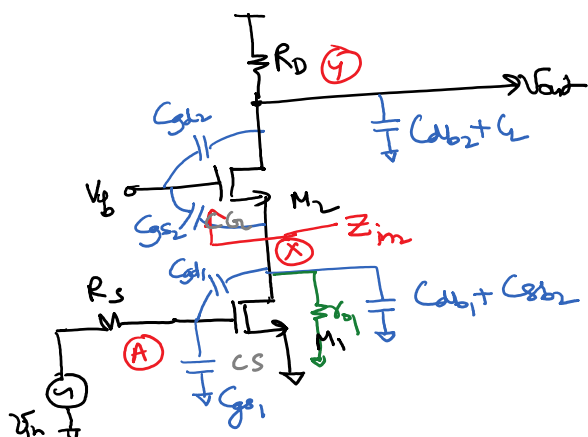

Miller Cap $\Rightarrow C_{gd}$

* Miller effect of C_{gd} is determined by the gain from A to X

* Assuming $R_D \leq r_o$

$$Z_{in2} = \frac{1}{g_{m2} + g_{mb2}}$$

$$A_{A \rightarrow X} = -g_{m1} \cdot (Z_{in2} || r_{o1})$$

* Assume M_1 & M_2 to be identical

$\Rightarrow C_{gd1}$ is multiplied by 2X, instead of $(1 + |A_v|)$

\hookrightarrow Miller effect is less significant in cascode amplifiers than in a stage

\hookrightarrow Miller killer!

$$\hookrightarrow -\frac{g_{m1}}{g_{m2} + g_{mb2}} \hookrightarrow -\frac{g_{m1}}{g_{m2}}$$

$\hookrightarrow -1$ if M_1 & M_2 are identical


Using Miller Approximation

$$\omega_{PA} = \frac{1}{R_A C_A} = \frac{1}{R_s \cdot \left[C_{gs1} + \left(1 + \frac{g_{m1}}{g_{m2} + g_{mbs2}} \right) C_{gs2} \right]}$$

Low- z node \Rightarrow higher frequency pole $\Rightarrow 2$

$$\omega_{px} = \frac{1}{R_x C_x} = \frac{1}{\frac{1}{(g_{m2} + g_{mbs2})} \cdot \left[2C_{gd1} + C_{db1} + C_{sb2} + C_{gs2} \right]}$$


$$\approx \frac{g_{m2}}{C_x}$$

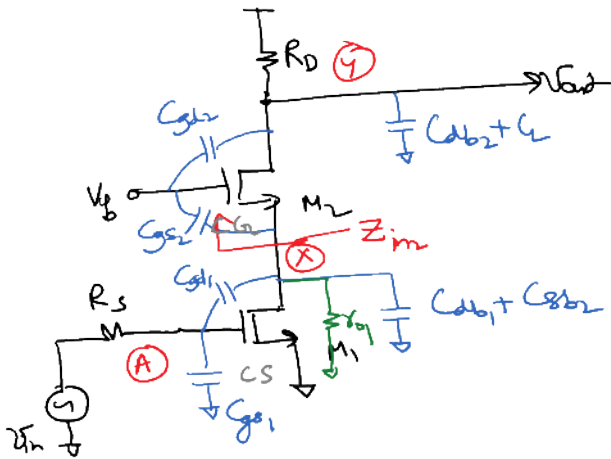


High- z node, low-frequency pole.

$$\omega_{py} = \frac{1}{R_D \parallel (g_{m2} r_{o2} r_{o5}) \cdot (C_{db2} + C_L + C_{gs2})}$$

$$\approx \frac{1}{R_D C_L}$$

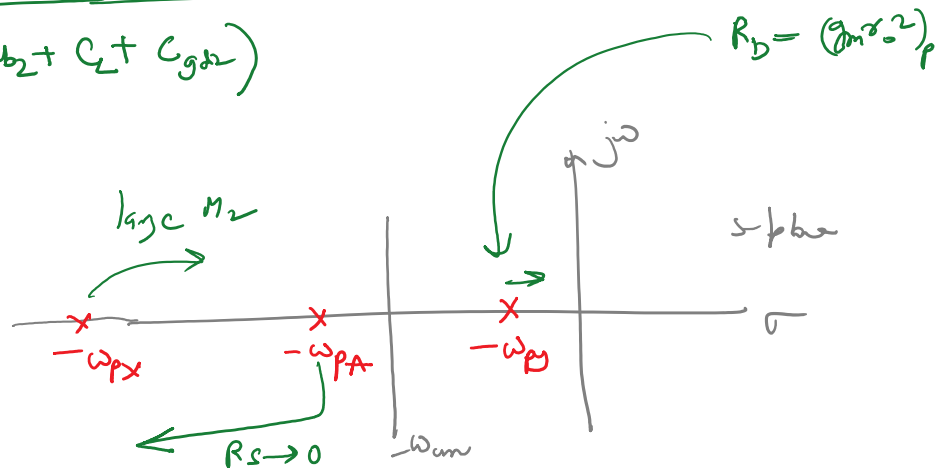


Slewing

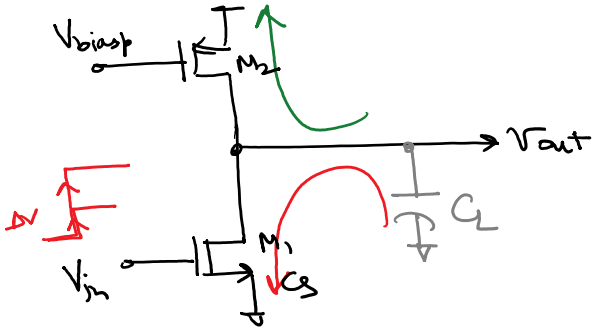

$$\frac{dV_{out}}{dt} = \frac{I_o}{C_L}$$

Class-A stage

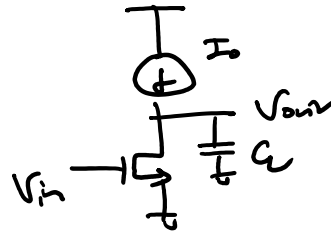


SR^+
no SR limitation when discharging.

$$\frac{V_{out}}{V_{in}} = - \frac{g_{m1}(r_{o1}||r_{o2})}{(1 + \frac{s}{\omega_p})}, \quad \omega_p = \frac{1}{(r_{o1}||r_{o2})C_L}$$

$$\omega_{um} = \frac{g_{m1}}{C_L}$$

1st order response

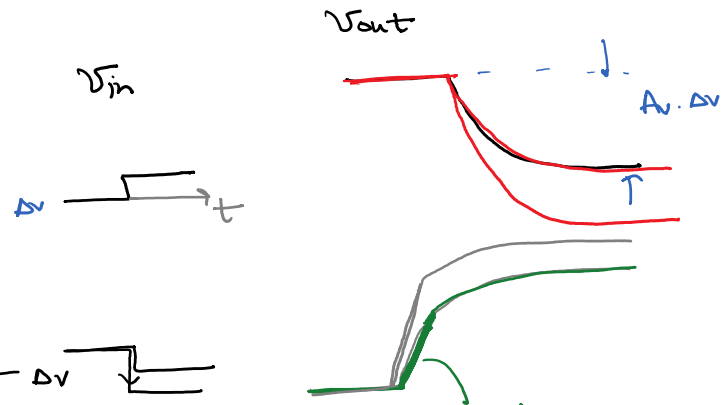

\Rightarrow slewing is a non linear behavior
 $\left| \frac{dV_{out}}{dt} \right| < SR^+ = \frac{I_o}{C_L}$