

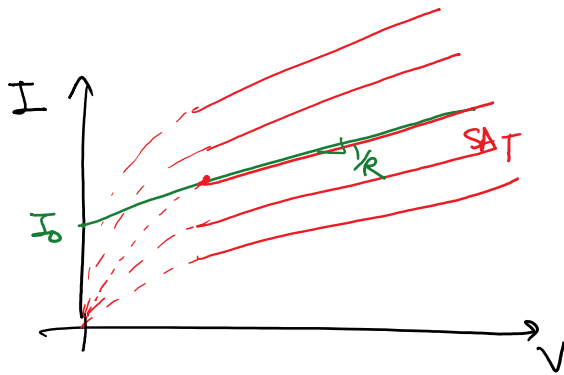


# ECE 515 - Lecture 1



Thursday, August 23, 2018 11:01 AM

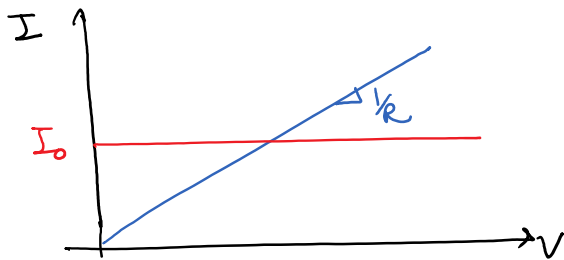

LVT<sub>s</sub>, HVT<sub>s</sub>



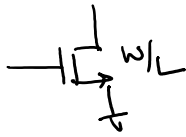


Triode

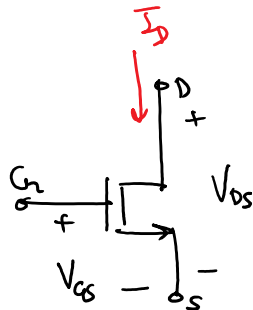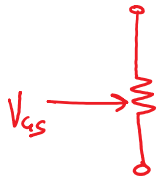

$I_D \uparrow$

$$I_D = f(V_{GS}, V_{DS})$$

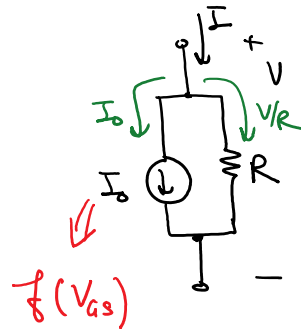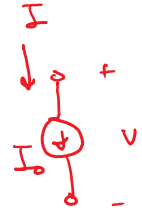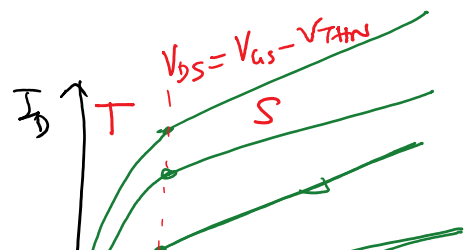


MOSFET in SATURATION

MOSFET

↳ VCCS with output resistance

Voltage Controlled Current Source

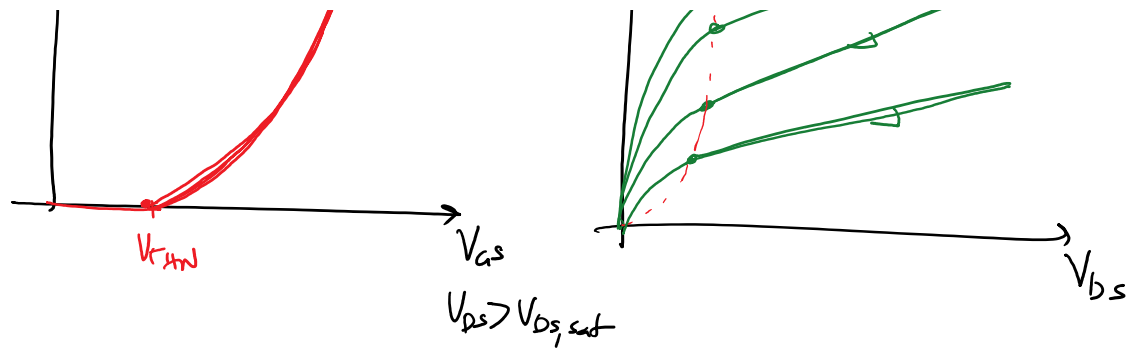

Saturation: Ideally  $V_{ds} > V_{ds,sat} = V_{gs} - V_{th}$

channel length modulation  $L \leq 5 \mu m$

# Long channel Equations

Short-channel effects  
BSIM models

$$I_D = \begin{cases} 0 & V_{GS} < V_{THN} \\ \frac{K_{PN} W}{L} \left[ (V_{GS} - V_{THN}) V_{DS} - \frac{V_{DS}^2}{2} \right] & V_{GS} > V_{THN} \text{ and } 0 < V_{DS} < V_{DS,sat} \\ \frac{1}{2} \frac{K_{PN} W}{L} (V_{GS} - V_{THN})^2 \left[ 1 + \lambda (V_{DS} - V_{DS,sat}) \right] & V_{GS} > V_{THN} \text{ and } V_{DS} > V_{DS,sat} \end{cases}$$

square-law


channel length modulation

CLM parameter

$K_{PN} = \mu_n C_{ox}$

mobility


oxide cap  
p.u. area

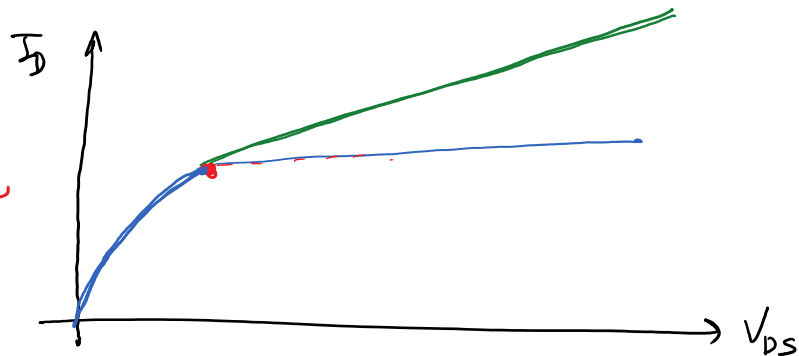

$V_{DS,sat} = V_{GS} - V_{THN} = V_{OV} \leftarrow \text{overdrive voltage}$

In triode:

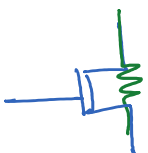$\beta = K_{PN} \frac{W}{L} \rightarrow \mu_n C_{ox}$




$$I_D = \frac{K_{PN} W}{L} \left( (V_{GS} - V_{THN}) V_{DS} - \frac{V_{DS}^2}{2} \right)$$


$$I_D = K_{PN} \frac{W}{L} \left[ V_{GS} - V_{THN} - \frac{V_{DS}}{2} \right]$$

$$R_{ch}^{-1} = \frac{\partial I_D}{\partial V_{DS}} = k_n \frac{W}{L} [V_{GS} - V_{THN} - V_{DS}]$$
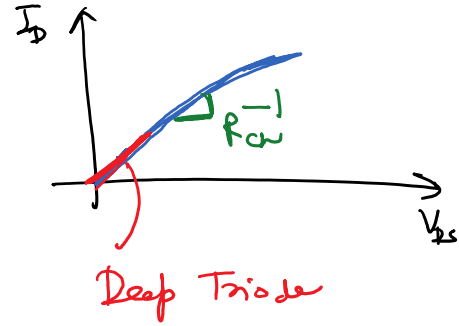
$$R_{ch} = \frac{1}{k_n \frac{W}{L} [V_{GS} - V_{THN} - V_{DS}]}$$



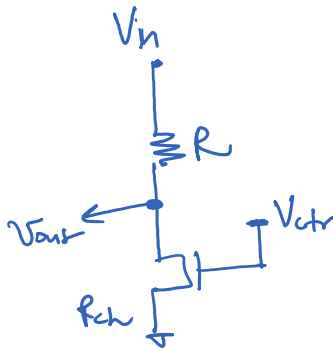
$$\approx \frac{1}{k_n \frac{W}{L} (V_{GS} - V_{THN})} \text{ in Deep Triode } V_{DS} \ll (V_{GS} - V_{THN})$$




Voltage controlled resistance

$$R_{ch} = R_{DS} = f(V_{GS} - V_{THN})$$
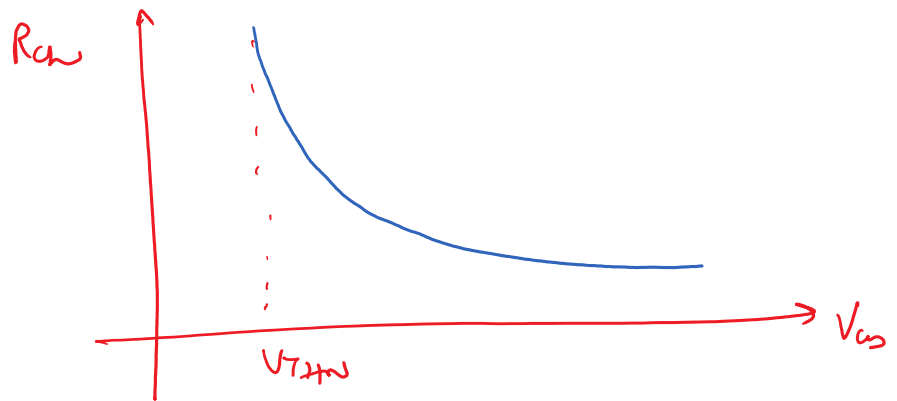
$$R_{ch} \propto \frac{1}{V_{GS} - V_{THN}}$$




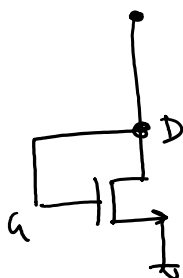



Diode - connected

$$V_{GS} = V_{DS} > V_{Thn}$$

always in SAT

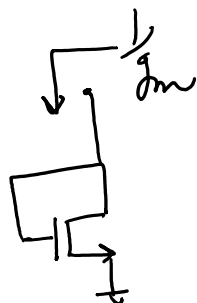

# Non linear Resistor

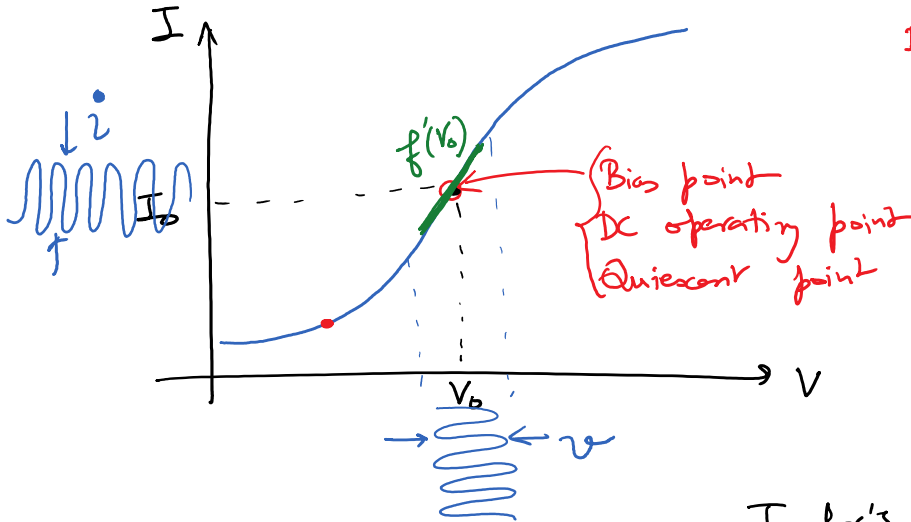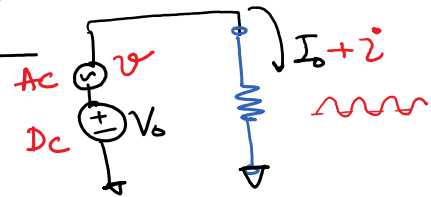

$$I = f(V) \text{ non-linear}$$

Taylor's series Expansion

$$I = f(V)$$

$$\Rightarrow I = \underbrace{f(V_0)}_{I_0} + \frac{f'(V_0)}{1} \underbrace{(V-V_0)}_v + \frac{f''(V_0)}{2} \underbrace{(V-V_0)^2}_{v^2} + \frac{f'''(V_0)}{6} \underbrace{(V-V_0)^3}_{v^3} + \dots$$

$$V = V_0 + v$$

$$\Rightarrow v = V - V_0$$

$$\underbrace{I - I_0}_i = f'(V_0) \cdot v + \frac{f''(V_0)}{2} v^2 + \frac{f'''(V_0)}{6} v^3 + \dots$$

$I_0 = f(V_0)$

$$\Rightarrow i = \underbrace{f'(V_0) \cdot v}_{\text{slope at bias point}} + \frac{f''(V_0)}{2} v^2 + \frac{f'''(V_0)}{6} v^3 + \dots \quad \text{--- (1)}$$

$$f'(V_0) = \left. \frac{\partial I}{\partial V} \right|_{V=V_0} \quad \text{Slope at the Bias point depends upon the bias point}$$

$v, i$  are small-signals, incremental signals, AC signals  
perturbation

$v$  is very small

$$i \approx \underbrace{f'(V_0)}_g v$$

$$i = g v$$

$$g = \left. \frac{\partial I}{\partial v} \right|_{v=V_0}$$

Small-signal parameter  
that depends upon the  
Bias point



Small-signal equivalent circuit



$$i = g v$$

slope at the bias point

from  $\sum_1^n$  ①  $f'(V_0)$

$$i = g_1 v + g_2 v^2 + g_3 v^3 + \dots$$

Distortion terms

Linearized equation


Can ignore distortion terms

if

$$g_2 v^2 < \frac{1}{10} g_1 v$$

$$v < \frac{g_1}{10 g_2}$$

# MOSFET small-signal parameters

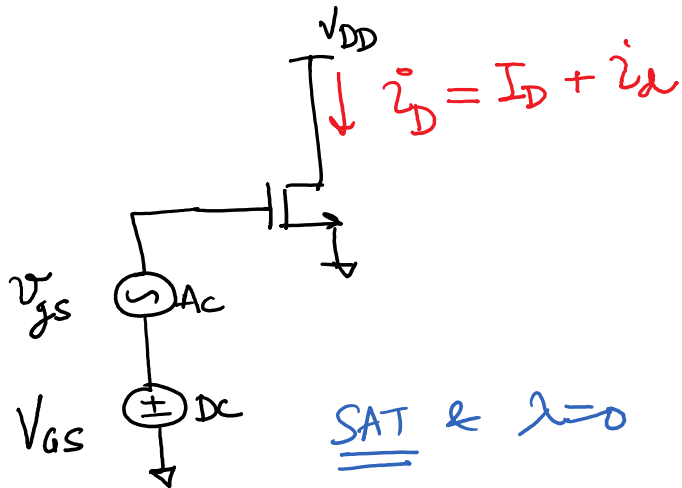

$$\underbrace{v_{GS}}_{\text{total voltage}} = \underbrace{V_{GS}}_{\text{DC}} + \underbrace{v_{gs}}_{\text{AC}}$$

$$\underbrace{i_D}_{\text{total current}} = \underbrace{I_D}_{\text{DC}} + \underbrace{i_d}_{\text{AC}}$$

SAT &  $\lambda = 0$

$$i_D = \frac{k_n}{2} \frac{W}{L} (v_{GS} - V_{THN})^2$$

$$I_D + i_d = \frac{k_n}{2} \frac{W}{L} (V_{GS} + v_{gs} - V_{THN})^2$$

$$i_d = g_m \cdot v_{gs}$$

$$g_m = \left. \frac{\partial i_D}{\partial v_{GS}} \right|_{v_{GS} = V_{GS}}$$