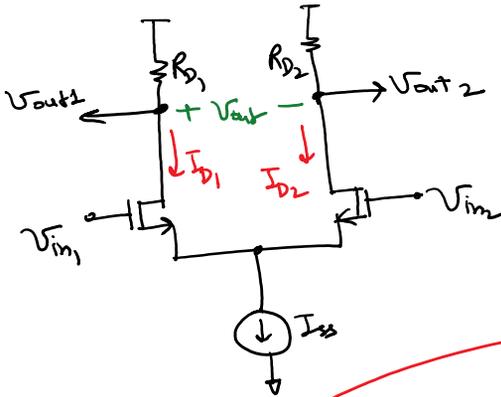


ECE 515 - Lecture 20

Thursday, November 1, 2018 11:07 AM

Large Signal Behavior:



$$V_{out1} = V_{DD} - I_{D1} R_{D1}$$

$$V_{out2} = V_{DD} - I_{D2} R_{D2}$$



$$\Rightarrow V_{out} = V_{out1} - V_{out2} = -(I_{D1} - I_{D2}) R_D$$


$R_D = R_{D1} = R_{D2}$

$$I_{D1} - I_{D2} = \underbrace{\frac{\beta}{2} (V_{in1} - V_{in2})}_{\text{linear}} \sqrt{\frac{4I_{SS}}{\beta} - (V_{in1} - V_{in2})^2}$$



decreases as $(V_{in1} - V_{in2}) \uparrow$

$$\approx \frac{\beta}{2} (V_{in1} - V_{in2}) \quad \text{for } |V_{in1} - V_{in2}| < \sqrt{\frac{4I_{SS}}{\beta}}$$

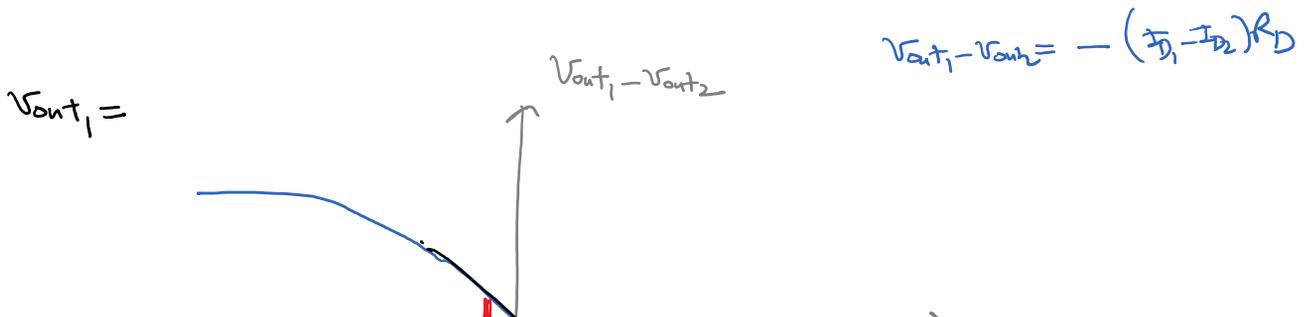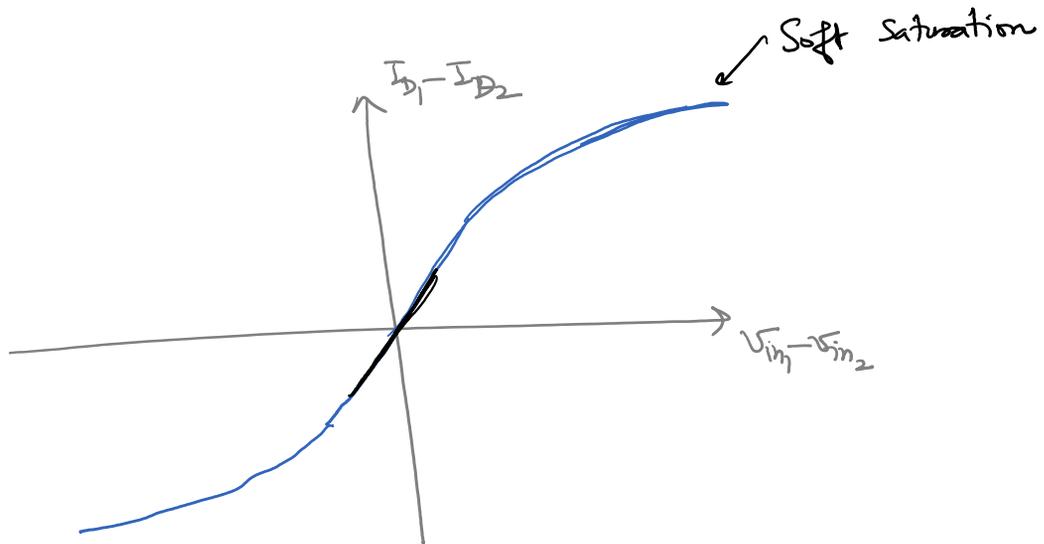


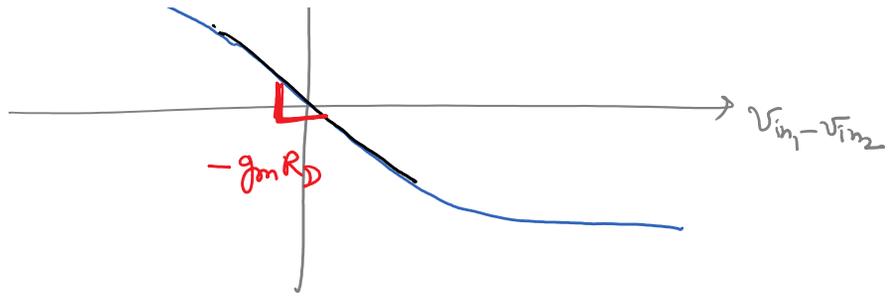

Source Degeneration

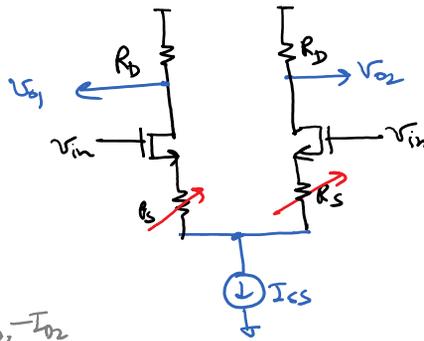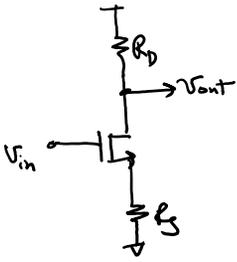

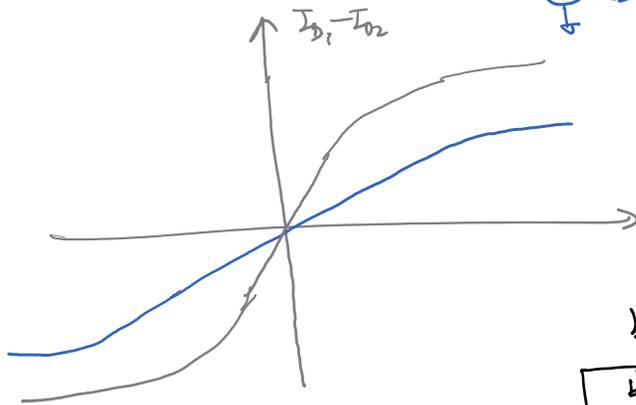
Linear gain stage
 Programmable gain stage
 ↳ $R_S \rightarrow$ Triode Transistor





more linear

$$|A_v| = \frac{g_m R_D}{1 + g_m R_S}$$

0 or V_{DD}

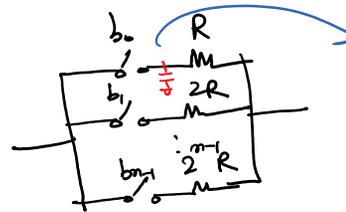

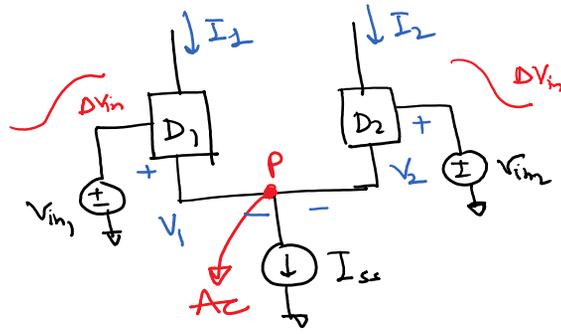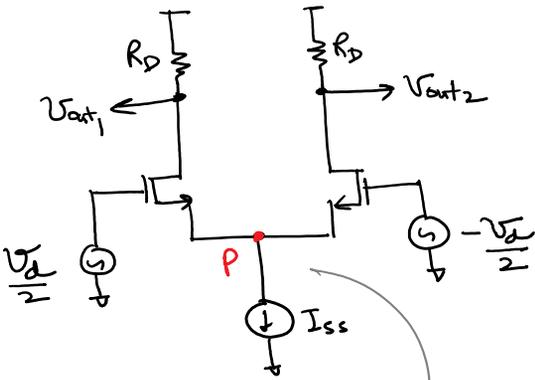Lemma: Consider the asymmetric circuit shown below



See proof in the book.

If V_{in1} changes from V_0 to $V_0 + \Delta V_{in}$
 & V_{in2} changes from V_0 to $V_0 - \Delta V_{in}$



Then, if the circuit remains linear

V_p doesn't change.

↳ P is effectively an AC ground.

* Due to symmetry in circuit with differential inputs

Differential Half Circuit

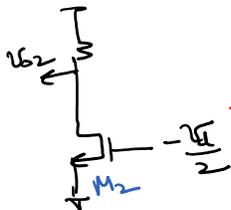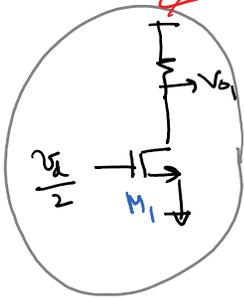

only valid for purely differential inputs

$$v_d = v_{i1} - v_{i2}$$

$$\frac{v_{out1}}{v_{in1}} = -g_m R_D$$

$$\frac{v_{out2}}{v_{in2}} = -g_m R_D$$

precise gain

$$-g_{m1,2} (R_D || r_{o1,2})$$

$$\frac{v_{out1} - v_{out2}}{v_{in1} - v_{in2}} = -g_m R_D$$



$$\frac{v_{out1}}{v_{in1} - v_{in2}} = -\frac{1}{2} g_m R_D$$

* What if the inputs are not fully-differential?

may not be DC voltage

$$V_{in1} = \left(\frac{V_{in1} - V_{in2}}{2} \right) + \left(\frac{V_{in1} + V_{in2}}{2} \right)$$

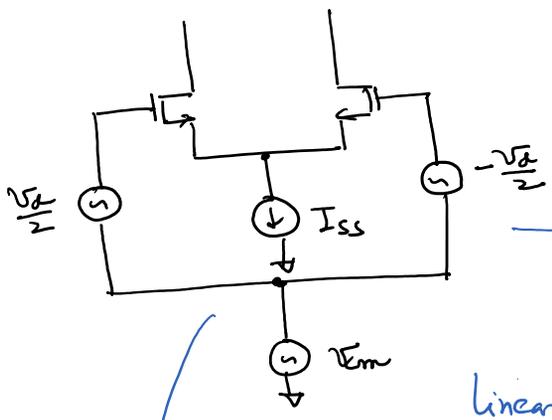
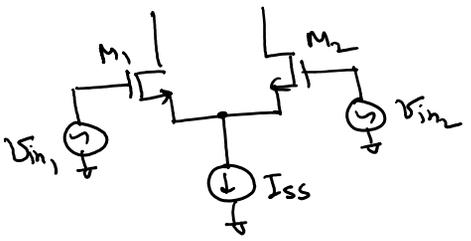
$$V_{in2} = \left(\frac{V_{in2} - V_{in1}}{2} \right) + \left(\frac{V_{in1} + V_{in2}}{2} \right)$$



Linear Superposition



Differential Circuit


Common Mode Circuit

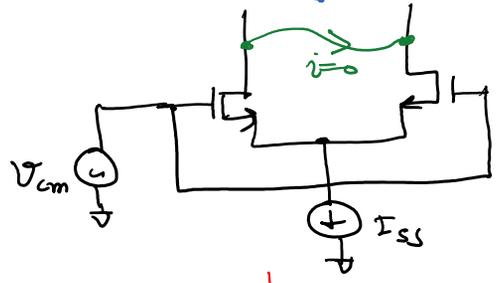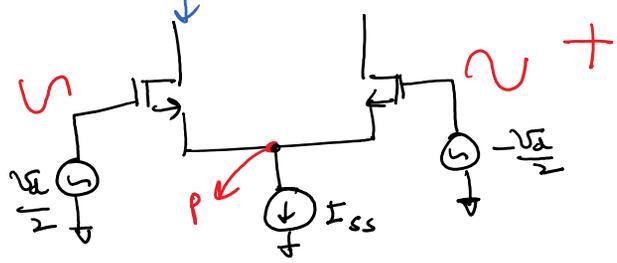


Differential Half Circuit

CM Equivalent circuit

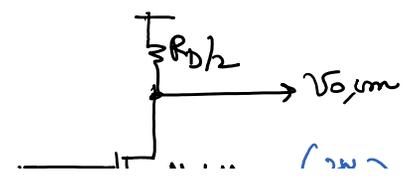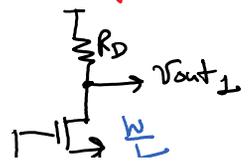

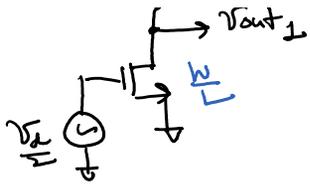

Differential gain
poles, zeros, f_{un}


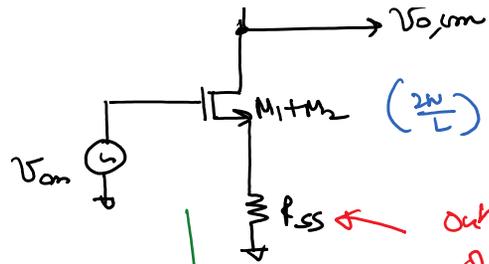


CM gain


output resistance
of the tail
current source.

Combine the results together

"Not showing CMFB loop"

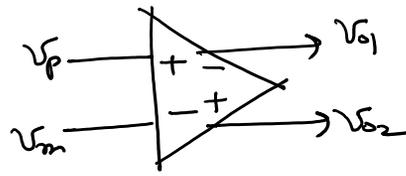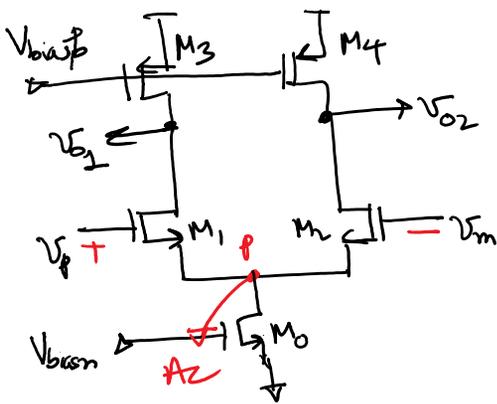

Differential half circuits


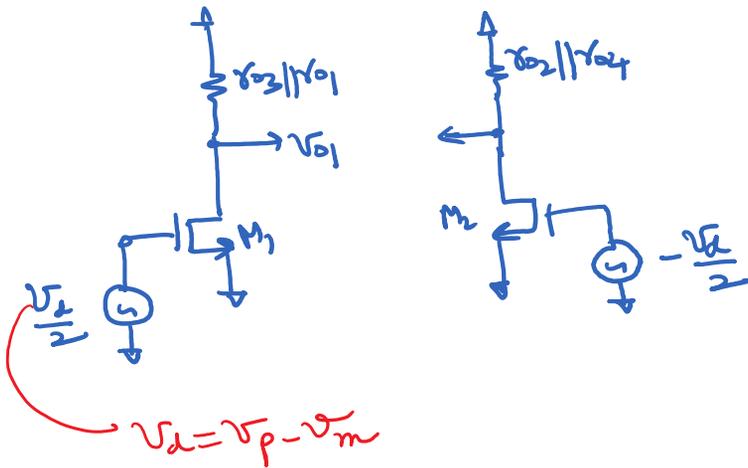


Differential gain

$$\frac{V_{d1} - V_{d2}}{V_p - V_m} = -g_{m1,2} (r_{D1,2} \parallel r_{D3,4})$$

$$A_{DM} = \frac{V_{d2} - V_{d1}}{V_p - V_m} = +g_{m1,2} (r_{D1,2} \parallel r_{D3,4})$$

CM equivalent circuit

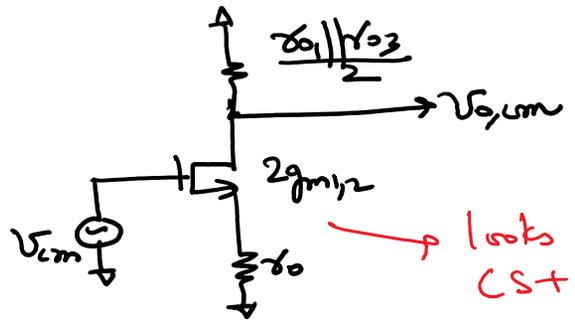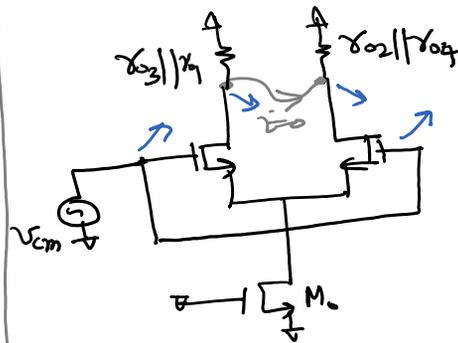

$$A_{CM} = - \frac{2g_{m1,2} \left(\frac{r_{D1} \parallel r_{D3}}{2} \right)}{1 + 2g_{m1,2} R_{SS} \rightarrow r_{D0}}$$

$$CMRR = \left| \frac{A_{V,DM}}{A_{V,CM}} \right| \text{ in dB}$$


$$\dots - g_{m1,2} (r_{D1,2} \parallel r_{D3,4}) \times (1 + 2g_{m1,2} R_{SS})$$

$$\downarrow \text{CMRR} = \frac{g_{m1,2} (\beta_{1,2} \parallel \beta_{2,1}) \times}{\cancel{2g_{m1,2}} \frac{(\beta_{1,2} \parallel \beta_{2,1})}{\cancel{2}}} \cdot (1 + 2g_{m1,2} R_{SS})$$


$$\text{CMRR} = 1 + 2g_{m1,2} R_{SS} \leq 2g_{m1,2} R_{SS}$$

for very high CMRR \Rightarrow we need $R_{SS} \rightarrow \infty$
 \Rightarrow Better use cascode current source.


Single-ended DIT Amp

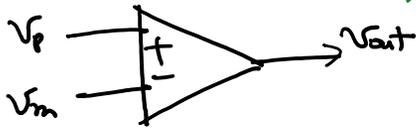

CMRR

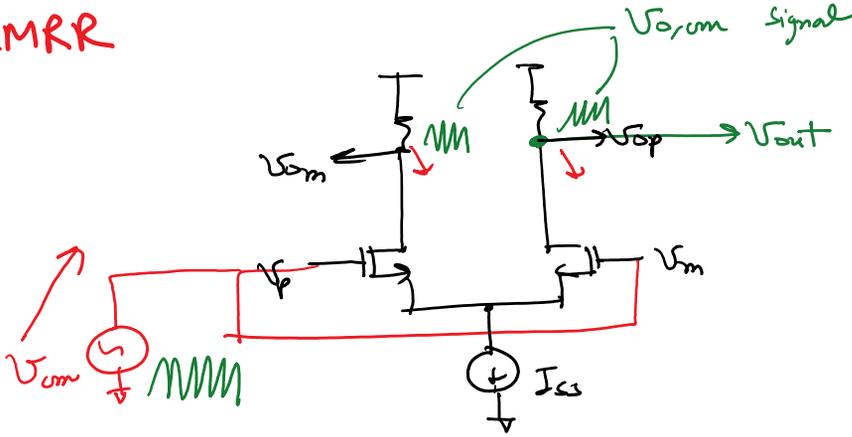

FD Amp



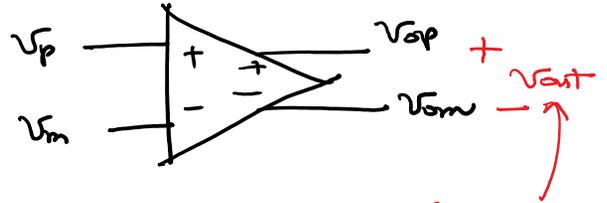


CM component cancels out!


CM gain = 0
 → CMRR → ∞
 unless there are circuit mismatches

→ CMRR is mostly used to characterize single-ended amplifiers

CMRR = 70 dB

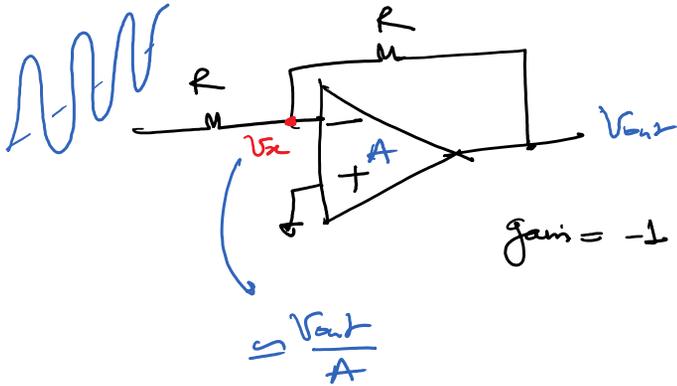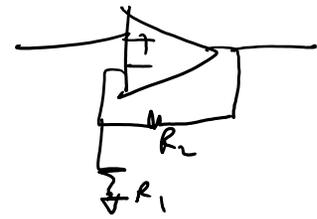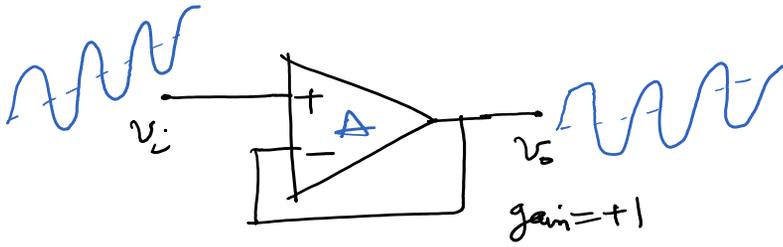

more tolerant to CM disturbances.

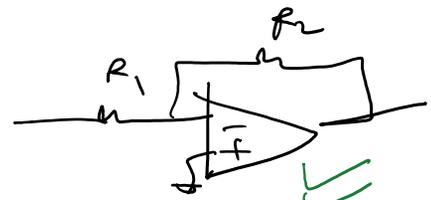

more tolerant to input CM disturbances.