
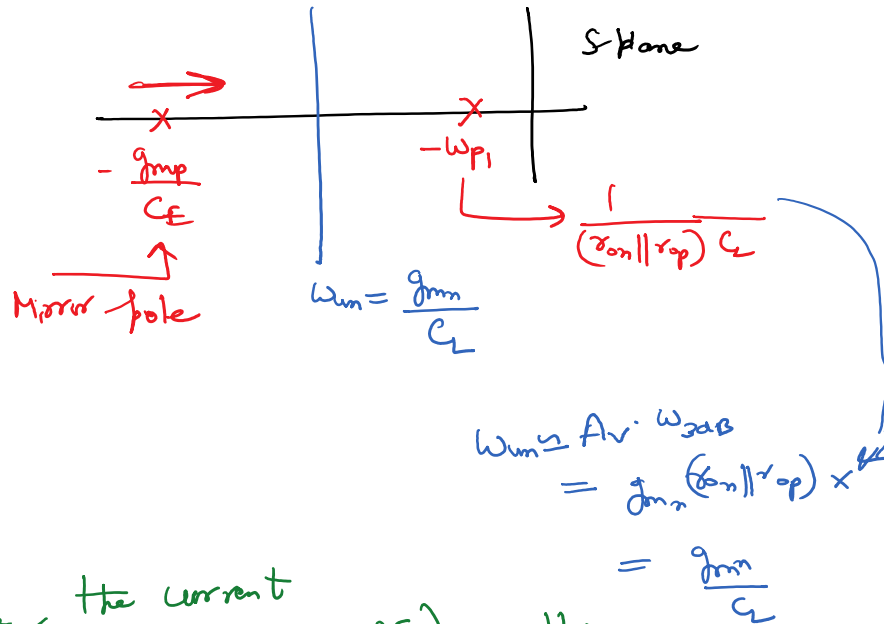


ECE 515 - Lecture 22

Thursday, November 8, 2018 11:08 AM

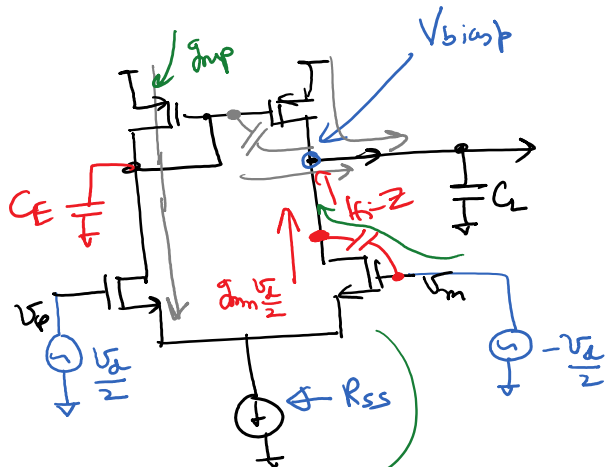

at the output node, the current $i_{d2} = g_m \frac{v_a}{2}$ and the signal $(-\frac{v_a}{2})$ coupled through C_{gd2} are of opposite polarity

→ RHP zero

$$\omega_{z2} = + \frac{g_{mn}}{C_{gd2}}$$

→ ω_T
very high frequency

$$\omega_T = \frac{g_m}{C_{gs}}$$

$$\omega_{z1} = - \frac{g_{mp}}{C_E} \leftarrow \text{LHP zero}$$

fast path



$$A_{fast}(s) = \frac{A_0}{(1 + s\omega_{p1})}$$

slow path:


$$A_{slow}(s) = \frac{A_0}{(1 + s/\omega_{p1})(1 + s/\omega_{p2})}$$


$$\begin{aligned} \frac{V_{out}}{V_{in}}(s) &= A_{slow}(s) + A_{fast}(s) \\ &= \frac{A_0}{(1 + s/\omega_{p1})} \left[\frac{1}{(1 + s/\omega_{p2})} + 1 \right] \\ &= \frac{A_0 (2 + s/\omega_{p2})}{(1 + s/\omega_{p1})(1 + s/\omega_{p2})} \end{aligned}$$
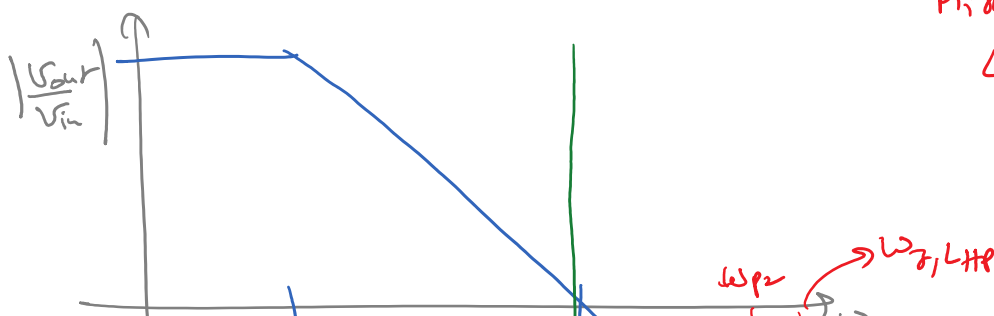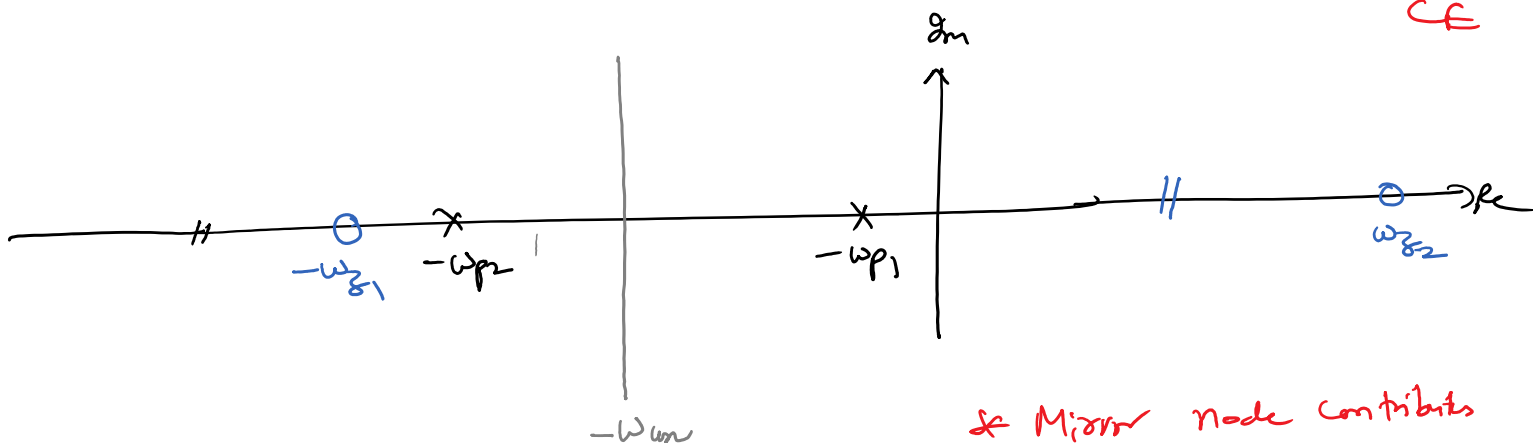
$$\begin{aligned} N(s) &= 0 \\ \Rightarrow s_z &= -2\omega_{p2} \\ \Rightarrow \omega_z &= -2\omega_{p2} \\ &= -\frac{2g_{mp}}{C_E} \end{aligned}$$





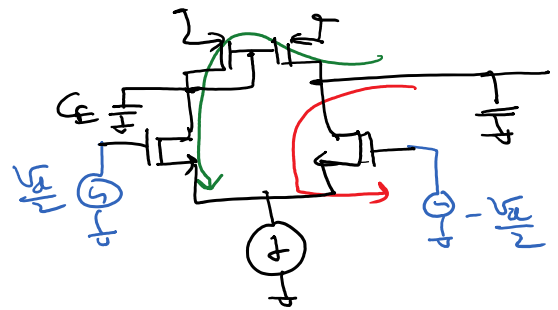* Mirror node contributes
Mirror pole &
LHP zero at
 $\frac{g_{mp}}{C_E} \leftarrow \frac{2g_{mp}}{C_E}$
frequencies



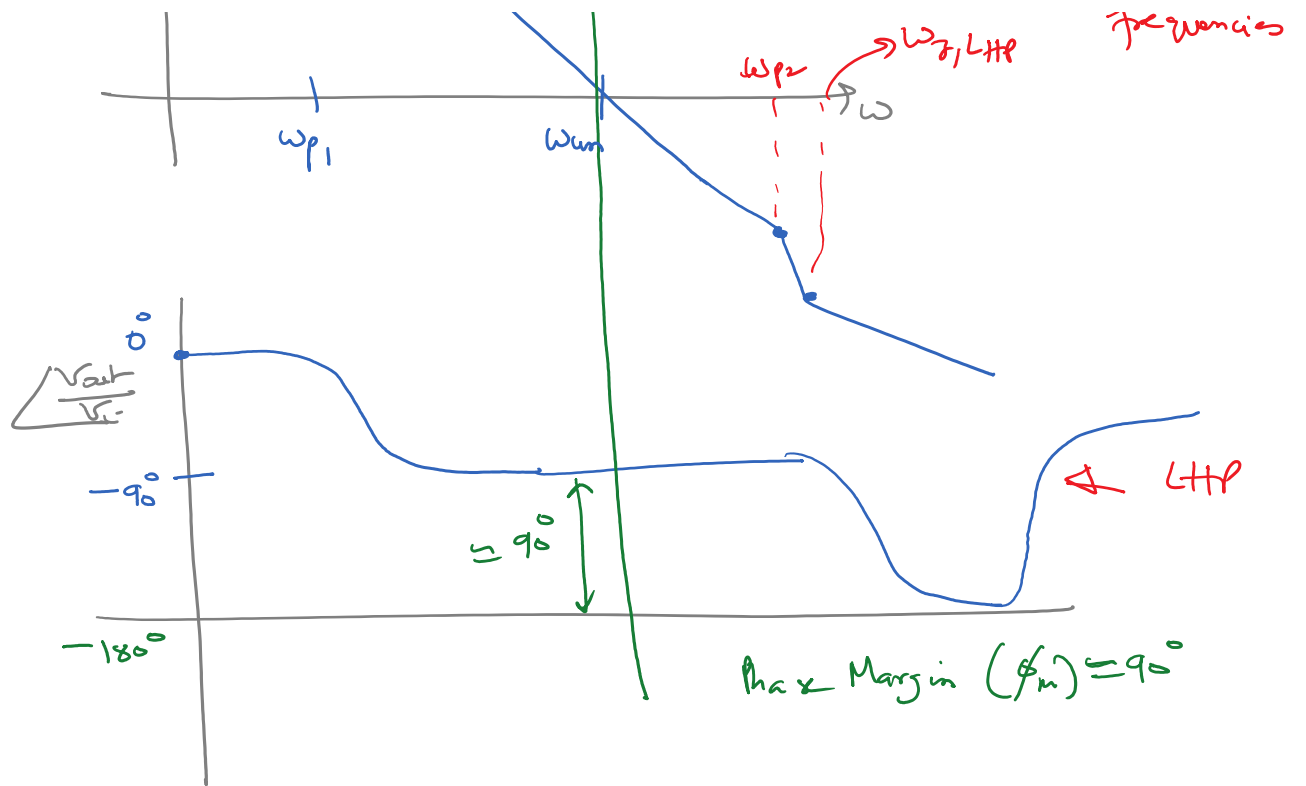

Operational Amplifiers (opamps) :

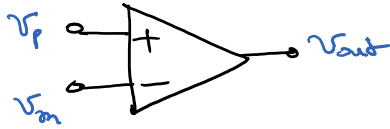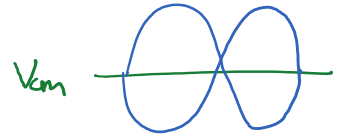


$$V_{out} = A(V_p - V_m)$$

Ideally $A \rightarrow \infty \Rightarrow$ for finite V_{out}
 $V_p \approx V_m$

$\hookrightarrow$ only in a negative feedback loop

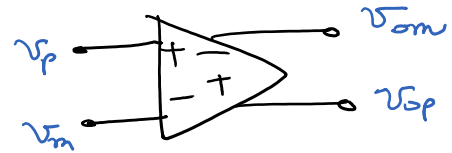Opamps $\rightarrow$ $\left\{ \begin{array}{l} A \rightarrow \infty \rightarrow \text{need high-gain} \\ R_{in} \rightarrow \infty \rightarrow \text{not a problem with CMOS} \\ R_{out} \rightarrow 0 \rightarrow \text{we will see about this} \end{array} \right.$




$$(V_{op} - V_{om}) = A(V_p - V_m)$$

$$\frac{V_{op} + V_{om}}{2} = V_{cm}$$

Need to stabilize the output
 Common-mode
 (CM feedback loop)
 CMFB.


Differential with CM-load

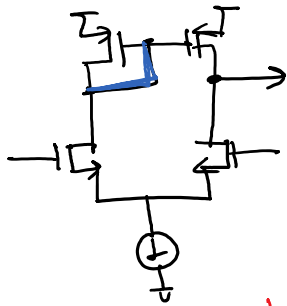


Ideally $\frac{W}{16L}$

$$\frac{W}{L}$$


$$V_{DD} \Delta \frac{V_{DD}}{2}$$

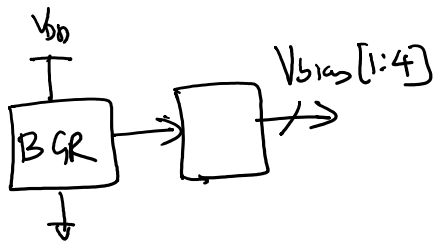

DC Replica Biasing Circuit

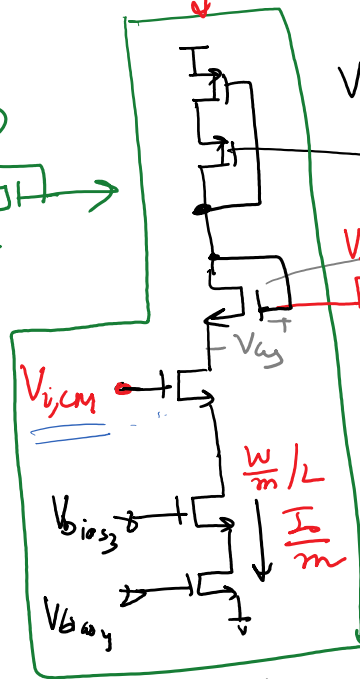

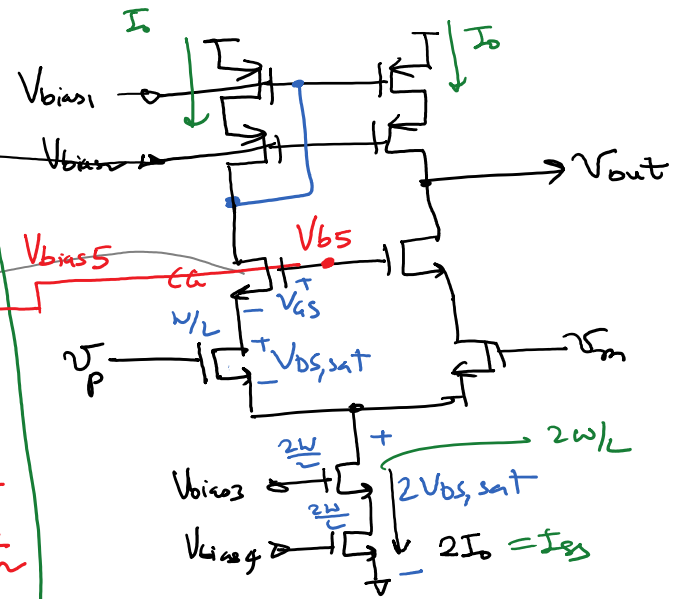transistors should have the same current density ($J = \frac{I}{W}$) as the main circuit



$$V_{b5} \Rightarrow 4V_{DS,sat} + V_{THN}$$

Multifinger layout of the MOSFET.

Telescopic Amplifier

$$A_v = g_{m1} \cdot (g_{m2} r_{on}^2) \parallel (g_{m3} r_{op}^2)$$

$$\approx g_{m1} \cdot \frac{g_{m2} r_{on}^2}{2}$$



$$= \frac{(g_{m2} r_{on})^2}{2}$$

if $g_{m2} r_{on}$ in nmos is 25

$$\Rightarrow A_v = 312.5$$

$$\Rightarrow 3 \times 100$$


$$40 + 5 = 45dB$$

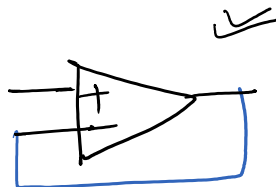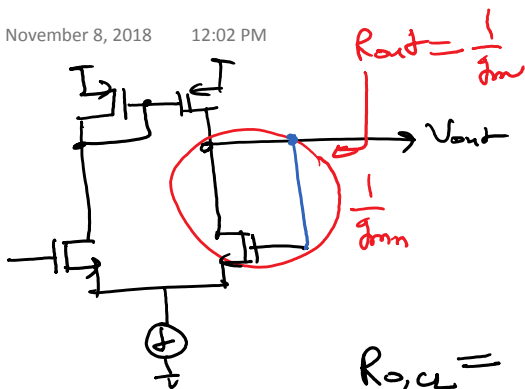

$$R_{o,c} = \frac{R_{o,c}}{1 + \text{loop gain}} \rightarrow \text{small output impedance}$$

$$\Rightarrow \frac{r_{op} || r_{on}}{g_{mn} \times (r_{op} || r_{on})} = \frac{1}{g_{mn}}$$

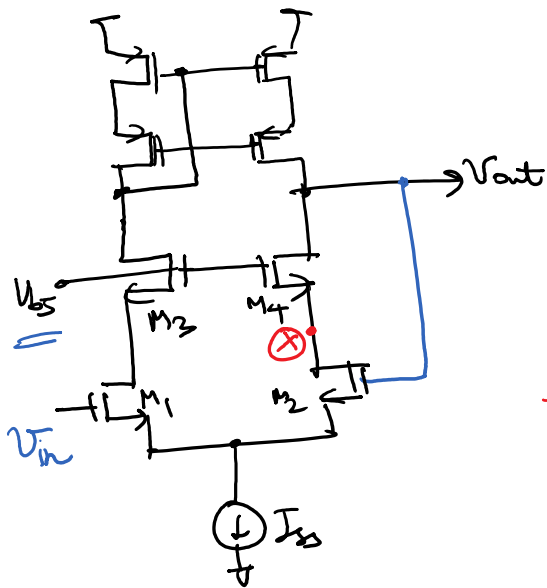* We should be able to short v_{out} to V_m of a Telescopic Opamp (single-stage)



Both M_2 & M_4 must be in saturation

for M_2 : $V_{DS2} > V_{DS,sat2}$

$$V_{D2} > V_{G2} - V_{THN}$$

$$V_x > V_{out} - V_{THN}$$

$$\Rightarrow \boxed{V_{out} \leq V_x + V_{THN}} \rightarrow \textcircled{1}$$

for M_4 : $V_{DS4} > V_{GS4} - V_{THN}$

$$\Rightarrow V_{D4} > V_{G4} - V_{THN}$$

$$\Rightarrow \boxed{V_{out} > V_{b5} - V_{THN}} \rightarrow \textcircled{2}$$

from $\textcircled{1}$ & $\textcircled{2}$:

$$V_{b5} - V_{THN} \leq V_{out} \leq$$