
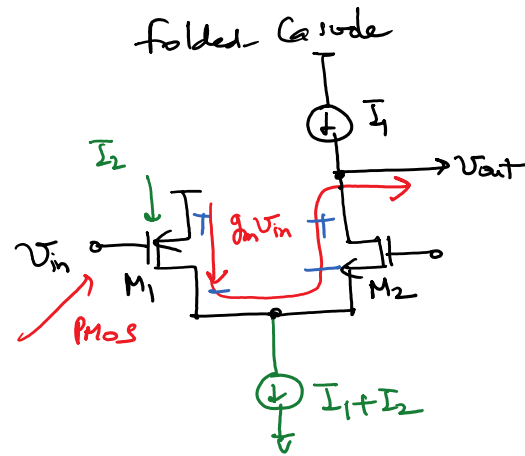


ECE 515- Lecture 23



Thursday, November 15, 2018 11:06 AM

Cascode

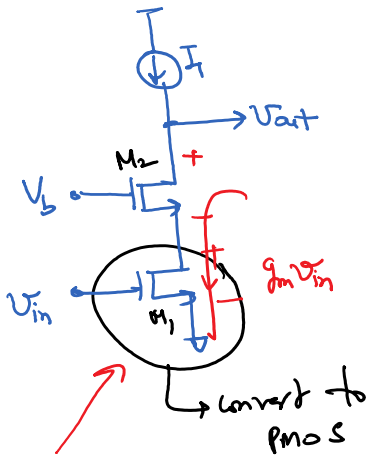

Small signal current is folded

folded Cascode Diffamp.

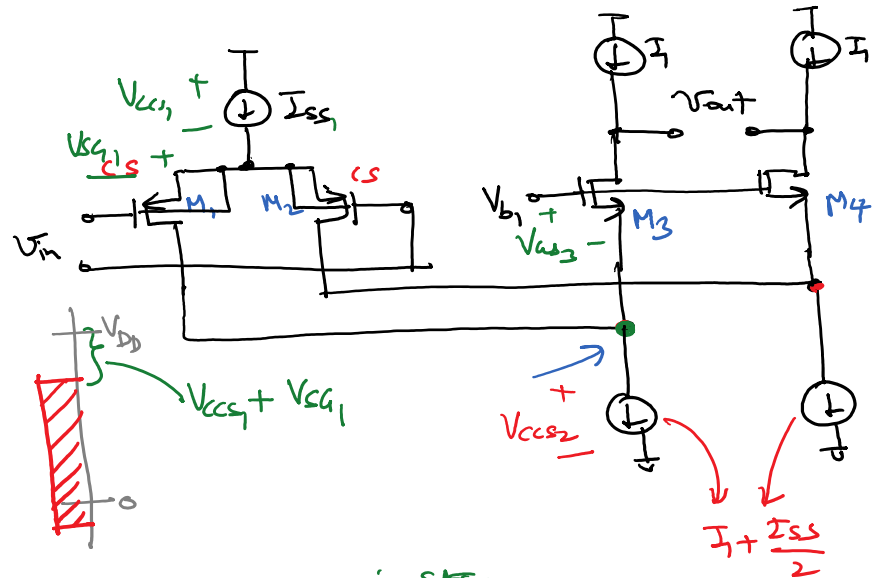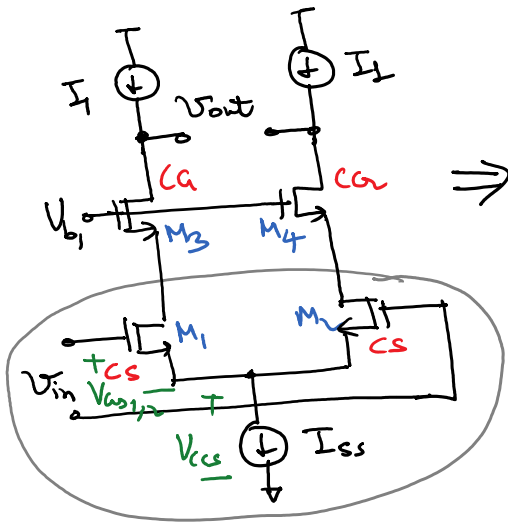

$$V_{GS1} + \frac{V_{SS}}{2} \leq V_{CM,in} \leq V_{b1} - V_{GS} + V_{THP}$$

* to keep M1 in SAT:

$$V_{SD1} \geq V_{SD,sat} = V_{SG1} - |V_{THP}|$$

$$\Rightarrow V_{GS} - V_{D1} \geq V_{GS} - V_{G1} - |V_{THP}|$$

$$\Rightarrow V_{G1} \geq V_{D1} - |V_{THP}|$$

$$V_{CM,in} \geq V_{b1} - V_{SG3} - |V_{THP}|$$


$$V_{GS3} + V_{CCS2}$$

$$= V_{CCS2} - |V_{THP}|$$

$$V_{DS,sat} - |V_{THP}| < 0$$

November 15, 2018 11:29 AM

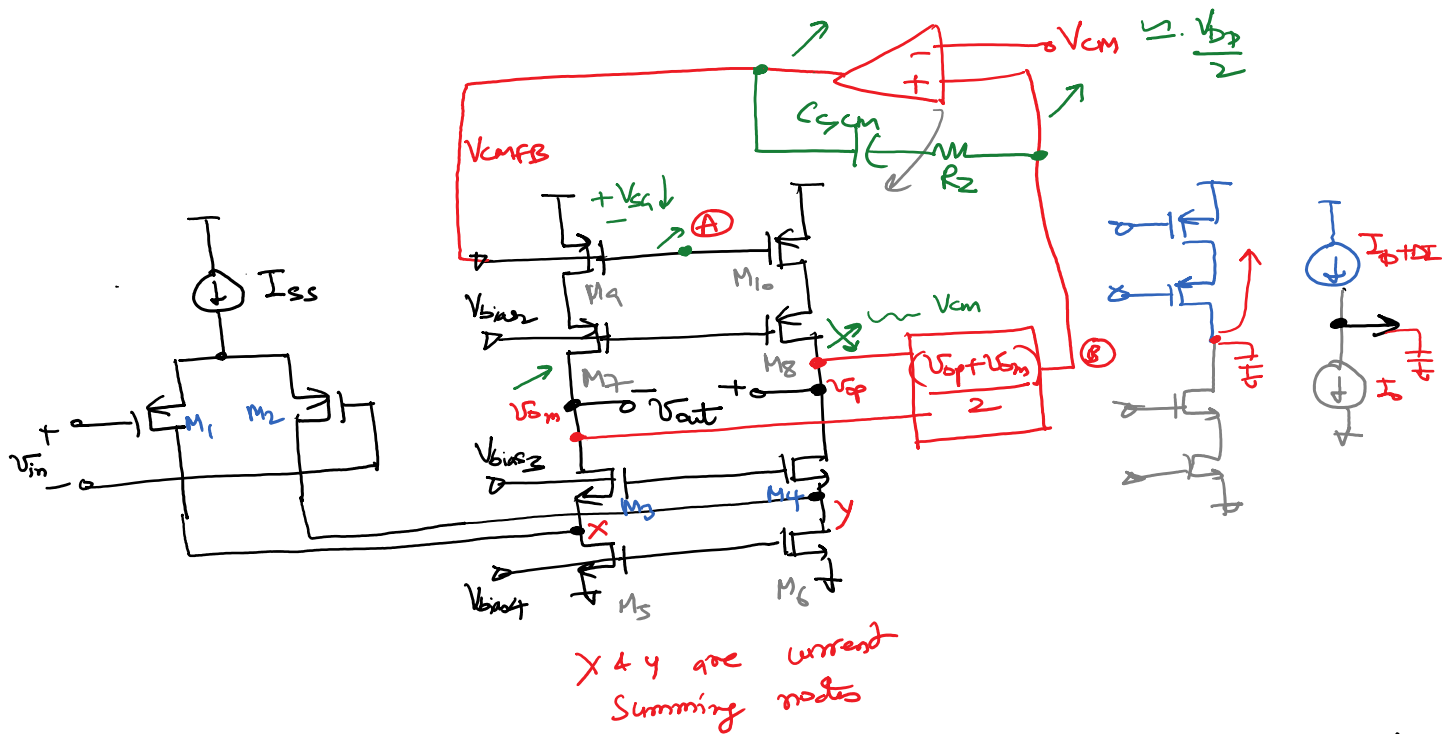Differential folded-Cascode opamp \rightarrow used widely in Switched Capacitor Circuits.



+ Two ^{independent} current sources (PMOS & NMOS cascode) fighting to set the out common-mode (DC) level.

L, solution is to make an current dependent upon another
 using a feedback loop to set the output CM-level
 (cancel) loop

x Common-mode feedback (CMFB) loop.



mode feedback

\hookrightarrow Need to compensate the CFB loop

$\hookrightarrow m \leq 60^\circ$




$$\angle PM \subseteq 60^\circ$$


Single-Ended folded Cascode Amplifier

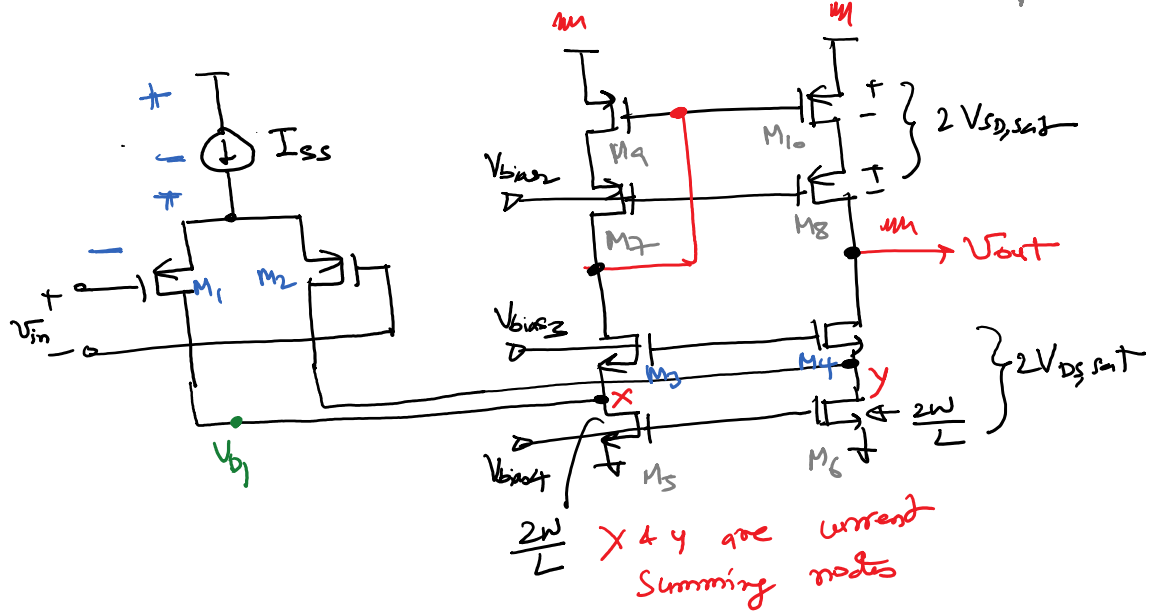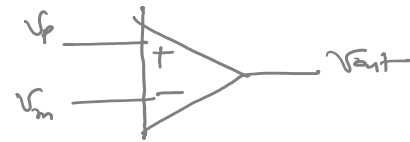


$$V_{cm, in} \leq V_{DD} - V_{css} - V_{sg1,2}$$

$$\begin{aligned} V_{cm, in} = V_{g1} &\geq V_{D1} - |V_{THP}| \\ &= V_{DS, sat5} - |V_{THP}| < 0 \end{aligned}$$

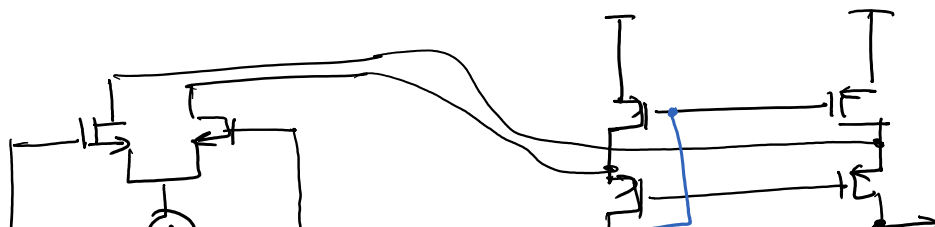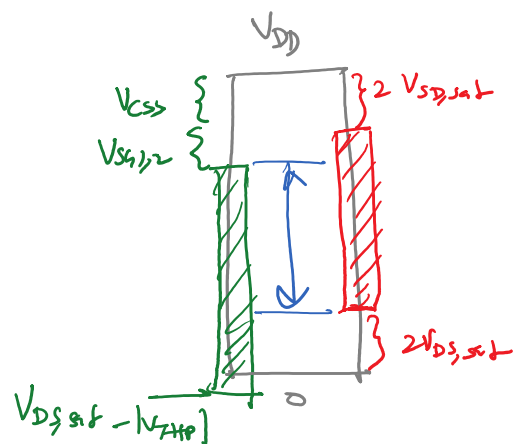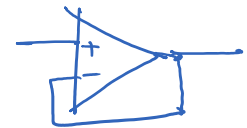


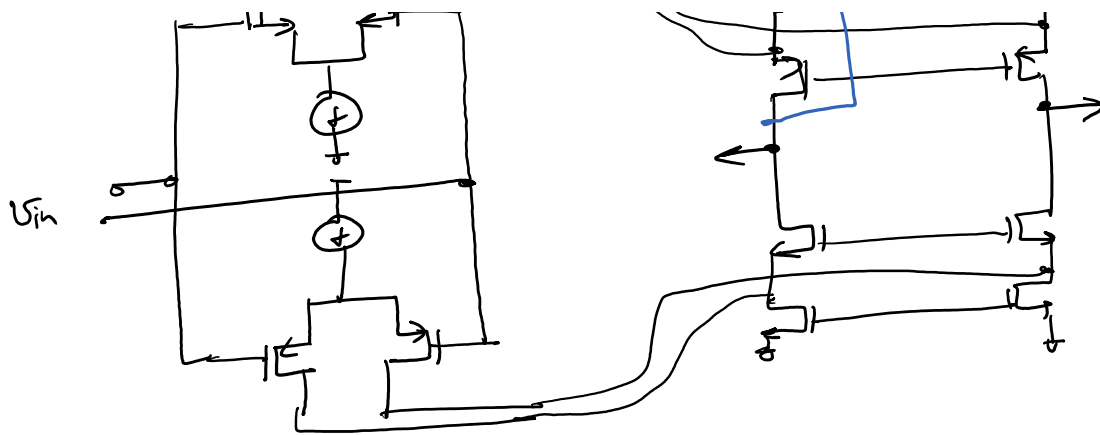

full rail-to-rail
input swing

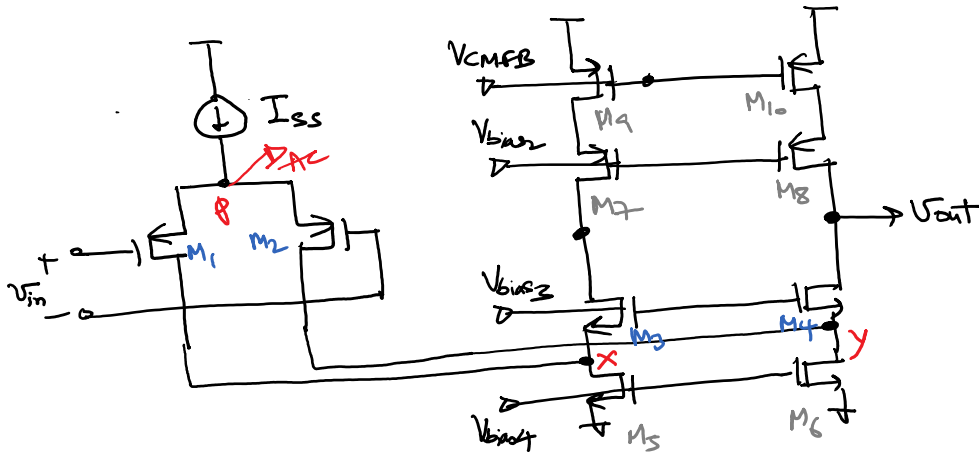

Differential Half Circuit

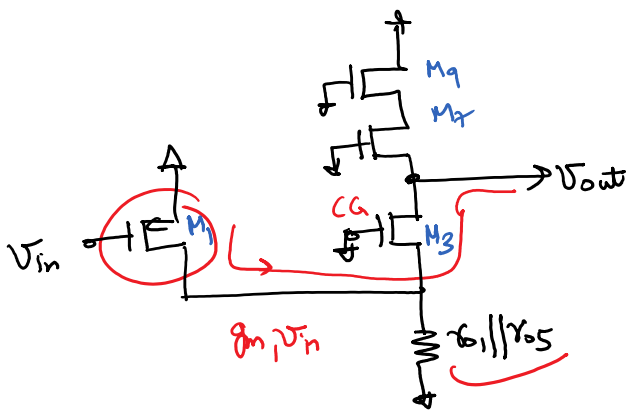

$$A_{v,DM} = -g_m \times R_{out}$$

$$R_{casp} \parallel R_{ceon}$$

$$= (g_{m7} r_{o7} r_{o9}) \parallel (g_{m3} r_{o3} \cdot r_{o1} \parallel r_{o5})$$

Assume all g_m 's are g_m
all r_o 's are r_o

$$\Rightarrow A_{v,DM} = -g_m \cdot (g_m r_o^2) \parallel (g_m r_o \cdot \frac{r_o}{2})$$

$$= -g_m \cdot g_m r_o^2 \parallel \frac{g_m r_o^2}{2}$$


$$1 \parallel \frac{1}{2}$$

$$\frac{\frac{1}{2}}{\frac{3}{2}} = \frac{1}{3}$$

$$= -\frac{1}{3} g_m^2 r_o^2$$

gain slightly smaller than Telescopic Stage

fc Pole locations :

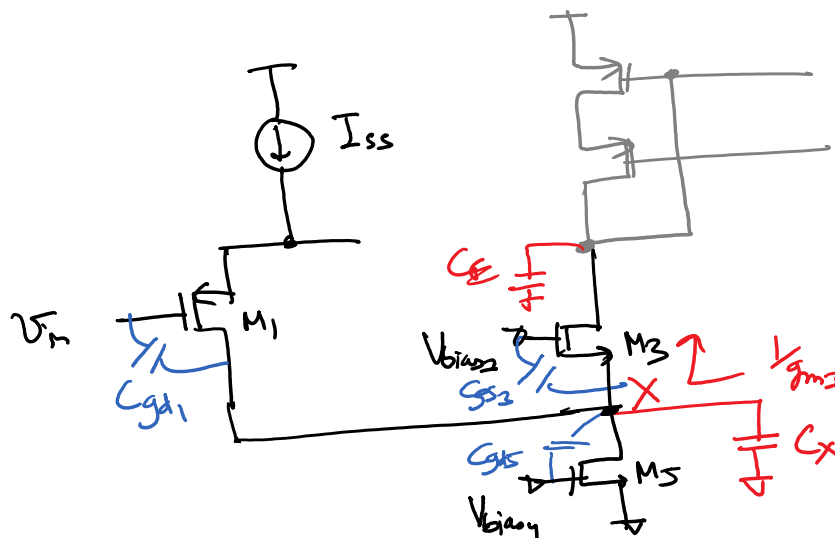

$$C_x = \underbrace{C_{gs3} + C_{db3}}_{M_3} + \underbrace{C_{db1} + C_{gd1}}_{M_1} + \underbrace{C_{gs5} + C_{db5}}_{M_5}$$

$$\omega_x \leq \frac{1}{\frac{1}{g_{m3}} \cdot C_x}$$

* Current summing node creates another pole,
hopefully at higher frequency $\omega_x \Rightarrow \omega_{um}$

$$\omega_{um} \leq \frac{g_{m1}}{C_L} \quad \leftarrow \text{single stage}$$