

ECE 515 - Lecture 3

Thursday, August 30, 2018 11:02 AM

g_m, g_{m_b}, r_o

AC Analysis

- ① Draw the DC picture
- short ac sources
 - open ac current


Find Bias points for all devices

- ② Using DC values from ①, find small-signal parameters (g_m, r_o , etc) for all devices



"Linearization step" • AC analysis




- ③ Draw AC picture → replace devices by small signal models
→ short all DC voltage sources
- Solve for

→ for all DC current sources A_k values

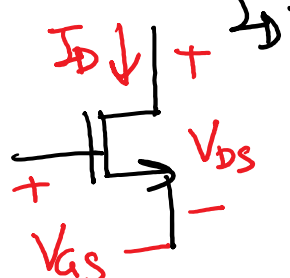
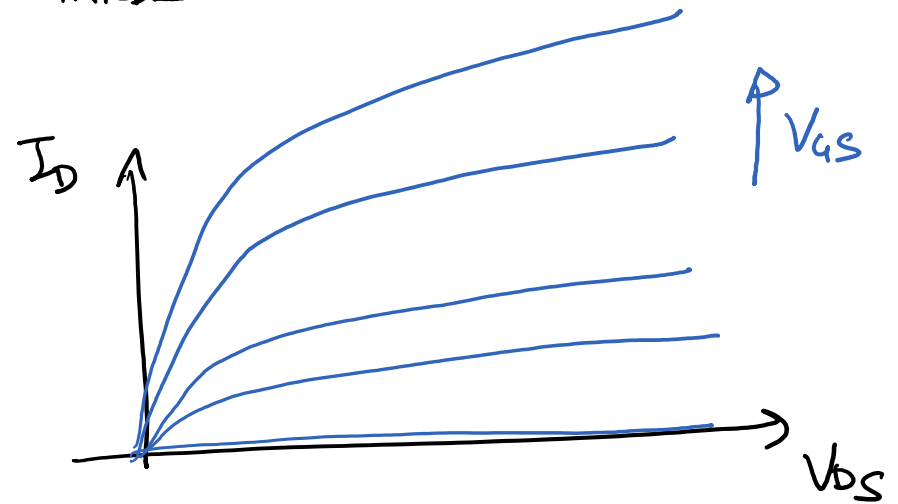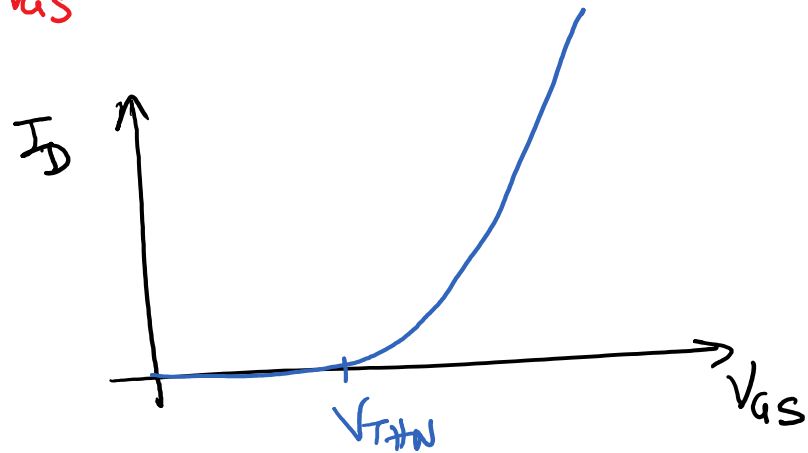
$$I_D = \begin{cases} \frac{1}{2} \mu_n \frac{W}{L} (V_{GS} - V_{THN})^2 & \text{SAT} \\ \mu_n \frac{W}{L} \left((V_{GS} - V_{THN}) V_{DS} - \frac{V_{DS}^2}{2} \right) & \text{TRIODE} \end{cases}$$



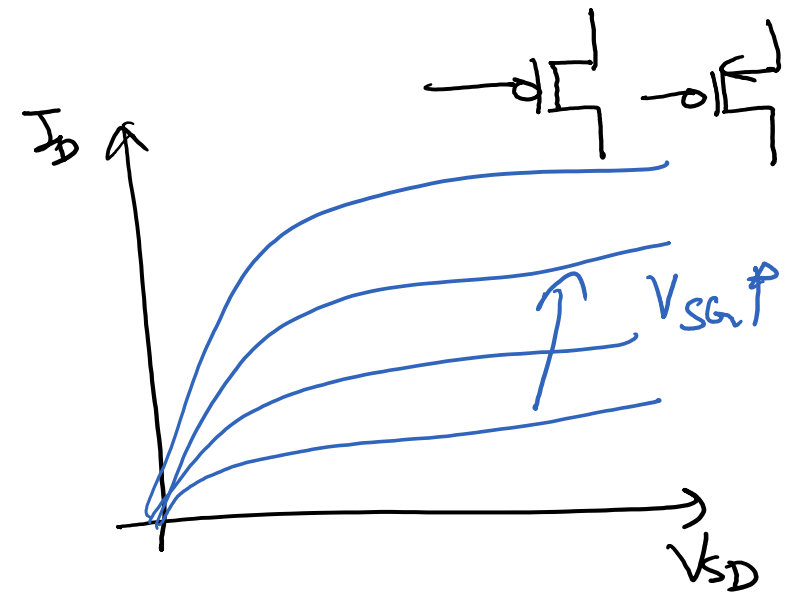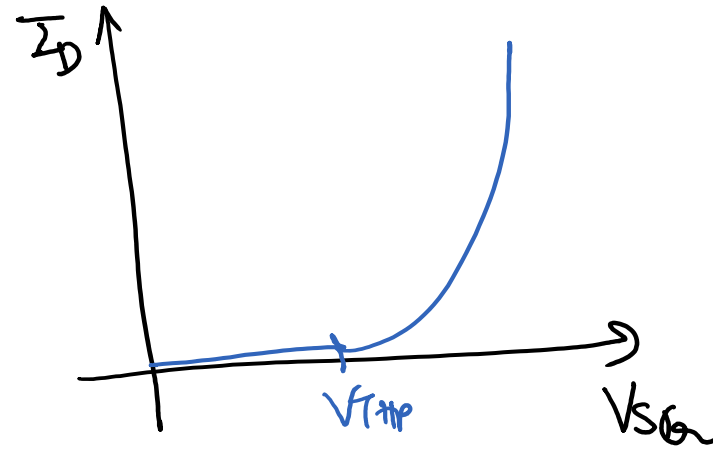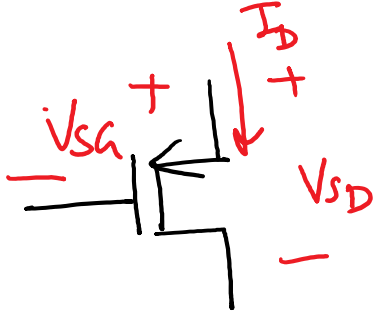


$I_D = \left\{ \begin{array}{l} \frac{1}{2} \mu_p \frac{W}{L} \cdot (V_{sg} - V_{thp})^2 \\ \mu_p \frac{W}{L} \left[(V_{sg} - V_{thp}) V_{sd} - \frac{V_{sd}^2}{2} \right] \end{array} \right.$

$$\frac{1}{2} \mu_p \frac{W}{L} \cdot (V_{sg} - V_{thp})^2$$

SAT

$$\mu_p \frac{W}{L} \left[(V_{sg} - V_{thp}) V_{sd} - \frac{V_{sd}^2}{2} \right]$$

TRIODE

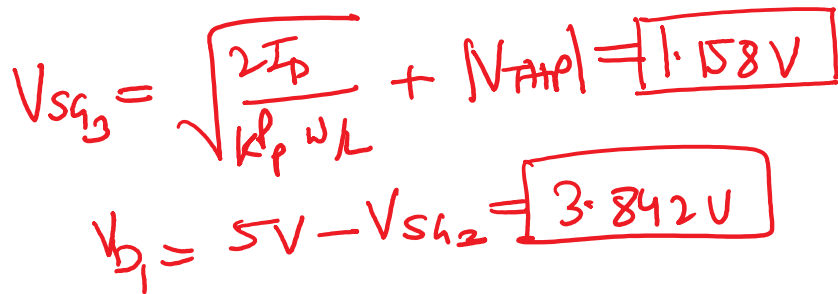

M_2 is in SAT ✓

M4

$V_{SG4} = 5V$ ← most likely in triode

$$I_D = k_p \frac{W}{L} \left[(V_{SG4} - V_{THP}) V_{SD} - \frac{V_{SD}^2}{2} \right]$$

$$\Rightarrow 20\mu = 40\mu \cdot \frac{30}{2} \left[4.1x V_{SD} - \frac{V_{SD}^2}{2} \right]$$



$$\Rightarrow V_{SD4} = 8.13 \text{ mV}$$

\Rightarrow

Equivalent circuit

Ac picture

$\lambda = 0$
 $\lambda = 0$

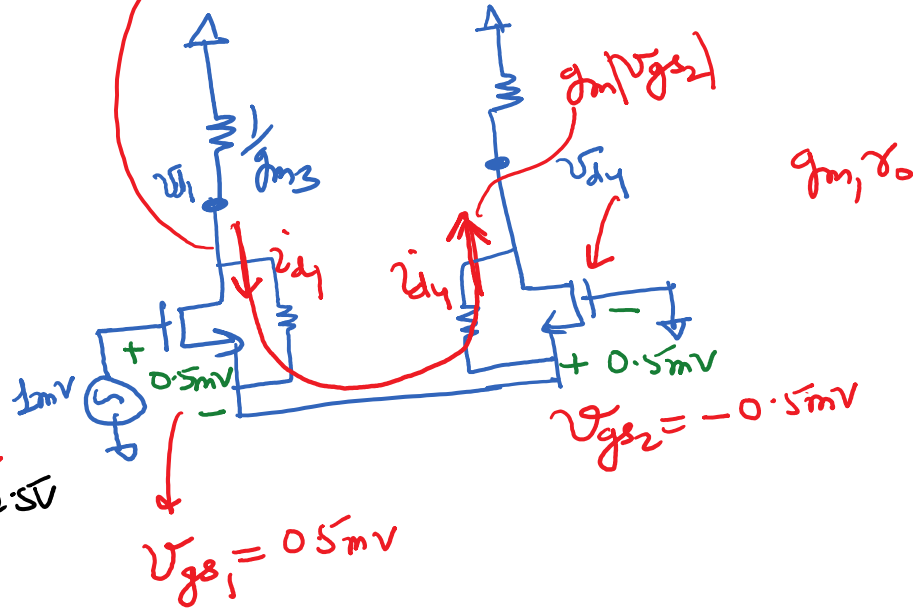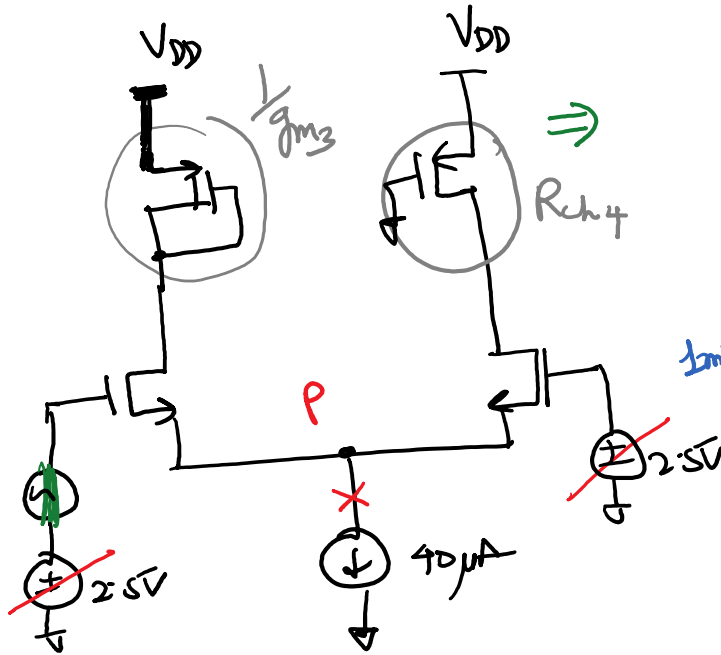

$$g_{m1} = g_{m2} = \sqrt{2\beta_n I_D} = 150 \frac{\mu A}{V}$$

$$\frac{1}{g_{m3}} = 6.67 k\Omega$$

$$R_{ch3} = 407 \Omega$$

$$\lambda_o = \frac{1}{A_{Dout}} = \infty$$

$$v_{d1} = v_{d2} = \frac{150 \mu A}{V} \times 0.5 mV = 75 nA$$

$$v_{d1} = 0 - 75 nA \times \frac{1}{g_{m3}} = -0.5 mV$$

$$v_{d1} = 75 nA \times R_{ch} = 0.03 mV$$

$$V_{D1} = 3.842$$

$$V_{d1} = -0.5 \text{ mV}$$

Superposition


$$V_{D1} = 3.842 - 0.5 \text{ mV} \sin(2\pi f_{in} t)$$

$$V_{D2} = 4.992 + 0.03 \text{ mV} \cdot \sin(2\pi f_{in} t)$$



Spectra

$\begin{cases} \bullet \text{ DC analysis} \\ \bullet \text{ op} \end{cases} \Rightarrow \begin{matrix} \text{dc operating point} \\ \text{DC node voltages} \end{matrix}$

• AC analysis

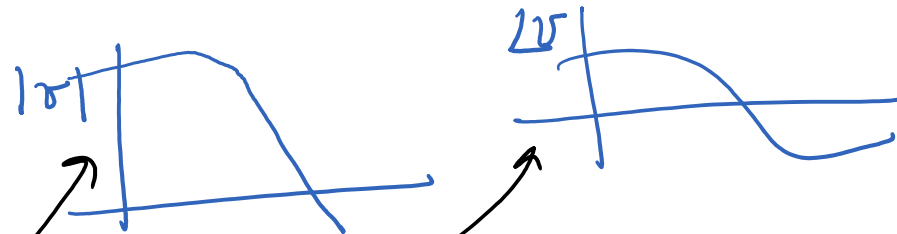


• tran

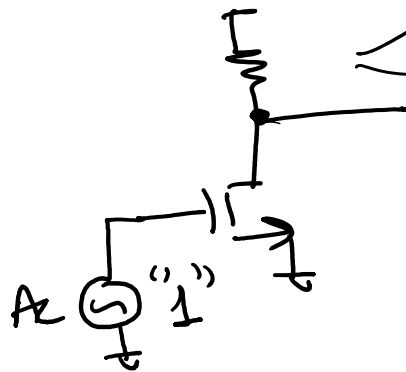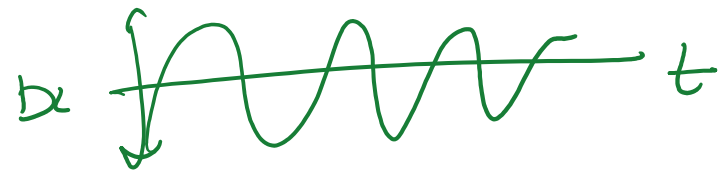

Thursday, August 30, 2018

11:52 AM

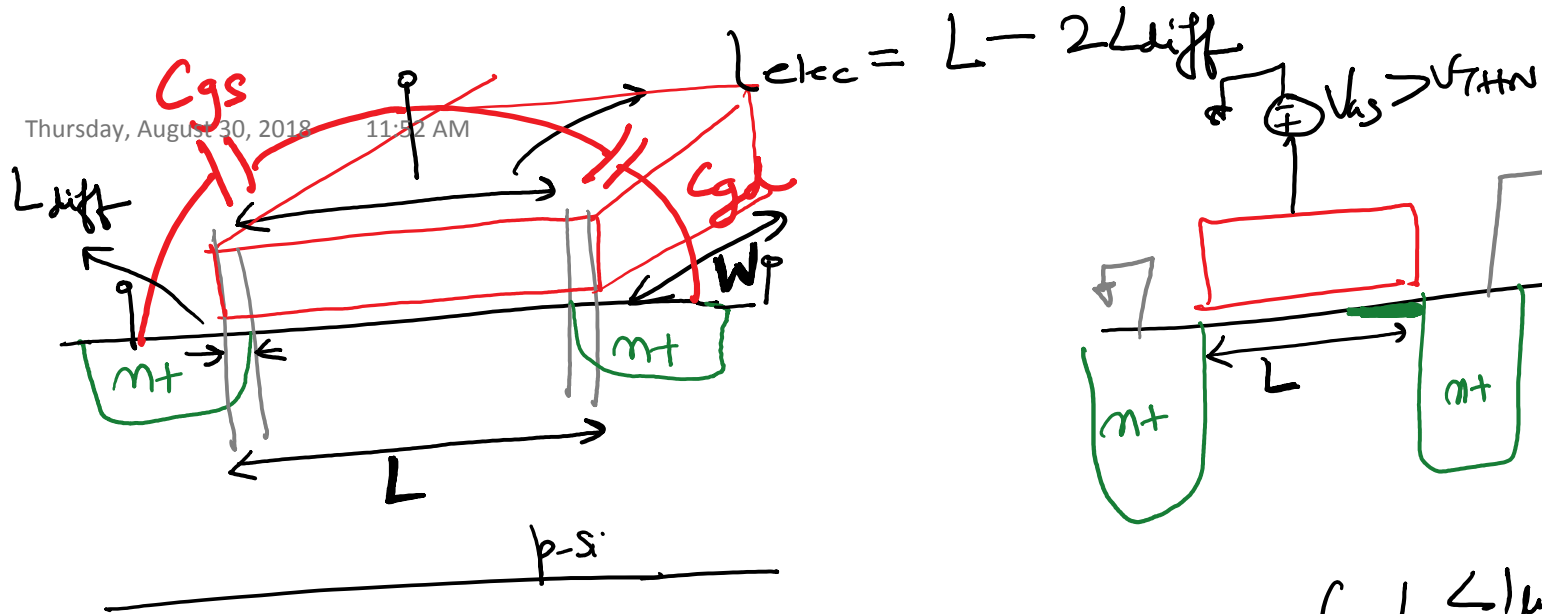

* In short-channel technologies. ($L < 1\mu m$)

$V_{ds} \uparrow$



$V_{thn} \downarrow$

DIBL

drain induced barrier lowering

* gate oxide are thin
 \rightarrow gate oxide leakage

Drift velocity

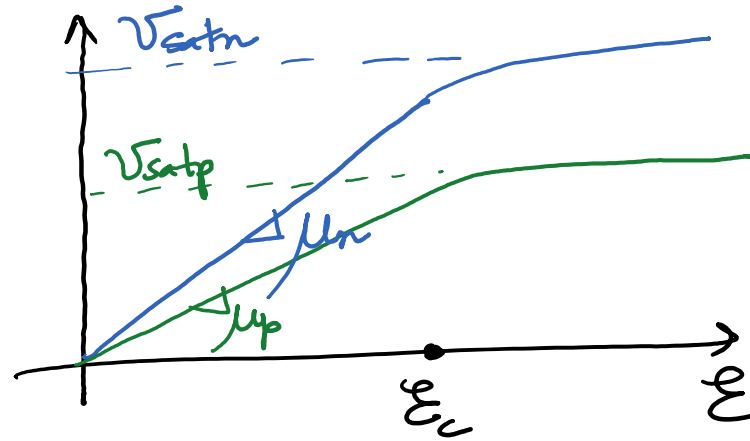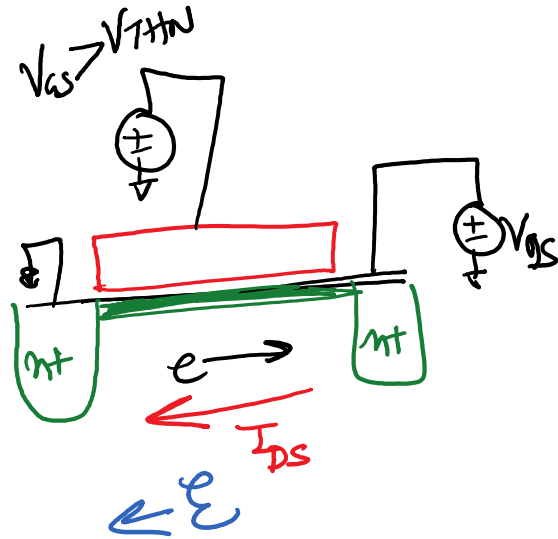

$$\mathcal{E} = \frac{V_{DS,sat}}{L}$$

$$L \downarrow \Rightarrow \mathcal{E} \uparrow$$




$$v_d = \mu_n \mathcal{E}$$

↑ mobility

μ_n, μ_p

$$\lambda \propto \frac{1}{L}$$

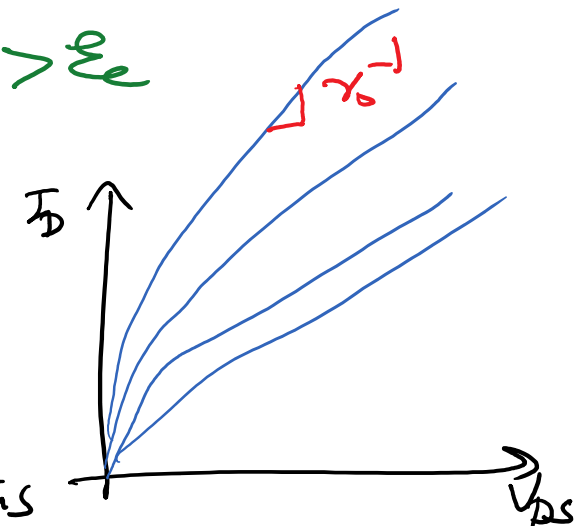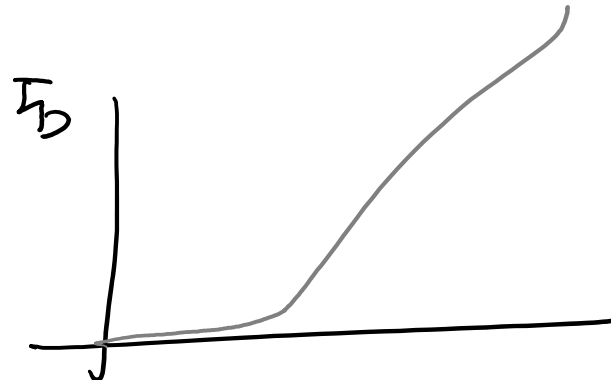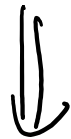
Drift velocity is saturated for $\mathcal{E} > \mathcal{E}_c$



output resistance gets smaller in short channel process



$g_{m\gamma_0} \downarrow$ with $L \downarrow$

MOSFET Transition frequency, f_T :

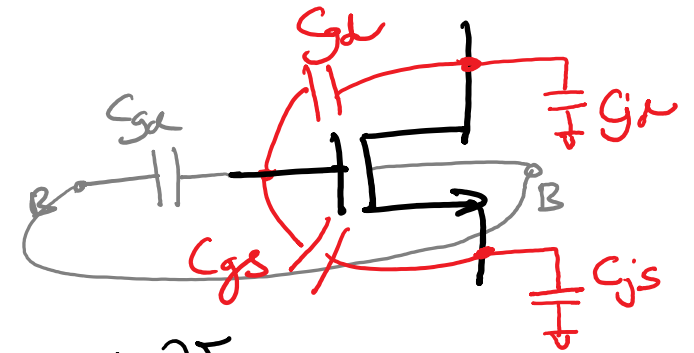

$$i_d = g_m V_{gs}$$

AC

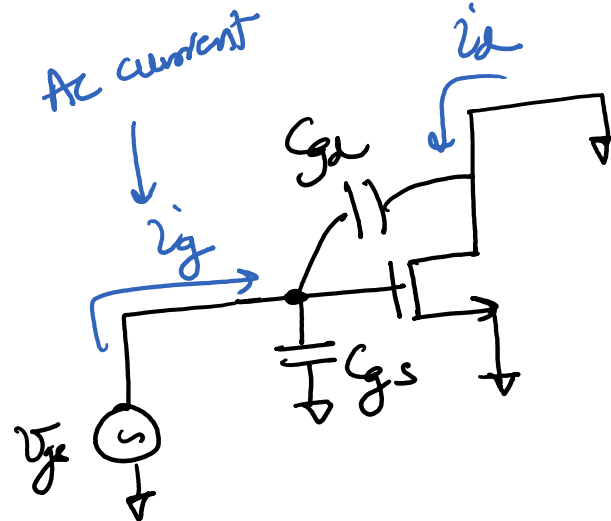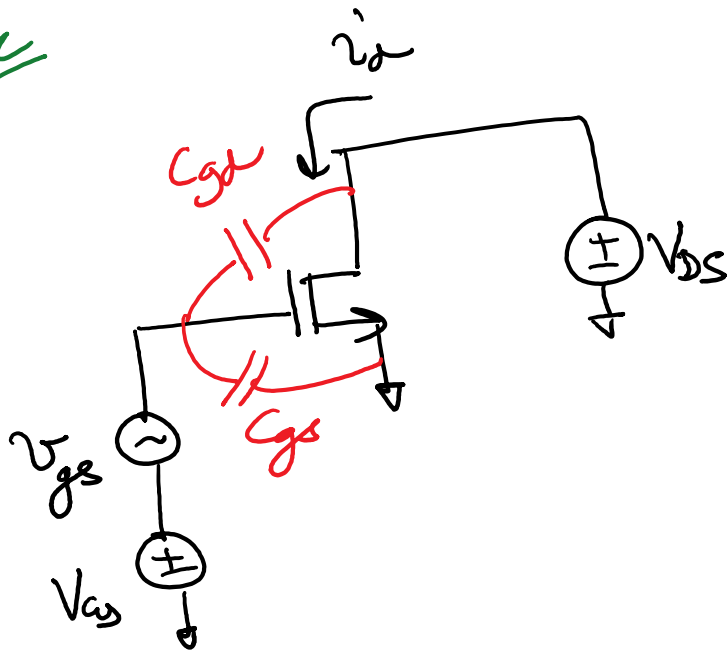

$$V_{gs} = i_g \times \frac{1}{s(C_{gd} + C_{gs})} \quad \text{--- (1)}$$

$$i_d = g_m V_{gs} \quad \text{--- (2)}$$

$$s \rightarrow j\omega$$

$$\Rightarrow \left| \frac{i_d}{i_g} \right| = \frac{g_m}{s(C_{gs} + C_{gd})} = 1 \Rightarrow f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$

$$\Rightarrow \left| \frac{v_d}{v_g} \right| = \frac{\omega_m}{s(C_{gd} + C_{gs})} = 1 \Rightarrow f_T = \frac{1}{2\pi(C_{gs} + C_{gd})}$$

Transition frequency