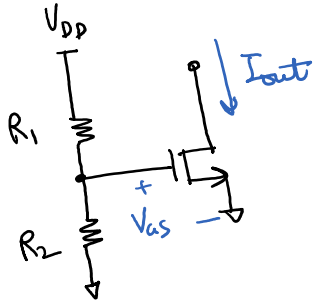


# ECE 515 - Lecture 5

Thursday, September 6, 2018 11:06 AM

## Current Mirrors:

Current Sources are widely used in IC Design






$$I_{out} \approx \frac{k_n}{2} \cdot \frac{W}{L} \left( \frac{R_2}{R_1 + R_2} V_{DD} - V_{THN} \right)^2$$

$I_{out}$  depends upon  $\rightarrow V_{DD}$ , process ( $V_{THN}$ ,  $k_n$ ), Temperature

$\Rightarrow I_{out}$  is poorly defined!  
 $\rightarrow$  PVT variations


Solution: Create a stable, "precise" current reference and "copy" the currents.

"Golden Reference"

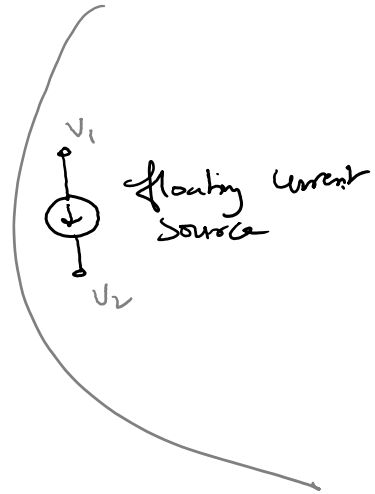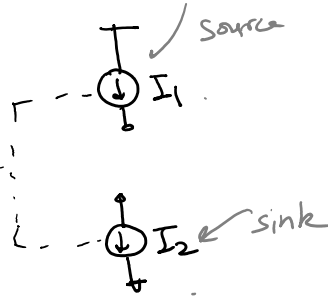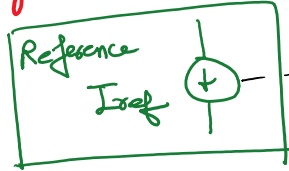

\* How to generate copies of a reference current?

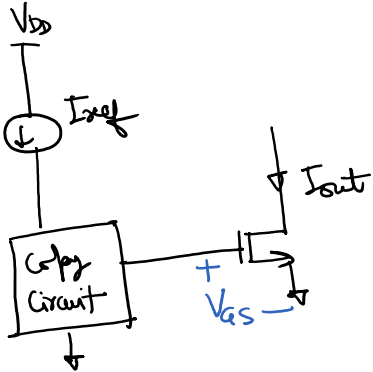
How to assure that  $I_{out} = I_{ref}$ ?





$$I_D = f(V_{gs}, V_{DS})$$

↓ Diode connect

$$I_D = f(V_{gs})$$

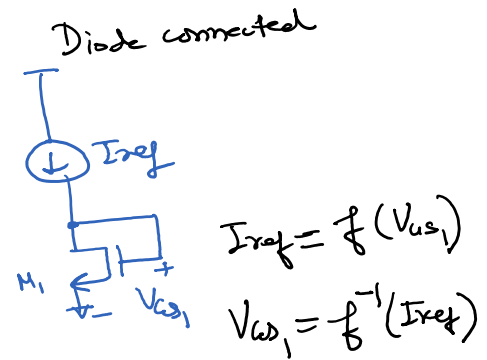

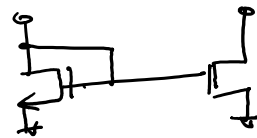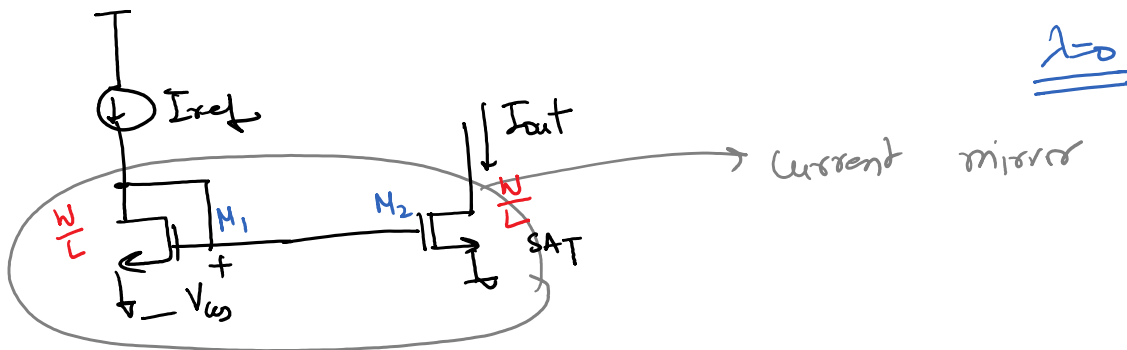

$$V_{gs} = f^{-1}(I_{ref}) \Rightarrow I_{out} = f(V_{gs}) = f(f^{-1}(I_{ref})) = I_{ref}$$

for  $\lambda=0$ ,

$$I_{ref} = \frac{1}{2} k_n \left(\frac{W}{L}\right)_1 (V_{gs} - V_{thn})^2$$

$$I_{out} = \frac{1}{2} k_n \left(\frac{W}{L}\right)_2 (V_{gs} - V_{thn})^2$$

$$\frac{I_{out}}{I_{ref}} = \frac{(W/L)_2}{(W/L)_1}$$



for the same  $L$ :  $L=L_2$

$$\frac{I_{out}}{I_{ref}} = \frac{W_2}{W_1}$$



$$I_{out} = \left(\frac{W_2}{W_1}\right) I_{ref}$$

\* Copy and scale currents by  $W$  ratio

Same Lengths

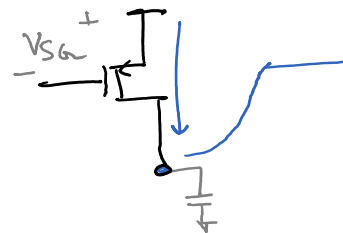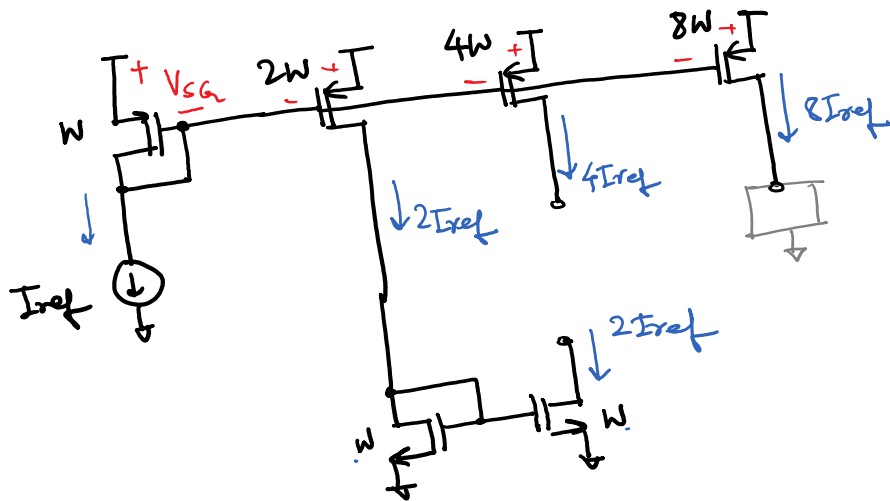

What happens when  $\lambda > 0$  ?

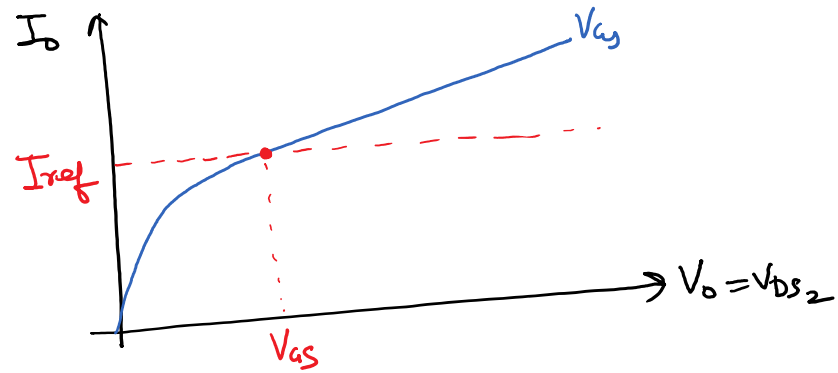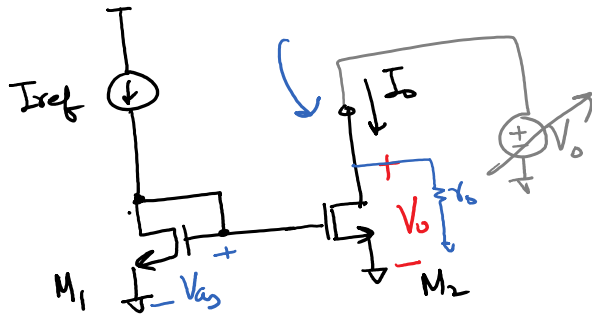

$\Rightarrow V_{DS2} = V_{DS1} = V_{GS1}$  for precise matching of currents

# Matching in Current Mirrors:



$I_{out}$

$I_{out}$  can significantly differ from  $I_{ref}$  due to

$\Delta(\frac{W}{L})$

$\Delta V_{thn}$

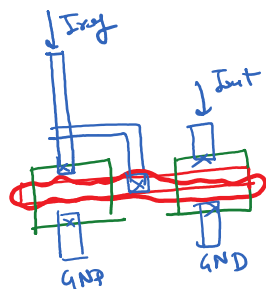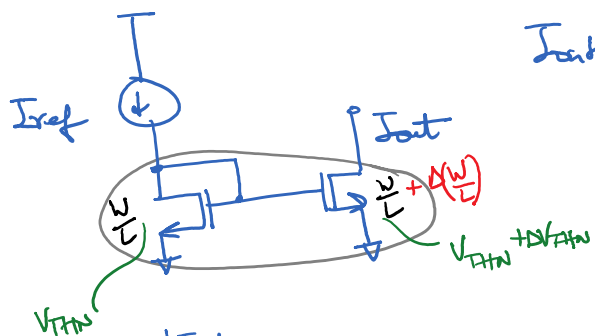$t_{ox} \rightarrow C_{ox}$   
major factors



If  $y = f(x_1, x_2, \dots)$  then

$$\Delta y = \underbrace{\frac{\partial f}{\partial x_1}}_{\text{sensitivity}} \cdot \underbrace{\Delta x_1}_{\text{mismatch}} + \frac{\partial f}{\partial x_2} \cdot \Delta x_2 + \dots$$

mismatch is weighed by sensitivity

$$I_D = \frac{k_p n}{2} \left(\frac{W}{L}\right) (V_{GS} - V_{THN})^2$$

$$\Delta I_D = \frac{\partial I_D}{\partial (W/L)} \cdot \Delta(W/L) + \frac{\partial I_D}{\partial (V_{GS} - V_{THN})} \cdot \Delta(V_{GS} - V_{THN})$$

$$= \frac{k_p n}{2} (V_{GS} - V_{THN})^2 \cdot \Delta(W/L) - k_p n \cdot \frac{W}{L} \cdot (V_{GS} - V_{THN}) \cdot \Delta V_{THN}$$

normalize by  $I_D$

$$\boxed{\frac{\Delta I_D}{I_D} = \frac{\Delta(W/L)}{W/L} - \frac{2 \Delta V_{THN}}{(V_{GS} - V_{THN})}}$$

$$\sigma_{\frac{\Delta I_D}{I_D}}^2 = \frac{\sigma_{\frac{\Delta(W/L)}{W/L}}^2}{(W/L)^2} + \frac{4 \sigma_{\Delta V_{THN}}^2}{(V_{GS} - V_{THN})^2}$$

To minimize current mismatch

① Overdrive should be large

$$\textcircled{2} \quad V_{\Delta THN} = \frac{A_{V_{THN}}}{\sqrt{W/L}}$$

$$V_{\Delta THN} \propto \frac{1}{\sqrt{W/L}}$$

large area

in sub $\mu$  designs, we end up with more parasitic capacitances



with large 'WL' area to  
contain mismatch.

↳ slower speed

Also for  $\lambda > 0$

$$\frac{I_{D2}}{I_{D1}} = \frac{(w/L)_2}{(w/L)_1} \cdot \frac{1 + \lambda (V_{DS2} - V_{DS,sat})}{1 + \lambda (V_{DS1} - V_{DS,sat})}$$

↳ dominant source of mismatch

↳ cascode