

CMOS COMPARATORS



COMPARATOR DESIGN CONSIDERATIONS

Comparator =


- Preamplifier (optional in some cases)
- + Reference Subtraction (optional for single-bit case)
- + Regenerative Latch

Design Considerations

- Accuracy (dynamic and static offset, noise, resolution)
- Settling time (tracking BW, regeneration speed)
- Sensitivity/resolution (gain)
- Metastability (ability to make correct decisions)
- Overdrive recovery (memory)
- Power consumption





EXAMPLE CMOS COMPARATOR

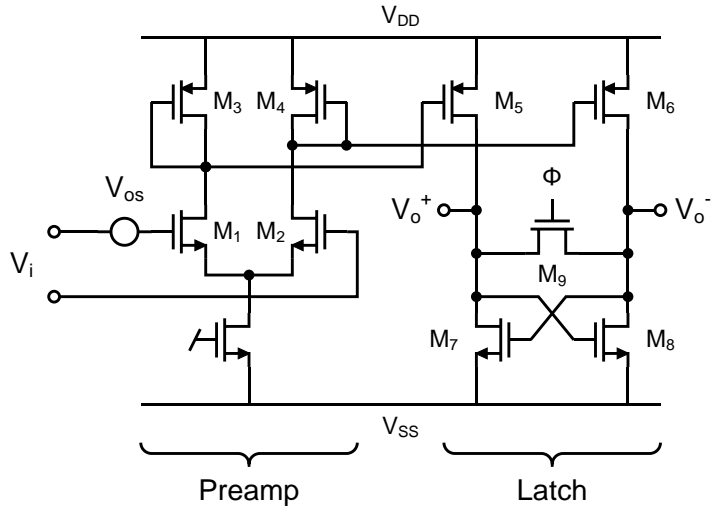

- ❑ Several Preamp and latch topologies are possible
- ❑ Input-referred offset V_{os} introduced due to:
 - Preamp input pair mismatch
 - PMOS loads and current mirror
 - Latch offset
 - Charge-Injection mismatch in the reset switch
 - Clock feed-through imbalance of the reset switch
 - Clock routing
 - Parasitic mismatch




LATCH REGENERATION

  

- Exponential regeneration due to positive feedback of cross-coupled pair M_7 and M_8



REGENERATION SPEED – LINEAR MODEL

 



$$\begin{cases} V_o^+ = -V_o^- \\ V_o^+ = -g_m \cdot V_o^- / sC_L \end{cases} \Rightarrow \begin{pmatrix} 1 & 1 \\ 1 & g_m/sC_L \end{pmatrix} \begin{pmatrix} V_o^+ \\ V_o^- \end{pmatrix} = 0$$

$$\Delta(s) = g_m/sC_L - 1 = 0 \Rightarrow s_p = g_m/C_L, \text{ single RHP pole}$$

$$V_{out}(t) = V_o \cdot \exp(t \cdot g_m / C_L)$$



REG. SPEED – LINEAR MODEL

  


V_o	$V_o(t=0)$	$t/(C_L/g_m)$
1V	100mV	2.3
1V	10mV	4.6
1V	1mV	6.9
1V	100 μ V	9.2


$$t = \frac{C_L}{g_m} \cdot \ln \left[\frac{V_o(t)}{V_o(0)} \right]$$




REG. SPEED – LINEAR MODEL

 

$$|A_{V1}| = \frac{g_{m1}}{g_{m3}}$$

 

$$|A_{V2}| = \frac{g_{m5} R_9}{2 - g_{m7} R_9}, \quad \frac{R_9}{2} < \frac{1}{g_{m7}} \text{ to be amplifier.}$$

 


$$V_o(0) = V_i(0) \cdot A_V = V_i(0) \cdot A_{V1} A_{V2}$$

$$V_o(t) = V_i(0) \cdot A_{V1} A_{V2} \cdot \exp(t \cdot g_m / C_L)$$



COMPARATOR METASTABILITY

 


$$V_o(t) = V_i(0) \cdot A_{V1} A_{V2} \cdot \exp(t \cdot g_m / C_L)$$

Curve	$A_{V1} A_{V2}$	$V_i(t=0)$
①	10	10 mV
②	10	1 mV
③	10	100 μ V
④	10	10 μ V

- Settling time is dependent upon initial signal and regenerative gain
- When input is sufficiently close to the comparator threshold
 - Comparator fails to produce valid logic outputs within $T/2$
 - Sets the comparator resolution (Δ)



COMPARATOR METASTABILITY

 

Assuming that the input is uniformly distributed over V_{FS} , then


$$BER = \frac{\Delta}{1LSB}$$

$$V_o(t) = V_i(0) \cdot A_{V1} A_{V2} \cdot \exp(t \cdot g_m / C_L)$$

- Cascade pre-amp stages for larger gain
- Pipelined multi-stage latches (with increased latency)
- pre-amp can be pipelined too



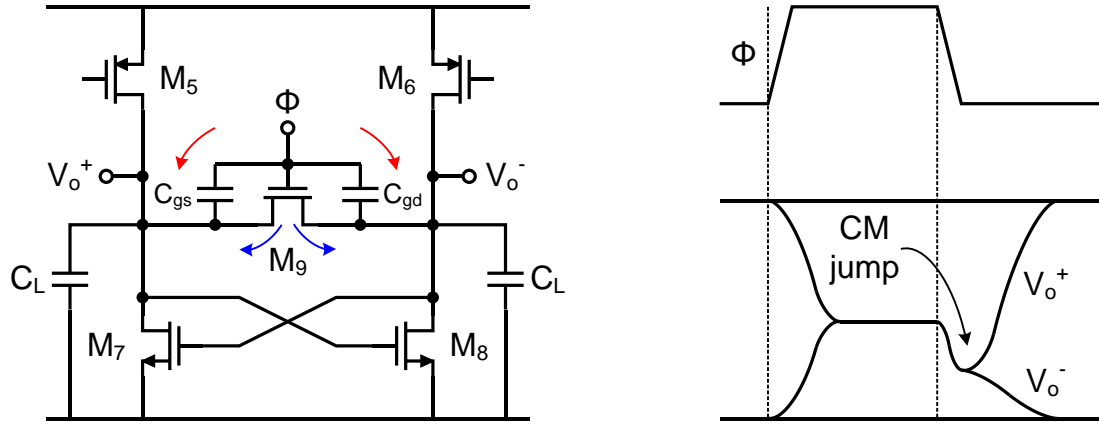
CHARGE-INJECTION AND CLOCK-FEEDTHROUGH IN LATCH



- In the above latch, regeneration starts when Φ goes low
 - Charge injection (CI) and clock-feedthrough (CF) introduce common-mode jump into V_o^+ and V_o^-
 - Mismatch/imbalance in CI and/or CF induces dynamic offset in the latch



DYNAMIC AND STATIC OFFSETS IN A LATCH

 

Dynamic offset induced due to:

- Imbalanced CI and CF
- Imbalanced load capacitance


$$\left. \begin{array}{l} 0.5V \text{ CM jump} \\ 10\% \text{ imbalance} \end{array} \right\} \Rightarrow 50mV \text{ offset}$$

Static offset induced due to:

- Mismatch in the cross-coupled pairs
- Mismatch in the signal input circuitry



CMOS COMPARATOR

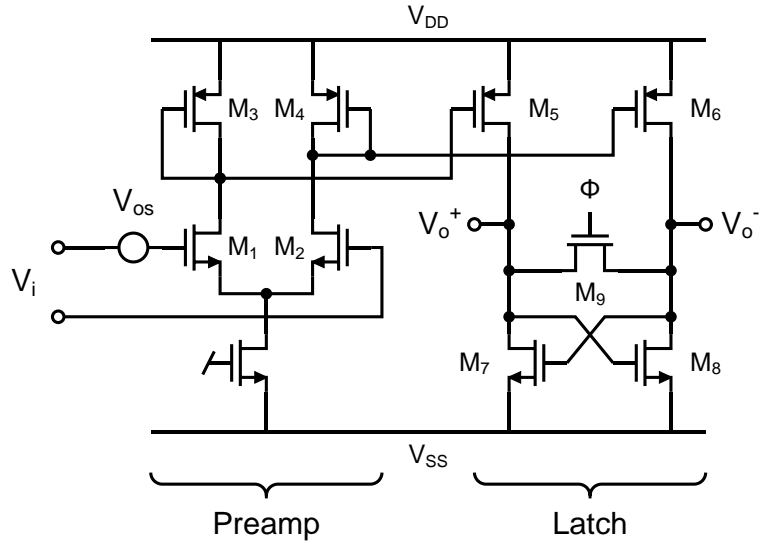


- Input-referred latch offset gets divided by the gain of the preamp
- Preamp introduces its own offset (mostly static due to V_{th} , W , and L mismatches)
- Preamp also reduces kickback noise

- Rapidly varying regeneration nodes couple kickback noise to the input
- Kickback noise disturbs reference voltages, must settle before next sample



COMPARATOR OFFSET

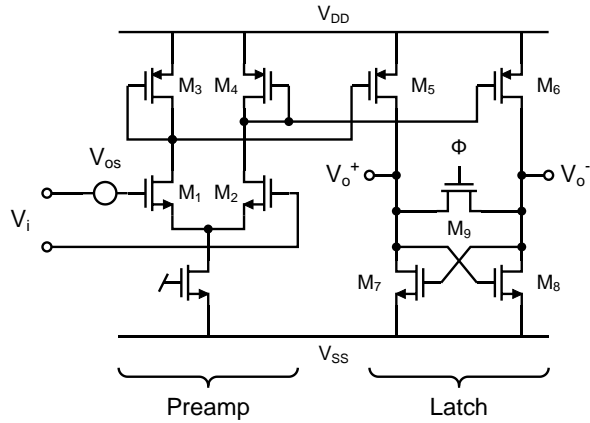

Differential pair mismatch:

$$V_{os}^2 = (\Delta V_{th})^2 + \frac{1}{4} V_{ov}^2 \left(\frac{\Delta \frac{W}{L}}{\frac{W}{L}} \right)^2$$

$$|A_{V1}| = \frac{g_{m1}}{g_{m3}} \quad |A_{V2}| = \frac{g_{m5} R_9}{2 - g_{m7} R_9}$$

Total input-referred comparator offset:

$$V_{os}^2 = V_{os,12}^2 + \frac{V_{os,34}^2 + V_{os,56}^2}{A_{V1}^2} + \frac{V_{os,78}^2}{A_{V1}^2 A_{V2}^2} + \frac{V_{os,dyn}^2}{A_{V1}^2 A_{V2}^2}$$



REVIEW: TRANSISTOR MATCHING

Suppose parameter P of two rectangular devices has a mismatch error of ΔP . The variance of parameter ΔP b/t the two devices is

$$\sigma^2(\Delta P) = \frac{A_P^2}{WL} + S_P^2 D^2,$$

1st term dominates
for small devices

where, W and L are the effective width and length, D is the distance


$$\text{Threshold: } \sigma^2(V_{th}) = \frac{A_{V_{th}}^2}{WL} + S_{V_{th}}^2 D^2$$

$$\text{Current factor: } \frac{\sigma^2(\beta)}{\beta^2} = \frac{A_\beta^2}{WL} + S_\beta^2 D^2$$

Ref: M. J. M. Pelgrom, et al., "Matching properties of MOS transistors," *IEEE Journal of Solid-State Circuits*, vol. 24, pp. 1433-1439, issue 5, 1989.



RECALL: DEVICE SIZING FOR MISMATCH

 

$$R_1 = R_S \cdot \frac{L}{W} \text{ with std } \sigma_{R1}$$

$$R_2 = R_S \cdot 10 \left(\frac{L}{W} \right) = 10R_1 \text{ with std } \sigma_{R2},$$

$$\sigma_{R2}^2 = \sum_{j=1}^{10} \sigma_{R_j}^2 = 10\sigma_{R1}^2 \Rightarrow \sigma_{R2} = \sqrt{10}\sigma_{R1}$$


$$\frac{\sigma_{R2}}{R_2} = \frac{\sqrt{10}\sigma_{R1}}{10R_1} = \frac{1}{\sqrt{10}} \left(\frac{\sigma_{R1}}{R_1} \right) \Rightarrow \frac{\sigma_R}{R} \propto \frac{1}{\sqrt{A}} = \frac{1}{\sqrt{WL}} \quad \text{"Spatial averaging"}$$



PRE-AMP DESIGN

A fully-differential gain-stage

 - Avoid or use simple CMFB
- Pre-amp gain reduces input referred offset due to the latch
- Autozero techniques for offset storage and reduction



Pre-amp open-loop gain vs tracking bandwidth trade-off

- Multiple stages of pre-amp limit bandwidth
 - Optimum value of stages 2-4


N stages:

$$|A_N(\omega)| = \left| \left(\frac{A_0}{1 + j \cdot \omega / \omega_0} \right)^N \right| = \left(\frac{A_0}{\sqrt{1 + (\omega / \omega_0)^2}} \right)^N$$

$$|A_N(\omega = \omega_{-3dB})| = \frac{A_0^N}{\sqrt{2}}, \quad \omega_{-3dB} = \omega_0 \sqrt{2^N - 1}$$



PRE-AMP (PA) AUTOZERO

 


- Finite preamp gain :


$$V_{OS,in} \approx \frac{V_{OS,pre-amp}}{A}$$

- For the overall comparator :
 
$$\sigma^2_{V_{OS,in}} \approx \frac{\sigma^2_{V_{OS,pre}}}{(1 + A_{pre})^2} + \frac{\sigma^2_{V_{OS,Latch}}}{A^2_{pre}}$$



PRE-AMP DESIGN: PULL-UP LOAD

 

- NMOS diodepull-up :

$$A_V = -\frac{g_{m1}}{g_{mL}} = -\sqrt{\frac{(W/L)_1}{(W/L)_L}}$$

- PMOS diodepull-up :

$$A_V = -\frac{g_{m1}}{g_{mL}} = -\sqrt{\frac{\mu_n (W/L)_1}{\mu_p (W/L)_L}}$$


- Resistorpull-up :

$$A_V = -g_{m1} \cdot R_L$$

- NMOS pull-up suffers from body-effect, affecting gain accuracy
- PMOS pull-up is free from body-effect, but subject to P/N mismatch
- Gain accuracy is the worst for resistive pull-up as resistors (poly, diffusion, well, etc.) don't track transistors; but it is

fast!

PRE-AMP DESIGN: MORE GAIN


 


$$A_v = -\frac{g_{m1}}{g_{m3}} \approx -\sqrt{\frac{\mu_n}{\mu_p} \left(\frac{I/2}{I/2 - I_p} \right) \frac{(W/L)_1}{(W/L)_3}}$$

- I_p diverts current away from PMOS diodes (M_3 & M_4), reducing $(W/L)_3$
- Higher gain without CMFB
- Needs biasing for I_p
- M_3 & M_4 may cut off for large V_{in} , resulting in a slow recovery



FASTER SETTLING PRE-AMP

  


$$\text{DMgain: } A_v^{\text{dm}} = -g_{m1} \cdot \left[\frac{1}{g_{m3}} \parallel \left(-\frac{1}{g_{m5}} \right) \parallel r_{o1} \parallel r_{o3} \parallel r_{o5} \right] \approx -\frac{g_{m1} r_{o1}}{3}$$

- NMOS diff-pair loaded with PMOS diodes and a PMOS cross-coupled latch
- High DM gain, low CM gain, good CMRR
- Simple, no CMFB required
- $(W/L)_{34} > (W/L)_{56}$ needs to be ensured for stability

Ref: K. Bult and A. Buchwald, "An embedded 240-mW 10-b 50-MS/s CMOS ADC in 1-mm²," *IEEE JSSC*, vol. 32, pp. 1887-1895, issue 12, 1997.

PRE-AMP EXAMPLE

 


- NMOS diff. pair loaded with PMOS diodes and resistors
- High DM gain, low CM gain, good CMRR
- Simple, no extra CMFB required
- Gain not well-defined

Ref: B.-S. Song et al., "A 1 V 6 b 50 MHz current-interpolating CMOS ADC," in *IEEE Symp. VLSI Circuits*, 1999, pp. 79-80.




LATCH DESIGN

- Regenerative latches for faster settling
 - See lecture notes
- At least one cross-coupled regenerative core
 - Numerous methods for applying the input initial signal for regeneration
 - Latches can have large static and dynamic offsets
- Large Regenerative gain for resolving small inputs
 - Metastability (**wrong or incomplete decisions**) when latch can't make decision
 - Pre-amp used for larger gain (slower tracking BW)
- **One topology doesn't fit all the applications**
 - Speed vs power consumption trade-off

 


STATIC LATCH EXAMPLE

 

- Active pull-up and pull-down
 - full CMOS logic levels
- Very fast!
- Q^+ and Q^- are not well defined in reset mode ($\Phi = 1$)
- Large short-circuit current in reset mode
- Zero DC current after full regeneration
- Supply is very noisy




SEMI-DYNAMIC LATCH EXAMPLE

 

- Latch is disabled in reset mode
 - less static current
- Pull-up not as fast
- Q^+ and Q^- are still not well defined in reset mode ($\Phi = 1$)
- Zero DC current after full regeneration
- Supply still very noisy




DYNAMIC LATCH EXAMPLE

 

- Zero DC current in reset mode
- Q^+ and Q^- **are both reset to “0”**
- Full logic level after regeneration
- Slow



DYNAMIC LATCH EXAMPLE 2

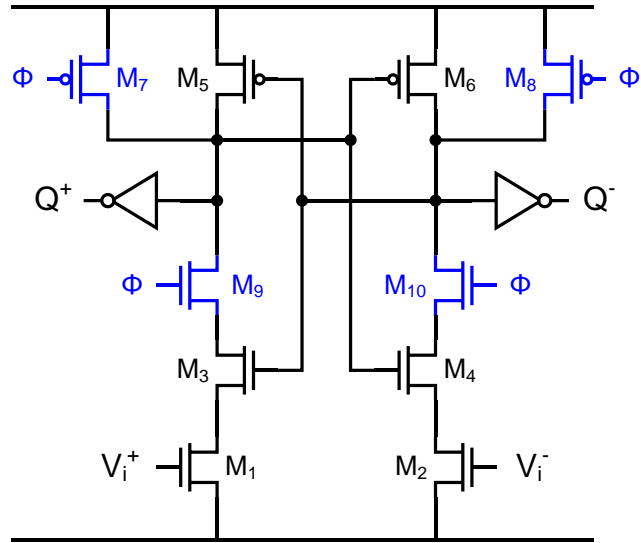


- Zero DC current in reset mode
- Q^+ and Q^- **are both reset to “0”**
- Full logic level after regeneration
- Slow

Ref: T. B. Cho and P. R. Gray, “A 10 b, 20 Msample/s, 35 mW pipeline A/D converter,” *JSSC*, vol. 30, pp. 166-172, issue 3, 1995.




CURRENT-STEERING/CML LATCH

 

- Current mode logic (CML) latch
- Constant bias current
 - supply very quiet
- Higher gain in tracking mode
- Cannot produce full logic levels
- Fast
 - Popular for high-speed designs




COMPARATOR WITH PA AUTOZERO

 

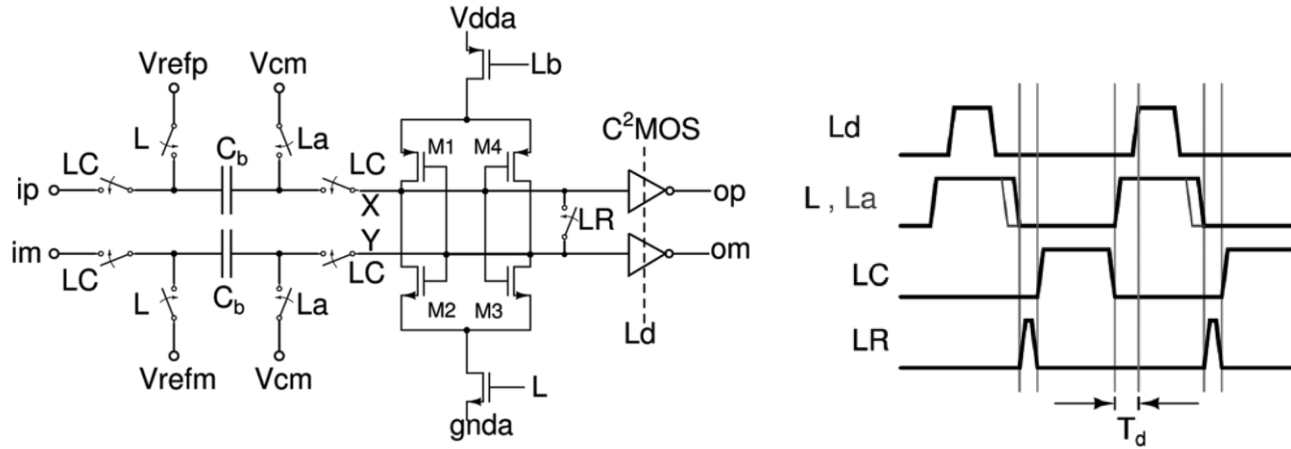I. Mehr and L. Singer, "A 55-mW, 10-bit, 40-Msample/s Nyquist-Rate CMOS ADC," IEEE JSSC March 2000, pp. 318-25.



LOW-POWER LATCH WITH REFERENCE SUBTRACTION






- Energy efficient comparator for medium speed data converters
- Large number of clock phases
 - Driving and routing at higher clock rates leads to more power consumption

S. Pavan, N. Krishnapura, R. Pandarinathan, P. Sankar, "A Power Optimized Continuous-time Delta-Sigma Modulator for Audio Applications," IEEE JSSC, vol. 43, no. 2, pp. 351-360, Feb. 2008.



AUTOZERO AND REFERENCE SUBTRACTION

 
 
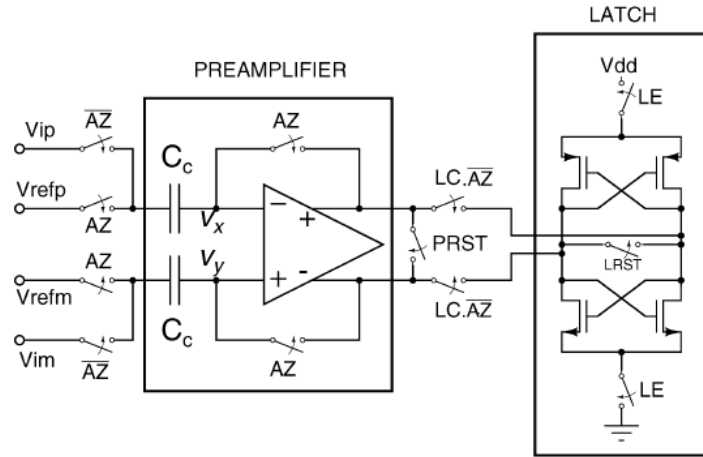


V. Srinivas, S. Pavan, A. Lachhwani, and N. Sasidhar, "A Distortion Compensating Flash Analog-to-Digital Conversion Technique," IEEE JSSC, vol. 41, no. 9, pp.

1959-1969, Sep. 2006.



CML BASED COMPARATOR

  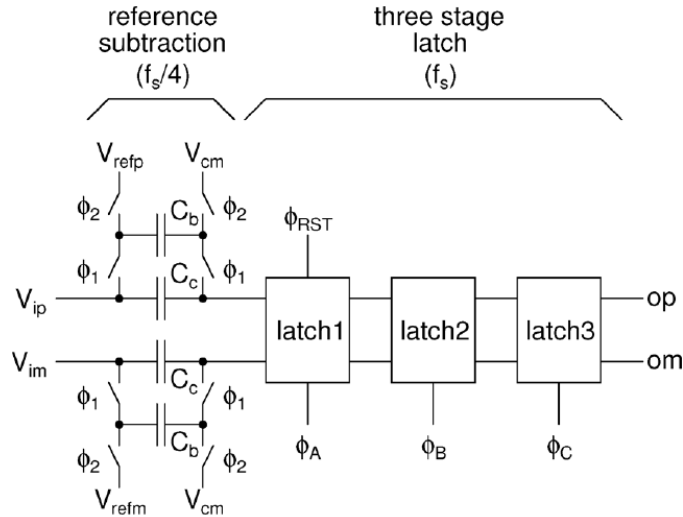

CML-Latch

V. Singh, N. Krishnapura, S. Pavan, B. Vighram, D. Behera, and N. Nigania, "A 16MHz BW 75dB DR CT $\Delta\Sigma$ ADC Compensated for More Than One Cycle Excess Loop Delay," IEEE JSSC, vol. 47, no. 8, Aug. 2012.




COMPARATORS FOR PIPELINED ADCS



- Pipelined ADCs employ at least 0.5 bit/stage redundancy
 - Can tolerate large offsets and large noise with appropriate redundancy
- Should consume negligible power in a good design
 - 50-100 μ W or less per comparator
- Lots of implementation options
 - Resistive/capacitive reference generation
 - Different pre-amp/latch topologies



COMPARATORS FOR PIPELINED ADCS

 


[Chiu 2004]

  

[Mehr 2000]




COMPARATOR EXAMPLE

 

A 6-b 1.3-Gsample/s A/D Converter in 0.35- μm CMOS IEEE JSSC, vol. 36, no. 12, Dec 2001.




LATCH EXAMPLE

 

A 0.9-V 60-W 1-Bit Fourth-Order Delta-Sigma Modulator With 83-dB Dynamic Range IEEE JSSC, vol. 43, no. 2, Feb. 2008




COMPARATOR EXAMPLE

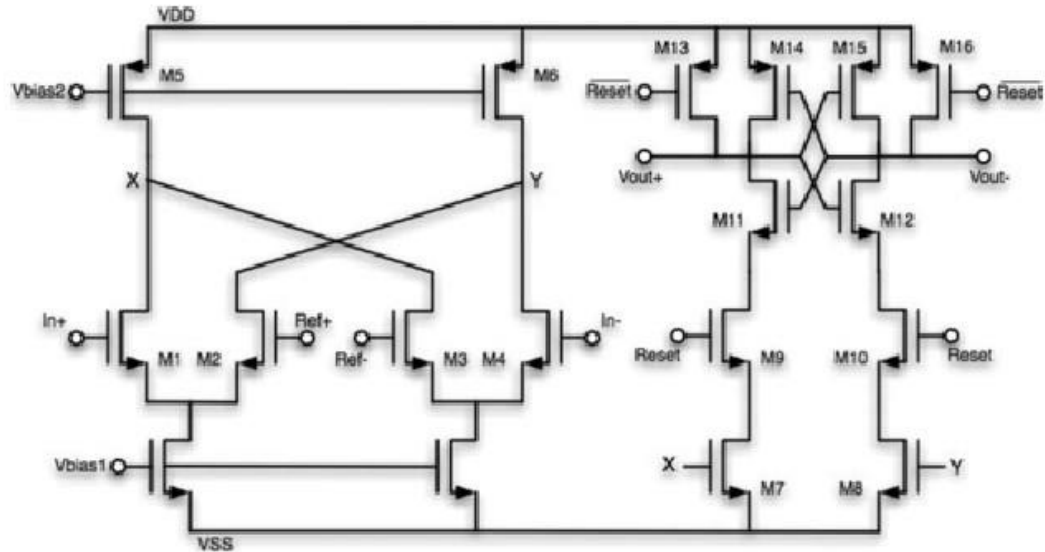

I. Galdi, 40 MHz IF 1 MHz Bandwidth Two-Path Bandpass $\Sigma\Delta$ Modulator With 72 dB DR Consuming 16 mW, IEEE JSSC, vol. 39, no. 8, pp. 1341–1346, Aug. 2004.





COMPARATOR EXAMPLE

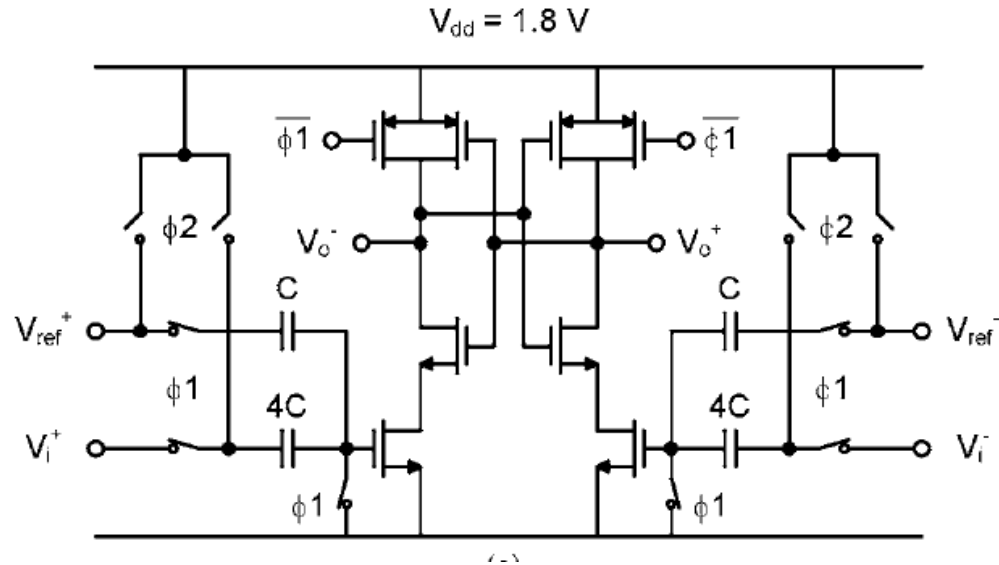

Y. Chiu, P. R. Gray, and B. Nikolic, "A 14-b 12-MS/s CMOS pipeline ADC with over 100-dB SFDR," IEEE JSSC, vol. 39, pp. 2139 - 2151, December 2004.




COMPARATOR EXAMPLE

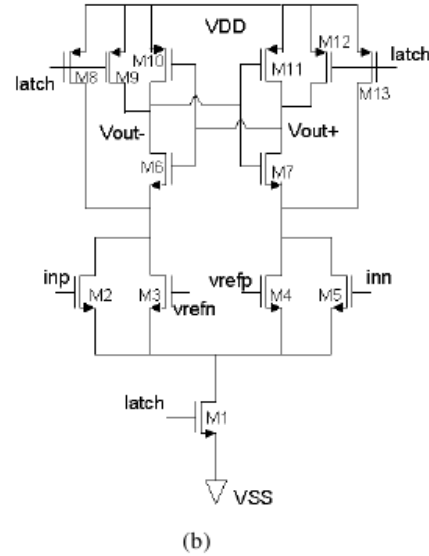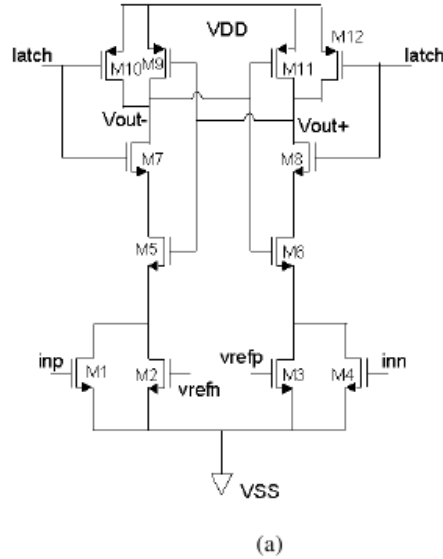

B. Min, P. Kim, F. W. Bowman, D. M. Boisvert, and A. J. Aude, "A 69-mW 10-bit 80-MSample/s pipelined CMOS ADC," IEEE JSSC, vol. 38, pp. 2031 - 2039, Dec. 2003.



COMPARATOR EXAMPLE

 

S. Limotyrakis, S. D. Kulchycki, D. Su, and B. A. Wooley, "A 150MS/s 8b 71mW time-interleaved ADC in 0.18 μ m CMOS,"
proc. IEEE ISSCC, pp. 258 - 259, Feb 2004.



EXERCISE

Compare the latches with respect to

- Static power dissipation
- Dynamic and Static Offsets
- Kickback noise at the input
- Number of clock phases
- Maximum achievable clock speed



REFERENCES

1. Rudy van de Plassche, “**CMOS Integrated Analog-to-Digital and Digital-to-Analog Converters**,” 2nd Ed., Springer, 2005.
2. Y. Chiu, *Data Converters Lecture Slides*, UT Dallas 2012.
3. N. Krishnapura, *Analog IC Design Lectures*, IIT Madras, 2008.
4. B. Boser, *Analog-Digital Interface Circuits Lecture Slides*, UC Berkeley 2011.

