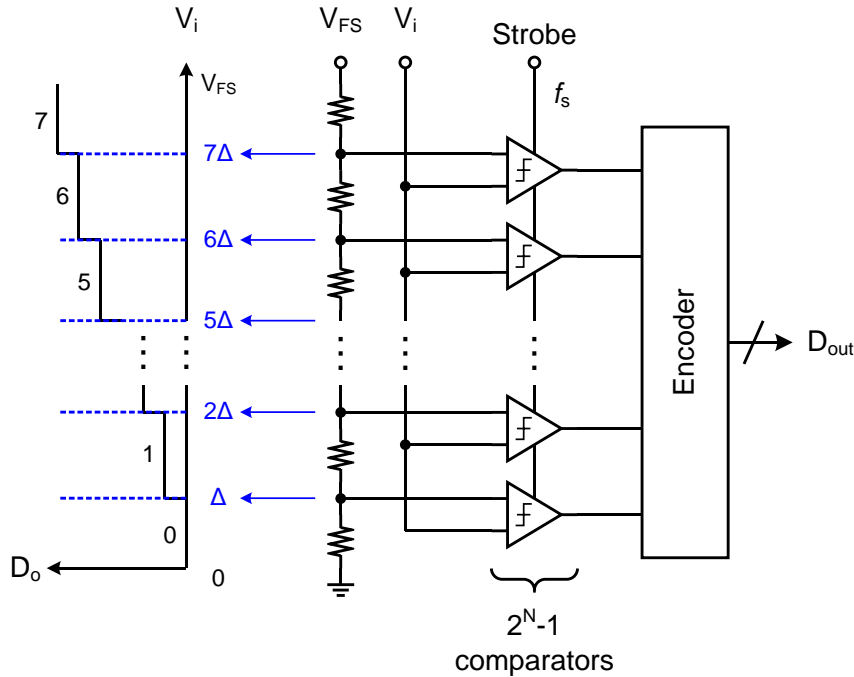


# FLASH ADCS




# FLASH ADC ARCHITECTURE




- Reference ladder consists of  $2^N$  matched resistors
- Input is compared to  $2^N - 1$  reference voltages
- Massive parallelism
- Very fast ADC architecture
- Latency =  $1 T_s = 1/f_s$
- Throughput =  $f_s$
- Complexity =  $2^N$




# THERMOMETER CODE

 

# THERMOMETER CODE

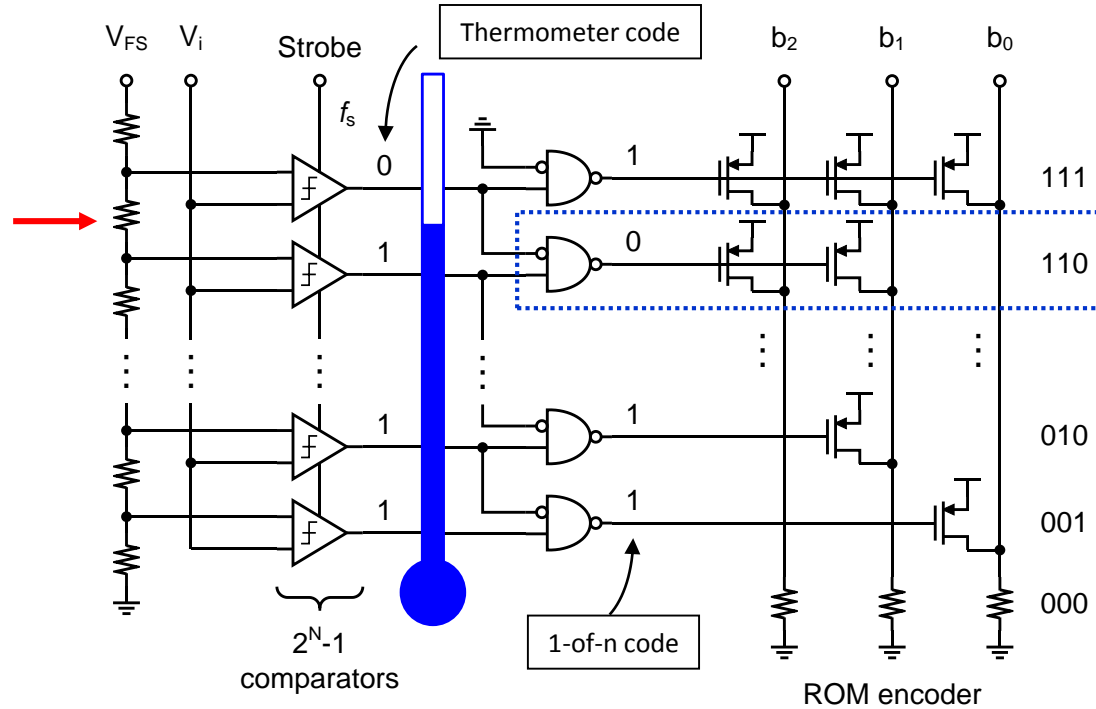


# FLASH ADC CHALLENGES: EXAMPLE

 

- $V_{DD} = 1.8 \text{ V}$
- 10-bit  $\rightarrow 1023$  comparators
- $V_{FS} = 1 \text{ V}$   $\rightarrow 1 \text{ LSB} = 1 \text{ mV}$
- $\text{DNL} < 0.5 \text{ LSB}$   $\rightarrow V_{os} < 0.5 \text{ LSB}$
- $0.5 \text{ mV} = 3\text{-}5 \sigma$   $\rightarrow \sigma = 0.1\text{-}0.2 \text{ mV}$
- $2^N - 1$  very large comparators
- Large area, large power consumption
- Very sensitive design
- Limited to resolutions of 4-8 bits

# FLASH ADC CHALLENGES

 

- $DNL < 0.5$  LSB
- Large Full-scale voltage ( $V_{FS}$ ) relaxes offset tolerance
- Small  $V_{FS}$  benefits conversion speed (settling, linearity of building blocks)



# ADC INPUT CAPACITANCE

$$\sigma^2(V_{th}) = \frac{A_{vth}^2}{WL} \quad C_g = 10 \text{ fF} / \mu\text{m}^2$$

- $N = 6$  bits  $\rightarrow 63$  comparators
- $V_{FS} = 1 \text{ V}$   $\rightarrow 1 \text{ LSB} = 16 \text{ mV}$
- $\sigma = \text{LSB}/4$   $\rightarrow \sigma = 4 \text{ mV}$
- $A_{VT0} = 10 \text{ mV} \cdot \mu\text{m}$   $\rightarrow L = 0.24 \mu\text{m},$   
 $W = 26 \mu\text{m}$


N (bits)	# of comp.	$C_{in}$ (pF)
6	63	3.9
8	255	250
10	1023	??!

- Small  $V_{OS}$  leads to large device sizes, hence large area and power
- Large comparator leads to large input capacitance, difficult to drive and difficult to achieve sufficient tracking bandwidth

M. Pelgrom, A. Duinmaijer, and A. Welbers, "Matching properties of MOS transistors," *IEEE Journal of Solid-State Circuits*, vol. 24, no. 5, pp. 1433-1439, 1989.



# FULLY-DIFFERENTIAL ARCHITECTURE

 

- $V_{FS}$  is effectively doubled
- 3-dB gain in SNR
- Better CMRR
- Noise immunity
- Input feedthrough is cancelled
- $C_{in}$  nonlinearity partially removed






# FLASH ADC DESIGN CONSIDERATIONS

- Use a dedicated S/H (or T/H) for better dynamic performance
  - Can be avoided when using the A/D inside a  $\Delta\Sigma$  loop
- Large input range for the quantizer has several benefits
  - Increased step-size ( $V_{\text{LSB}}$ ) relaxes offset requirements on the comparators
  - Reduced matching requirements result in small input cap to the S/H, easier to drive
  - Reduced input cap results in smaller clock routing parasitics – power savings in clock drivers
- Comparator Design
  - See comparator design notes/slides




# FLASH ADC: REFERENCE LADDER

 


- Differential reference ladder
- Decaps on the reference taps
  - large  $RC$  time-constant will not allow reference restoration after kickback noise
  - Small  $R$  will lead to power dissipation
  - Optimize  $RC$  time-constant value
- Subtract references from the input in a differential manner
  - Several topologies are possible
- Several architectures for the digital backend
  - May need to pipeline digital logic at high sampling rates  $>500$  MS/s



# REFERENCE GENERATOR (FOR $V_{REFP}$ AND $V_{REFM}$ )

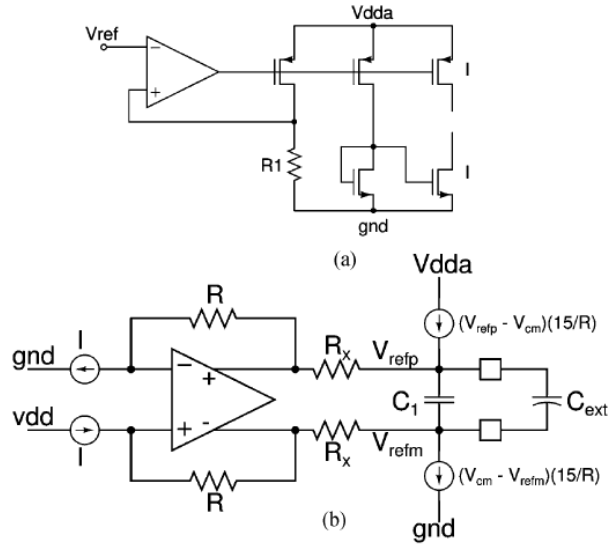

[Brooks 1994]

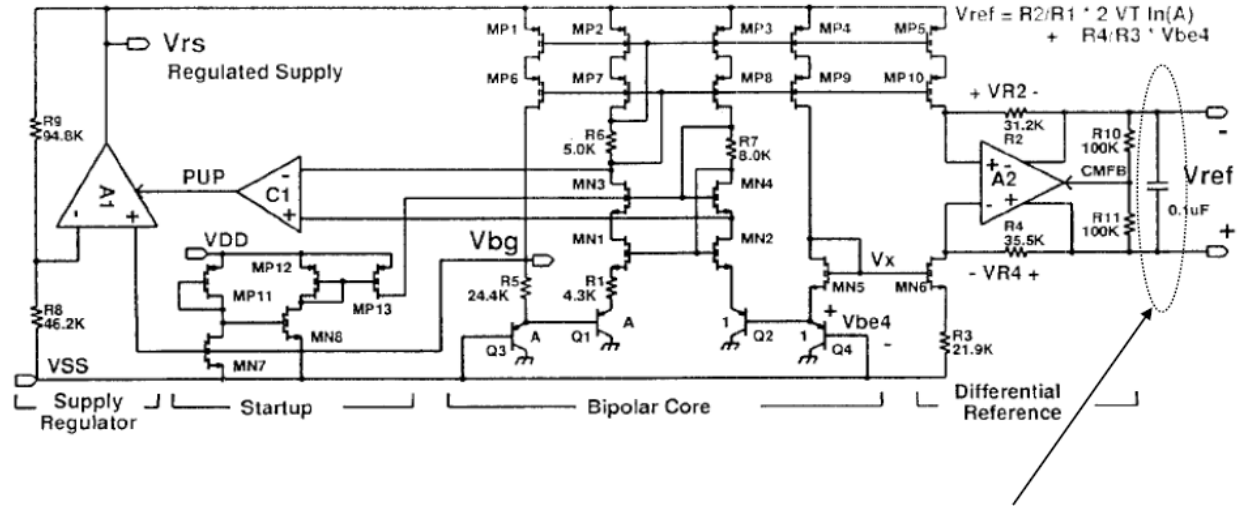


External decoupling caps provide dynamic currents  
 $\Rightarrow$  Low power reference buffer



# FLASH ADC: REFERENCE SUBTRACTION



# REFERENCE SUBTRACTION: SCHEME I

 


- Employ reference ladder for subtraction
- Choose current ( $I$ ) such that differential voltage drop across  $R = 1 V_{\text{LSB}}$
- Ladder is part of the signal path
  - Comparator input cap load the resistor taps
  - Excess delay

$$A_{\text{max}} = \frac{0.5V_{\text{dd}} - \Delta V}{2}$$

Paton, S., Di Giandomenico, A., Hernandez, L., Wiesbauer, A., Potscher, T., & Clara, M. (2004). A 70-mW 300-MHz CMOS continuous-time  $\Sigma\Delta$  ADC with 15-MHz bandwidth and 11 bits of resolution. *IEEE Journal of Solid State Circuits*, 39(7), 1056–1063.



# REFERENCE SUBTRACTION: SCHEME II

 


- Source followers to buffer  $v_{in}$ 
  - reduced swing, varies with PVT
- Ladder is part of the signal path
  - Comparator input cap load the resistor taps
  - Excess delay

Arias, J., Kiss, P., Prodanov, V., Boccuzzi, V., Banu, M., Bisbal, D., et al. (2006). A 32-mW 320-MHz continuous-time complex  $\Sigma\Delta$  ADC for multi-mode wireless-LAN receivers. *IEEE Journal of Solid State Circuits*, 41(2), 339–351.



# REFERENCE SUBTRACTION: SCHEME III

 


- Differential difference amplifier for subtracting the reference
  - followed by a zero crossing detector
- Relaxes the impedance requirements on the ladder
- Mismatch in differential pairs and tail current sources results in comparator offset
  - current trimming (see the reference below)
- Finite BW of the amplifier causes excess delay

Mitteregger, G., Ebner, C., Mechnig, S., Blon, T., Holuigue, C., & Romani, E. (2006). A 20-mW 640-MHz CMOS continuous-time  $\Sigma\Delta$  ADC with 20-MHz signal bandwidth, 80-dB dynamic range and 12-bit ENOB. *IEEE Journal of Solid State Circuits*, 41(12), 2641–2649.




# REFERENCE SUBTRACTION: SCHEME IV

 

- Switched-capacitor reference subtraction
  - Pay attention to charge injection
- ADC can handle large input swing
- Slow when auto-zeroing preamp is used
  - Large settling time constant
  - Reference subtraction in background



# EXAMPLE: FULLY-DIFFERENTIAL COMPARATOR

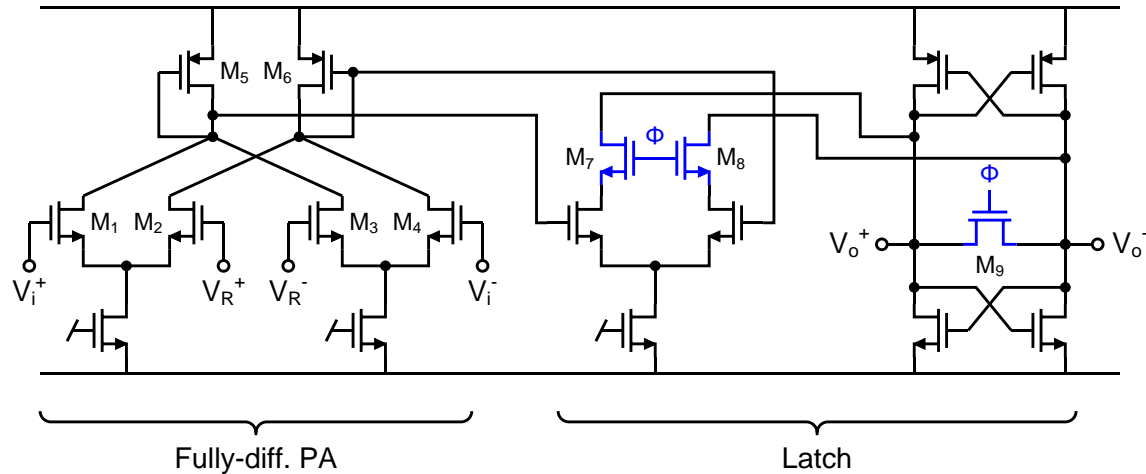


- Double-balanced, fully-differential preamp
- Switches (M<sub>7</sub>, M<sub>8</sub>) added to stop input propagation during regeneration
- Active pull-up PMOS added to the latch



# FLASH ADC: ERRORS



# FLASH ADC ERRORS

 


- SHA-less
- Signal and clock propagation delay
- $2^N - 1$  PAs + latches must be matched
- Synchronized clock strobe signal is critical

Going parallel is fast, but also gives rise to inherent problems...




# PREAMP INPUT COMMON MODE

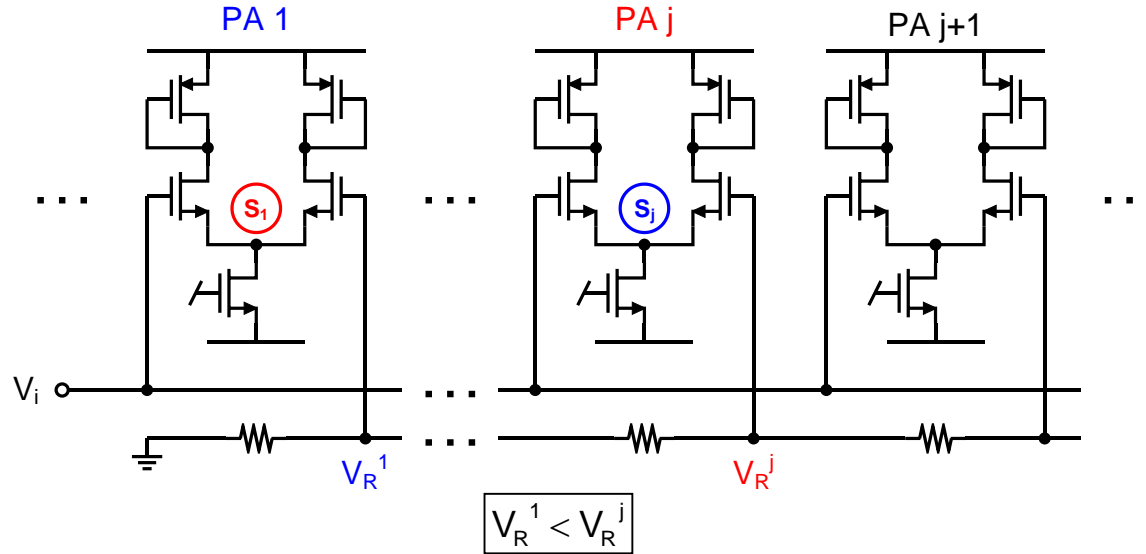

Input CM difference creates systematic mismatch (offset, gain,  $C_{in}$ , tracking BW, and CMRR) among preamps



# SAMPLING APERTURE ERROR


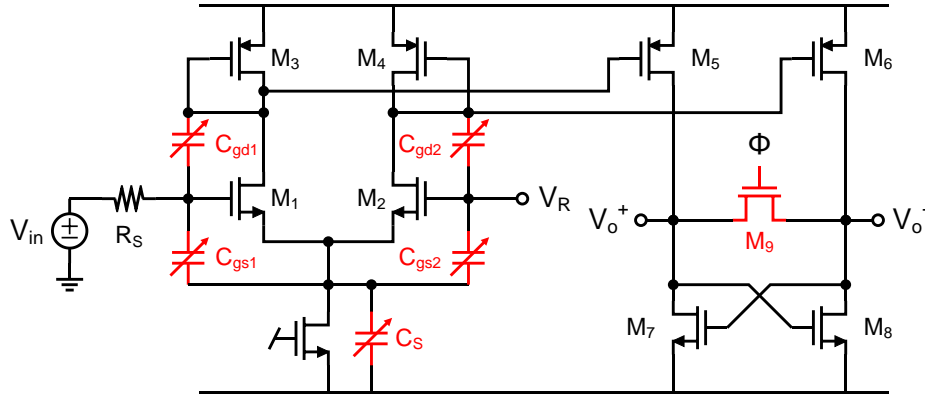


$\Phi$	Mode
"high"	Track
"low"	Regenerate

- Preamplifier delay and  $V_{THN}$  of sampling switch ( $M_9$ ) are both signal-dependent  $\rightarrow$  signal-dependent sampling point (aperture error)
- A major challenge of distributing clock signals across  $2^N - 1$  comparators in flash ADC with minimum clock skew (routing,  $V_{THN}$  mismatch of  $M_9$ , etc.)




# NONLINEAR INPUT CAPACITANCE

  

Signal-dependent input bandwidth ( $1/R_S C_{in}$ ) introduces distortion




# INPUT SIGNAL FEEDTHROUGH

 

Feedthrough of  $V_{in}$  to the reference ladder through the serial connection of  $C_{gs1}$  and  $C_{gs2}$  disturbs the reference voltages

# COMPARATOR METASTABILITY

 

Assuming that the input is uniformly distributed over  $V_{FS}$ , then

$$BER = \frac{\Delta}{1LSB}$$


$$V_o(t) = V_i(0) \cdot A_{v1} A_{v2} \cdot \exp(t \cdot g_m / C_L)$$

- Cascade preamp stages (typical flash comparator has 2-3 PA stages)
- Use pipelined multi-stage latches; PA can be pipelined too
- **Avoid branching off comparator logic outputs**






# COMPARATOR METASTABILITY

 

Logic levels can be misinterpreted by digital gates (branching off, diff. outputs)




# BUBBLES (SPARKLES) IN THERMOMETER CODE

 


Static/dynamic comparator errors cause bubbles in thermometer code



# BUBBLES (SPARKLES)

 


Comparator offset

 

Timing error



# BUBBLE-TOLERANT BOUNDARY DETECTOR

 

- 3-input NAND
- Detect “011” instead of “01” only
- “Single” bubble correction
- Biased correction

Ref: J. G. Peterson, “A monolithic video A/D converter,” *IEEE Journal of Solid-State Circuits*, vol. 14, pp. 932-937, issue 6, 1979.



# BUILT-IN BIAS

	Ⓐ	Ⓑ	Ⓒ	Ⓓ
	0	0	0	0
	0	0	0	0
	0	0	1	0
① →	0	0	0	1
② →	1	0	0	1
③ →	0	1	1	0
	1	1	1	0
	1	0	1	1
	1	1	1	1
	1	1	1	1

Case	“011” Det.	“001” Det.
A	③	①
B	Fail	②
C	②	Fail
D	Fail	Fail

Inspecting more neighboring comparator outputs improves performance



# MAJORITY VOTING LOGIC

$$C_j^* = C_{j-1}C_j + C_jC_{j+1} + C_{j-1}C_{j+1}$$

	(A)		(B)		(C)		(D)	
	0	0	0	0	0	0	0	0
	0	0	0	0	0	0	0	0
	0	0	0	0	1	0	0	0
① →	0	0	0	0	0	0	1	1
② →	1	0	0	0	0	0	1	1
③ →	0	1	1	1	1	1	0	0
	1	1	1	1	1	1	0	0
	1	1	0	1	1	1	1	1
	1	1	1	1	1	1	1	1
	1	1	1	1	1	1	1	1

Case	"011" Det.	Majority voting
A	③	②
B	Fail	②
C	②	②
D	Fail	Fail

Ref: C. W. Mangelsdorf, "A 400-MHz input flash converter with error correction," *IEEE Journal of Solid-State Circuits*, vol. 25, pp. 184-191, issue 1, 1990.



# GRAY ENCODING

$$G_1 = T_1 \bar{T}_3 + T_5 \bar{T}_7$$

$$G_2 = T_2 \bar{T}_6$$

$$G_3 = T_4$$

Only one transition  
b/t adjacent codes

Thermometer	Gray	Binary
0 0 0 0 0 0 0	0 0 0	0 0 0
1 0 0 0 0 0 0	0 0 1	0 0 1
1 1 0 0 0 0 0	0 1 1	0 1 0
1 1 1 0 0 0 0	0 1 0	0 1 1
1 1 1 1 0 0 0	1 1 0	1 0 0
1 1 1 1 1 0 0	1 1 1	1 0 1
1 1 1 1 1 1 0	1 0 1	1 1 0
1 1 1 1 1 1 1	1 0 0	1 1 1
$T_1 \ T_2 \ T_3 \ T_4 \ T_5 \ T_6 \ T_7$	$G_3 \ G_2 \ G_1$	$B_3 \ B_2 \ B_1$

- One comparator output is ONLY used once → No branching!
- Gray encoding fails benignly in the presence of bubbles
- Codes are also robust over metastability errors



# GRAY ENCODING

Thermometer	Gray	Decimal
1 1 1 1 1 1 1 1 1 1 1 1 0 0	1 0 1 1	13
1 1 1 1 1 1 1 1 1 1 1 0 1 0	1 0 0 0	15
1 1 1 1 1 1 1 1 1 1 1 0 0 1	1 0 1 0	12

$$\begin{aligned}G_1 &= T_1 \overline{T_3} + T_5 \overline{T_7} \\G_2 &= T_2 \overline{T_6} \\G_3 &= T_4\end{aligned}$$

Conversion of Gray code to binary code is quite time-consuming → “quasi” Gray code

Ref: Y. Akazawa, et al., “A 400MSPS 8b flash AD conversion LSI,” in *IEEE International Solid-State Circuits Conference*, Dig. Tech. Papers, 1987, pp. 98-99.






# FLASH ADC: BINARY DECODERS



# GRAY ENCODED ROM DECODER

 


Thermometer-to-Binary Decoders for Flash Analog-to-Digital Converters

Erik Säll and Mark Vesterbacka



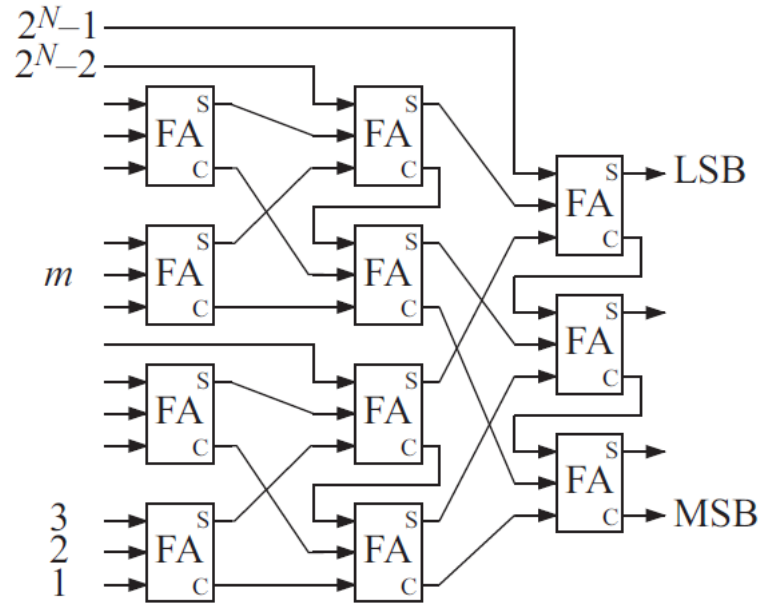
# WALLACE TREE ADDER (1<sup>st</sup> ADDER)




Wallace tree decoder for an  $N = 4$ -bit flash ADC.



# FOLDED WALLACE TREE DECODER

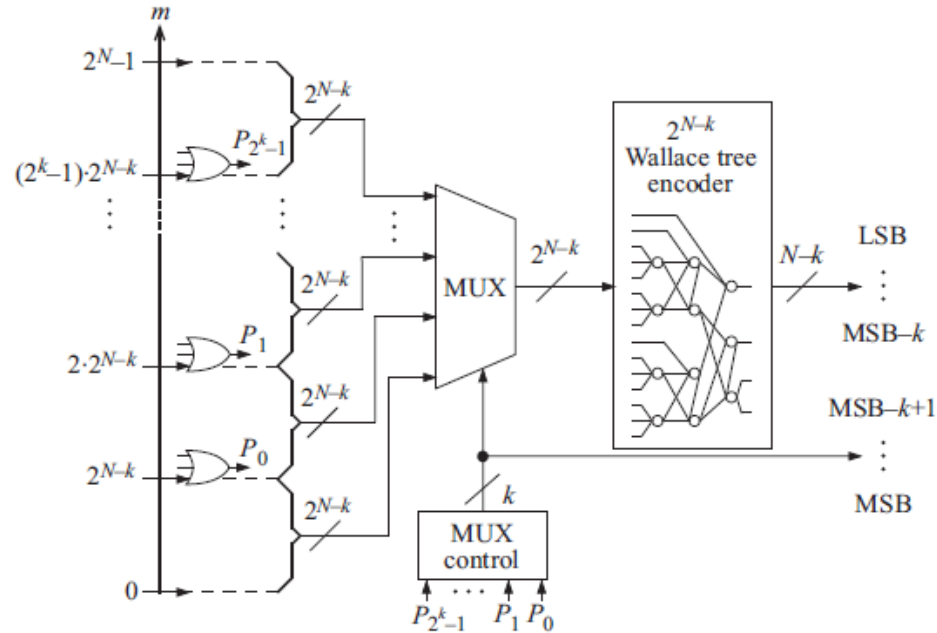


# MUX-BASED DECODER

 

Multiplexer-based decoder for  $N = 4$  bits.



# COMPARISON OF DECODER SCHEMES

 


- Mostly custom design at higher speeds
- Pipeline the digital backend at high-sampling rates to meet clock timing
  - $T_{pd} < T_{CK} - (t_{pcq} + t_{setup})$
  - $T_{cd} > t_{hold} - t_{ccq}$



# FLASH ADC: OTHER TECHNIQUES



# OFFSET AVERAGING (1)

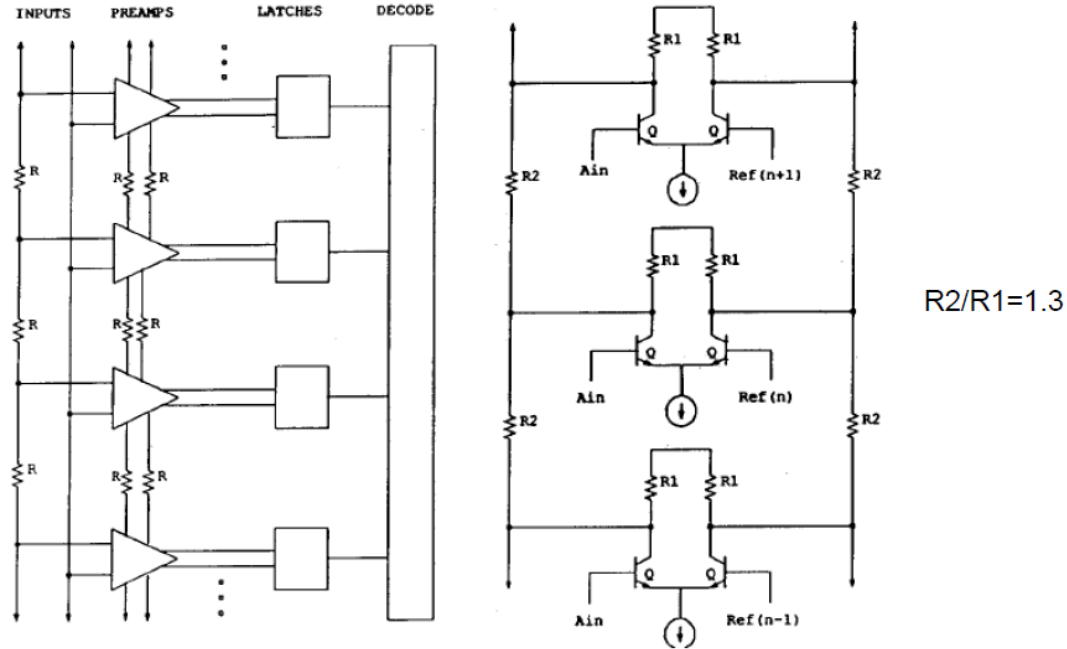


[Kattmann & Barrow, ISSCC 1991]







# OFFSET AVERAGING (2)

 


[Bult & Buchwald, JSSC 12/1997]

  

[Scholtens & Vertregt, JSSC 12/2002]



# FLASH ADC WITH AVERAGING

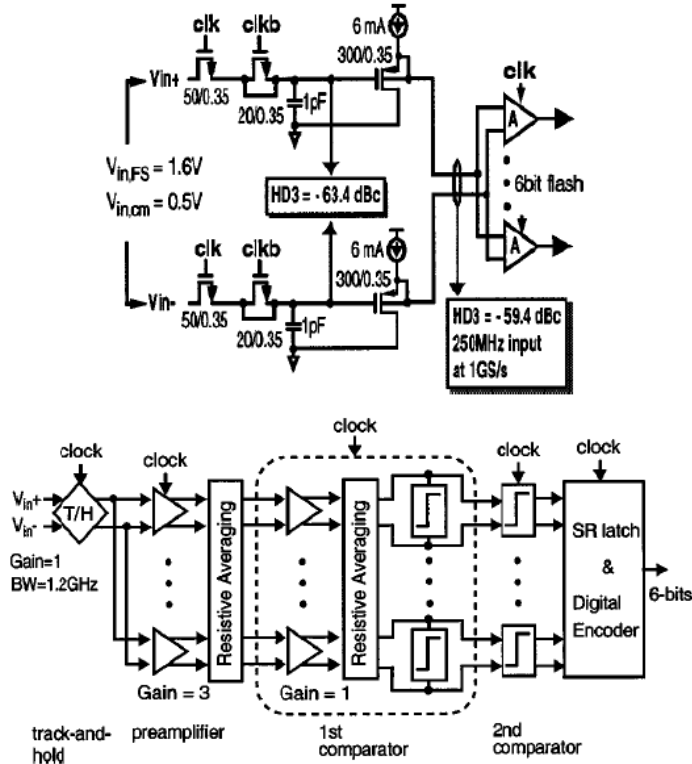


[Choi & Abidi, JSSC 12/2001]

Resolution	6 bits
Conversion Rate	1.3 GS/s
INL/DNL @ $F_s = 1$ GHz	0.35 LSB / 0.2 LSB
Input Range	1.6 $V_{p-p}$ differential
Input Capacitance (T/H)	1 pF
Bit Error Rate @ $f_s = 1$ GHz	$< 10^{-10}$
SFDR @ $f_{in} = 100$ MHz	$> 44$ dB up to 1.3 GS/s
SNDR @ $f_{in} = 630$ MHz @ $f_{in} = 650$ MHz	35 dB @ 1 GS/s 32 dB @ 1.3 GS/s
Power Dissipation (50% due to logic and clock)	500 mW @ 1 GS/s 545 mW @ 1.3 GS/s
Voltage Supply	3.3 V
Active/Total Die Area	2x0.4 mm <sup>2</sup> / 2.2x2.2 mm <sup>2</sup>
Technology	0.35-μm CMOS

Averaging networks designed to reduce input referred offset by 3x


# OFFSET CALIBRATION

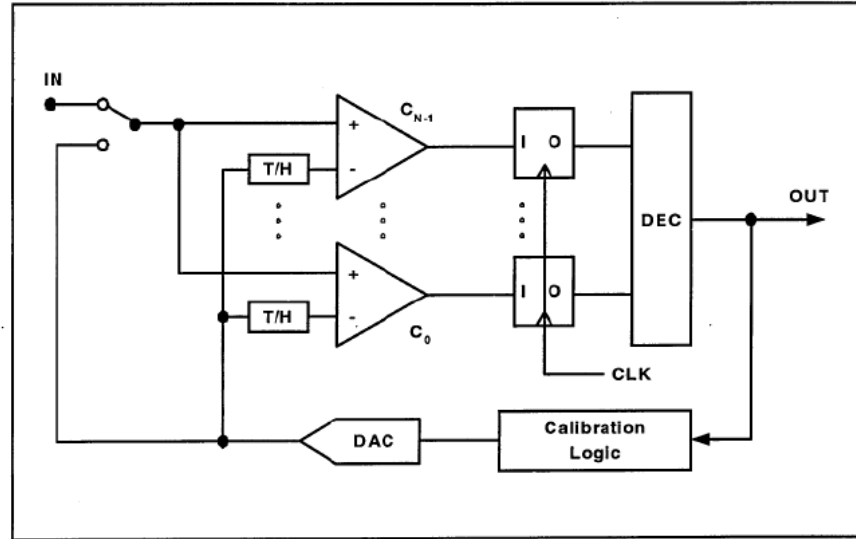

S. Sutardja, "360 Mb/s (400 MHz) 1.1 W 0.35 $\mu$ m CMOS PRML read channels with 6 burst 8-20 $\times$  over-sampling digital servo," ISSCC Dig. Techn. Papers, Feb. 1999.




# COMPARATOR WITH OFFSET CORRECTING DAC

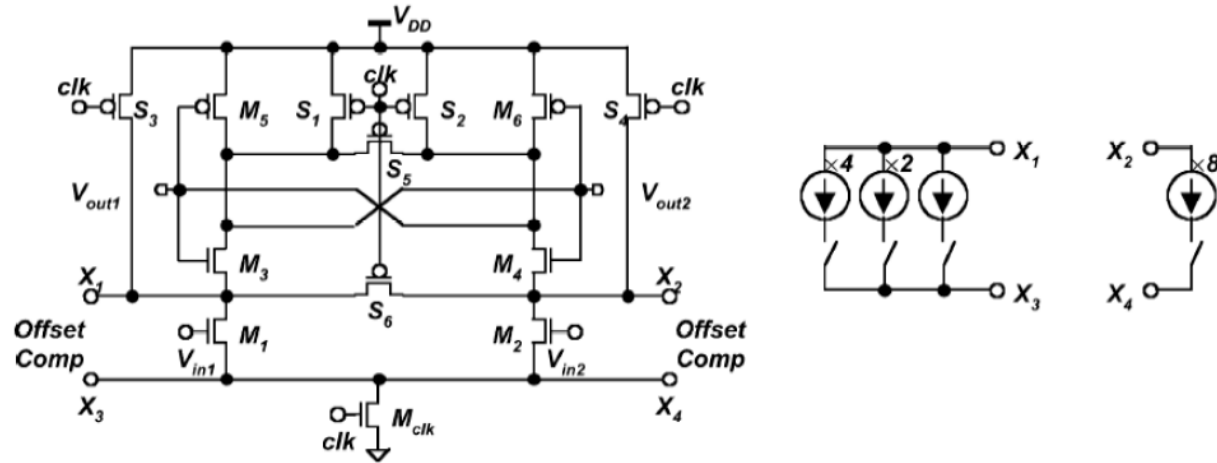

[K.-L.J. Wong and C.-K.K. Yang, "Offset compensation in comparators with minimum input-referred supply noise," JSSC, May 2004.]




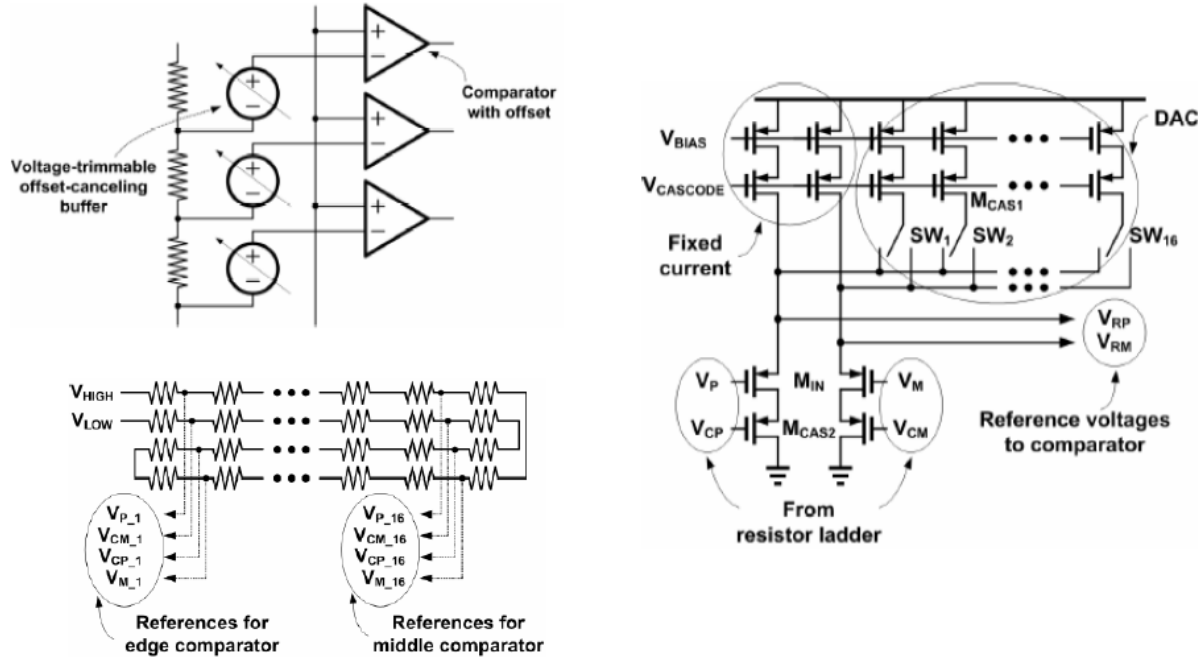
# HIGH-PERFORMANCE FLASH WITH CALIBRATION (1)



[Park & Flynn, "A 3.5 GS/s 5-b Flash ADC in 90 nm CMOS," CICC 2006]

 
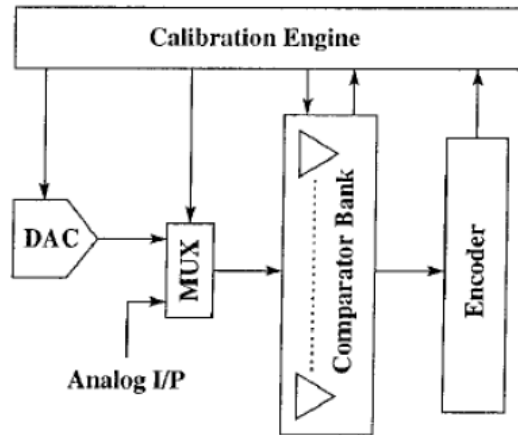
# COMPARATOR REDUNDANCY (1)

- Idea: Build a "sea of imprecise comparators", then determine which ones to use...




C. Donovan, M. P Flynn, "A 'digital' 6-bit ADC in 0.25- $\mu$ m CMOS," IEEE J. Solid-State Circuits, pp. 432-437, March 2002.

# COMPARATOR REDUNDANCY (2)

 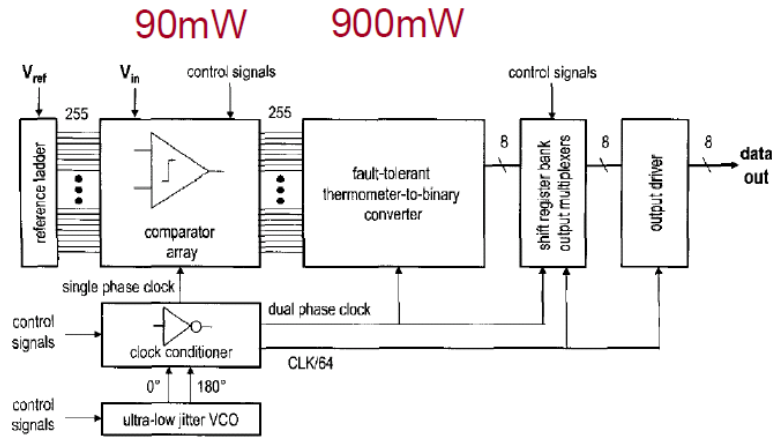

 a)  
Classical  $n$  bit flash ADC:  
Use of  $2^n-1$  precise  
comparators







b)  
This  $n$  bit flash ADC:  
Use of  $4 \times 2^{n-1}$   
comparators with  
overlapping decision  
levels

Fig. 1 Illustration of the ADC operation scheme.

Paulus et al., "A 4GS/s 6b flash ADC in 0.13um CMOS," *VLSI Circuits Symposium*, 2004



# STOCHASTIC FLASH ADC

    

- Fully synthesized ADC using 'digital' comparator cells (large offsets)
- Use more than 1 comparator for a reference threshold
  - Use 'detection theory' to make accurate decisions around a threshold, by using more than one observation
- Low speed designs (<20 MS/s)

A 6b Stochastic Flash Analog-to-Digital Converter  
Without Calibration or Reference Ladder

Skvler Weaver<sup>1</sup>, Benjamin Hershberg<sup>1</sup>, Daniel Knierim<sup>2</sup>, and Un-Ku Moon<sup>1</sup>





# FLASH ADC: CASE STUDY




# CASE STUDY: DISTORTION COMPENSATING FLASH ADC

IEEE JOURNAL OF SOLID-STATE CIRCUITS, VOL. 41, NO. 9, SEPTEMBER 2006

1959
 
## A Distortion Compensating Flash Analog-to-Digital Conversion Technique

Venkata Srinivas, Shanthi Pavan, Ashish Lachhwani, and Naga Sasidhar



# T/H DISTORTION

 


Fig. 2. Flash ADC behavior with an ideal track-and-hold.

 


Fig. 3. Flash ADC behavior with a real track-and-hold having static nonlinearity.



# PRE-DISTORTED REFERENCES



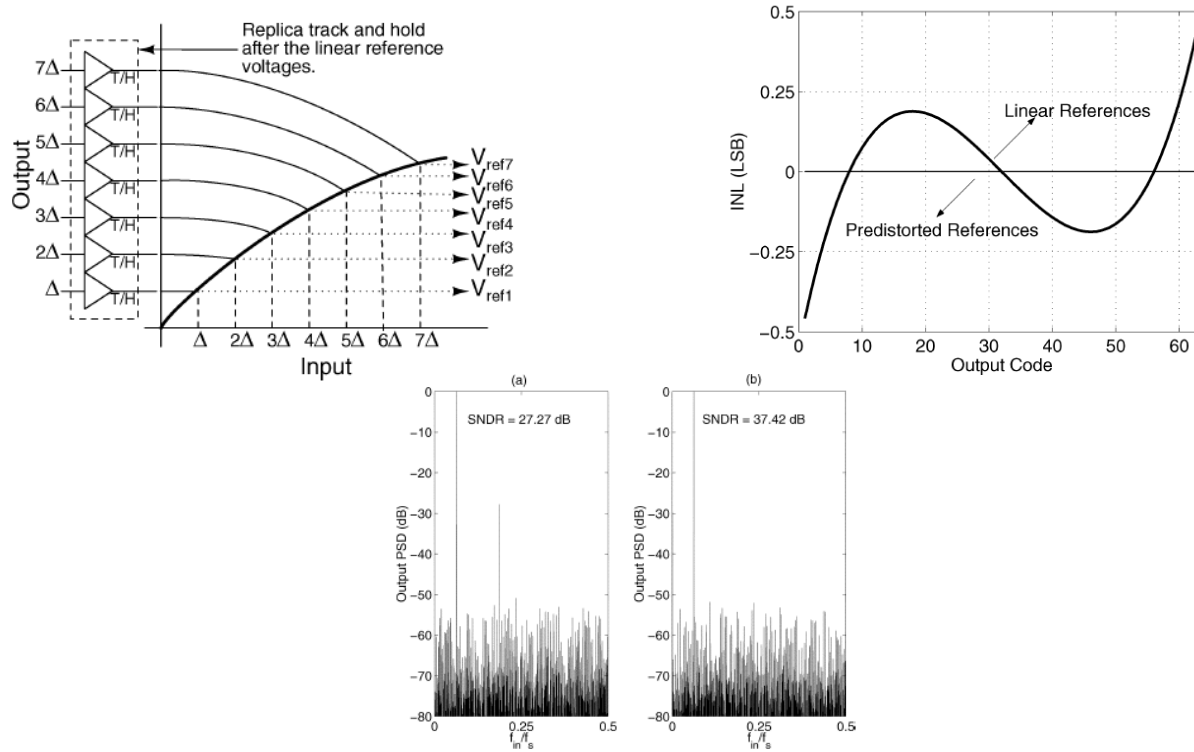
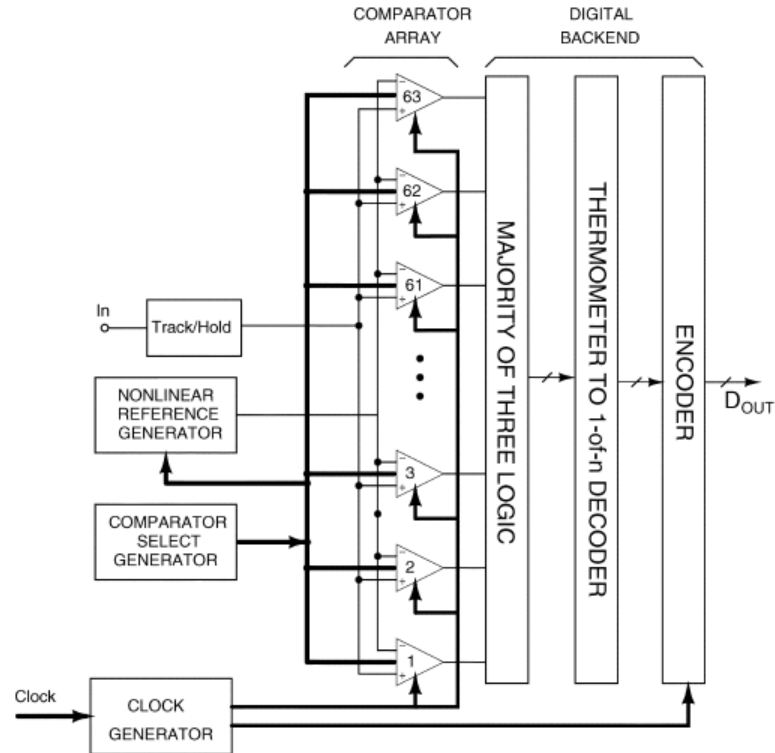


Fig. 5. ADC output spectrum with track-and-hold having static nonlinearity with (a) linear references and (b) predistorted references.



# ADC ARCHITECTURE

 

# T/H CIRCUIT

 


# COMPARTMENT

 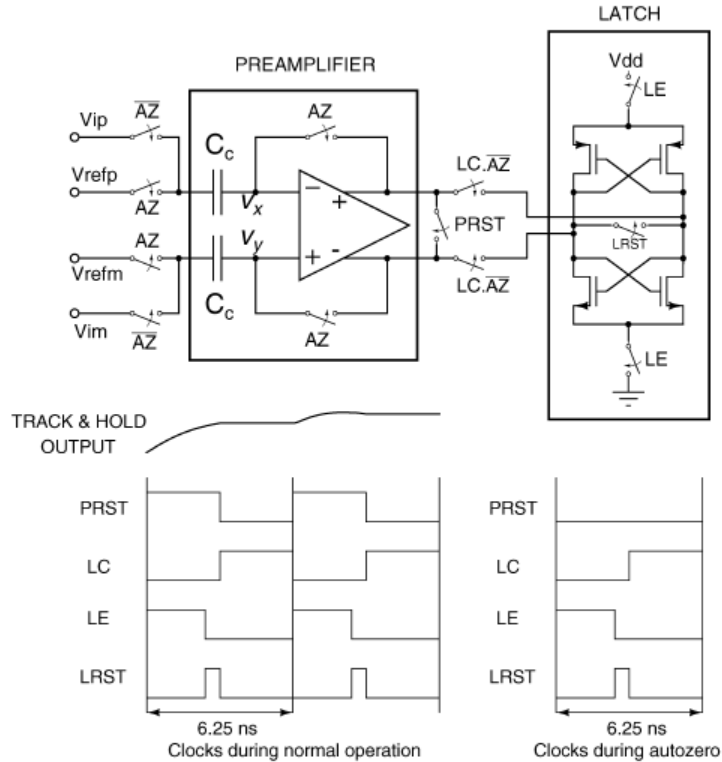

Schematic of the preamplifier.

# NON-LINEAR REFERENCE GENERATOR

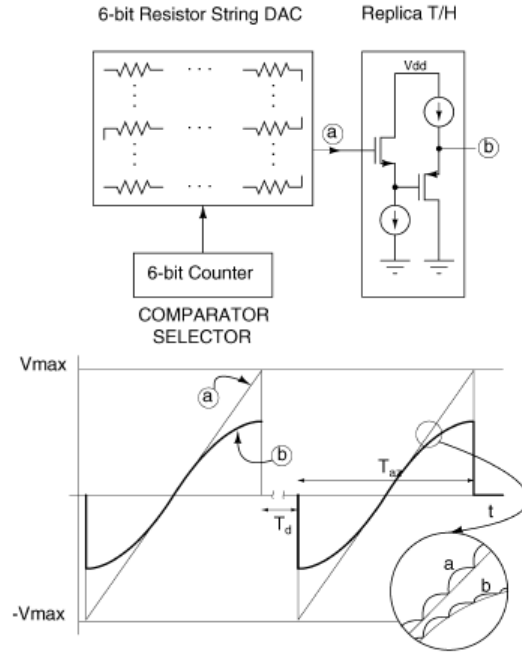

g. 12. Nonlinear reference generator.

 


Fig. 13. Linear reference generator.



# ADC TESTING

 
 


Fig. 19. Normalized output spectrum of the ADC.



 


Fig. 20. Illustration of (a) continuous background autozero mode and (b) discontinuous background autozero mode.

 

# TEST RESULTS

 

SUMMARY OF ADC PERFORMANCE

Resolution	6 bits
Technology	0.35- $\mu$ m CMOS 2P4M
Supply voltage	3.3 V
Nominal input swing	3.4 $V_{pp}$ differential
DNL (nominal input range)	0.3 LSB
INL (nominal input range)	0.3 LSB
SNDR	36.0 dB @ $f_{in} = 49.9$ MHz, $f_s = 100$ MHz 33.6 dB @ $f_{in} = 79.9$ MHz, $f_s = 160$ MHz
Power consumption	50 mW @ $f_s = 160$ MHz
Active Area	2.0 $\times$ 0.4 mm <sup>2</sup>
Chip package	DIP40

Figure of Merit 
$$\frac{\text{Energy}}{(\text{conversion\_step})} = \frac{P_{\text{diss}}}{2^{\text{ENOB}} \times f_{\text{samp}}}$$



# REFERENCES

1. Rudy van de Plassche, “**CMOS Integrated Analog-to-Digital and Digital-to-Analog Converters**,” 2<sup>nd</sup> Ed., Springer, 2005.
2. N. Krishnapura, *Analog IC Design Lectures*, IIT Madras, 2008.
3. Y. Chiu, *Data Converters Lecture Slides*, UT Dallas 2012.
4. B. Boser, *Analog-Digital Interface Circuits Lecture Slides*, UC Berkeley 2011.

