# Delta-Sigma Analog-to-Digital Converters

**Oversampling Data Converters Basics** 

Vishal Saxena



# **Oversampling and Noise-Shaping**





# Oversampling



- Oversampling ratio (*OSR*)
- □ Conversion bandwidth:  $f_{\rm B} = f_{\rm s}/2$ · OSR
- $\Box \quad SQNR = 6.02 \cdot N + 1.76 + 10 \cdot \log_{10}(OSR)$
- □ 0.5 bits increase in resolution per doubling in OSR

# Oversampling



File: oversampling1.m

# Oversampling



File: oversampling1.m

# **Oversampling with Feedback**



- □ Can we use feedback with high loop-gain  $(A \cdot k_q)$  to reduce the error e=|u-v|?
- □ Since quantizer output can not be equal to the input

$$A \cdot k_q \to \infty \Longrightarrow e = |u - v| \to \infty$$

□ The loop will be unstable as the error gets unbounded

# **Oversampling with Feedback**



- Use large loop-gain in the signal band and small loop-gain at higher frequencies
- $\Box \quad \text{At low frequencies } e = |u v| \to 0$
- □ At high frequencies, low loop-gain stabilizes the loop
- $\Box \quad L(z) \text{ is the loop-filter}$
- □ This feedback arrangement is called a (noise) modulator

# **First-order Modulator**



- Differencing (Δ) followed by an accumulator (Σ)
  - ΔΣ modulator
- $\Box \quad \text{At low frequencies } e = |u v| \to 0$

# First-order Noise Shaping



Linearized model for the modulator

$$V(z) = z^{-1} U(z) + (1 - z^{-1}) E(z)$$
  
STF NTF

- Noise transfer function (NTF)
  - (1-z<sup>-1</sup>) : first-order differentiator
  - High-pass shaping of quantization noise
- Gignal transfer function (STF)
  - Unit delay

#### First-order ΔΣ Modulator





File: First\_Order\_DSM.m

### First-order $\Delta\Sigma$ Modulator SQNR



In-band quantization noise (IBN)

$$\frac{\Delta^2}{12} \cdot \frac{\pi^2}{3} \cdot OSR^{-3}$$

- $\Box \quad SQNR = 6.02 \cdot N 3.4 + 30 \cdot \log_{10}(OSR)$
- 1.5 bits increase in resolution per doubling in OSR
- Out-of-band noise is filtered out using a digital filter

$$IBN = \int_{0}^{\frac{\pi}{OSR}} S_{\nu}(e^{j\omega}) d\omega$$
$$= \frac{\Delta^2}{12} \int_{0}^{\frac{\pi}{OSR}} |NTF(e^{j\omega})| \cdot d\omega$$
$$= \frac{\Delta^2}{12} \int_{0}^{\frac{\pi}{OSR}} 4\sin^2(\omega/2) \cdot d\omega$$
$$\approx \frac{\Delta^2}{12} \int_{0}^{\frac{\pi}{OSR}} \omega^2 \cdot d\omega$$
in
$$= \frac{\Delta^2}{12} \cdot \frac{\omega^3}{3} \Big|_{0}^{\frac{\pi}{OSR}}$$
$$= \frac{\Delta^2 \pi^2}{36 \cdot OSR^3}$$

### Delta-Sigma ( $\Delta\Sigma$ ) ADC



- □ Use oversampling ( $f_s = 2 \cdot OSR \cdot BW$ ) to shape the quantization noise out of the signal band
- □ Use low-resolution ADC and DAC to higher much higher resolution
- Digitally filter out the out-of band shaped (modulated) noise
- □ Trades-off SQNR with oversampling ratio (OSR)

# Second-Order Noise Shaping



Linearized model for the modulator 

$$V(z) = z^{-1}U(z) + (1 - z^{-1})^{2}E(z)$$

- Second-order noise-shaping In-band quantization noise (IBN):  $\frac{\Delta^2}{12} \cdot \frac{\pi^4}{5} \cdot OSR^{-5}$ 
  - 2.5 bits increase in resolution per doubling in OSR
- Can be extended to higher orders

#### Second-order $\Delta\Sigma$ Modulator



File: Second\_Order\_DSM.m

## Second-order $\Delta\Sigma$ Modulator



#### **D** NTF(z) = $(1-z^{-1})^2$

- Two zeroes at DC
- Out-of-Band Gain (OBG) (i.e gain at  $\omega \approx \pi$ ) = 4

# 2<sup>nd</sup> order DSM



© Vishal Saxena

0.9

### 2<sup>nd</sup> order DSM: contd.



#### Comparison: 1<sup>st</sup> and 2<sup>nd</sup> order modulator waveforms





- □ NTF(z) =  $(1-z^{-1})$
- $\bigcirc$  OBG = 2
- $\square Max LSB jump = 1$

- NTF(z) =  $(1-z^{-1})^2$ • OBG = 4
  - $\square Max LSB jump = 3$

# Higher-Order $\Delta\Sigma$ Modulators

# Higher-Order NTFs



- Higher order noise shaping
  - Reduced in-band noise, higher SQNR
- $\Box \quad \text{For } NTF = (1-z^{-1})^{-N}, \text{ in-band noise (IBN): } \frac{\Delta^2}{12} \cdot \frac{\pi^{2N}}{(2N+1)} \cdot OSR^{-(2N+1)}$ 
  - Ideally (N+1/2) bits increase in resolution per doubling in OSR

# Higher-Order NTFs



NTF gain increases at high frequencies (around ω≈π)
Can we go on increasing the order?

# Third-order $\Delta\Sigma$ Modulator Example



- $\Box$  *NTF*(*z*) =  $(1-z^{-1})^{3}$
- $\Box$  OBG = 8, Full-scale input.
- □ Unstable after few samples (look at quantize input (*y*) blowing up!).
  - Signature for ΔΣ instability
  - Worst case for a single-bit quantizer.

File: Third\_Order\_DSM.m

# Third-order $\Delta\Sigma$ Modulator Example



- □ Stable for 50% of full-Scale amplitude
- □ Signal dependent stability
  - Need to develop intuition for modulator stability
  - Reference: Stability theory from the Yellow Bible of delta-sigma

File: Third\_Order\_DSM.m

# Systematic NTF Design

- □ NTFs of the form  $(1-z^{-1})^N$  have stability issues
  - The OBG (2<sup>N</sup>) are too high
- □ A larger OBG causes more wiggling at the quantizer input
  - This saturates the quantizer for even smaller inputs
  - Irrecoverable quantizer saturation causes loop instability
- For high-OBG the maximum stable (input) amplitude (MSA) is small
- □ The stability is worse for low quantizer resolutions
- Thus we need to reduce OBG while maintaining high inband noise shaping

# Systematic NTF Design Procedure

- Introduce poles into the NTF
- $\square \quad NTF(z) = \frac{(1 z^{-1})^{N}}{D(z)}$
- NTF realizability criterion
  - No delay-free loops in the modulator
    - First sample of the NTF impulse response (i.e. h[0])=1
  - $\Rightarrow$  NTF( $\infty$ )=1
  - $\Rightarrow D(z=\infty)=1$
- Commonly used pole positions: Butterworth, Inverse Chebyshev and maximally flat poles (maxflat)



# **NTF Response with Poles**



Select appropriate OBG for the NTF to assure stability
Trade-off between stability and increased in-band noise

MSA vs SQNR for a given order and quantizer resolution

# Systematic NTF Design Example

#### Specifications

SQNR > 120 dB

#### • A signal bandwidth which results in an OSR = 64

- Study optimal clock rate for the given process and quantizer design.
- Designer's Choice
  - Order = 3
  - Quantizer levels (nLev) = 16
  - Butterworth high-pass response for the NTF

#### □ Use MATLAB for finding coefficients of the HPF response.

- $[b,a] = butter(order, \omega_{3dB}, 'high')$
- The cutoff frequency  $\omega_{3dB}$  specifies the transfer function.



□ Start with cutoff frequency  $ω_{3dB} = π/8$ , for the butterworth HPF H(z).
□ Derive a realizable NTF using NTF(z)=H(z)/b<sub>0</sub>

- Map the NTF response to a loop-filter architecture (details later)
- Simulate the modulator for all possible amplitudes and input tone frequencies.
- □ Compute the peak SQNR and MSA.
  - simulateDSM function in the toolbox.
  - Can use Risbo's method shown later



Peak SNR = 107 dB
MSA = 0.9

© Vishal Saxena

- If SNR is not enough, repeat the entire procedure with a higher cutoff frequency for the Butterworth HPF
  - IBN ↓, SQNR ↑
  - OBG  $\uparrow$  and MSA  $\downarrow$
- If SNR is too high, repeat the entire procedure with a lower cutoff frequency for the Butterworth HPF
  - IBN  $\uparrow$ , SQNR  $\downarrow$
  - OBG  $\downarrow$  and MSA  $\uparrow$



□  $ω_{3dB} = π/4$ . □ Peak SNR = 119 dB, OBG = 2.25, MSA = 0.8



 $\Box \qquad \omega_{3dB}=2\pi/7.$ 

- □ Peak SNR = 121 dB, OBG = 2.54, MSA = 0.8.
  - Design closed !

- An advanced version of this iterative process is implemented as the function synthesizeNTF in the deltasigma Toolbox.
  - Several 'opt' params for NTF zero (and pole) optimization
  - Use synthesizeChebyshevNTF for low OSR and low OBG designs.

# **NTF-Zero** Optimization

- □ Spread zeros in the signal band to minimize in-band noise
  - Complex zeros on the unit circle
  - 8dB increase in SQNR for 3<sup>rd</sup> order modulator
- Bandwidth normalized NTF-zero locations obtained by toolbox function ds\_optzeros(order, 1)
- Already implemented in synthesizeNTF function for opt=1



© Vishal Saxena

# 2<sup>nd</sup> order DSM: NTF Zero Optimization



$$NTF(z) = (1 - e^{j0.06}z^{-1})(1 - e^{-j0.06}z^{-1})$$

File: Second\_Order\_DSM\_Zero\_Opt.m Set variable opt=1.
# 2<sup>nd</sup> order DSM: NTF Zero Optimization contd.



•5.5 dB increase in SQNR.

NTF pole (if any) optimization to be discussed later.

© Vishal Saxena

# Estimating MSA (Maximum Stable Amplitude)

- □ MSA is found through extensive simulation
- Simulate for input sinusoids of varying amplitudes for all possible signal frequencies in the signal band.
  - For every input amplitude compute in-band SNR.
  - Beyond the MSA, the NTF poles move out of the unit circle.
  - Noise shaping is disrupted and the in-band SNR drops.
  - At this point the quantizer input (y[n]) blows up.
- simulateSNR function in the toolbox does exactly the same
- □ Time consuming and often impractical for iterative design

# Estimating MSA using Risbo's Method



- □ Use a slow ramp input from 0 to FS value.
  - Plot log<sub>10</sub>|y[n]|. Observe where this plot blows up.
  - Take 90% of the input amplitude where log<sub>10</sub>|y[n]| blows up as a conservative estimate for MSA.
  - Estimated MSA is close to that predicted by the sinewave input method.
- Much quicker than the sinewave technique (simulateSNR function)

### Estimating MSA using Risbo's Method



File: MSA\_Risbo\_Method.m

# Simulation with input with MSA



# Simulated SNR with input with MSA



# Simulation with input with 1.2\*MSA



# Simulation with input with 1.2\*MSA





Area above and below the 0-dB axis are equal.



Butterworth NTF.

Area above and below the 0-dB axis are equal.



Inverse Chebyshev NTF.

Area above and below the 0-dB axis are equal.



Better in-band performance results in worse out-of-band performance.



Complex NTF zeros result in better in-band performance for the same OBG.



Higher-order NTF results in better in-band performance for the same OBG.

# Loop Filter Architectures

## **Loop-Filter Architectures**

Several loop-filter discrete-time architectures possible
 Toolbox function realizeNTF maps the synthesized NTF to loop-filter co-efficients

[a,g,b,c] = realizeNTF(H, form);

- Dynamic Range Scaling (DRS) performed to scale loopfilter states to a bounded value
  - Scaling performed using ABCD matrix representation of the loopfilter
  - See any introductory text on Linear Systems

```
ABCD = stuffABCD(a,g,b,c,form);
[ABCDs umax] = scaleABCD(ABCD, nLev, f0, xLim);
[a,g,b,c] = mapABCD(ABCDs, form);
```

### CIFB (Cascade of Integrators with Distributed Feedback)



- □ Cascade of delaying integrators:
  - Feedback coefficients a's realize the zeros of L<sub>1</sub> and thus the NTF and STF poles.
  - Feed-in coefficients b's determine zeros of L<sub>0</sub> and thus the STF zeros.
  - State scaling coefficients c's are used for dynamic range scaling.

### CRFB (Cascade of Resonators with Distributed Feedback)



- Combine a non-delaying and a delaying integrator with local feedback around them, to form a stable resonator
  - Local feedback coefficients g's realize the complex zeros in the NTF.
  - Implements NTF with complex  $ze_{z_i} = e^{\pm j\sqrt{g_1}}$
- For odd-order, use an integrator in the front to avoid noise coupling due to g

### CIFF (Cascade of Integrators with Feed-Forward Summation)



- Feedforward summation of states
- $\Box \quad \text{For } b_1 = b_{N+1} = 1 \text{ and } b_2 \text{ to } b_N = 0, \text{ STF} = 1$ 
  - Loop-filter only processes quantization noise, low power and distortion
- Feedforward loop-filters typically result in lower-power implementation

### CRFF (Cascade of Resonators with Feed-Forward Summation)



- □ Use resonators with feedforward summation
  - Implements NTF with complex zeros
- For odd-order, use an integrator in the front to avoid noise coupling due to g

# **CIFB** Example 1

CIFB, order = 4All NTF zeros at z=1, i.e. opt =0. OBG = 3, OSR = 16, nLev = 15. Only single input coupling is used b(2:end) = 0Maxflat poles in STF  $\mathbf{a} = [0.16 \ 0.86 \ 1.9 \ 2.1]$  $\mathbf{b} = [0.16\ 0\ 0\ 0]$ **c** = [1 1 1 1]  $g = [0 \ 0]$ 



#### File: CIFB\_4<sup>th</sup>\_Order\_1.m

# CIFB Example 1 contd. : NTF and STF



States



File: CIFB\_4<sup>th</sup>\_Order\_1.m

# Spectrum



File: CIFB\_4<sup>th</sup>\_Order\_1.m

# Topologies

- □ CRFB with single feed-in
  - CRFB\_4<sup>th</sup>\_Order\_1.m
- Low-distortion CRFB topology
  - CRFB\_4<sup>th</sup>\_Order\_2.m
- □ CIFB with single feed-in and optimized NTF zeros
  - CIFB\_Opt\_4<sup>th</sup>\_Order\_1.m
- Low-distortion CIFB topology with optimized NTF zeros
  - CIFB\_Opt\_4<sup>th</sup>\_Order\_2.m

# **CIFF Example 1**





# CIFF Example 1 contd. : NTF and STF



# States



#### File: CIFF\_4<sup>th</sup>\_Order\_1.m

# Spectrum



# CIFF Example 2

CIFF, order = 4All NTF zeros at z=1, i.e. opt =0. OBG = 3, OSR = 16, nLev = 15. Only single input feed-in used b(2:end)=0 $\mathbf{a} = [2.1 \ 1.9 \ 0.86 \ 0.16]$  $\mathbf{b} = [1 \ 0 \ 0 \ 0 \ 0]$ **c** = [1 1 1 1] **g** = [0 0] 



# CIFF Example 2 contd. : NTF and STF



□ Notice the significant STF peaking !

#### File: CIFF\_4<sup>th</sup>\_Order\_2.m

States



- Last integrator output has significant signal content
  - Use dynamic range scaling.
  - Last integrator will burn more power in this case.

# Spectrum



File: CIFF\_4<sup>th</sup>\_Order\_2.m

# Topologies

- Low-distortion CRFF topology
  - CRFF\_4<sup>th</sup>\_Order\_1.m
- □ CRFF with single feed-in
  - CRFF\_4<sup>th</sup>\_Order\_2.m
- Low-distortion CIFF topology with optimized NTF zeros
  - CIFF\_Opt\_4<sup>th</sup>\_Order\_1.m
- CIFF with single feed-in and optimized NTF zeros
  - CIFF\_Opt\_4<sup>th</sup>\_Order\_2.m
- □ STF peaking in FF topologies with single feed-in is an issue
  - CT FF DSM will have STF peaking as full-feedforward branch can't be used.
  - The feed-in coefficients b's can be strategically used to realize CIFF/CRFB topology with better out-of-band STF attenuation.

## $\Delta\Sigma$ Modulator Architectures

Cascade/ MASH architecture:



•Eg. Two first order modulators are used to implement second order modulator.

•Stability concerns are relaxed but mismatch in the two forward paths should be properly monitored.

## $\Delta\Sigma$ Modulator Architectures

Feedforward modulators



•Most popular architecture.

- •Input signal is summed at Nth stage integrator output.
- •Summation block may be required at higher order modulators.
- •Multibit quantizer is necessary.
# Key Terminologies :

- □ SQNR Signal to quantization noise ratio
  - Thermal/electrical noise are not included.
- □ SNR Signal to noise ratio
  - Distortion is not included.
- SDNR Signal to noise and distortion ratio
  - All noise sources are included.
- ENOB Effective number of bits (resolution)
  - This is very important than actual number of output bits
- Dynamic Range (DR)
  - Measured with input of the modulator shorted.
- Harmonic Distortion
  - THD is usually total harmonic distortion. Or Third??
- Spur Free Dynamic Range (SFDR)
  - Very key parameter in communication systems

### Frequency Domain Measurements



## Spurious (tone) Free Dynamic Range (SFDR)



### References

#### **Data Conversion Fundamentals**

- A.1 M. Gustavsson, J. Wikner, N. Tan, *CMOS Data Converters for Communications*, Kluwer Academic Publishers, 2000.
- A.2 B. Razavi, Principles of Data Conversion System Design, Wiley-IEEE Press, 1994.
- A.3 ADC and DAC <u>Glossary</u> by Maxim.
- A.4 B. Murmann, "ADC Performance Survey 1997-2009," [Online].
- A.5 S. Pavan, N. Krishnapura, EE658: Data Conversion Circuits Course at IIT Madras [Online].
- A.6 The Fundamentals of FFT-Based Signal Analysis and Measurement, T.I. App Note here.

### References

#### **Delta-Sigma Data Converters**

- **B.1** R. Schreier, G. C. Temes, *Understanding Delta-Sigma Data Converters*, Wiley-IEEE Press, 2005 (the Green Bible of Delta-Sigma Converters).
- **B.2** S. R. Norsworthy, R. Schreier, G. C. Temes, *Delta-Sigma Data Converters: Theory, Design, and Simulation*, Wiley-IEEE Press, 1996 (the Yellow Bible of Delta-Sigma Converters).
- **B.3** S. Pavan, N. Krishnapura, "Oversampling Analog to Digital Converters Tutorial," 21<sup>st</sup> International Conference on VLSI Design, Hyderabad, Jan, 2008.
- **B.4** S. H. Ardalan, J. J. Paulos, "An Analysis of Nonlinear behavior in Delta-Sigma Modulators," *IEEE TCAS*, vol. 34, no. 6, June 1987.
- **B.5** R. Schreier, "An Empirical Study of Higher-Order Single-Bit Delta-Sigma Modulators," *IEEE TCAS-II*, vol. 40, no. 8, pp. 461-466, Aug. 1993.
- **B.6** J. G. Kenney and L. R. Carley, "Design of multibit noise-shaping data converters," *Analog Integrated Circuits Signal Processing Journal*, vol. 3, pp. 259-272, 1993.
- **B.7** L. Risbo, "Delta-Sigma Modulators: Stability Analysis and Optimization," Doctoral Dissertation, Technical University of Denmark, 1994 [Online].
- **B.8** R. Schreier, J. Silva, J. Steensgaard, G. C. Temes, "Design-Oriented Estimation of Thermal Noise in Switched-Capacitor Circuits," *IEEE TCAS-I*, vol. 52, no. 11, pp. 2358-2368, Nov. 2005.

### References

#### **CAD** for Mixed-Signal Design

- **D.1** K. Kundert, "Principles of Top-Down Mixed-Signal Design," *Designer's Guide Community* [Online].
- **D.2** R. Schreier, Matlab Delta-Sigma Toolbox, 2009 [Online], [Manual], [One page summary].
- **D.3** Jose de la Rosa, "SIMSIDES Toolbox: An Interactive Tool for the Behavioral Simulation of Discrete-and Continuous-time SD Modulators in the MATLAB," University of Sevilla, Spain, [Contact the authors for the software].
- **D.4** P. Malcovati, Simulink Delta-Sigma Toolbox 2, 2009. Available [Online].

#### **Example Datasheets**

- E.1 A 16-bit, 2.5MHz/5 MHz/10 MHz, 30 MSPS to 160 MSPS Dual Continuous Time Sigma-Delta ADC – <u>AD9262</u>, Analog Devices, 2008.
- E.2 A 24-bit, 192 kHz Multi-bit Audio ADC <u>CS5340</u>, Cirrus Logic, 2008.