

# Pipelined Analog-to-Digital Converters


Vishal Saxena

# Multi-Step A/D Conversion Basics

# Motivation for Multi-Step Converters

- ❑ Flash A/D Converters
  - Area and power consumption increase exponentially with
  - number of bits  $N$
  - Impractical beyond 7-8 bits
- ❑ Multi-step conversion-Coarse conversion followed by fine conversion
  - Multi-step converters
  - Sub-ranging converters
- ❑ Multi step conversion takes more time
  - Pipelining to increase sampling rate
- ❑ Objective: Understand digital redundancy concept in multi-step converters

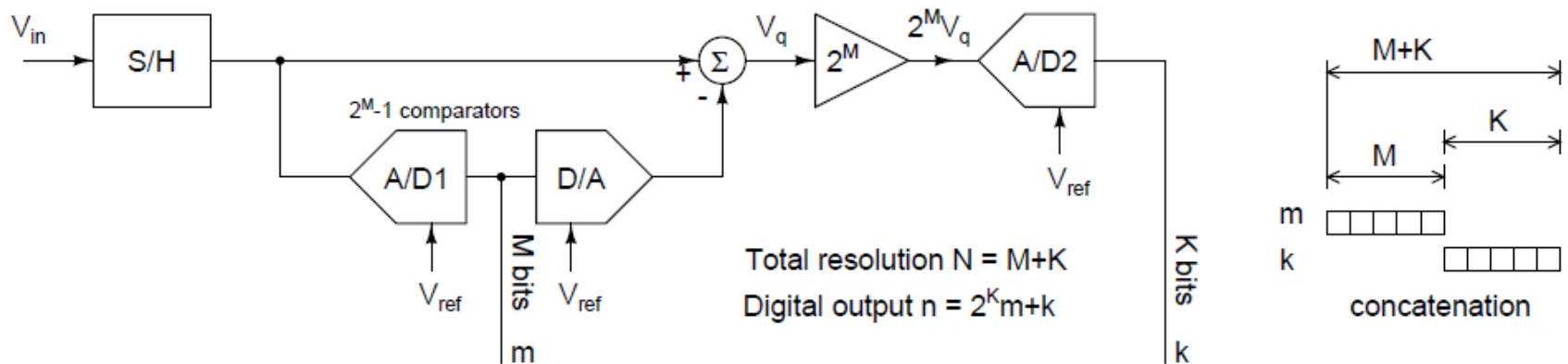
# Two-step A/D Converter - Basic Operation




- ❑ Second A/D quantizes the quantization error of first A/D converter
- ❑ Concatenate the bits from the two A/D converters to form the final output
- ❑ Also called as **two-step Flash ADC**
 
# Two-step A/D Converter - Basic Operation

- ❑ A/D1, DAC, and A/D2 have the same range  $V_{\text{ref}}$
- ❑ Second A/D quantizes the quantization error of first A/D
  - Use a DAC and subtractor to determine residue  $V_q$
  - Amplify  $V_q$  to full range of the second A/D
- ❑ Final output  $n$  from  $m, k$ 
  - A/D1 output is  $m$  (DAC output is  $m/2^M V_{\text{ref}}$ )
  - A/D2 input is at  $k^{\text{th}}$  transition ( $k/2^K V_{\text{ref}}$ )
  - $V_{\text{in}} = k/2^K V_{\text{ref}} \times 1/2^M + m/2^M V_{\text{ref}}$
  - $V_{\text{in}} = (2^K m + k)/2^{M+K} V_{\text{ref}}$
- ❑ Resolution  $N = M + K$ 
  - output  $\Rightarrow n = 2^K m + k$
  - Concatenate the bits from the two A/D converters to form the final output



 
# Two-step A/D Converter – Example with $M=3$ , $K=2$





- ❑ Second A/D quantizes the quantization error of first A/D
- ❑ Transitions of second A/D lie between transitions of the first, creating finely spaced transition points for the overall A/D

# Residue $V_q$

 

- $V_q$  vs.  $V_{in}$ : Discontinuous transfer curve
  - Location of discontinuities: Transition points of A/D1
  - Size of discontinuities: Step size of D/A
  - Slope: unity


# Two-step A/D Converter—Ideal A/D1

  

- ❑ A/D1 transitions exactly at integer multiples of  $V_{ref}/2^M$
- ❑ Quantization error  $V_q$  limited to  $(0, V_{ref}/2^M)$
- ❑  $2^M V_q$  exactly fits the range of A/D2



 
# Two-step A/D converter—M bit accurate A/D1





- ❑ A/D1 transitions in error by up to  $V_{ref}/2^{M+1}$  ( $= 0.5$  LSB)
- ❑ Quantization error  $V_q$  limited to
  - $(-V_{ref}/2^{M+1}, 3V_{ref}/2^{M+1})$ —a range of  $V_{ref}/2^{M-1}$
- ❑  $2^M V_q$  overloads A/D2
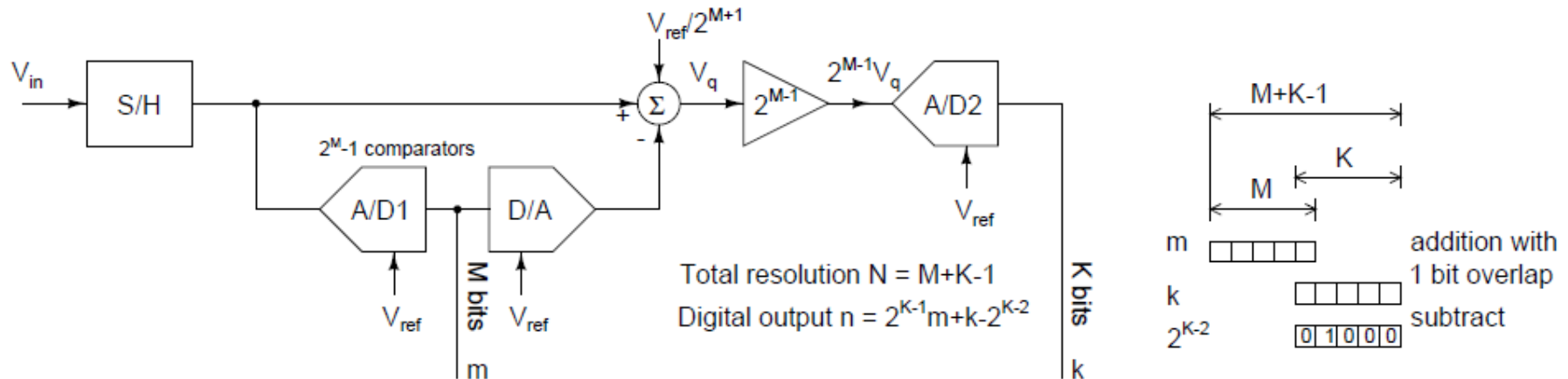
# Two-step A/D with Digital Redundancy (DR)




- ❑ Reduce interstage gain to  $2^{M-1}$
- ❑ Add  $V_{ref}/2^{M+1}$  ( $0.5 \text{ LSB}_1$ ) offset to keep  $V_q$  positive
- ❑ Subtract  $2^{K-2}$  from digital output to compensate for the added offset
  - Digital code in A/D2 corresponding to  $0.5 \text{ LSB}_1 = (V_{ref}/2^{M+1})/(V_{ref}/2^{K+1}) = 2^{K-2}$
- ❑ Overall accuracy is  $N = M + K - 1$  bits
  - A/D1 contributes  $M - 1$  bits
  - A/D2 contributes  $K$  bits; 1 bit redundancy
- ❑ Output  $n = 2^{K-1}m + k - 2^{K-2}$
  
# Two-step A/D with DR: Ideal A/D1 Scenario



- $2^{M-1}V_q$  varies from  $V_{ref}/4$  to  $3V_{ref}/4$
- $2^{M-1}V_q$  outside this range implies errors in A/D1
 
# Two-step A/D with DR: M-bit accurate A/D1




- ❑  $2^{M-1} V_q$  varies from 0 to  $V_{ref}$
- ❑ A/D2 is not overloaded for up to 0.5 LSB errors in A/D1
- ❑ **Issue:** Accurate analog addition of  $0.5 \text{ LSB}_1$  is difficult

# Two-step A/D with DR: M-bit accurate A/D1



- ❑ Recall that output  $n = 2^{K-1}m + k - 2^{K-2}$
- ❑ A/D1 Transition shifted to the left
  - $m$  greater than its ideal value by 1
  - $k$  lesser than its ideal value by  $2^{K-1}$
  - A/D output  $n = 2^{K-1}m + k - 2^{K-2}$  doesn't change
- ❑ A/D1 Transition shifted to the right
  - $m$  lesser than its ideal value by 1
  - $k$  greater than its ideal value by  $2^{K-1}$
  - A/D output  $n = 2^{K-1}m + k - 2^{K-2}$  doesn't change
- ❑ 1 LSB error in  $m$  can be corrected
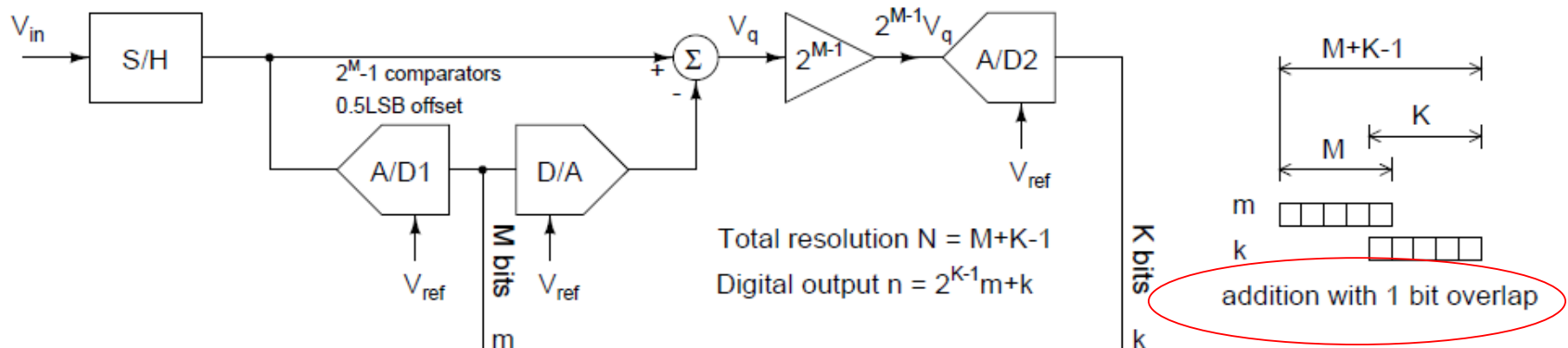
# Two-step A/D with Digital Redundancy (II)





- ❑ Use reduced interstage gain of  $2^{M-1}$
- ❑ **Modification:** Shift the transitions of A/D1 to the right by  $V_{ref}/2^{M+1}$  ( $0.5\text{LSB}_1$ ) to keep  $V_q$  positive
  - Eliminates analog offset addition and achieves same effect as last scheme
- ❑ Overall accuracy is  $N = M + K - 1$  bits
  - A/D1 contributes  $M - 1$  bits, A/D2 contributes  $K$  bits; 1 bit redundancy
- ❑ Output  $n = 2^{K-1}m + k$ , no digital subtraction needed
  - ✓ Simpler digital logic
  
# Two-step A/D with DR(II)-Ideal A/D1 Scenario



- $2^{M-1}V_q$  varies from 0 to  $3V_{ref}/4$ ;  $V_{ref}/4$  to  $3V_{ref}/4$  except the first segment
- $2^{M-1}V_q$  outside this range implies errors in A/D1
  
# Two-step A/D with DR (II): M-bit acc. A/D1




- $2^{M-1} V_q$  varies from 0 to  $V_{ref}$
- A/D2 is not overloaded for up to 0.5 LSB errors in A/D1



# Two-step A/D with DR(II): M-bit acc. A/D1


- Recall that output  $n = 2^{K-1}m + k$
  
- A/D1 Transition shifted to the left
  - $m$  greater than its ideal value by 1
  - $k$  lesser than its ideal value by  $2^{K-1}$
  - A/D output  $n = 2^{K-1}m + k$  doesn't change
  
- A/D1 Transition shifted to the right
  - $m$  lesser than its ideal value by 1
  - $k$  greater than its ideal value by  $2^{K-1}$
  - A/D output  $n = 2^{K-1}m + k$  doesn't change
  
- 1 LSB error in  $m$  can be corrected

# Two-step A/D with DR (III)

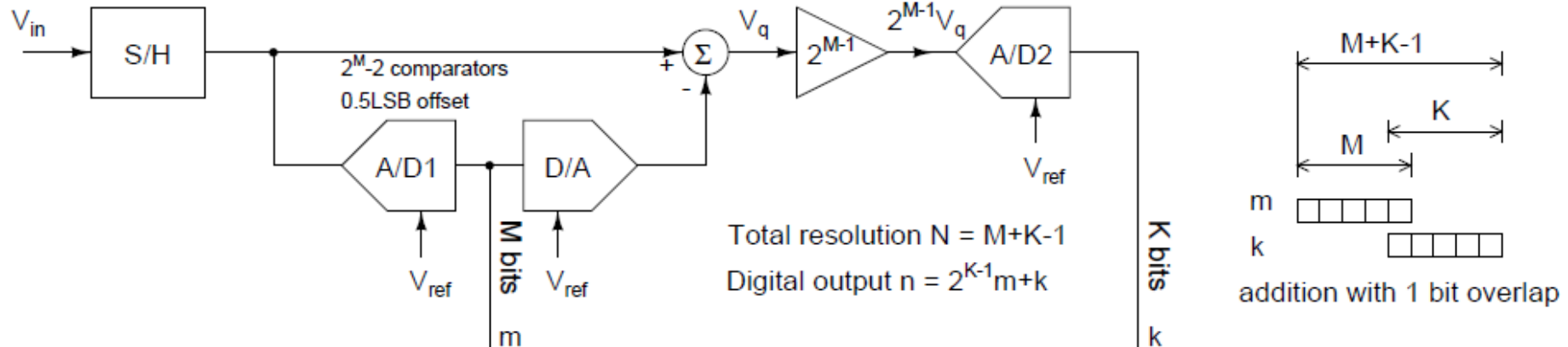


- ❑  $0.5 \text{ LSB } (V_{ref}/2^{M-1})$  shifts in A/D1 transitions can be tolerated
- ❑ If the last transition ( $V_{ref} - V_{ref}/2^{M-1}$ ) shifts to the right by  $V_{ref}/2^{M-1}$ , the transition is effectively nonexistent
  - Still the A/D output is correct
- ❑ Remove last comparator  $\Rightarrow$   $M$  bit A/D1 has  $2^M - 2$  comparators set to  $1.5V_{ref}/2^M, 2.5V_{ref}/2^M, \dots, V_{ref} - 1.5V_{ref}/2^M$
- ❑ Reduced number of comparators

# Two-step A/D with DEC (III)-Ideal A/D1

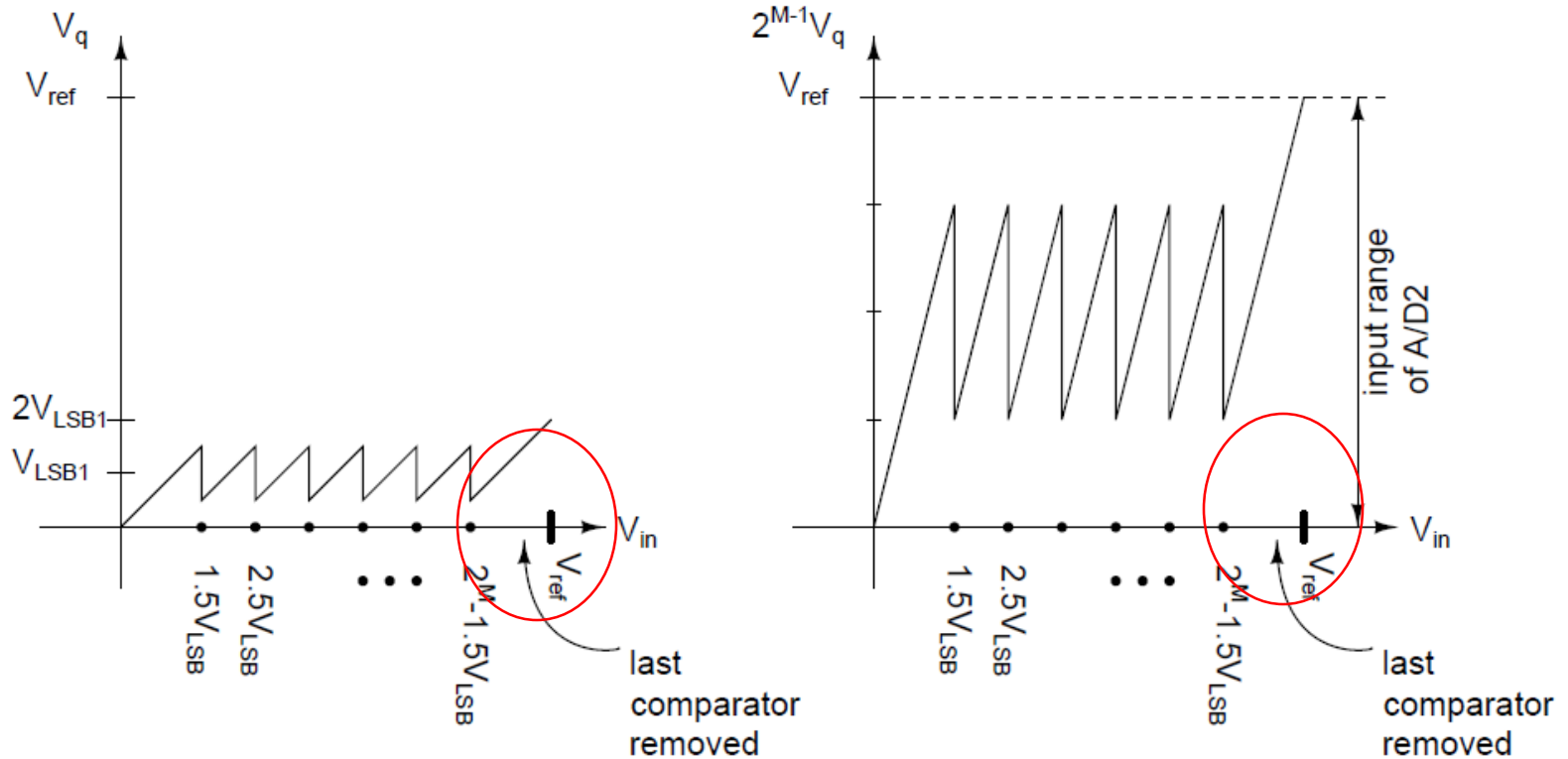

- ❑  $2^{M-1}V_q$  varies from 0 to  $3V_{ref}/4$ ;  $V_{ref}/4$  to  $3V_{ref}/4$  except the first and last segments
- ❑  $2^{M-1}V_q$  outside this range implies errors in A/D1
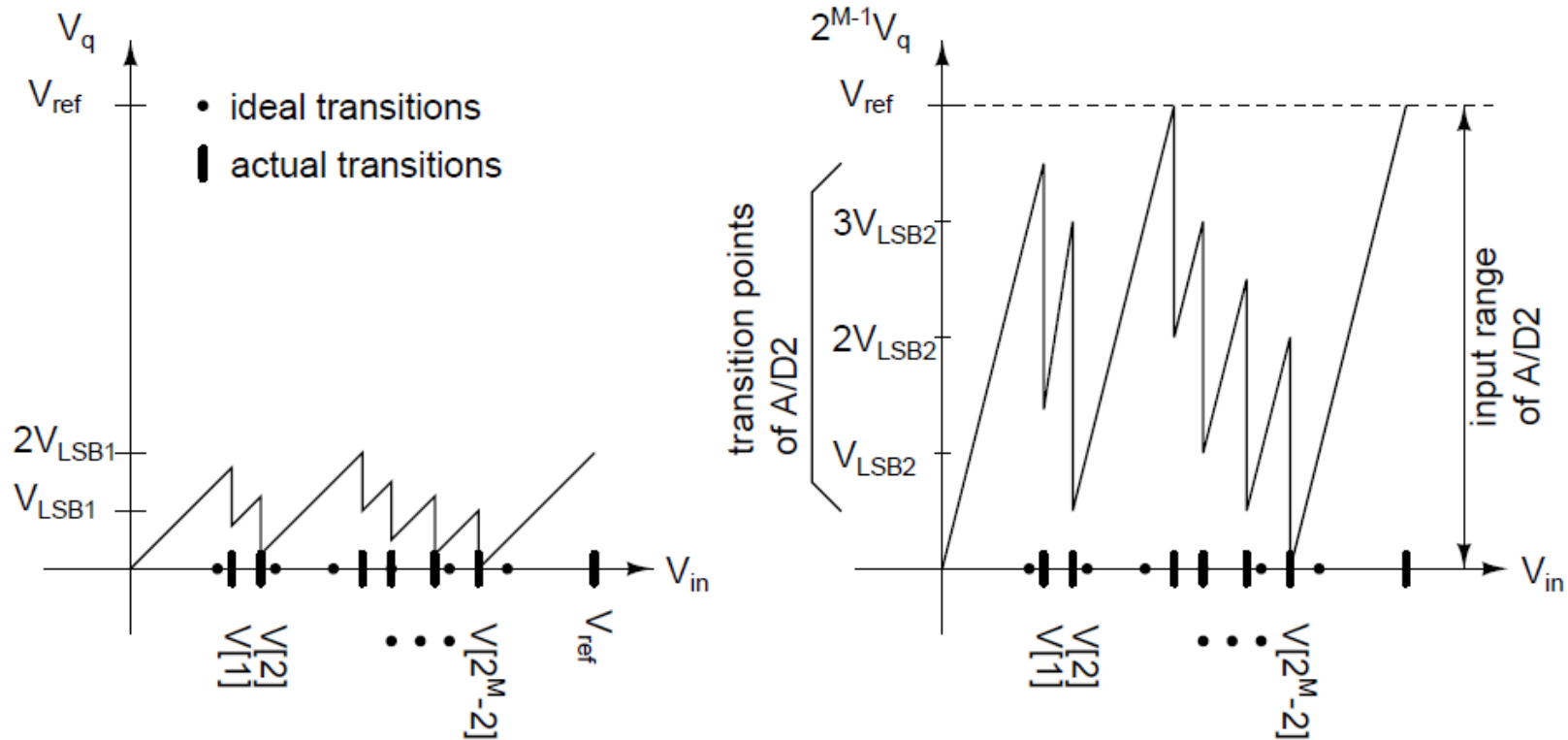
# Two-step A/D with DR (III): M bit acc. A/D1



- $2^{M-1}V_q$  varies from 0 to  $V_{ref}$
- A/D2 is not overloaded for up to 0.5 LSB errors in A/D1


# Two-step A/D with DR(III): M-bit acc. A/D1

- Recall that output  $n = 2^{K-1}m + k$
  
- A/D1 Transition shifted to the left
  - $m$  greater than its ideal value by 1
  - $k$  lesser than its ideal value by  $2^{K-1}$
  - A/D output  $n = 2^{K-1}m + k$  doesn't change
  
- A/D1 Transition shifted to the right
  - $m$  lesser than its ideal value by 1
  - $k$  greater than its ideal value by  $2^{K-1}$
  - A/D output  $n = 2^{K-1}m + k$  doesn't change
  
- 1 LSB error in  $m$  can be corrected

# Multi-step Converters

- ❑ Two-step architecture can be extended to multiple steps
- ❑ All stages except the last have their outputs digitally corrected from the following A/D output
- ❑ Number of effective bits in each stage is one less than the stage A/D resolution
- ❑ Accuracy of components in each stage depends on the accuracy of the A/D converter following it
- ❑ Accuracy requirements less stringent down the pipeline, but optimizing every stage separately increases design effort
- ❑ Pipelined operation to obtain high sampling rates
- ❑ Last stage is not digitally corrected

# Multi-step or Pipelined A/D Converter

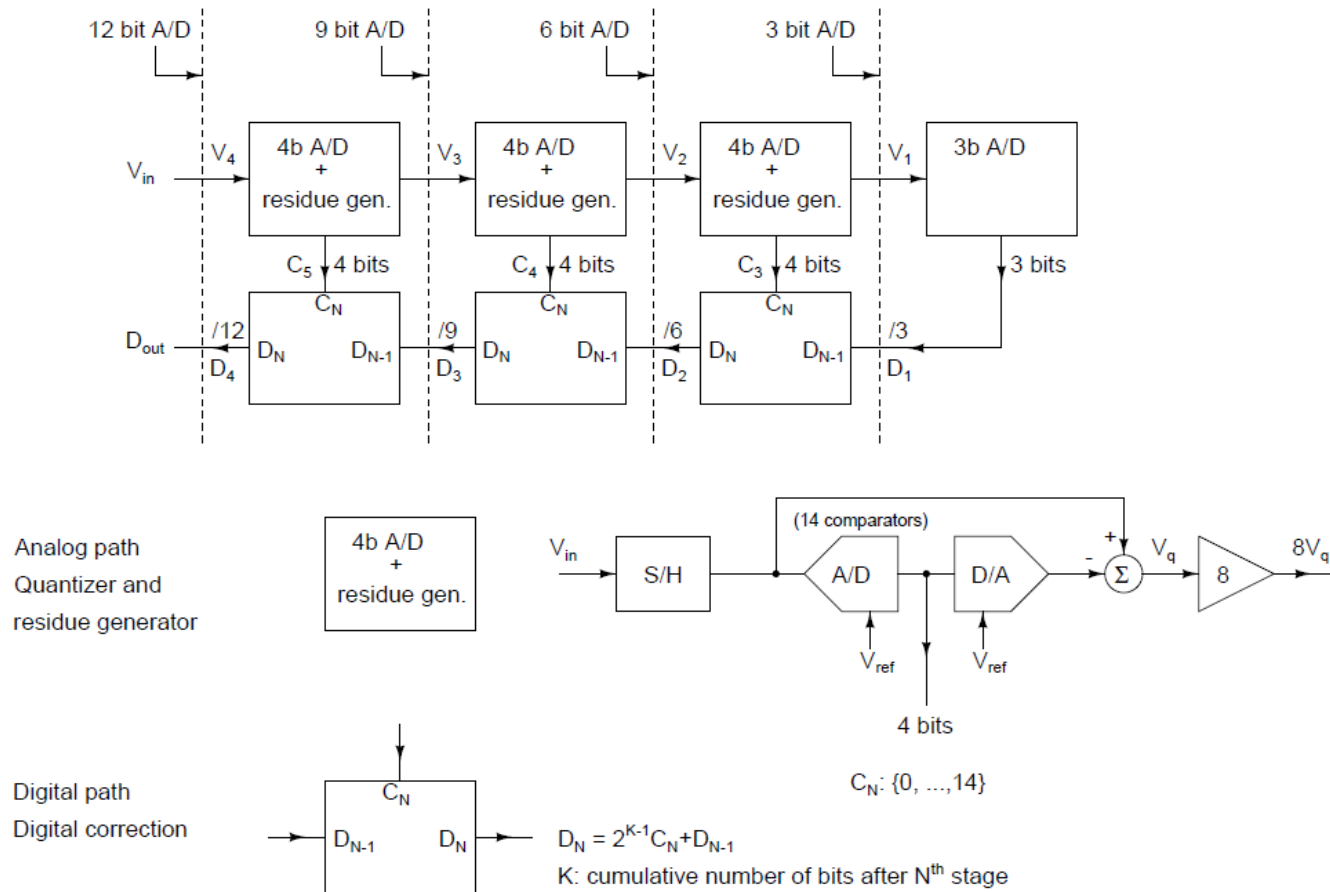

- ❑ 4,4,4,3 bits for an effective resolution of 12 bits
- ❑ 3 effective bits per stage
- ❑ Digital outputs appropriately delayed (by  $2^{K-1}$ ) before addition

# Multi-step Converter Tradeoffs



- ❑ Large number of stages, fewer bits per stage
  - Fewer comparators, low accuracy-lower power consumption
  - Larger number of amplifiers: power consumption increases
  - Larger latency
- ❑ Fewer stages, more bits per stage
  - More comparators, higher accuracy designs
  - Smaller number of amplifiers-lower power consumption
  - Smaller latency
- ❑ Typically 3-4 bits per stage easy to design



# 1.5b/Stage Pipelined A/D Converter


- ❑ To resolve 1 effective bit per stage, you need  $2^2 - 2$ , i.e. two comparators per stage
- ❑ Two comparators result in a 1.5 bit conversion (3 levels)
- ❑ Using two comparators instead of three (required for a 2 bit converter in each stage) results in significant savings

# 1.5b/Stage Pipelined A/D Converter

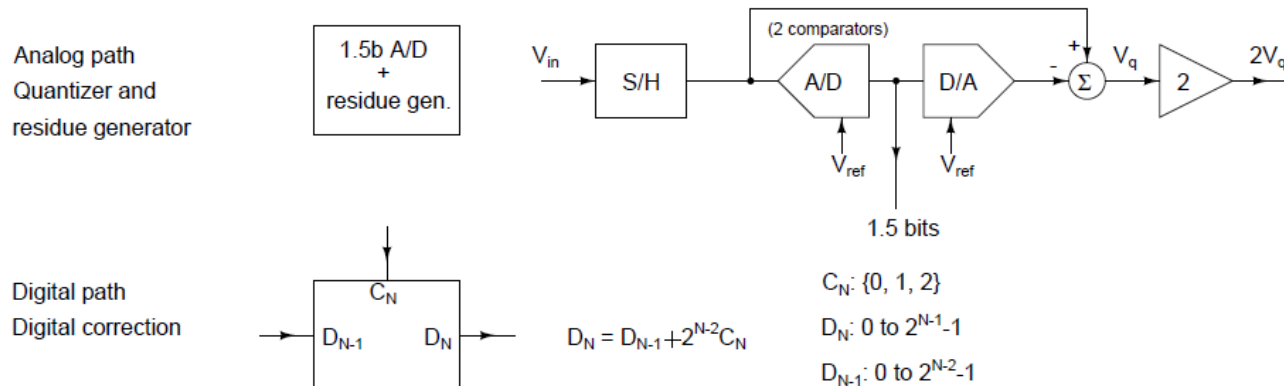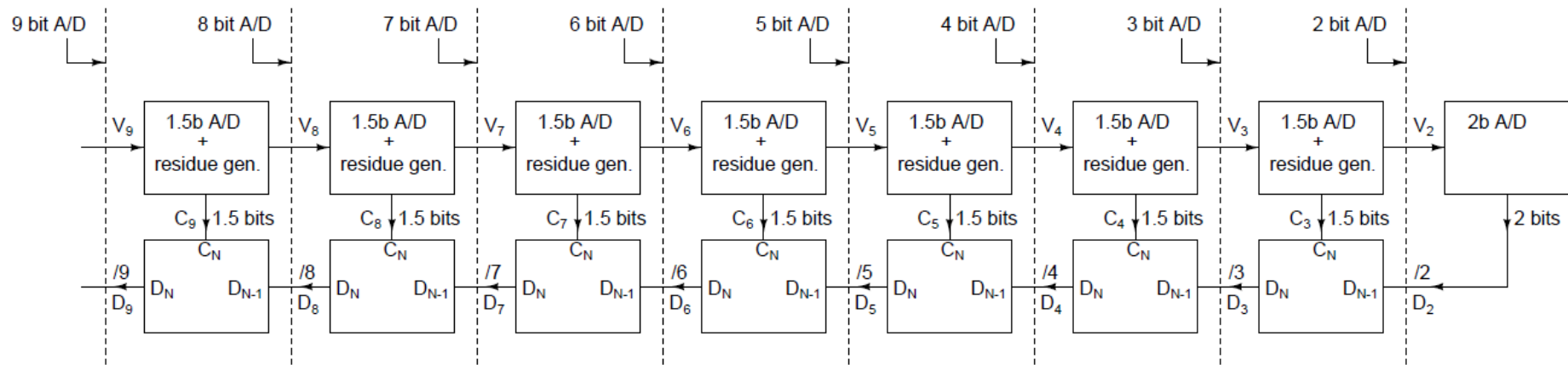


- ❑ Digital outputs appropriately delayed (by  $2^{N-2}$ ) before addition
- ❑ Note the 1-bit overlap when  $C_N$  is added to  $D_{N-1}$ 
  - Use half adders for stages 2 to N

# SC Amplifiers


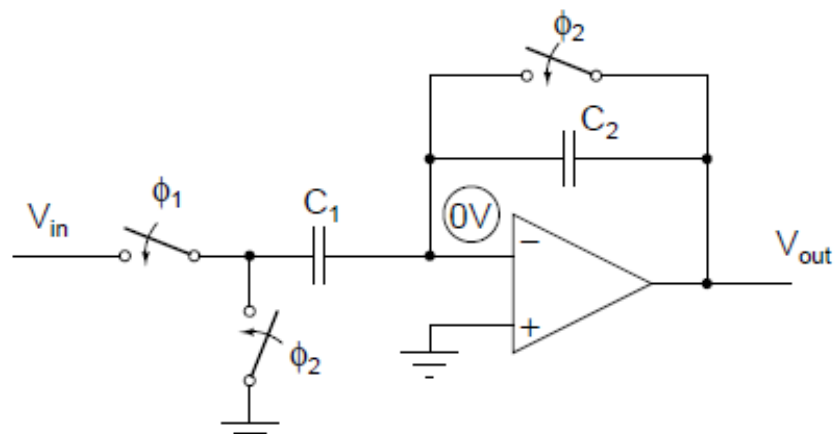


$$V_{out} = -(C_1/C_2)V_{in}$$

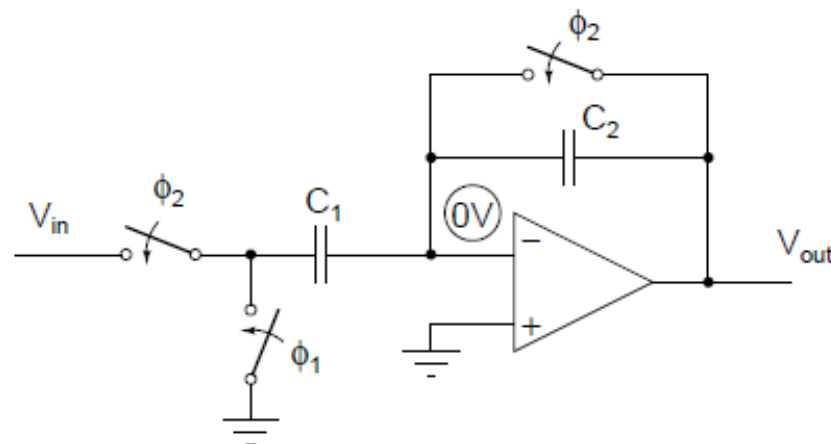

$$V_{out} = +(C_1/C_2)V_{in}$$

  
# SC Realization (I) of DAC and Amplifier



$m$ : output of A/D1



- ❑ Pipelined A/D needs DAC, subtractor, and amplifier
- ❑  $V_{in}$  sampled on  $C$  in  $\Phi_2$  (positive gain)
- ❑  $V_{ref}$  sampled on  $m/2^M C$  in  $\Phi_1$  (negative gain).
- ❑ At the end of  $\Phi_1$ ,  $V_{out} = 2^{M-1} (V_{in} - m/2^M V_{ref})$

# SC Realization of DAC and Amplifier

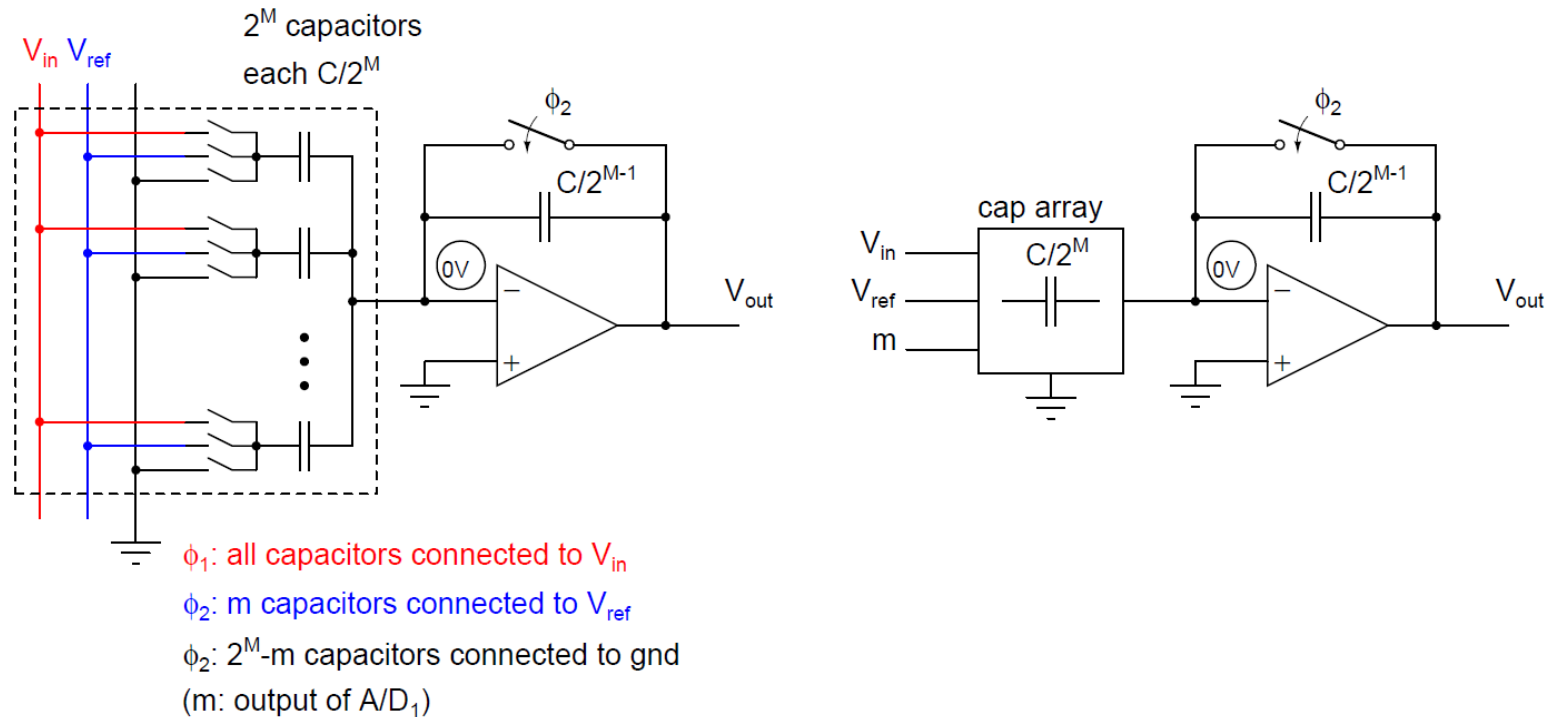

- $m/2^M C$  realized using a switched capacitor array controlled by A/D<sub>1</sub> output

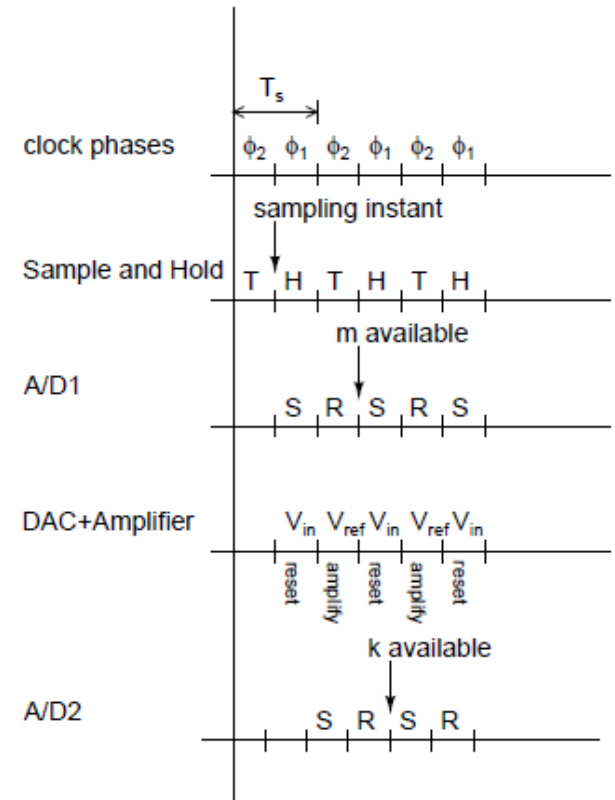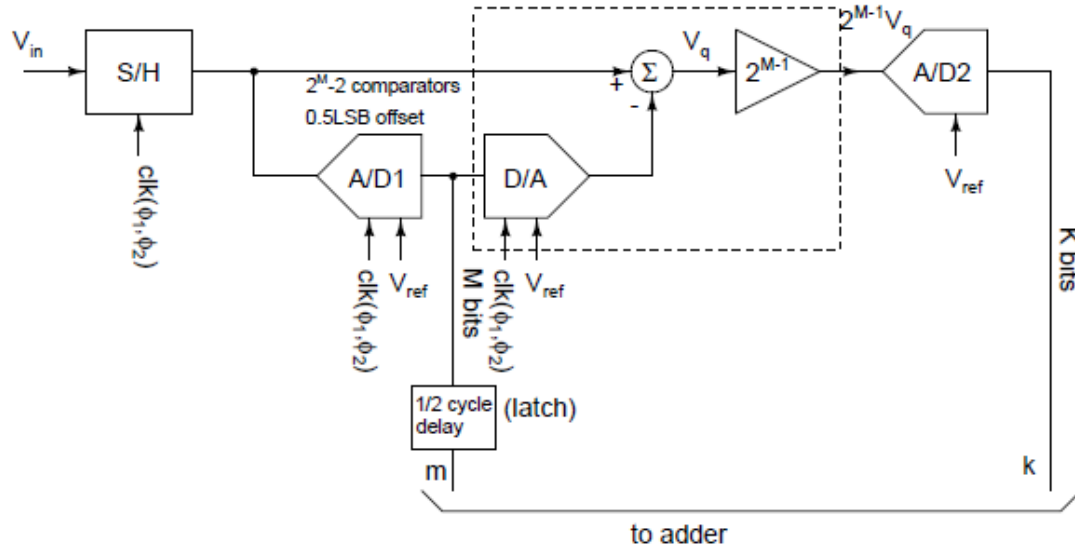
# Two stage converter timing and pipelining



# Two stage converter timing and pipelining

- $\Phi_1$ 
  - S/H holds the input  $V_i[n]$  from the end of previous  $\Phi_2$
  - A/D1 samples the output of S/H
  - Amplifier samples the output of S/H on  $C$
  - Opamp is reset
- $\Phi_2$ 
  - S/H tracks the input
  - A/D1 regenerates the digital value  $m$
  - Amplifier samples  $V_{\text{ref}}$  of S/H on  $m/2^M C$
  - Opamp output settles to the amplified residue
  - A/D2 samples the amplified residue
- $\Phi_2$ 
  - A/D2 regenerates the digital value  $k$ .  $m$ , delayed by  $\frac{1}{2}$  clock cycle, can be added to this to obtain the final output
  - S/H, A/D1, Amplifier function as before, but on the next sample  $V_i[n+1]$
- In a multistep A/D, the phase of the second stage is reversed when compared to the first, phase of the third stage is the same as the first, and so on

# Effect of opamp offset

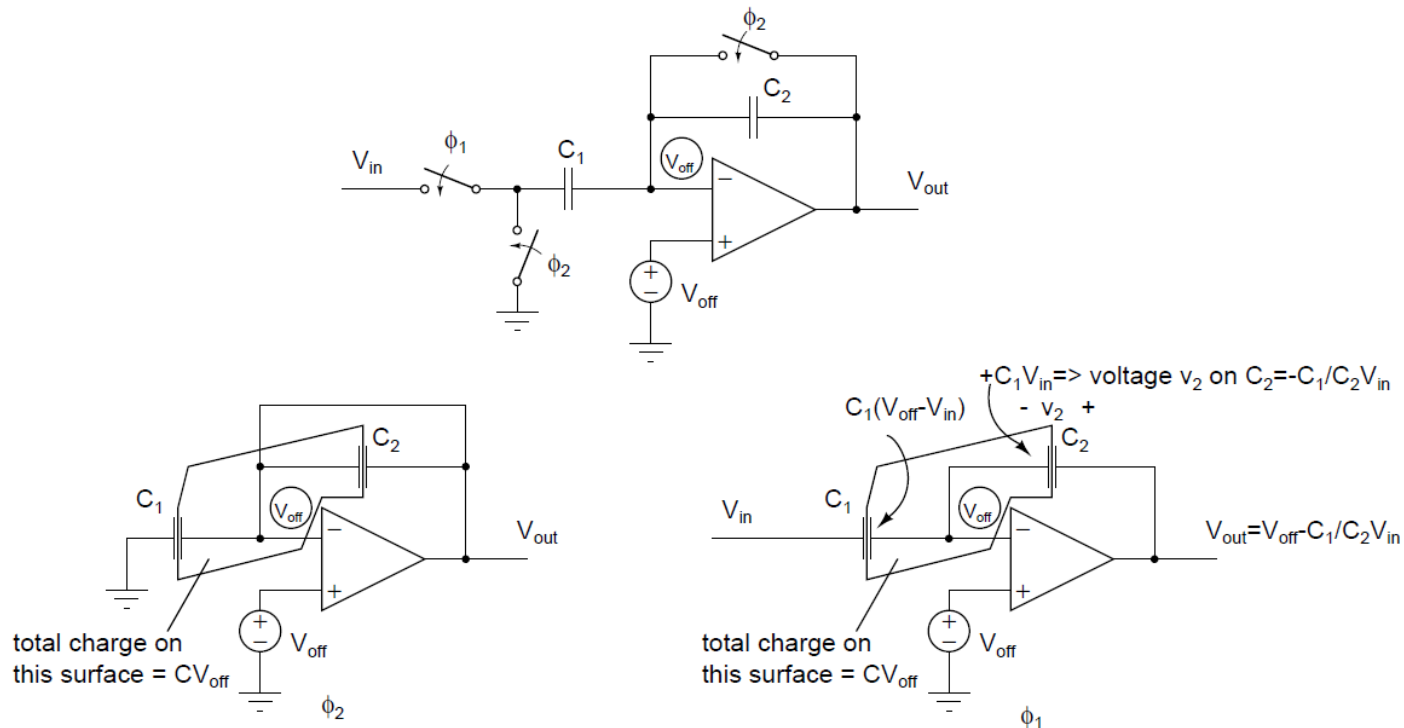

- ❑  $\Phi_2$ :  $C_1$  is charged to  $V_{in} - V_{off}$  instead of  $V_{in}$ 
  - input offset cancellation; no offset in voltage across  $C_2$
- ❑  $\Phi_2$ :  $V_{out} = -C_1/C_2 V_{in} + V_{off}$ 
  - Unity gain for offset instead of  $1 + C_1/C_2$  (as in a continuous time amplifier)




# Circuit Non-idealities

- ❑ Random mismatch
  - Capacitors must be large enough (relative matching  $\propto \frac{1}{\sqrt{WL}}$  to maintain DAC and amplifier accuracy
- ❑ Thermal noise
  - Capacitors must be large enough to limit noise below 1 LSB
  - Opamp's input referred noise should be small enough.
- ❑ Opamp DC gain
  - Should be large enough to reduce amplifier's output error to  $V_{ref} / 2^{K+1}$
- ❑ Opamp Bandwidth
  - Should be large enough for amplifier's output settling error to be less than  $V_{ref} / 2^{K+1}$


# Opamp Power Consumption

- ❑ Opamp power consumption a large fraction of the converter power consumption
- ❑ Amplification only in one phase
- ❑ Successive stages operate in alternate phases
- ❑ Share the amplifiers between successive stages


# MDAC Stages: With Offset Cancellation

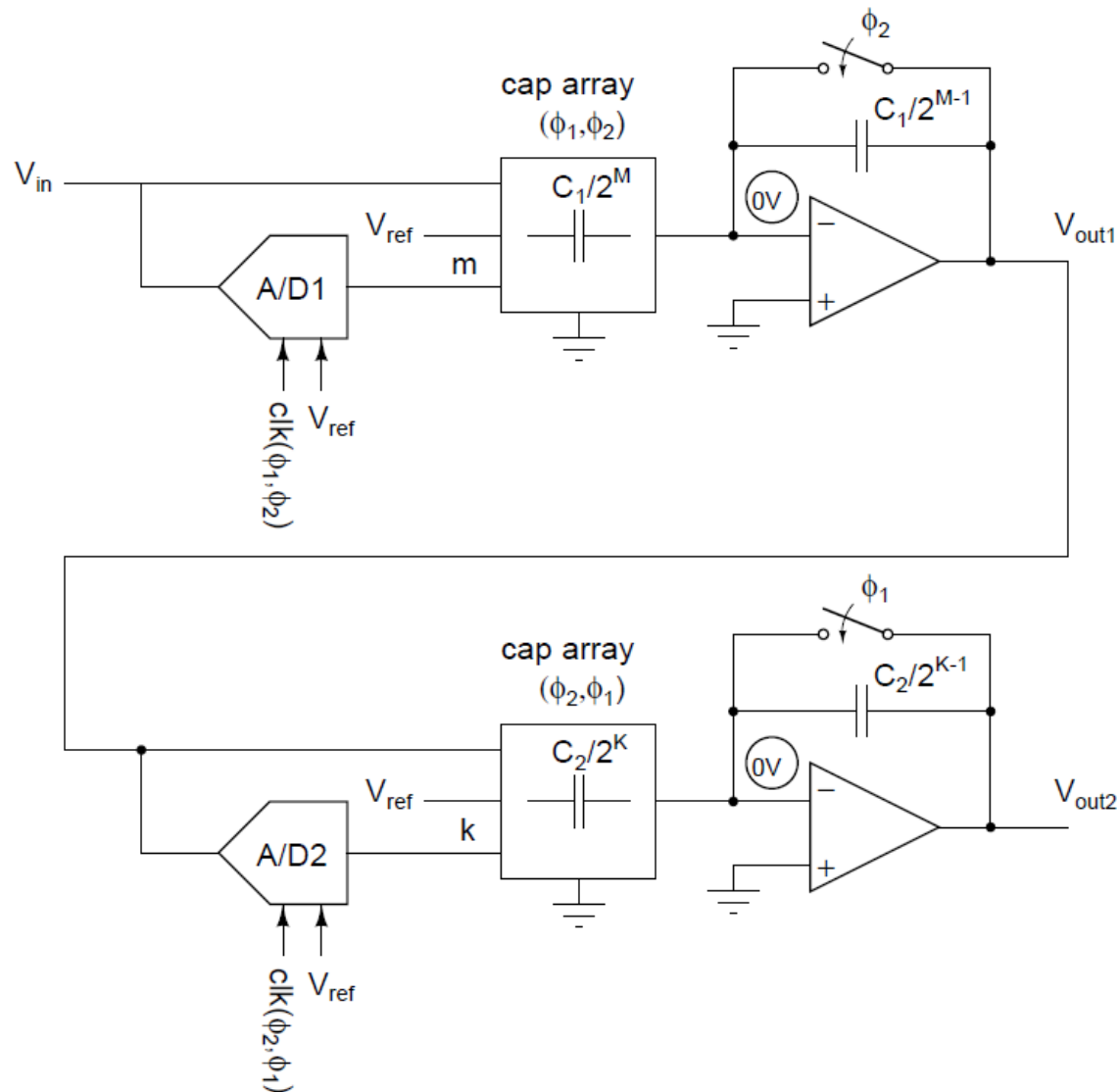

# MDAC Stages: With Offset Cancellation

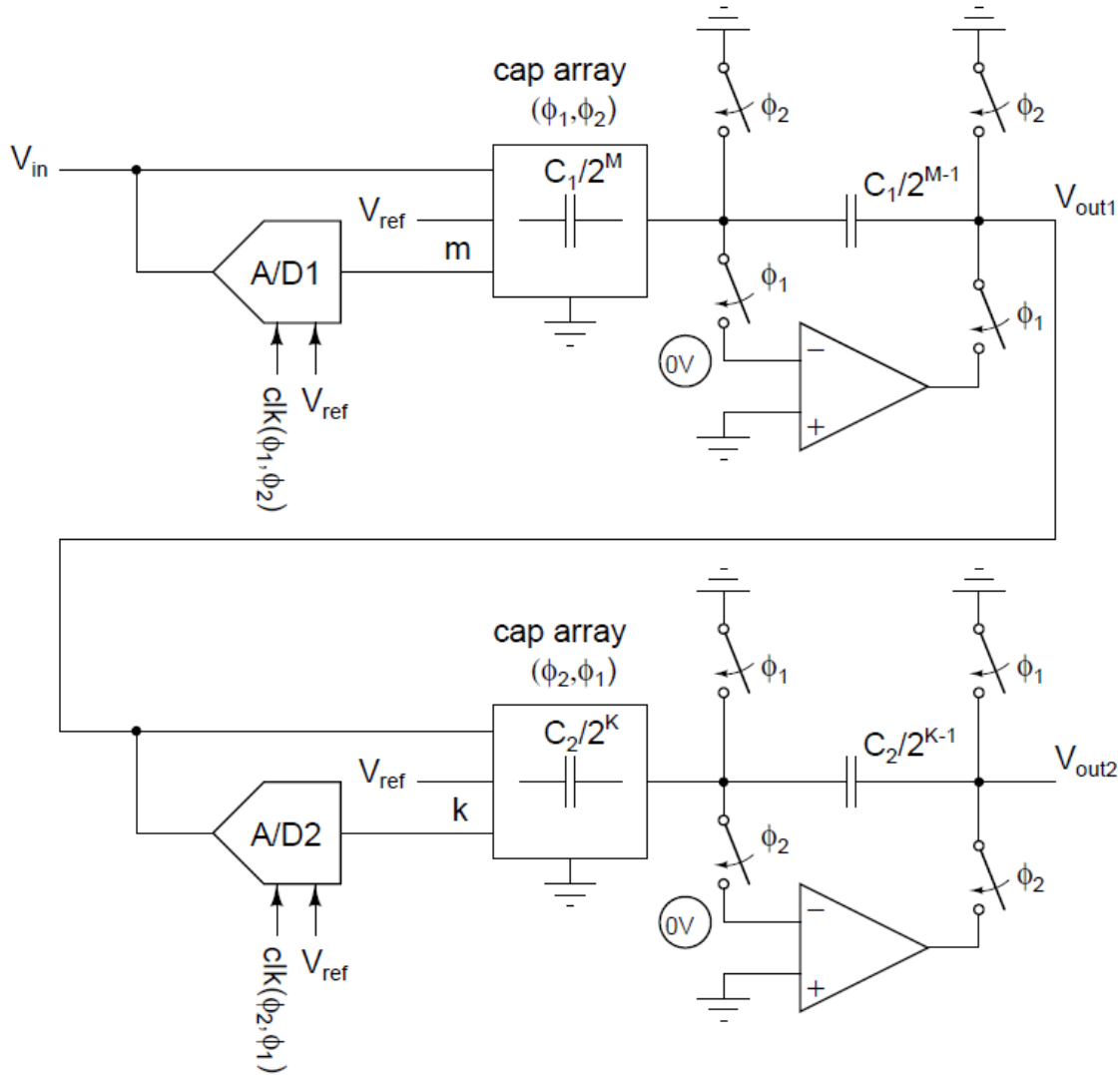

# MDAC Stages: Opamp Sharing

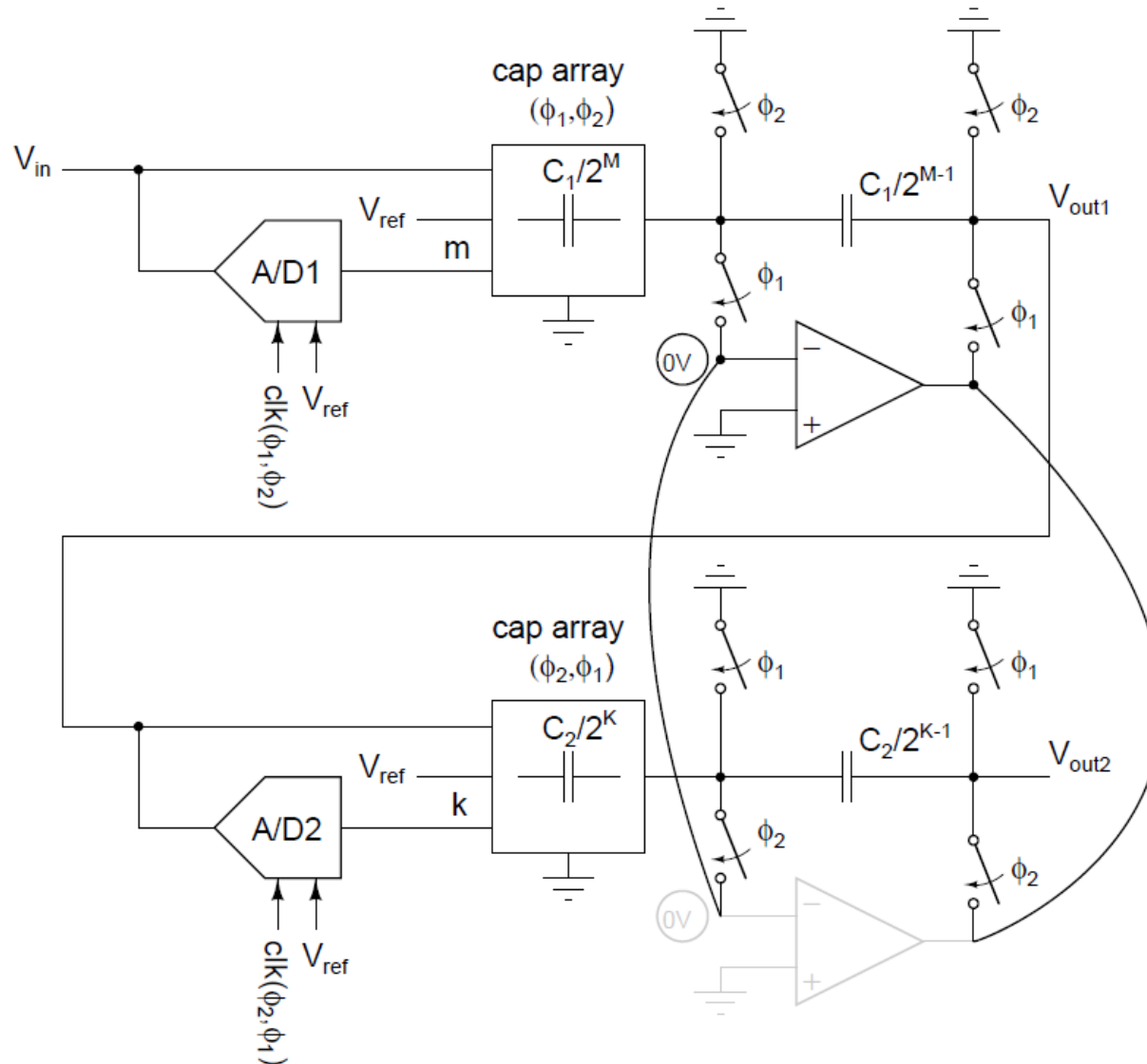



# Opamp Sharing

- ❑ First stage uses the opamp only in  $\phi_1$
- ❑ Second stage uses the opamp only in  $\phi_2$
- ❑ Use a single opamp
  - Switch it to first stage in  $\phi_1$
  - Switch it to second stage in  $\phi_2$
- ❑ Reduces power consumption
- ❑ Cannot correct for opamp offsets
- ❑ Memory effect because of charge storage at negative input of the opamp

# Opamp Sharing: Split Amp

- ❑ Alternate stages with more and fewer bits e.g. 3-1-3-1
- ❑ Optimized loading
- ❑ Use a two stage opamp for stage 1 (High gain)
- ❑ Use a single stage opamp for stage 2 (Low gain)
- ❑ Use a single two stage opamp
  - Use both stages for stage 1 of the A/D
  - Use only the second stage for stage 2 of the A/D
  - Feedback capacitor in stage 2 of the A/D appears across the second stage of the opamp—Miller compensation capacitor
- ❑ Further Reduces power consumption

# Opamp Sharing: Split Amp

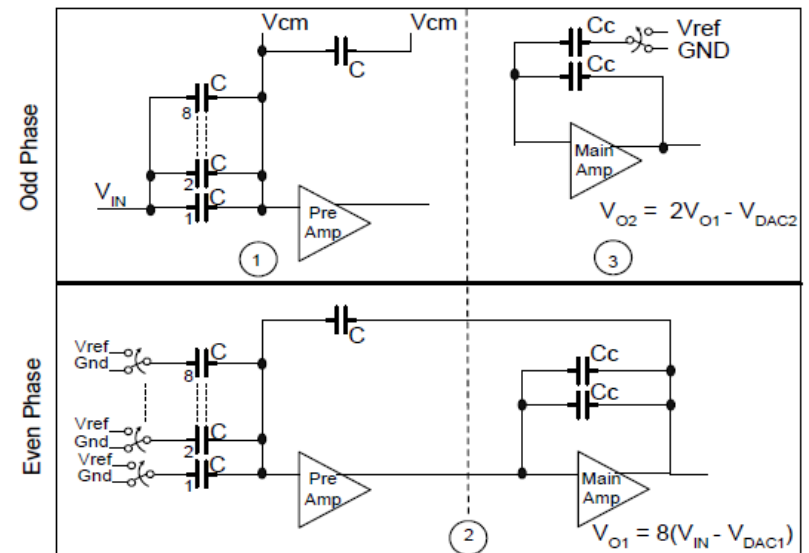 

(1)- Sampling for high bits stage. (2)- Amplify for high bits stage and sampling for low bits stage (3)- Amplify for low bits stage


## 18.4 A 30mW 12b 21MSample/s Pipelined CMOS ADC

Suhas Kulhali, Visvesvaraya Penkota, Ravishankar Asv




# Pipelined A/D Implementation

# Pipelined ADC Architecture

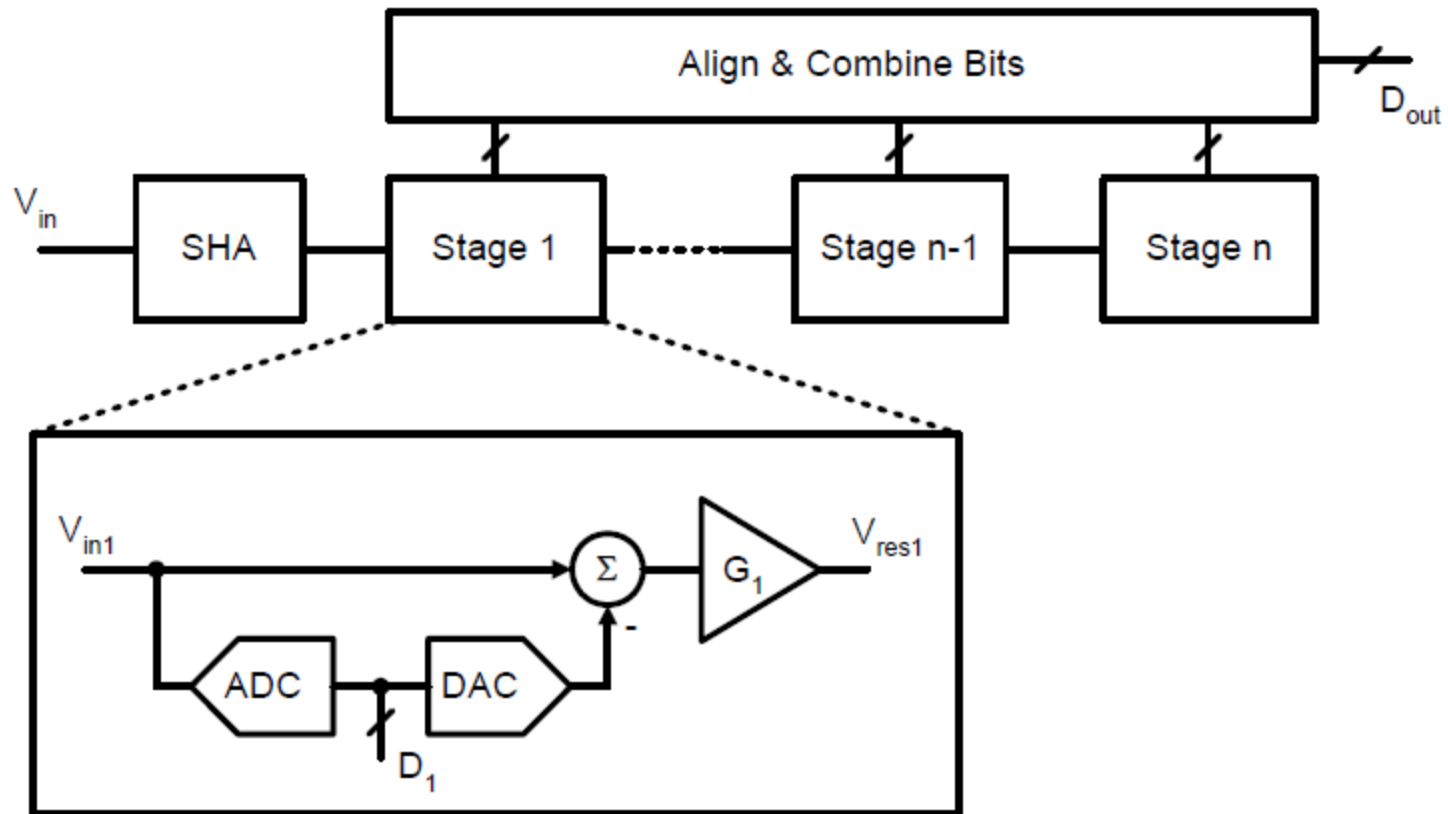


# Concurrent Stage Operation

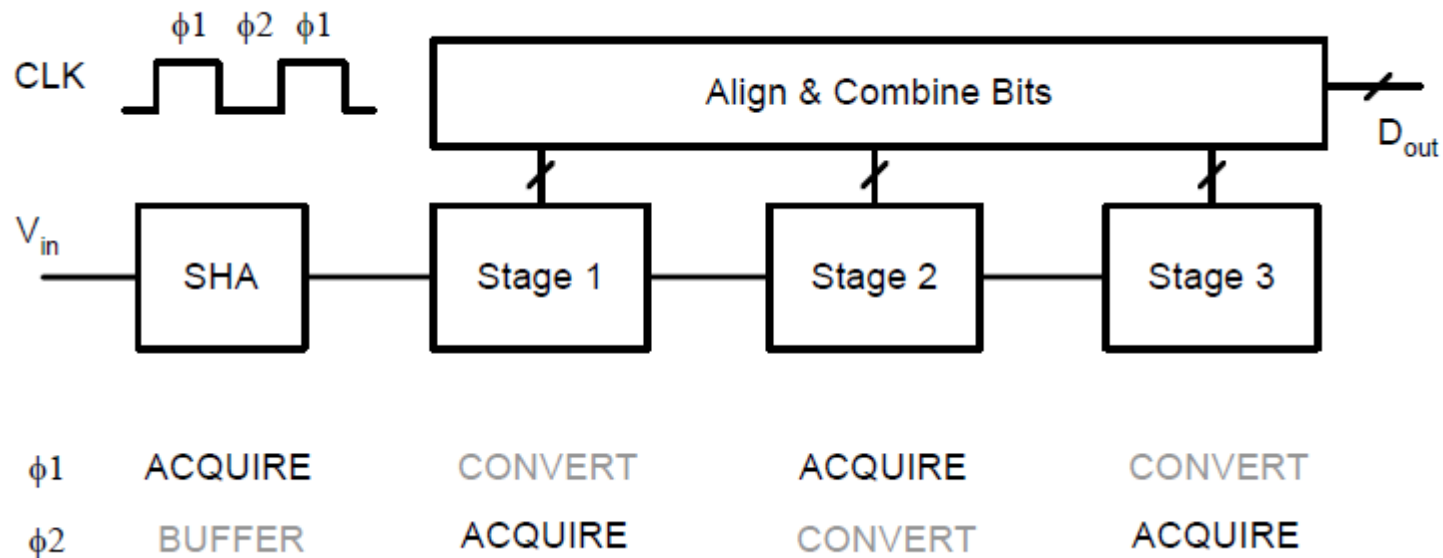


- ❑ Dedicated S/H for better dynamic performance
- ❑ Pipelined MDAC stages operate on the input and pass the scaled residue to the to the next stage
- ❑ New output every clock cycle, but each stage introduces 0.5 clock cycle latency

# Data Alignment

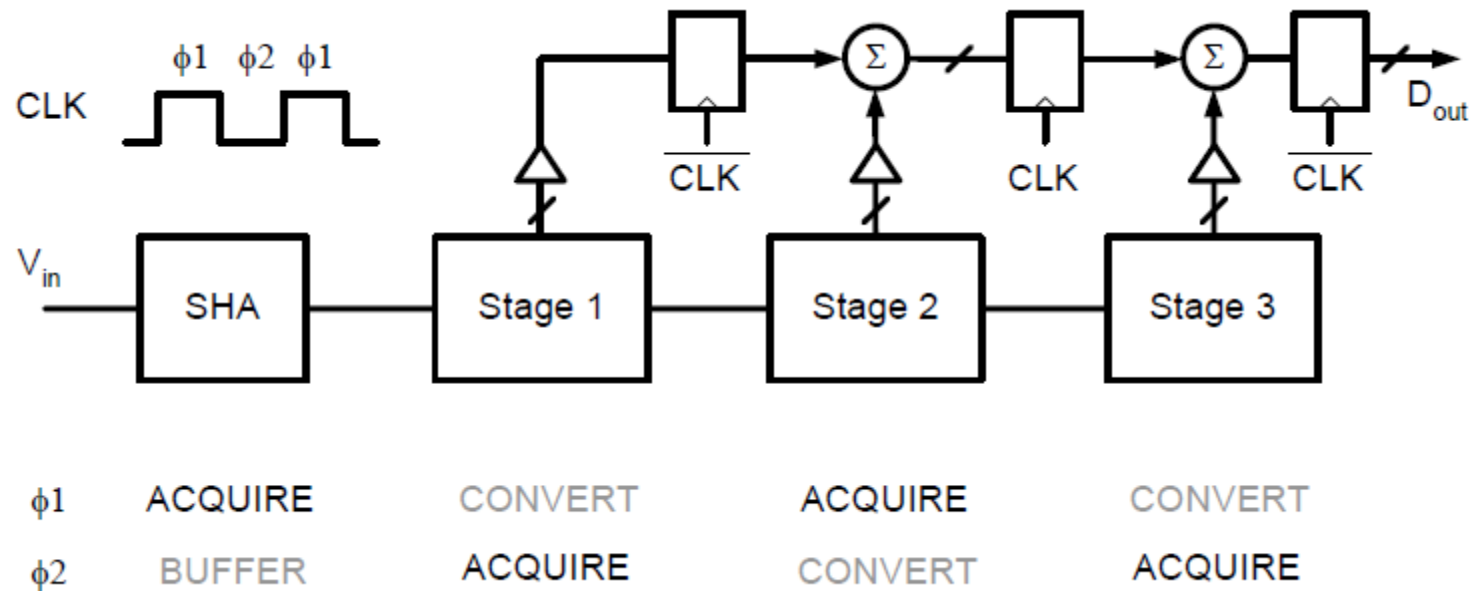

- ❑ Digital shift register aligns sub-conversion results in time
- ❑ Digital output is taken as weighted sum of stage bits


# Latency

 


[Analog Devices, AD9226 Data Sheet]

# Combining the Bits: Ideal MDAC

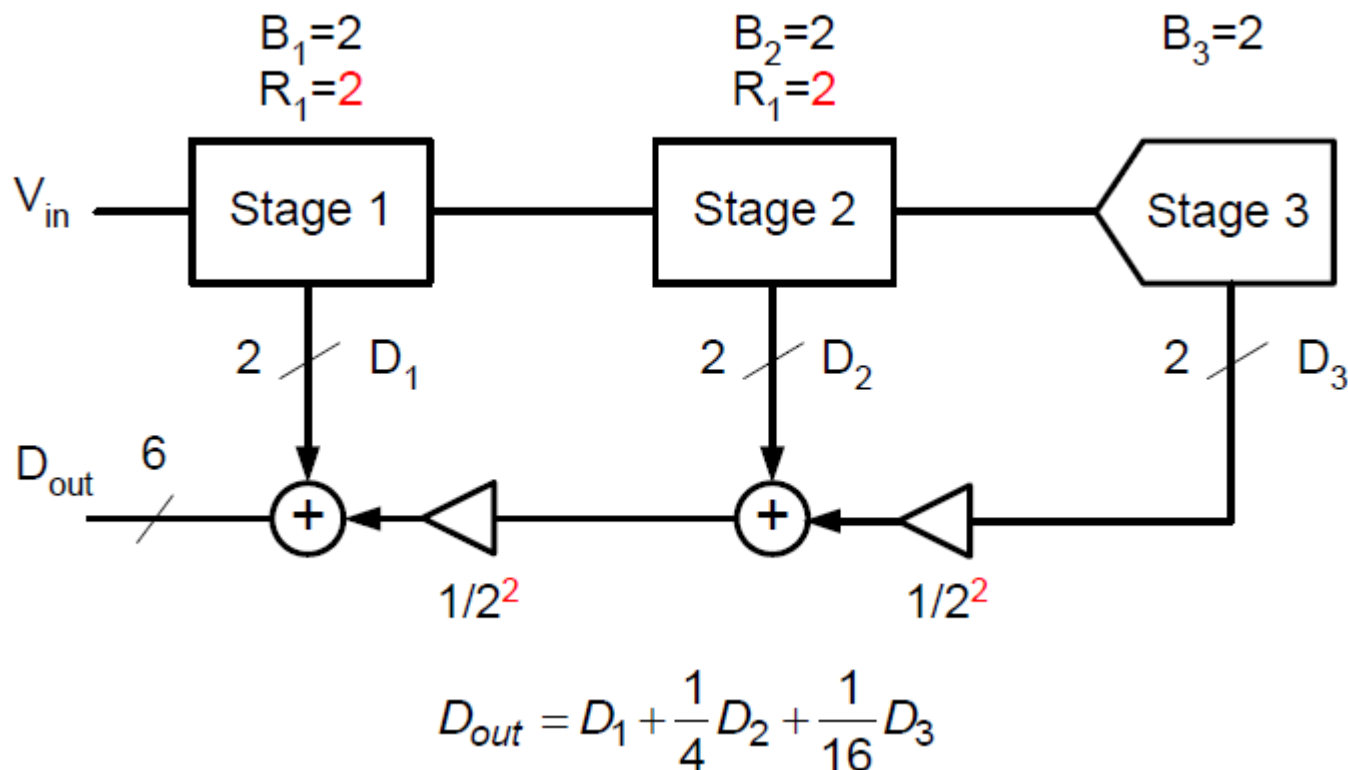- Example 1: Three 2-bit stages, no redundancy




# Combining the Bits contd.

 


# Combining the Bits: With Redundancy

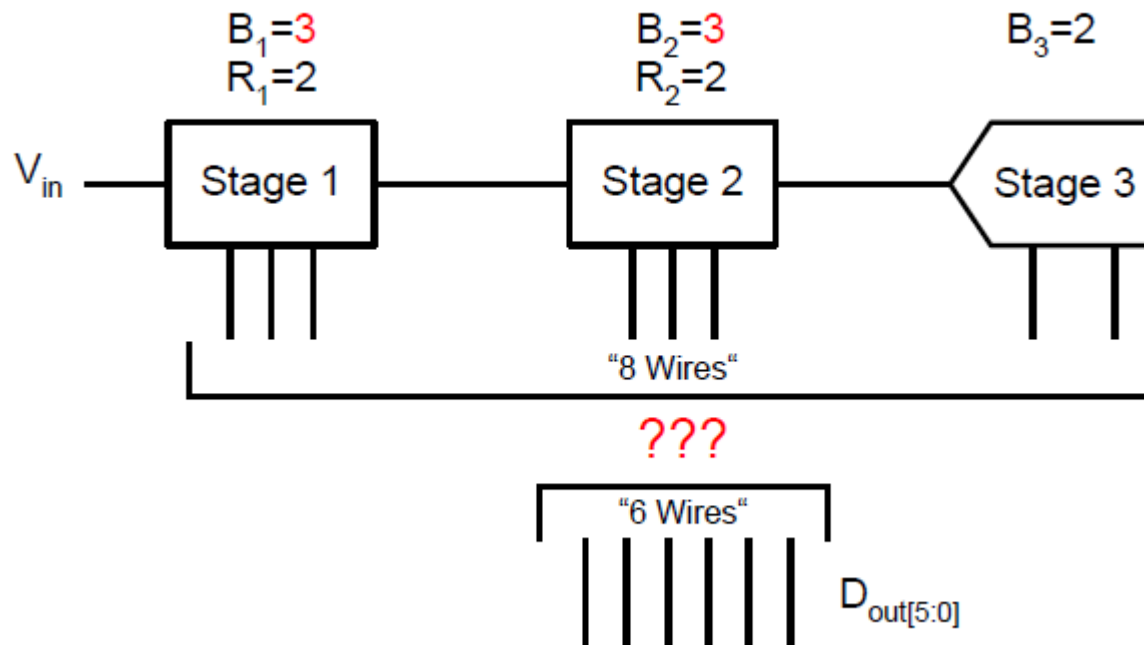- Example2: Three 2-bit stages, one bit redundancy in stages 1 and 2 (6-bit aggregate ADC resolution)







# Combining the Bits: With Redundancy

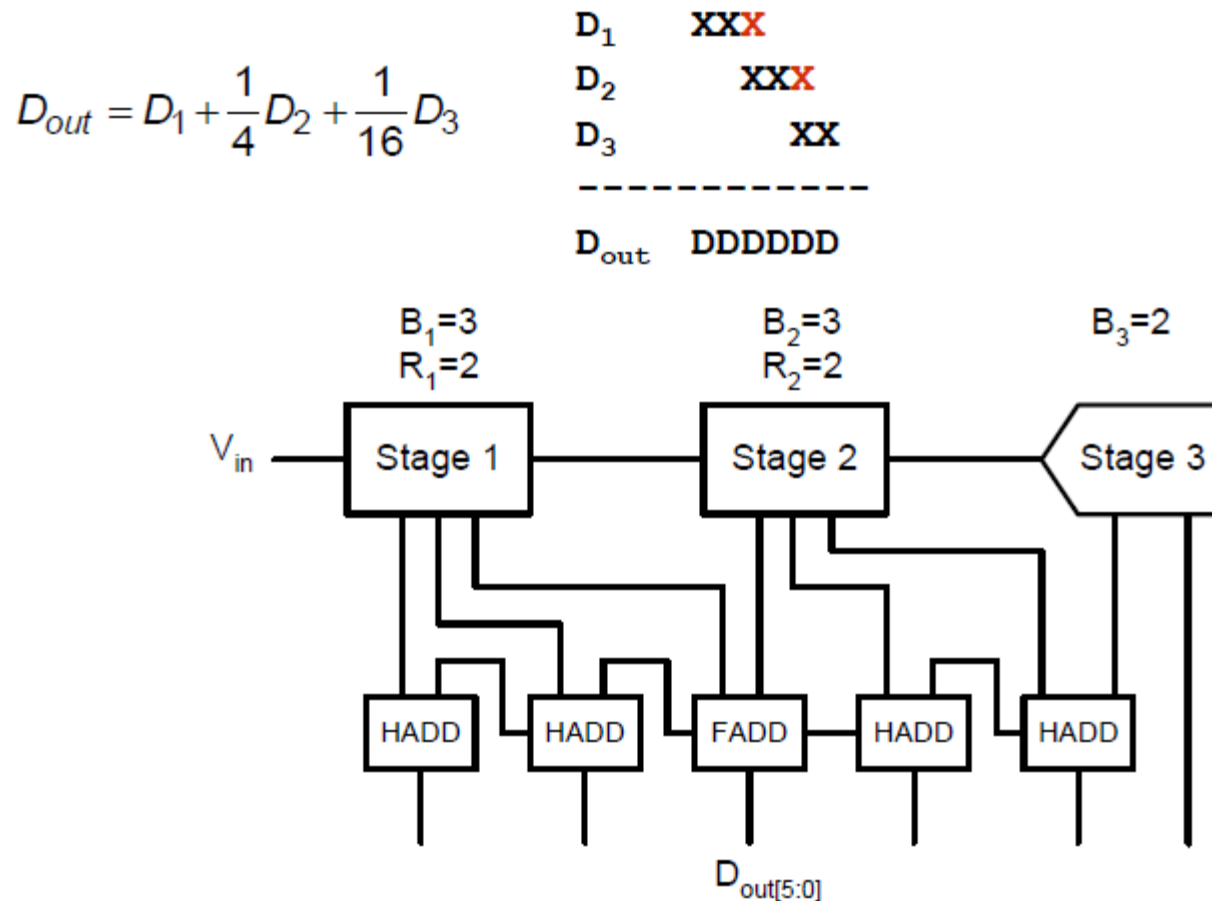


- ❑ Bits overlap by the amount of redundancy
- ❑ Need half adders for addition

# A 1.5-Bit Stage

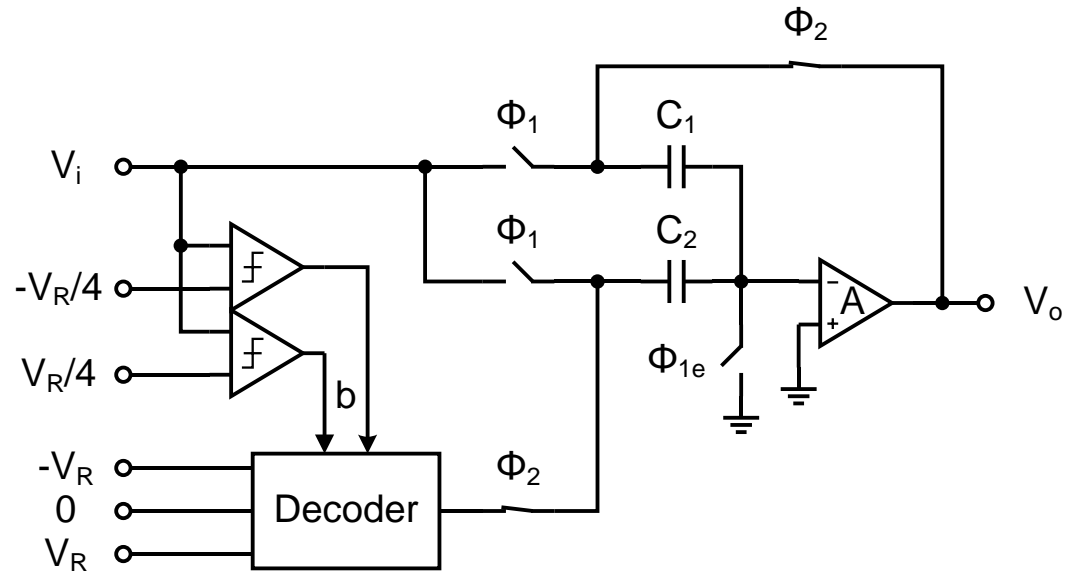 


- 2X gain + 3-level DAC + subtraction all integrated
- Digital redundancy relaxes the tolerance on CMP/RA offsets

# A 1.5-Bit Stage: Residue Plot

 

$$V_o = \begin{cases} \left(1 + \frac{C_s}{C_f}\right) V_i - \frac{C_s}{C_f} V_{ref} & \text{if } V_i > V_{ref}/4 \\ \left(1 + \frac{C_s}{C_f}\right) V_i & \text{if } -V_{ref}/4 \leq V_i \leq +V_{ref}/4 \\ \left(1 + \frac{C_s}{C_f}\right) V_i + \frac{C_s}{C_f} V_{ref} & \text{if } V_i < -V_{ref}/4 \end{cases}$$


# A 1.5-Bit Stage

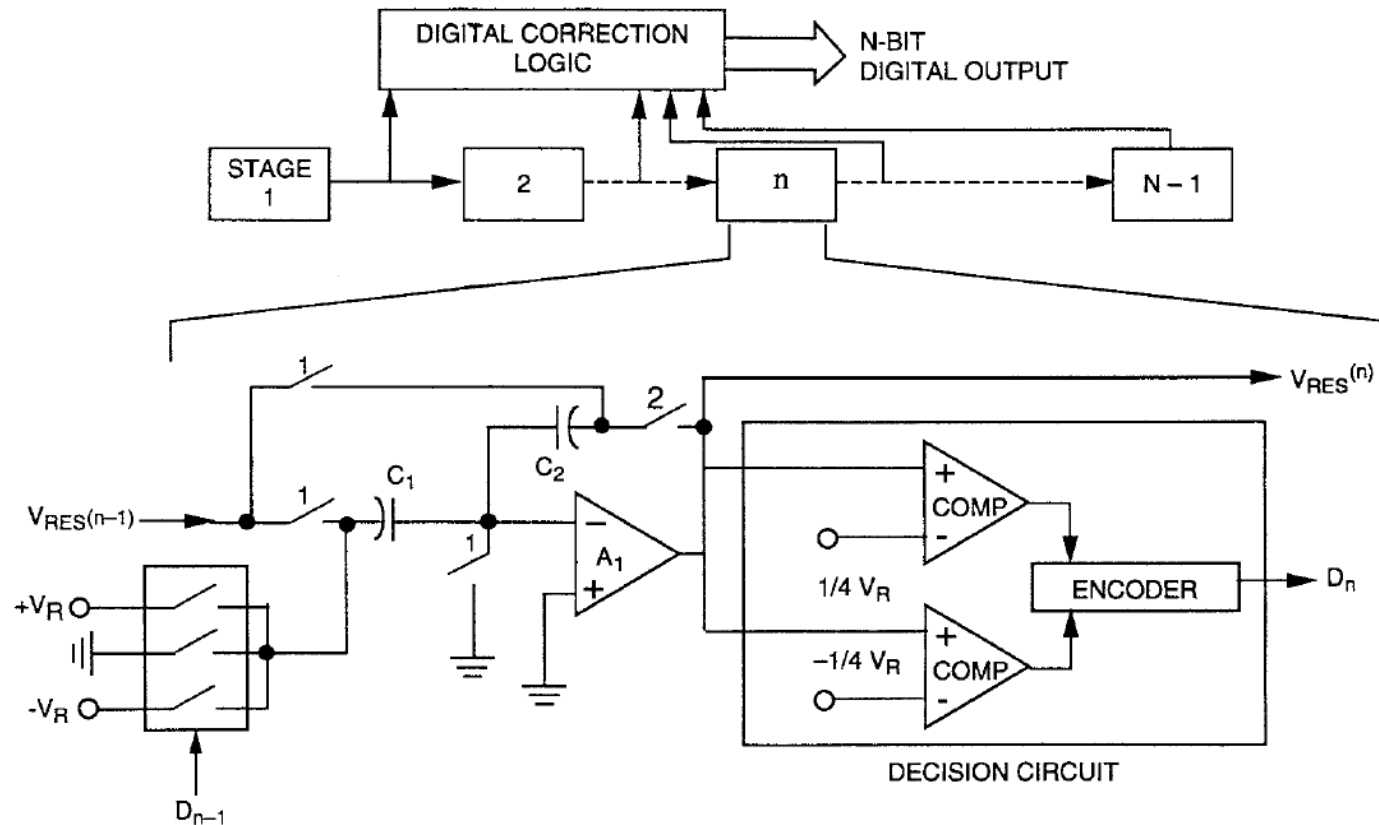

A 250-mW, 8-b, 52-Msamples/s Parallel-Pipelined A/D Converter with Reduced Number of Amplifiers

Krishnaswamy Nagaraj, *Senior Member, IEEE*, H. Scott Fetterman, Joseph



# A 1.5-Bit Stage: Opamp Sharing

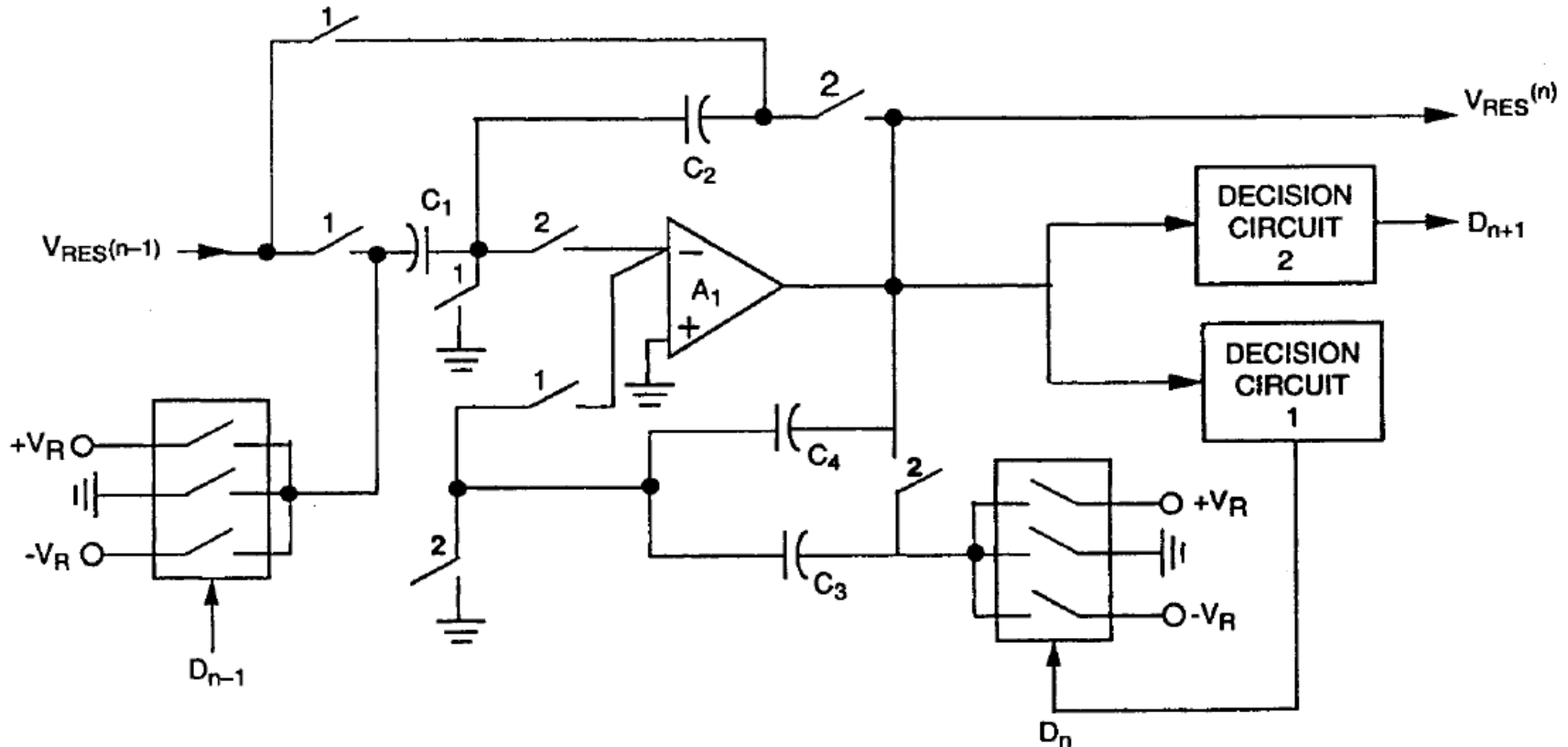


A 250-mW, 8-b, 52-Msamples/s Parallel-Pipelined A/D Converter with Reduced Number of Amplifiers

Krishnaswamy Nagaraj, *Senior Member, IEEE*, H. Scott Fetterman, Joseph

# A 1.5-Bit Stage: Opamp Sharing contd.

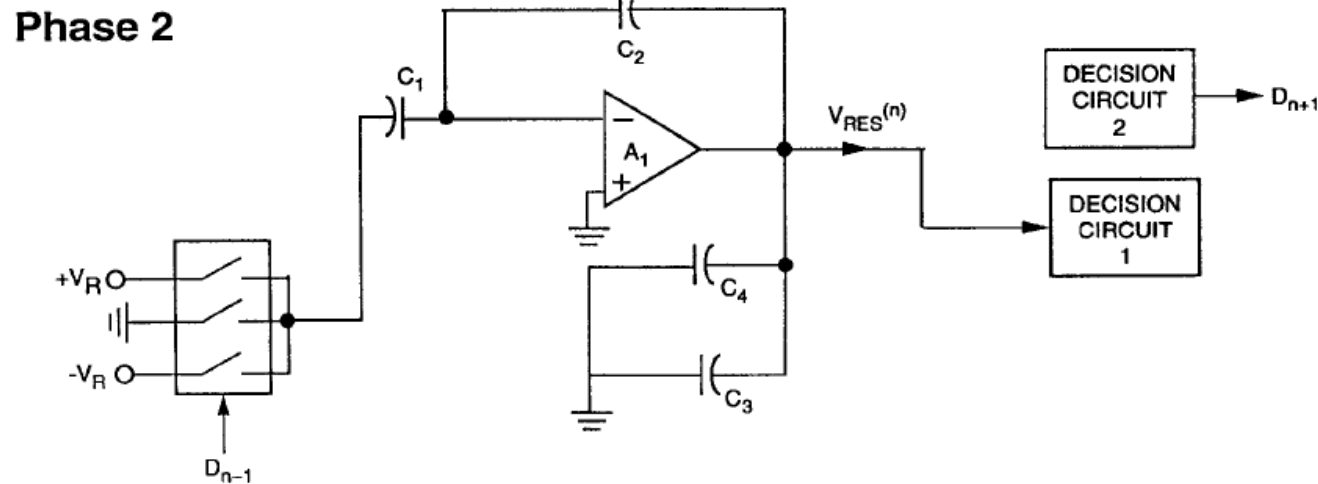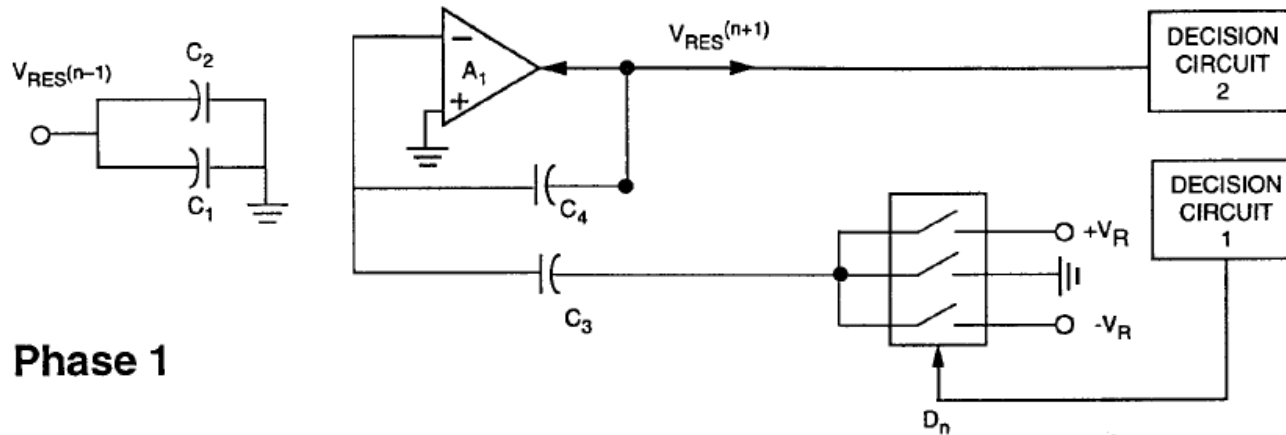


# Timing Diagram of Pipelining

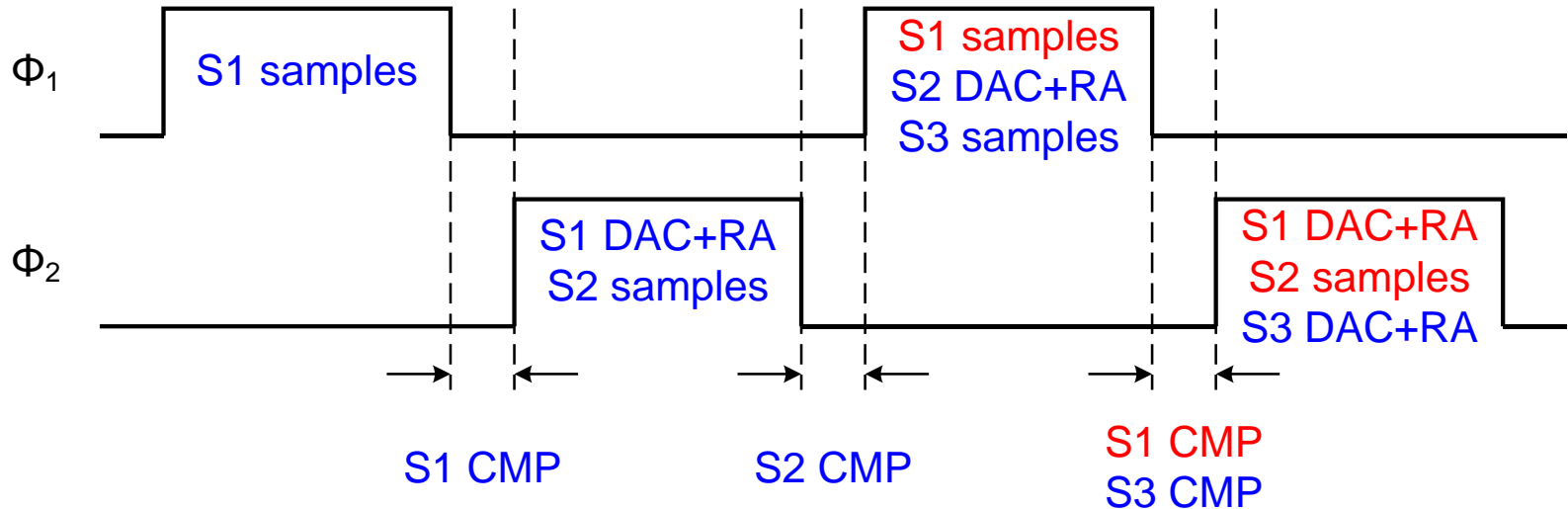

- Two-phase non-overlapping clock is typically used, with the coarse ADCs operating within the non-overlapping times
- All pipelined stages operate simultaneously, increasing throughput at the cost of latency (what is the latency of pipeline?)


# 1.5-Bit Decoding Scheme

 

$b$	0	1	2
$b-1$	-1	0	+1
$C_2$	$+V_R$	0	$-V_R$





# Stage 1 Matching Requirements

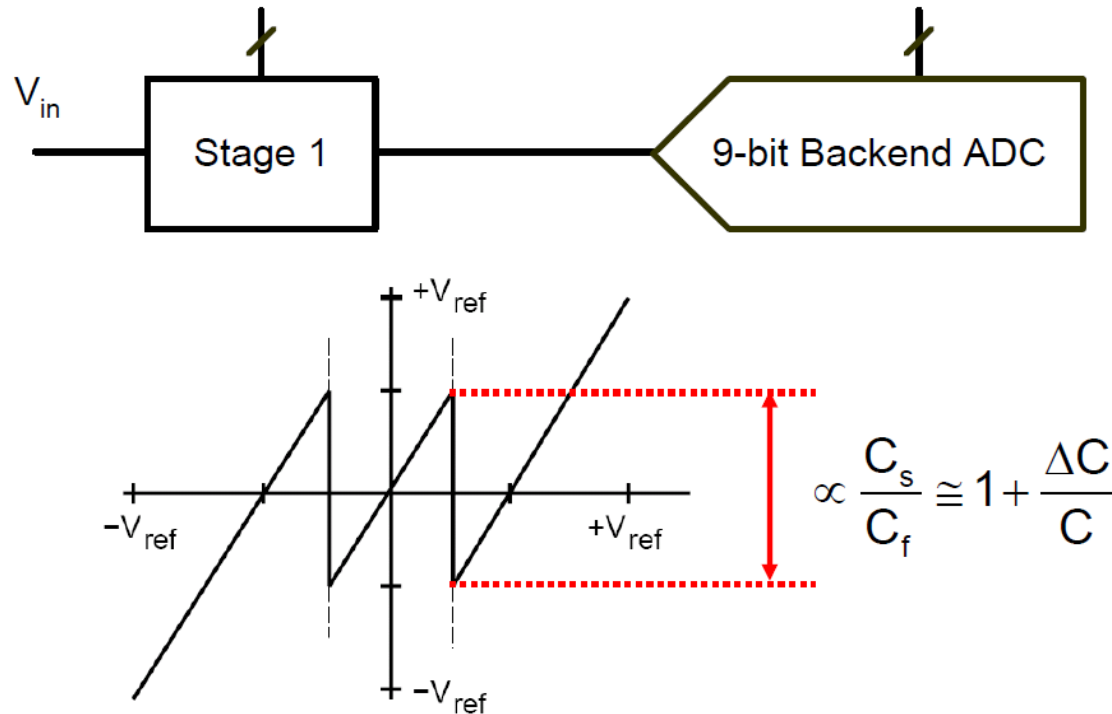

- Error in residue transition must be accurate to within a fraction of 9-bit backend LSB
  - Typically want  $\Delta C/C \sim 0.1\%$  or better

# 1.5b/stage Residues

  


- Residues after every stage with ideal MDACs


# Capacitor Matching

- ❑ 0.1% "easily" achievable in current technologies
  - Even with metal sandwich caps, see e.g. [Verma 2006]
    - Beware of metal density related issues, "copper dishing"
  - For MIMCap matching data see e.g. [Diaz 2003]
- ❑ What if we needed much higher resolution than 10 bits?
  - Digital calibration
  - Multi-bit first stage
    - Each extra bit resolved in the first stage alleviates precision requirements on residue transition by 2x
    - For fixed capacitor matching, can show that each (effective) bit moved into the first stage
      - Improves DNL by 2x
      - Improves INL by  $\sqrt{2}$ x
    - Multi-bit examples: [Singer 1996] [Kelly 2001] [Lee 2007]

# A 2.5-Bit Stage

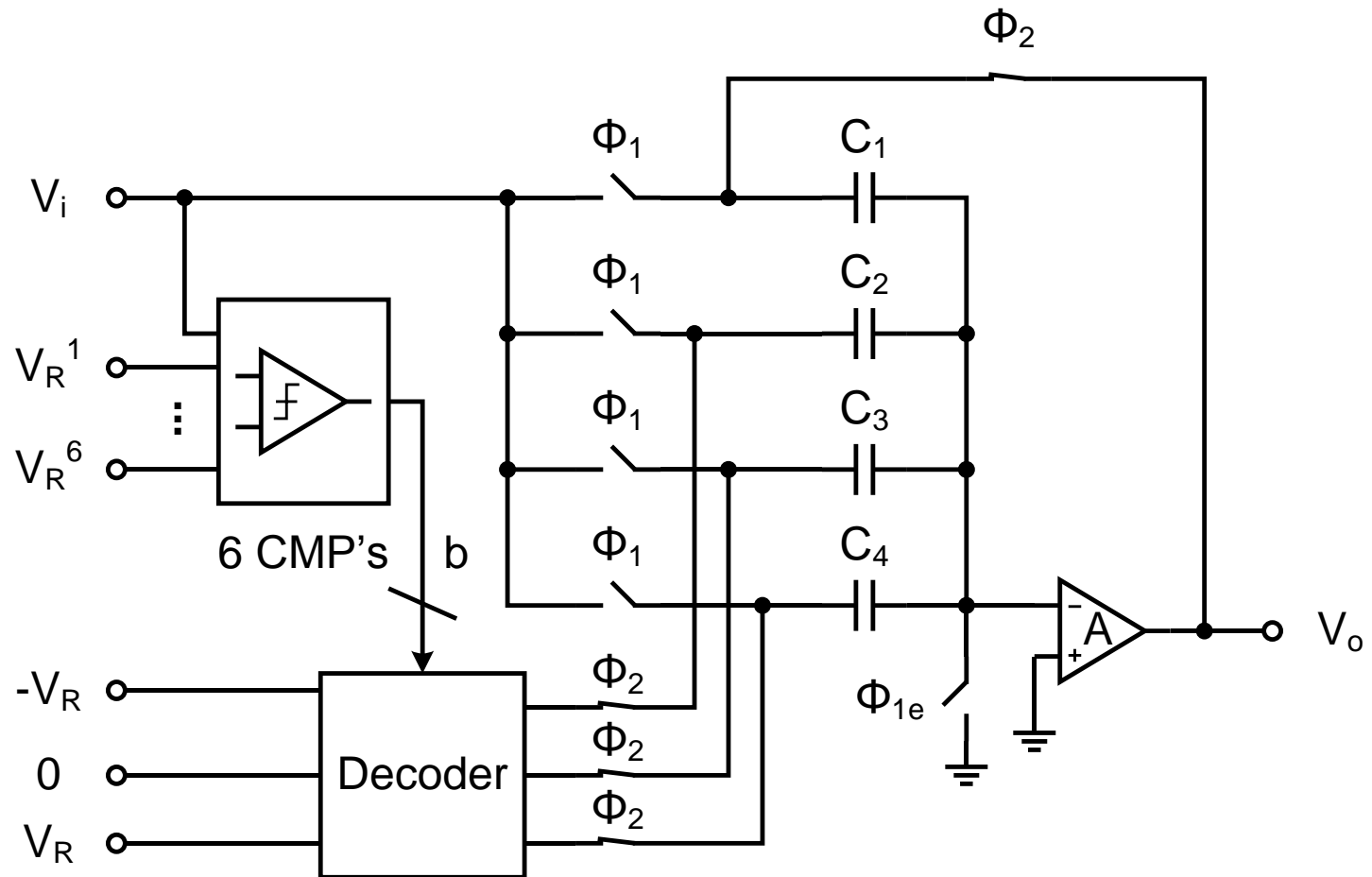

## 2.5-Bit RA Transfer Curve

 

- 6 comparators + 7-level DAC are required
- Max tolerance on comparator offset is  $\pm V_R/8$

## 2.5-Bit Decoding Scheme

b	0	1	2	3	4	5	6
b-3	-3	-2	-1	0	+1	+2	+3
b <sub>1</sub>	-1	-1	-1	0	+1	+1	+1
b <sub>2</sub>	-1	-1	0	0	0	+1	+1
b <sub>3</sub>	-1	0	0	0	0	0	+1
C <sub>2</sub>	+V <sub>R</sub>	+V <sub>R</sub>	+V <sub>R</sub>	0	-V <sub>R</sub>	-V <sub>R</sub>	-V <sub>R</sub>
C <sub>3</sub>	+V <sub>R</sub>	+V <sub>R</sub>	0	0	0	-V <sub>R</sub>	-V <sub>R</sub>
C <sub>4</sub>	+V <sub>R</sub>	0	0	0	0	0	-V <sub>R</sub>

- 7-level DAC,  $3 \times 3 \times 3 = 27$  permutations of potential configurations → multiple choices of decoding schemes!
- Choose the scheme to minimize decoding effort, balance loading for reference lines, etc.

# Design Parameters

- ❑ Stage resolution, stage scaling factor
- ❑ Stage redundancy
- ❑ Thermal noise/quantization noise ratio
- ❑ Opamp architecture
  - Opamp sharing?
- ❑ Switch topologies
- ❑ Comparator architecture
- ❑ Front-end SHA vs. SHA-less design
- ❑ Calibration approach (if needed)
- ❑ Time interleaving?
- ❑ Technology and technology options (e.g. capacitors)

A very complex optimization problem!


# Thermal Noise Considerations

- ❑ Total input referred noise
  - Thermal noise + Quantization noise
  - Costly to make input thermal noise smaller than quantization noise
- ❑ Example:  $V_{FS}=1V$ , 10-bit ADC
  - $E_q = \frac{V_{LSB}^2}{12} = \frac{1}{12} \left( \frac{1}{2^{10}} \right)^2 = (280 \mu V_{rms})^2$
  - Design for total input referred thermal noise  $280 \mu V_{rms}$  or larger is SNR target allows
- ❑ Total input referred thermal noise of the ADC is the sum of thermal noise contribution from all stages
  - How should the thermal noise (kT/C) of the stages be distributed?



# Stage Scaling

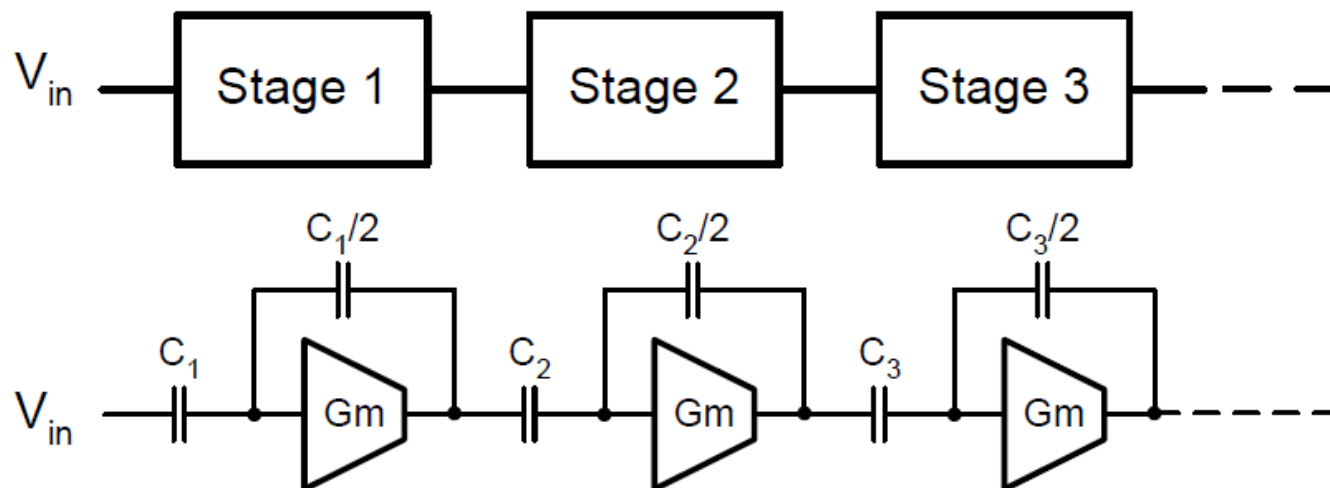
- Example: Pipeline using 1-bit (effective) stages ( $G=2$ )



- Total input referred noise power

$$N_{\text{tot}} \propto kT \left[ \frac{1}{C_1} + \frac{1}{4C_2} + \frac{1}{16C_3} + \dots \right]$$

# Stage Scaling contd.

 


$$N_{tot} \propto kT \left[ \frac{1}{C_1} + \frac{1}{4C_2} + \frac{1}{16C_3} + \dots \right]$$

If we make all caps the same size, backend stages contribute very little noise

- Wasteful, because Power  $\sim G_m \sim C$

# Stage Scaling contd.


 


$$N_{tot} \propto kT \left[ \frac{1}{C_1} + \frac{1}{4C_2} + \frac{1}{16C_3} + \dots \right]$$



- How about scaling caps down by  $2^M=4X$  every stage?
  - Same amount of noise from each stage
  - All stages contribute significant noise
  - Noise from the first stage must be reduced
  - Power  $\sim G_m$  and  $C$  goes up!

# Stage Scaling contd.

## Extreme 1: All Stages the Same Size

  

## Extreme 2: All Stages Contribute the Same Noise

  


[Cline 1996]



- Optimum capacitor scaling lies approximately midway between these two extremes

# Stage Scaling contd.

Extreme 1: All Stages the Same Size

 

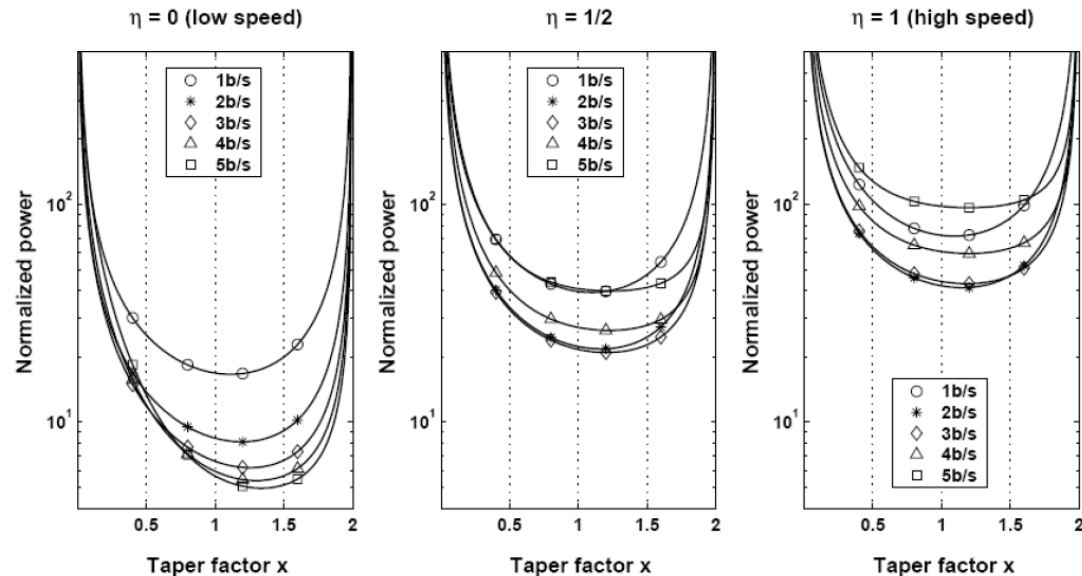 
Extreme 2: All Stages Contribute the Same Noise



- Optimum capacitor scaling lies approximately midway between these two extremes [Cline 1996]
- Capacitor scaling factor  $2^{RX}$ 
  - $x=1 \rightarrow$  scaling exactly by the stage gain [Chiu 2004]
 
# Optimum Stage Scaling

- Start by assuming caps are scaled precisely by stage gain
  - E.g. for 1-bit effective stages, caps are scaled by 2




- Refine using first pass circuit information & Excel spreadsheet
  - Use estimates of OTA power, parasitics, minimum feasible sampling capacitance etc.
  - Can develop optimization subroutines in MATLAB

# How Many Bits per Stage?

- ❑ Low per-stage resolution (e.g. 1-bit effective)
  - – Need many stages
  - + OTAs have small closed loop gain, large feedback factor
    - High speed
- ❑ High per-stage resolution (e.g. 3-bit effective)
  - + Fewer stages
  - – OTAs can be power hungry, especially at high speed
  - – Significant loading from flash-ADC
- ❑ Qualitative conclusion
  - Use low per-stage resolution for very high speed designs
  - Try higher resolution stages when power efficiency is most important constraint

# Power Tradeoff with Stage Resolution

 

$\eta$  = parasitic cap at output/total sampling cap in each stage (junctions, wires, switches, ...)

- ❑ Power tradeoff is nearly flat!
- ❑ ADC power varies only ~2X across different stage resolutions



# Examples

Reference	[Yoshioka, 2007]	[Jeon, 2007]	[Loloe 2002]	[Bogner 2006]
Technology	90nm	90nm	0.18um	0.13um
Bits	10	10	12	14
Bits/Stage	1-1-1-1-1-1-1-3	2-2-2-4	1-1-1-1-1-1-1-1-1-1-2	3-3-2-2-4
SNDR [dB]	~56	~54	~65	~64
Speed [MS/s]	80	30	80	100
Power [mW]	13.3	4.7	260	224
mW/MS/s	0.17	0.16	3.25	2.24




- Low power is possible for a wide range of architectures!

# Cap Sizing Recap

- ❑ Choosing the "optimum" per-stage resolution and stage scaling scheme is a non-trivial task
  - –But – optima are shallow!
- ❑ Quality of transistor level design and optimization is at least as important (if not more important than) architectural optimization...
- ❑ Next, look at circuit design details
  - Assume we're trying to build a 10-bit pipeline
    - ~0.13um CMOS or smaller
    - Moderate to high-speed ~100MS/s
    - 1-bit effective/stage, using "1.5-bit" stage topology
    - Dedicated front-end SHA

  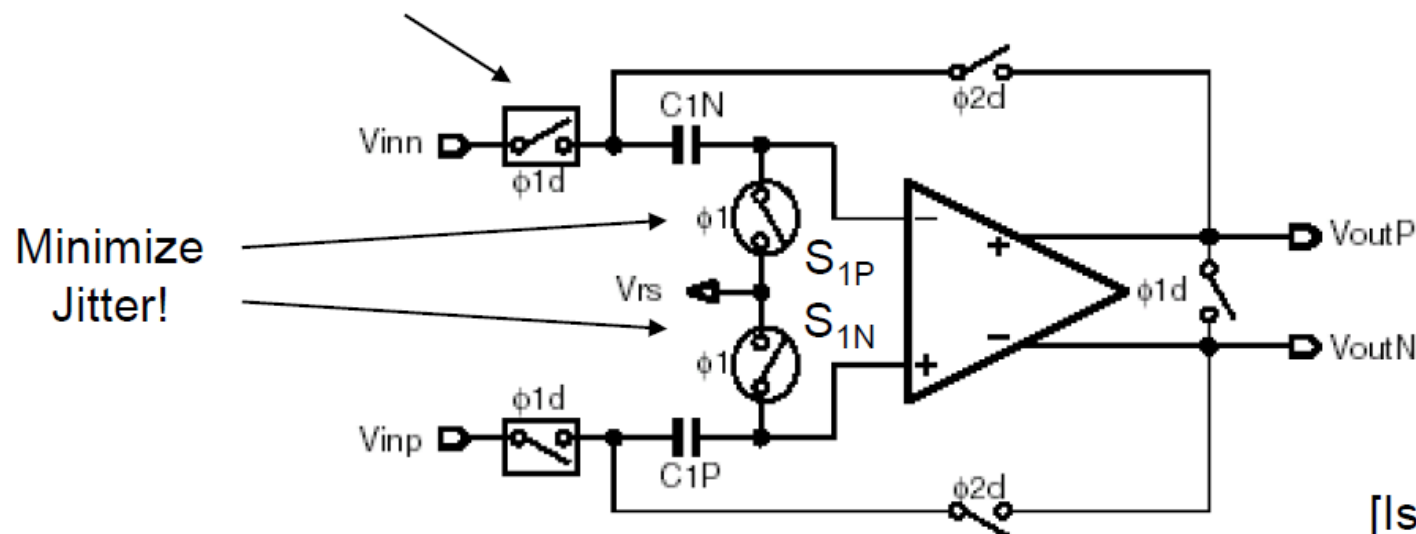
# Front-End SHA

Need constant  $R_{ON}$  here to minimize signal dependent charge injection from  $S_{1N}$ ,  $S_{1P}$



# SHA-less Architectures

- ❑ Motivation
  - SHA can burn up to 1/3 of total ADC power
- ❑ Removing front-end SHA creates acquisition timing mismatch issue between first stage MDAC & Flash

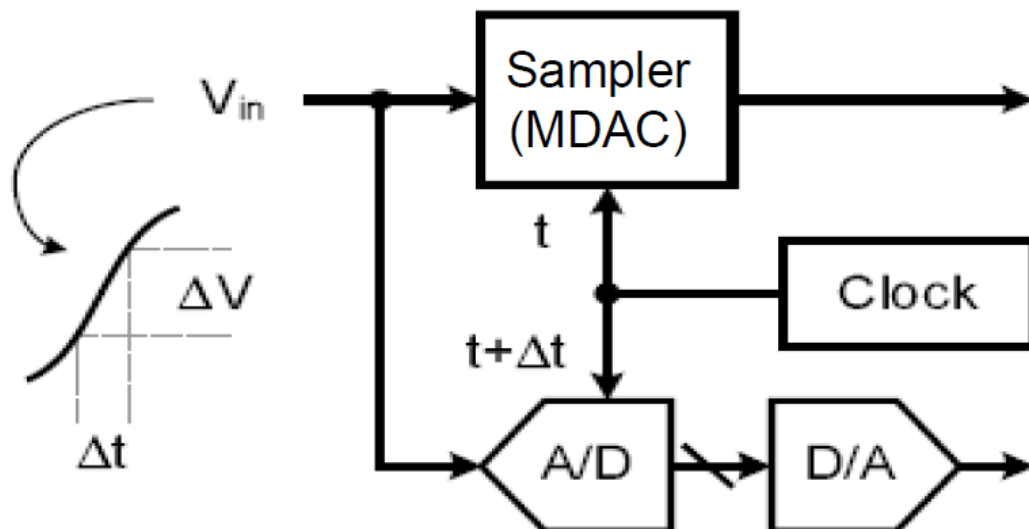


[Chiu 2004]

# SHA-less Architectures contd.

## ❑ Strategies

- Use first stage with large redundancy; this can help absorb fairly large skew errors
- Try to match sampling sub-ADC/MDAC networks
  - Bandwidth and clock timing

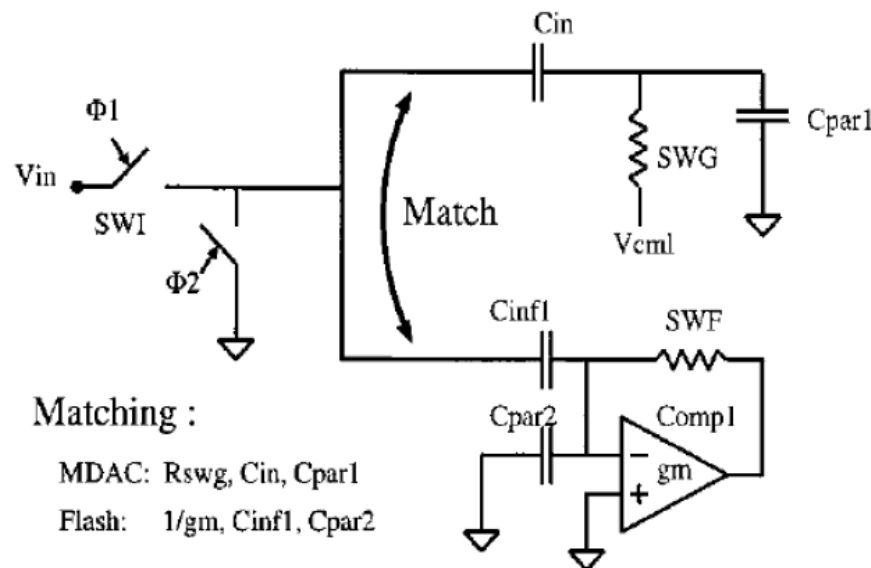


[Mehr 2000]


# Pipelined A/D Conversion Errors
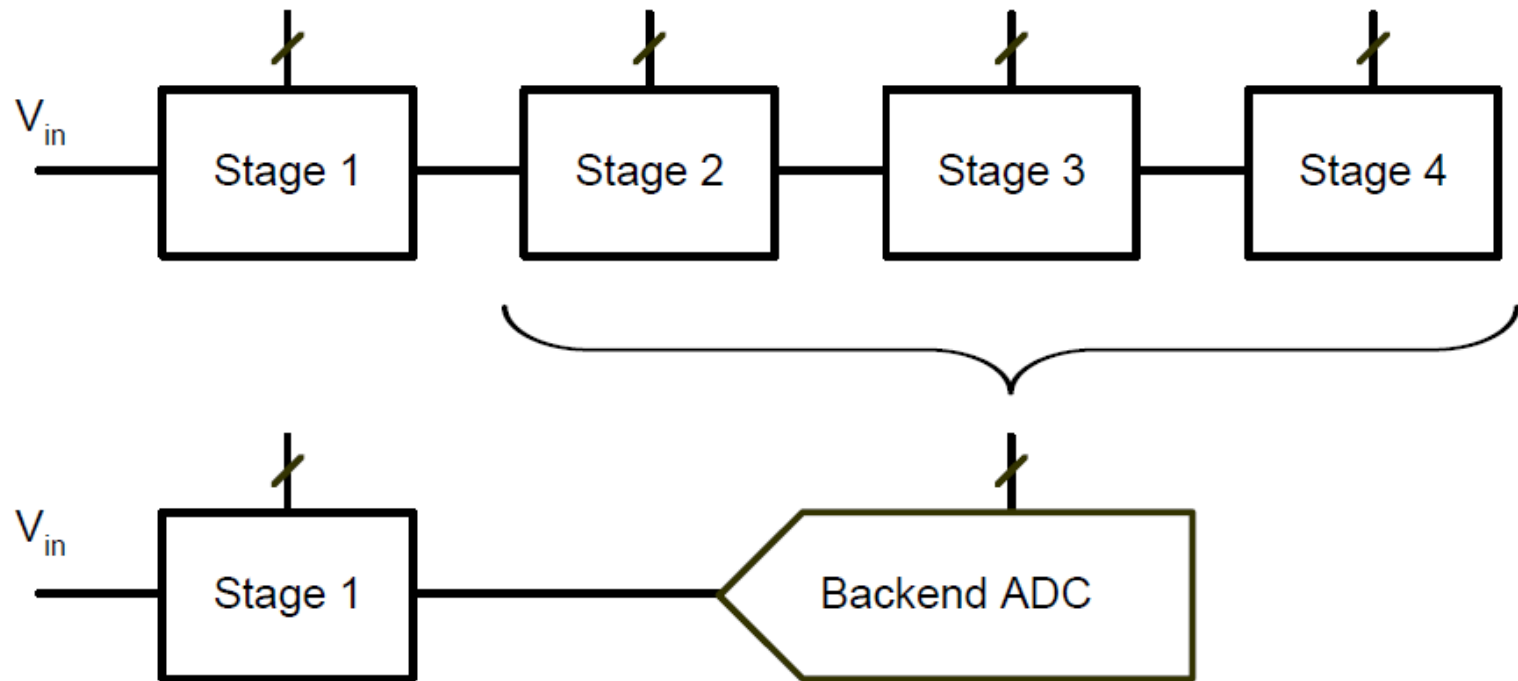
# Pipeline Decomposition

- Often convenient to look at pipeline as single stage plus backend ADC



# Resulting Model

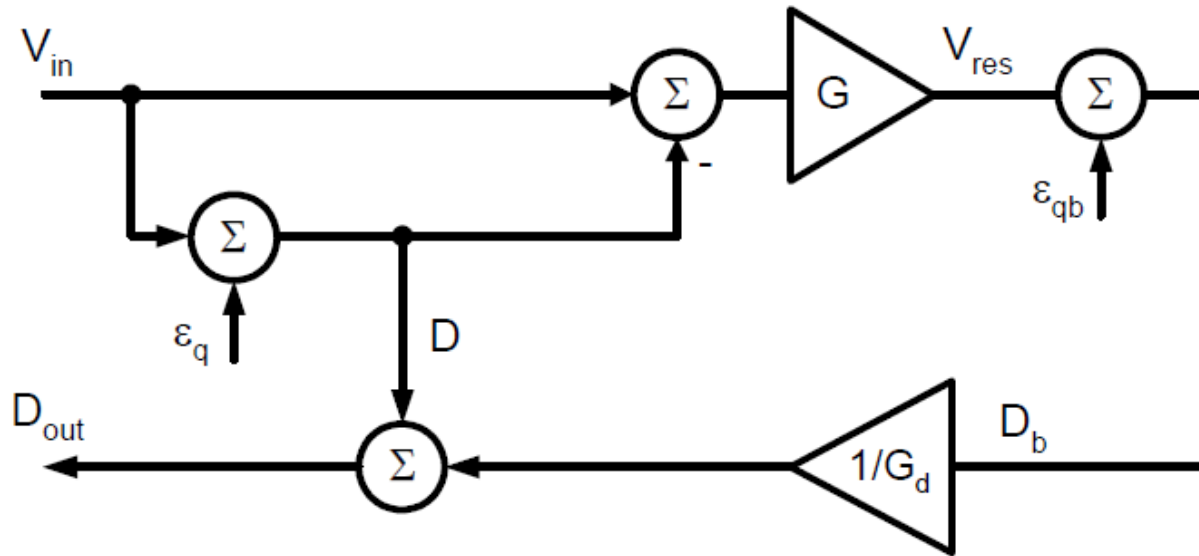


$$D_{out} = V_{in} + \epsilon_q \left( 1 - \frac{G}{G_d} \right) + \frac{\epsilon_{qb}}{G_d}$$

With  $G_d = G$



# Canonical Extension

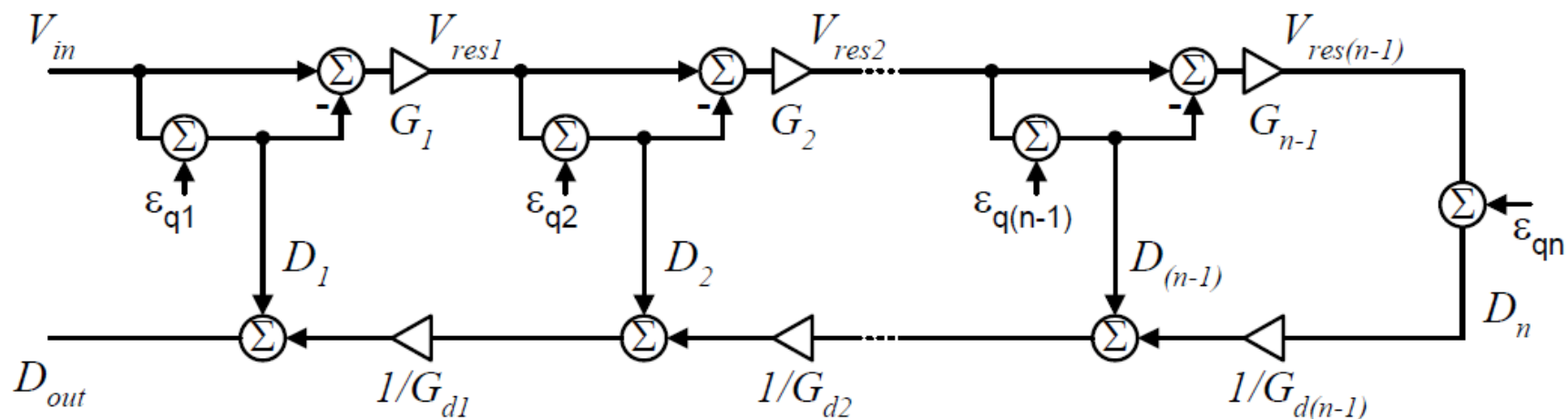

$$D_{out} = V_{in} + \epsilon_{q1} \left( 1 - \frac{G_1}{G_{d1}} \right) + \frac{\epsilon_{q2}}{G_{d1}} \left( 1 - \frac{G_2}{G_{d2}} \right) + \dots + \frac{\epsilon_{q(n-1)}}{\prod_{j=1}^{n-2} G_{dj}} \left( 1 - \frac{G_{(n-1)}}{G_{d(n-1)}} \right) + \frac{\epsilon_{qn}}{\prod_{j=1}^{n-1} G_{dj}}$$

- First stage has most stringent precision requirements
- Note that above model assumes that all stages use same reference voltage (same full scale range)
  - This is true for most designs, one exception is [Limotyrakis 2005]


# General Result – Ideal Pipeline ADC

- With ideal DACs and ideal digital weights ( $G_{dj}=G_j$ )

$$D_{out} = V_{in} + \frac{\varepsilon_{qn}}{\prod_{j=1}^{n-1} G_j} \quad \Rightarrow \quad B_{ADC} = B_n + \sum_{j=1}^{n-1} \log_2 G_j$$

- The only error in  $D_{out}$  is that of last quantizer, divided by aggregate gain
- Aggregate ADC resolution is independent of sub-ADC resolutions in stage 1...n-1 (!)
- Makes sense to define "effective" resolution of  $j^{th}$  stage as  $R_j = \log_2(G_j)$

# Gain Errors

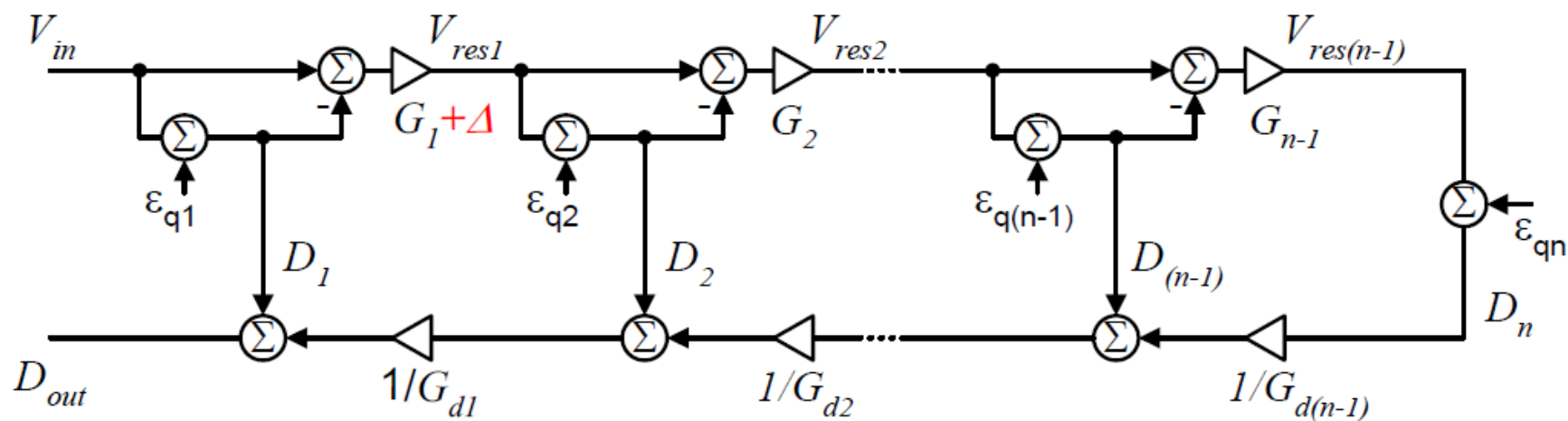



$$D_{out} = V_{in} + \epsilon_{q1} \left( 1 - \frac{G_1 + \Delta}{G_{d1}} \right) + \dots + \frac{\epsilon_{qn}}{\prod_{j=1}^{n-1} G_{dj}}$$

- Want to make  $G_{d1} = G_1 + \Delta$


# Digital Gain Calibration (1)

- Error in analog gain is not a problem as long as "digital gain term" is adjusted appropriately
- Problem
  - Need to measure analog gain precisely
- Example
  - Digital calibration of a 1-bit first stage with 1-bit redundancy ( $R=1$ ,  $B=2$ )
- Note
  - Even if all  $G_{dj}$  are perfectly adjusted to reflect the analog gains, the ADC will have non-zero DNL and INL, bounded by  $\pm 0.5\text{LSB}$ . This can be explained by the fact that the residue transitions may not correspond to integer multiples of the backend-LSB. This can cause non-uniformity in the ADC transfer function (DNL, INL) and also non-monotonicity (see [Markus, 2005]).
  - In case this cannot be tolerated
    - Add redundant bits to ADC backend (after combining all bits, final result can be truncated back)
    - Calibrate analog gain terms

# Digital Gain Calibration (2)

 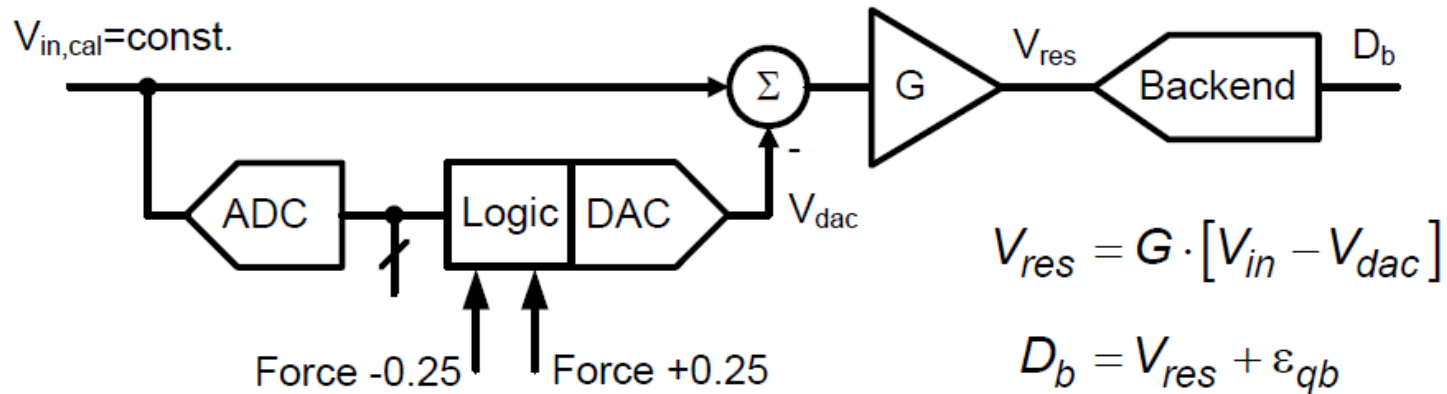


# Digital Gain Calibration (3)

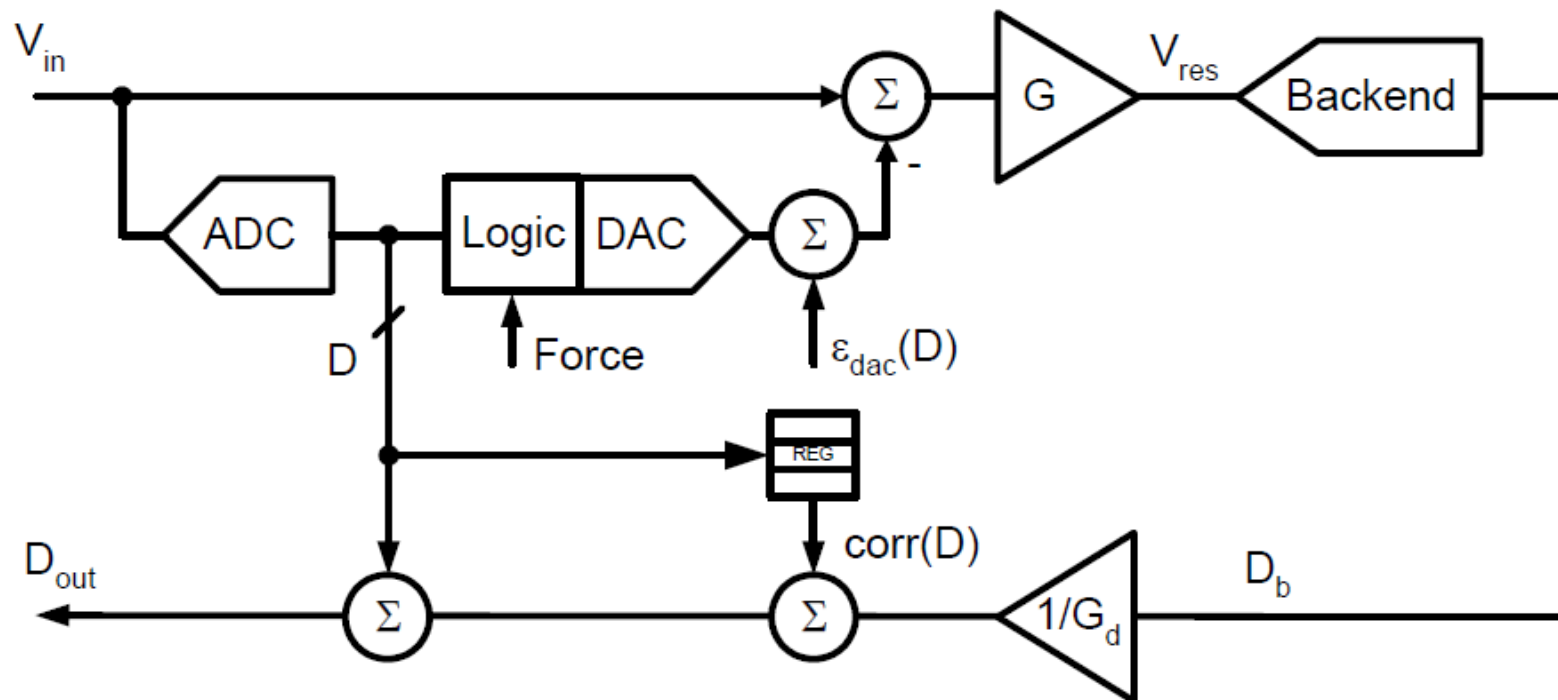

- Essentially same concept as gain calibration
  - Step through DAC codes and use backend to measure errors
- Store coefficients for each DAC transition in a look-up table

# Recursive Stage Calibration

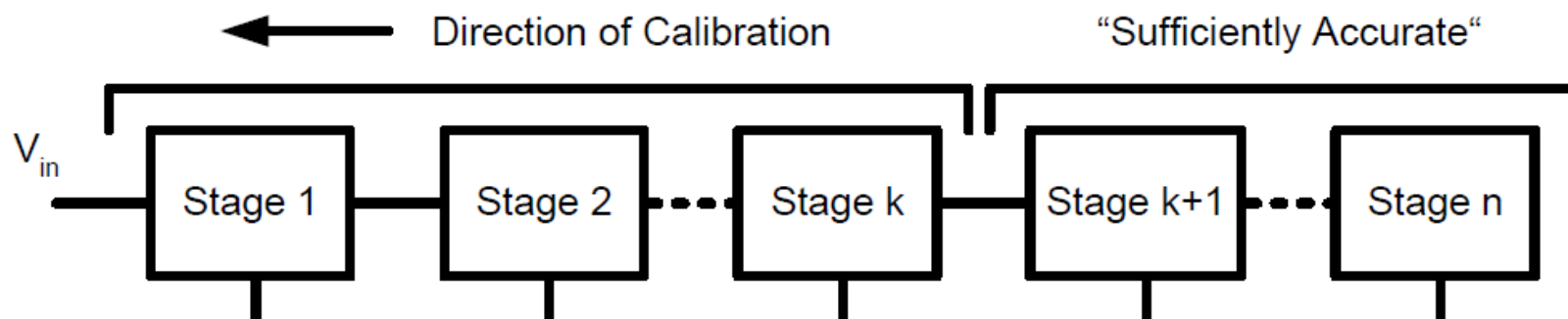

- First few stages have most stringent accuracy requirements
  - Errors of later stages are attenuated by aggregate gain
- Commonly used algorithm [Karanicolas 1993]
  - Take ADC offline
  - Measure least significant stage that needs calibration first
  - Move to next significant stage and continue toward stage 1

# References

1. Rudy van de Plassche, "CMOS Integrated Analog-to-Digital and Digital-to-Analog Converters," 2<sup>nd</sup> Ed., Springer, 2005.
2. M. Gustavsson, J. Wikner, N. Tan, *CMOS Data Converters for Communications*, Kluwer Academic Publishers, 2000.
3. N. Krishnapura, *Pipelined Analog to Digital Converters Slides*, IIT Madras, 2009.
4. Y. Chiu, *Data Converters Lecture Slides*, UT Dallas 2012.
5. B. Boser, *Analog-Digital Interface Circuits Lecture Slides*, UC Berkeley 2011.
6. K. Nagaraj et al., "A 250-mW, 8-b, 52-Msamples/s parallel-pipelined A/D converter with reduced number of amplifiers", *IEEE Journal of Solid-State Circuits*, pp. 312-320, vol. 32, no. 3, March 1997.
7. S. Kulhalli et al., "A 30mW 12b 21MSample/s pipelined CMOS ADC", *2002 IEEE International Solid State Conference*, pp. 18.4, vol. I, pp. 248-249, 492, vol. II.
8. N. Sasidhar et al., "A Low Power Pipelined ADC Using Capacitor and Opamp Sharing Technique With a Scheme to Cancel the Effect of Signal Dependent Kickback", *IEEE Journal of Solid State Conference*, pp. 2392-2401, vol. 44, no. 9, Sep 2009.



# References

## ❑ Implementation

- T. Cho, "Low-Power Low-Voltage Analog-to-Digital Conversion Techniques using Pipelined Architectures, PhD Dissertation, UC Berkeley, 1995, <http://kabuki.eecs.berkeley.edu/~tcho/Thesis1.pdf>.
- L. A. Singer et al., "A 14-bit 10-MHz calibration-free CMOS pipelined A/D converter," VLSI Circuit Symposium, pp. 94-95, Jun. 1996.
- A. Abo, "Design for Reliability of Low-voltage, Switched-capacitor Circuits," PhD Dissertation, UC Berkeley, 1999, <http://kabuki.eecs.berkeley.edu/~abo/abothesis.pdf>.
- D. Kelly et al., "A 3V 340mW 14b 75MSPS CMOS ADC with 85dB SFDR at Nyquist," ISSCC Dig. Techn. Papers, pp. 134-135, Feb. 2001.
- A. Loloe, et. al, "A 12b 80-MSs Pipelined ADC Core with 190 mW Consumption from 3 V in 0.18-um, Digital CMOS", Proc. ESSCIRC, pp. 467-469, 2002
- B.-M. Min et al., "A 69-mW 10-bit 80-MSample/s Pipelined CMOS ADC," IEEE JSSC, pp. 2031-2039, Dec. 2003.
- Y. Chiu, et al., "A 14-b 12-MS/s CMOS pipeline ADC with over 100-dB SFDR," IEEE JSSC, pp. 2139-2151, Dec. 2004.
- S. Limotyrakis et al., "A 150-MS/s 8-b 71-mW CMOS time-interleaved ADC," IEEE JSSC, pp. 1057-1067, May 2005.
- T. N. Andersen et al., "A Cost-Efficient High-Speed 12-bit Pipeline ADC in 0.18-um Digital CMOS," IEEE JSSC, pp. 1506-1513, Jul 2005.

# References

- P. Bogner et al., "A 14b 100MS/s digitally self-calibrated pipelined ADC in 0.13um CMOS," ISSCC Dig. Techn. Papers, pp. 832-833, Feb. 2006.
- D. Kurose et al., "55-mW 200-MSPS 10-bit Pipeline ADCs for Wireless Receivers," IEEE JSSC, pp. 1589-1595, Jul. 2006.
- S. Bardsley et al., "A 100-dB SFDR 80-MSPS 14-Bit 0.35um BiCMOS Pipeline ADC," IEEE JSSC, pp. 2144-2153, Sep. 2006.
- A. M. A. Ali et al., "A 14-bit 125 MS/s IF/RF Sampling Pipelined ADC With 100 dB SFDR and 50 fs Jitter," IEEE JSSC, pp. 1846-1855, Aug. 2006.
- S. K. Gupta, "A 1-GS/s 11-bit ADC With 55-dB SNDR, 250-mW Power Realized by a High Bandwidth Scalable Time-Interleaved Architecture," IEEE JSSC, 2650-2657, Dec. 2006.
- M. Yoshioka et al., "A 0.8V 10b 80MS/s 6.5mW Pipelined ADC with Regulated Overdrive Voltage Biasing," ISSCC Dig. Techn. Papers, pp. 452-453, Feb. 2007.
- Y.-D. Jeon et al., "A 4.7mW 0.32mm<sup>2</sup> 10b 30MS/s Pipelined ADC Without a Front-End S/H in 90nm CMOS," ISSCC Dig. Techn. Papers, pp. 456-457, Feb. 2007.
- K.-H. Lee et al., "Calibration-free 14b 70MS/s 0.13um CMOS pipeline A/D converters based on highmatching 3D symmetric capacitors," Electronics Letters, pp. 35-36, Mar. 15, 2007.
- K. Honda et al., "A Low-Power Low-Voltage 10-bit 100-MSample/s Pipeline A/D Converter Using Capacitance Coupling Techniques," IEEE JSSC, pp. 757-765, Apr. 2007.

# References

- ❑ **Per-Stage Resolution and Stage Scaling**
  - D. W. Cline et al., "A power optimized 13-b 5 MSamples/s pipelined analog-to-digital converter in 1.2um CMOS," IEEE JSSC, Mar. 1996
  - Y. Chiu, "High-Performance Pipeline A/D Converter Design in Deep-Submicron CMOS," PhD Dissertation, UC Berkeley, 2004.
  - H. Ishii et al., "A 1.0 V 40mW 10b 100MS/s pipeline ADC in 90nm CMOS," Proc. CICC, pp. 395-398, Sep. 2005.
- ❑ **OTA Design, Noise**
  - B. E. Boser, "Analog Circuit Design with Submicron Transistors," Presentation at IEEE Santa Clara Valley, May 19, 2005, <http://www.ewh.ieee.org/r6/scv/ssc/May1905.htm>
  - B. Murmann, EE315A Course Material, <http://ccnet.stanford.edu/cgi-bin/handouts.cgi?cc=ee315a>
  - R. Schreier et al., "Design-oriented estimation of thermal noise in switched-capacitor circuits," IEEE TCAS I, pp. 2358-2368, Nov. 2005.
- ❑ **Capacitor Matching Data**
  - C. H. Diaz et al., "CMOS technology for MS/RF SoC," IEEE Trans. Electron Devices, pp. 557-566, Mar. 2003.
  - A. Verma et al., "Frequency-Based Measurement of Mismatches Between Small Capacitors," Proc. CICC, pp. 481-484, Sep. 2006.
- ❑ **Reference Generator**
  - T. L. Brooks et al., "A low-power differential CMOS bandgap reference," ISSCC Dig. Techn. Papers, pp. 248-249, Feb. 1994.

# References

## □ Digitally-Assisted Pipelined

- B. Murmann et al., "A 12-bit 75-MS/s Pipelined ADC using Open-Loop Residue Amplification," IEEE JSSC, pp. 2040-2050, Dec. 2003.
- J. Fiorenza et al., "Comparator-Based Switched-Capacitor Circuits for Scaled CMOS Technologies," IEEE JSSC, pp. 2658-2668, Dec. 2006.
- E. Iroaga et al. "A 12b, 75MS/s Pipelined ADC Using Incomplete Settling," IEEE JSSC, pp. 748-756, Apr. 2007.
- J. Hu, N. Dolev and B. Murmann, "A 9.4-bit, 50-MS/s, 1.44-mW Pipelined ADC using Dynamic Residue Amplification," VLSI Circuits Symposium, June 2008.