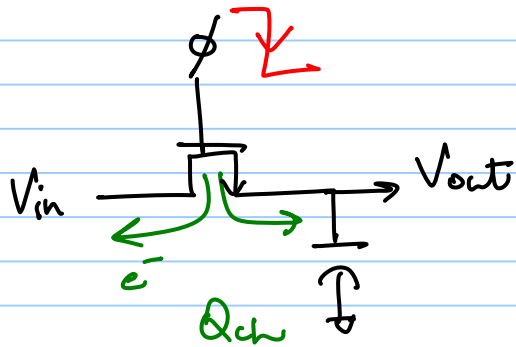


ECE 517 - Lecture 15



$V_{out} = V_{in}$ ideal

$$\Rightarrow V_{in} \left(1 + \frac{WLC_{ox}}{C_H} \right) + \underbrace{\gamma \frac{WLC_{ox}}{C_H} \sqrt{2\phi_B + V_{in}}}_{\text{distortion}} - \underbrace{\frac{WLC_{ox}}{C_H} (V_{DD} - V_{THN} + \gamma \sqrt{2\phi_B})}_{\text{offset}}$$

Body factor

Charge injection errors

- gain error ✓
- offset error ✓
- nonlinearity ✗

↓ figure of merit
foM of switch


$$F \triangleq (\tau \Delta V)^{-1} \quad \text{large value is desired}$$

$$\begin{aligned} \tau &= R_{on} C_H \\ &= \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{DD} - V_{in} - V_{THn})} \cdot C_H \end{aligned}$$

$$\Delta V = \frac{W L C_{ox} (V_{DD} - V_{in} - V_{THn})}{C_H}$$

$$F = \frac{1}{\tau \Delta V} = \frac{\mu_n}{L^2} \leftarrow \text{Benefit by scaling / length } (L)$$

② clock feedthrough:

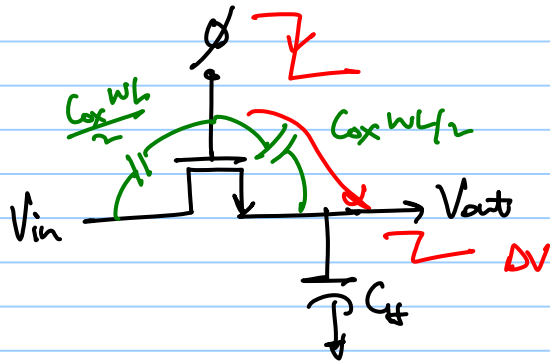



$$\Delta V = V_{clk} \cdot \frac{W' C_{ov}}{W C_{ov}' + C_{ff}}$$

overlap capacitance

$$W \uparrow \Rightarrow \Delta V \uparrow$$

for precision $C_{ff} \Rightarrow C_{ov}' W$

③ Thermal Noise

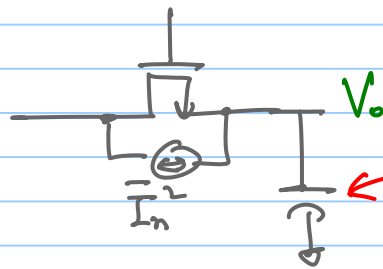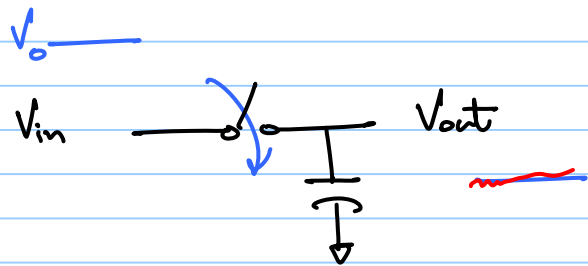

$C_{\#}$ is determined by the $\frac{kT}{C}$ noise considerations

Sampled noise on the capacitor


$$V_{n,rms} = \sqrt{\frac{kT}{C_{\#}}}$$

$$SNR = 20 \log_{10} \left(\frac{V_o}{V_{n,rms}} \right)$$

$C_{\#} \uparrow$ for higher $SNR \Rightarrow ENOB$

Charge Injection Cancellation:

① Dummy Switch

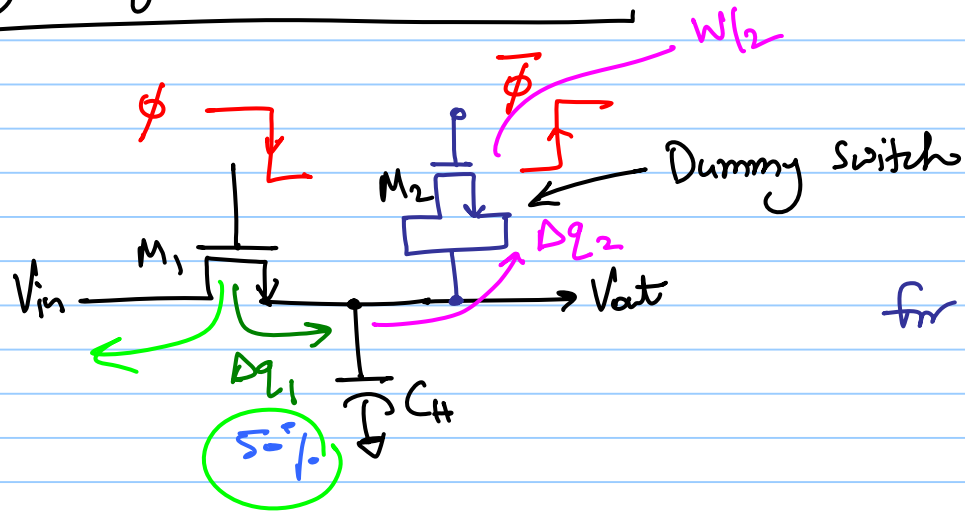

for perfect cancellation

$$\Delta Q_1 = \Delta Q_2$$


$$\frac{W_1 L_1 C_{ox}}{2} (V_{clk} - V_{in} - V_{th1}) = W_2 L_2 C_{ox} (V_{clk} - V_{in} - V_{th2})$$

for $W_2 = \frac{W_1}{2}$ & $L_2 = L_1$, this scheme may work.

* Also helps cancel clock feedthrough

Q3

Complementary Switches

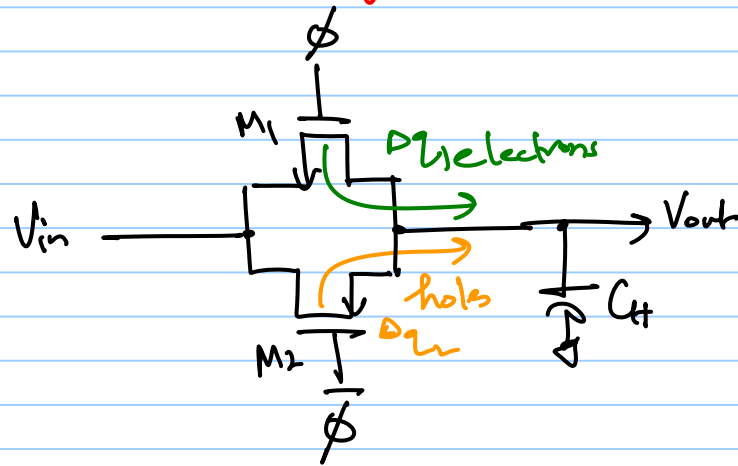

for perfect cancellation of \vec{e}^{\pm} by holes
 $\Delta q_1 = \Delta q_2$

$$\frac{W_1 L_1 C_{ox}}{2} (V_{clk} - V_{in} - V_{thp}) = \frac{W_2 L_2 C_{ox}}{2} (V_{in} - |V_{thn}|)$$


$$\Rightarrow V_{clk} - V_{in} - V_{thp} = V_{in} - |V_{thn}|$$

$$\Rightarrow V_{in} = \frac{(V_{clk} - V_{thn} + |V_{thp}|)}{2}$$

* Also, this circuit doesn't provide clock-feedthru cancellation
 $C_{ov,pmos} \neq C_{ov,nmos}$

cancellation only occurs for one particular value of V_{in}

③ Differential Circuits

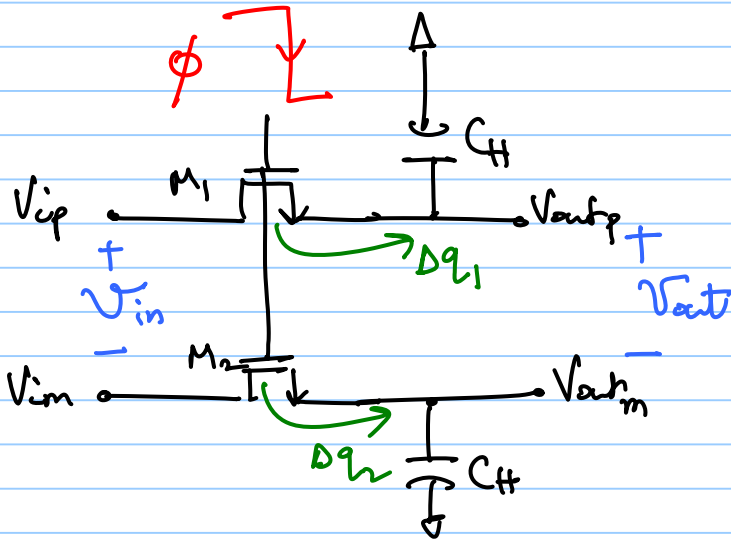

$$\Delta q_1 - \Delta q_2 = WL C_{ox} [(V_{inp} - V_{inm}) + (V_{thnp} - V_{thnm})]$$

$$= WL C_{ox} [\underbrace{V_{in}}_{\text{odd function of } V_{in}} + \gamma (\sqrt{2\phi_B + V_{inp}} - \sqrt{2\phi_B + V_{inm}})]$$

odd function of V_{in}

* DC offset due to CT is cancelled

Non-linear term remains

$$\begin{aligned} & \sqrt{2\phi_B + V_{cm} + \frac{V_{in}}{2}} - \sqrt{2\phi_B + V_{cm} - \frac{V_{in}}{2}} \\ &= f(V_{in}) - f(-V_{in}) \quad : \text{ odd function} \end{aligned}$$

Odd function


$$f(v_{in}) - f(-v_{in})$$



Taylor series
has only odd order
terms.

All DC and even order terms are cancelled out


↳ fully differential circuit eliminates all
even-order non-linearity

Sample and Hold (Buffer) Circuits

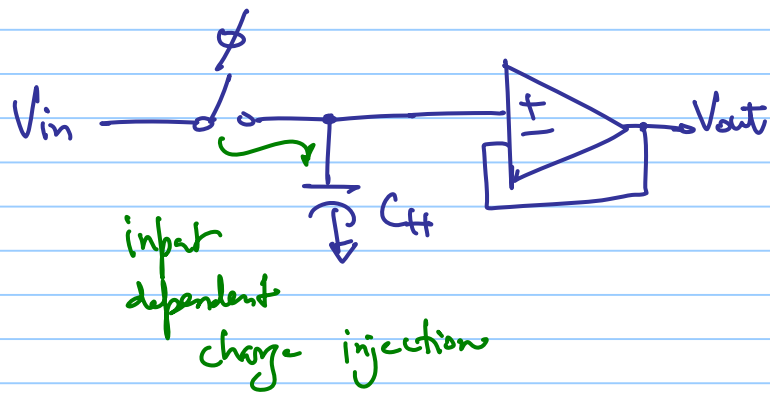

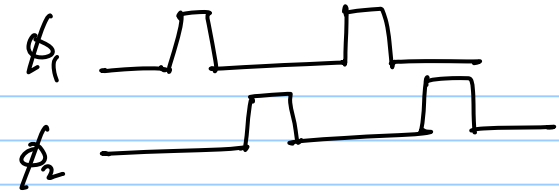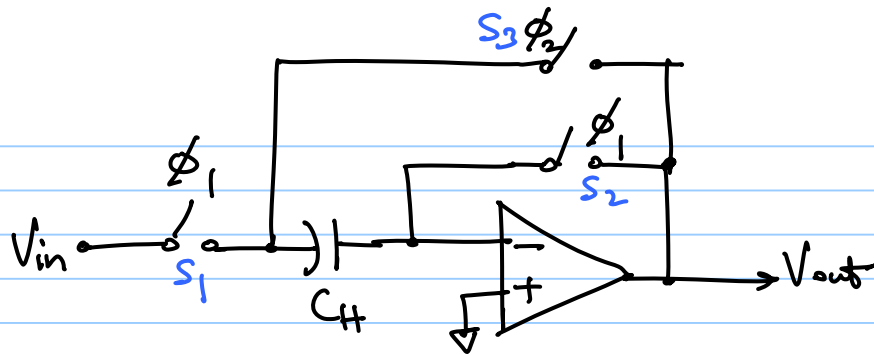



Sampling Mode ($\phi_1=1, \phi_2=0$)

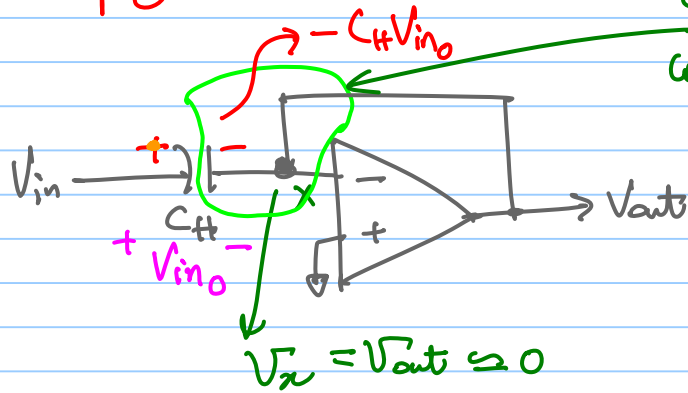


charge is conserved on this surface

Hold Mode ($\phi_1=0, \phi_2=1$)

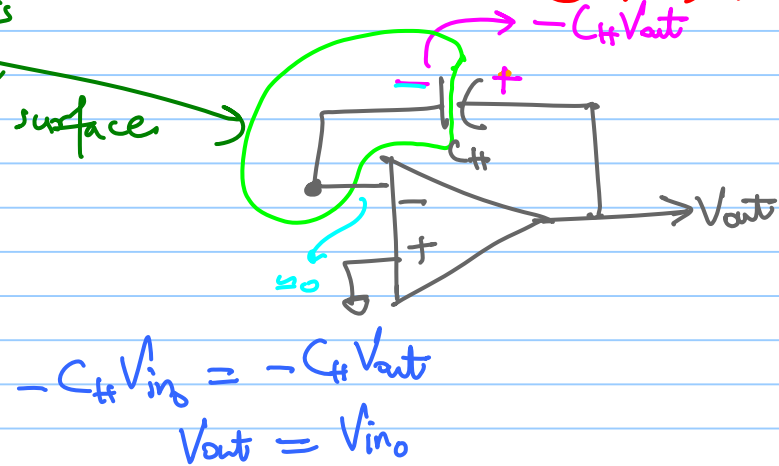

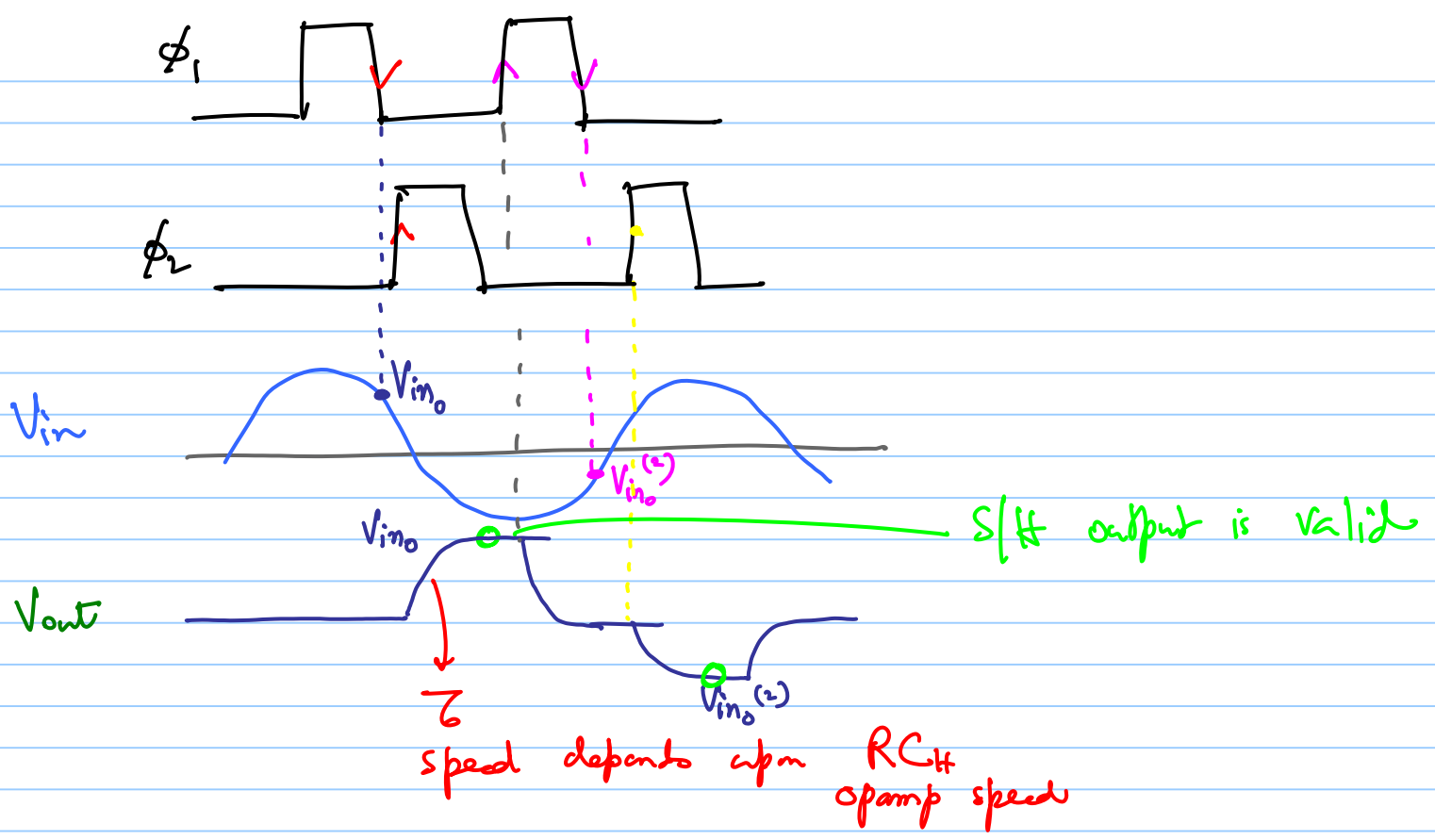

Slow motion recap of this S/H circuit

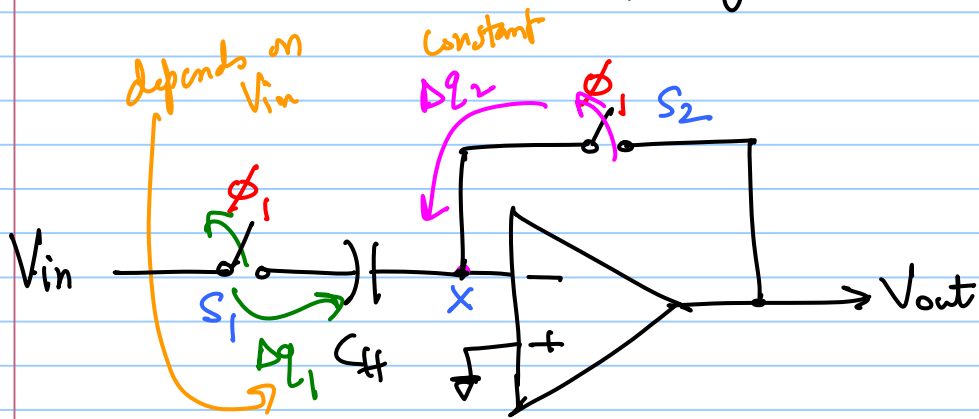

* When S_1 turns off: ΔQ_1 is injected into C_f

$$\Delta Q_1 = WL C_{ox} (V_{clk} - V_{in} - V_{THN1})$$

↳ $f(V_{in})$

* When S_2 turns off: ΔQ_2 is injected into C_f


$$\Delta Q_2 = WL C_{ox} (V_{clk} - V_{THN2})$$

↳ constant charge independent of V_{in}

↳ offset not distortion

can be

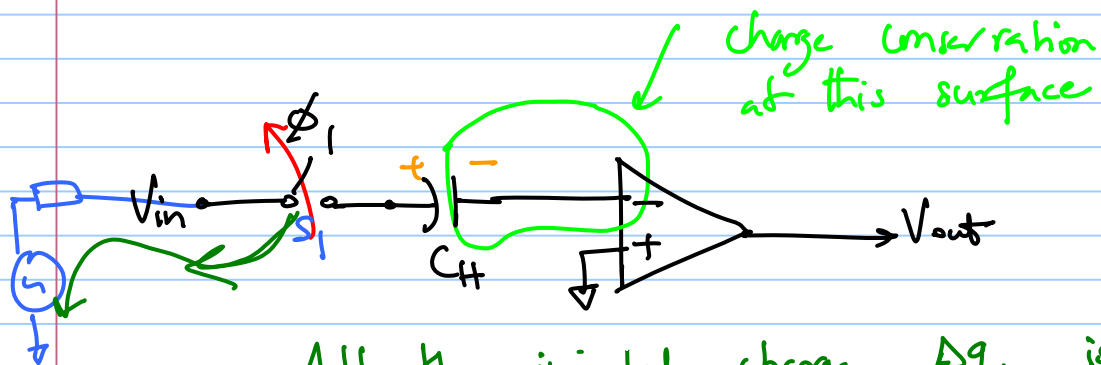cancelled by fully differential operation



All the injected charge Δq_1 is absorbed into source V_{in}
 \hookrightarrow none of Δq_1 is stored on C_{ff}

Bottom plate Sampling

$\phi_{1a} \Rightarrow \phi_1$ falling edge is advanced!

