
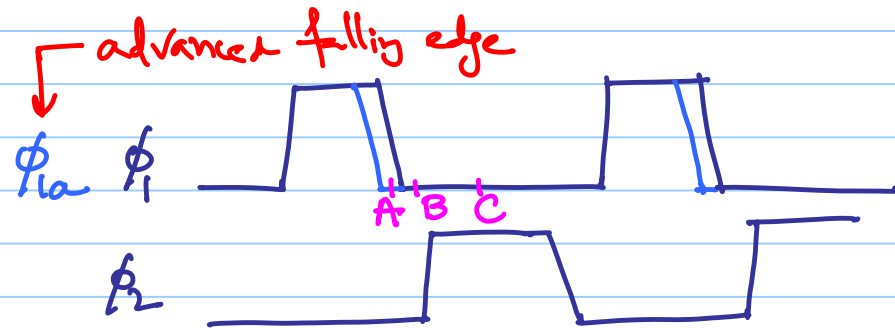


# ECE 517 - Lecture 16

Note Title


3/9/2017

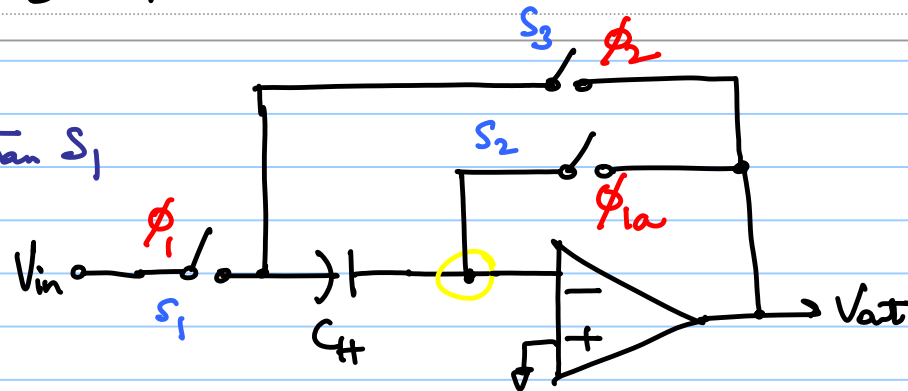Turnoff switch  $S_2$  earlier than  $S_1$   
 $\Rightarrow \phi_{1a}$  & advanced falling edge



(A)

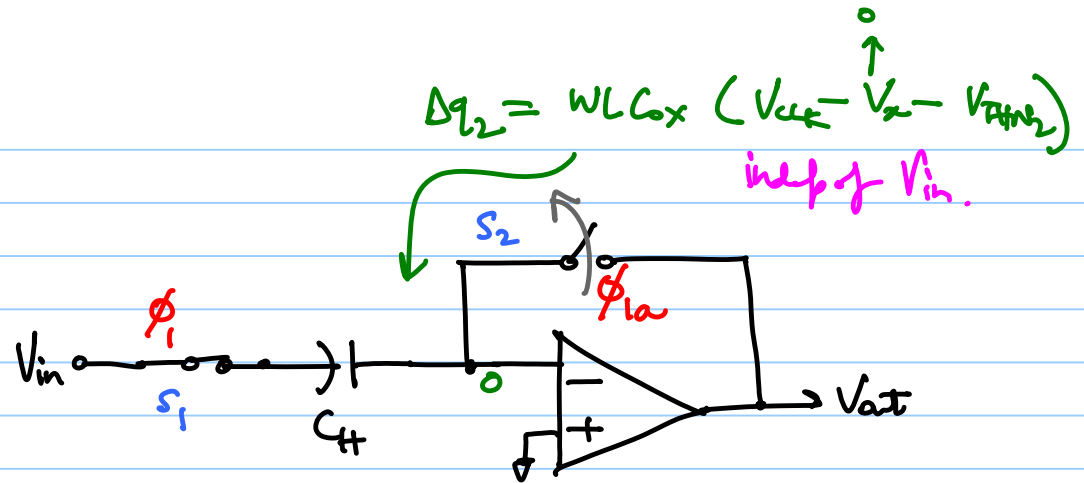
$$\Delta q_2 = WLC_{ox}(V_{clk} - V_{THN2}) \checkmark$$



(B)

$$\Delta q_1 = WLC_{ox}(V_{clk} - V_{in} - V_{THN1})$$

Aug  $q_1$  is absorbed into  $V_{in}$

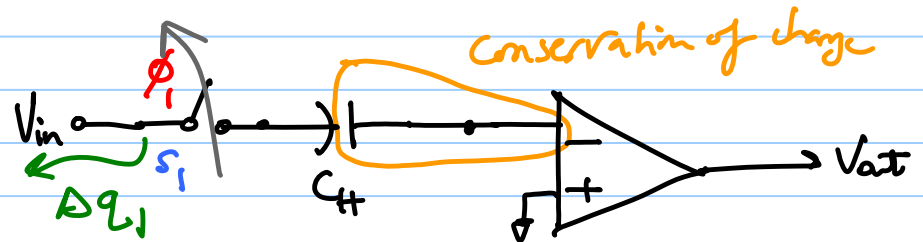

③

$V_{in} = 0$

Total charge at node-X =  $V_X \leq 0$


$$C_X V_X - (V_{out} - V_X) C_H = 0 \rightarrow \textcircled{1}$$

$$\Rightarrow V_X = - \frac{V_{out}}{A} \rightarrow \textcircled{2}$$



$$- (C_X + C_H) \frac{V_{out}}{A} - V_{out} C_H = 0$$

$$\Rightarrow V_{out} = 0$$

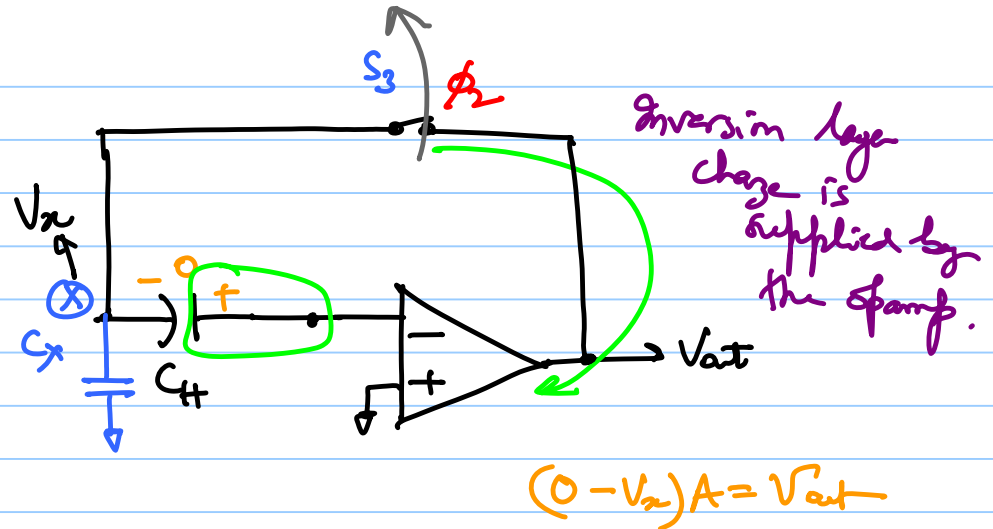$\Rightarrow$  This result is independent of  $\Delta L_1$



## Bottom Plate Sampling

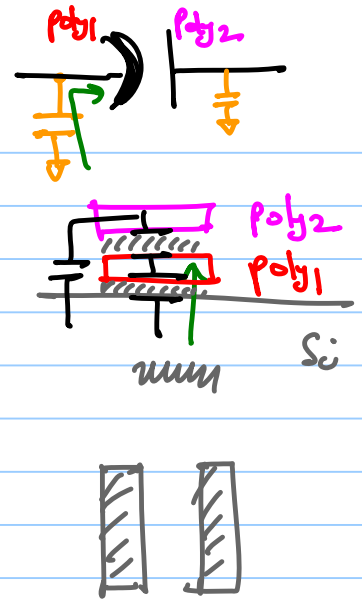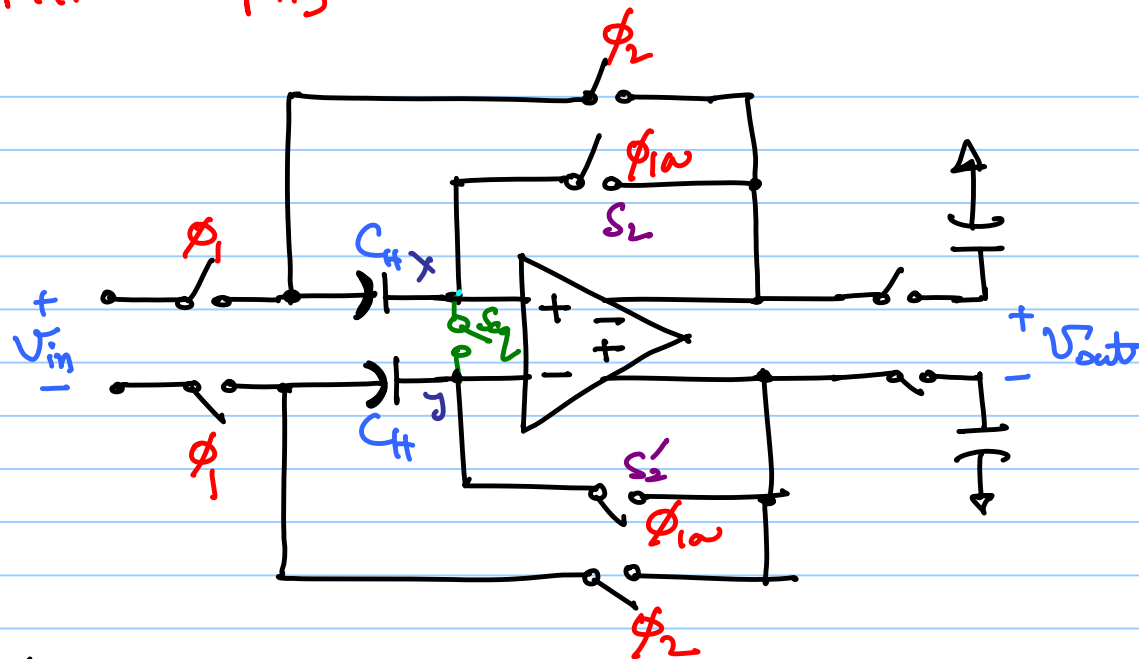

\*  $S_2 \Delta S'$  CT mismatch  $\rightarrow$  creates CM disturbance at  $X \& Y$   
 $\hookrightarrow$  add another switch  $S_{eq}$


$s_2$



turns off slightly after  $s_2$  &  $s_2'$   
but before  $s_1$  &  $s_1'$

↳ equalizes (averages out) the charge at  
nodes  $x+y$

Finite gain:

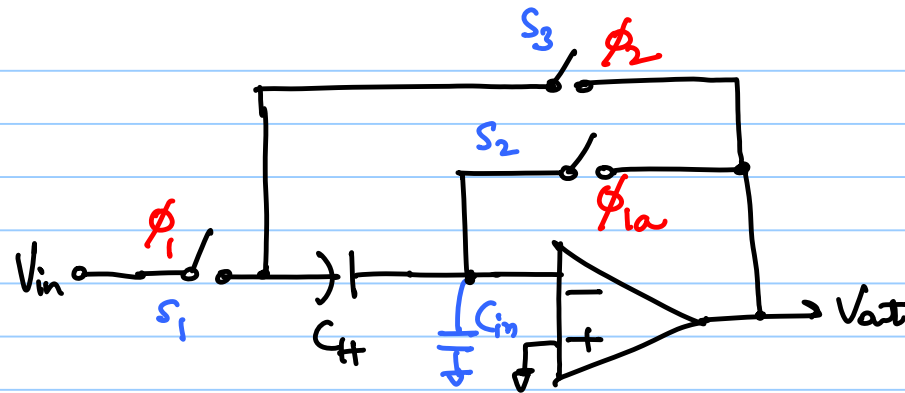

$f_s$   
 $f_{osc}$  ← opamp unity gain frequency  
 $A_v$  ← DC gain  
 $SR$  ← slew rate  
 offset

$$V_{out} \approx V_0 \left[ 1 - \underbrace{\frac{1}{A_v} \left( \frac{C_{in}}{C_H} + 1 \right)}_{\epsilon} \right]$$

$\epsilon \rightarrow$  precision

feedback factor in  $\phi_2$  mode

$$\beta = \frac{C_H}{C_H + C_{in}}$$

$\Sigma x.$

$$C_{in} = 0.5 \text{ pF}$$

$$C_H = 2 \text{ pF}$$



$$A_v \geq 1250$$

$> 60 \text{ dB}$



for a precision of 0.1%.

with  $C_{in} = 0 \Rightarrow 1000 \Rightarrow 60 \text{ dB}$

$\Rightarrow$

S/H

gain error  
settling error


o/p error

$$< \frac{1}{2} \text{ LSB} = \frac{V_{ref}}{2^{n+1}}$$

Thermal noise  $\Rightarrow \propto \sqrt{\frac{kT}{C}}$  should also be well below  $\frac{1}{2} \text{ LSB}$ .

## Speed Consideration:

### a) Sample Mode

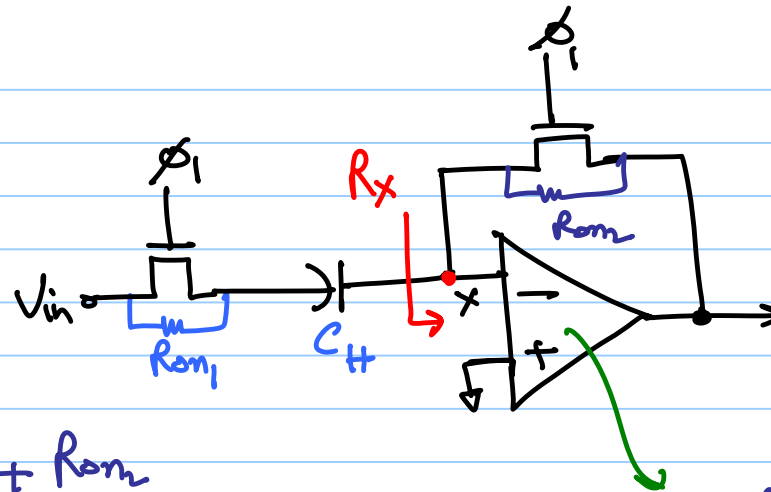


See Razavi  
for more  
analysis

$$R_x \approx \frac{R_o + R_{on2}}{1 + g_m R_o}$$



time constant for <sup>the</sup> sampling phase
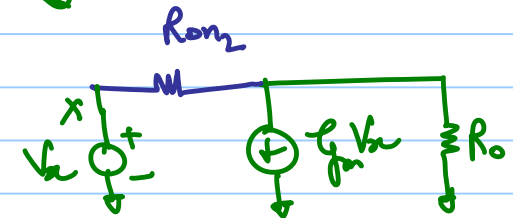
$$\tau_{\text{samp}} = \left( R_{on1} + \frac{1}{g_m} \right) C_H$$





## b) Amplification Mode

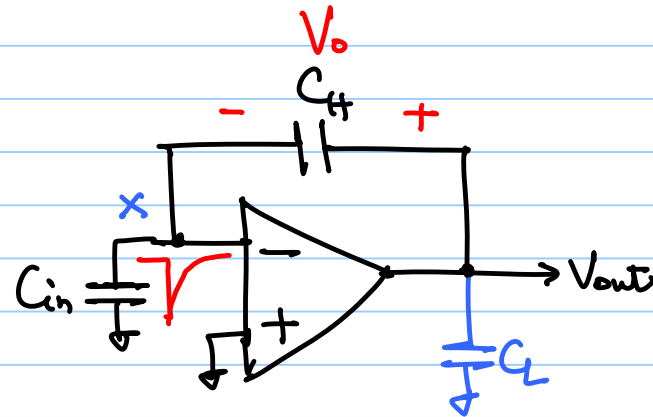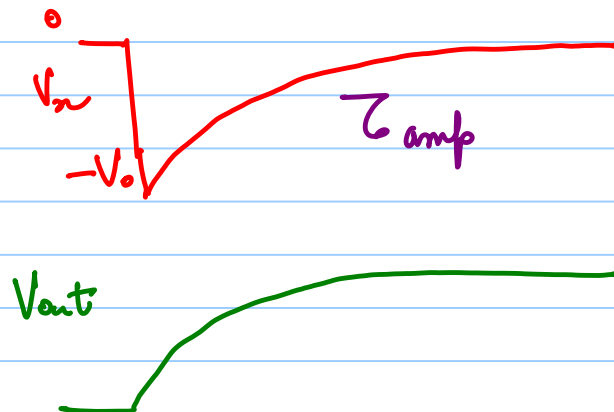

$$\tau_{amp} = \frac{C_L C_{in} + C_{in} C_H + C_H C_L}{g_m C_H}$$

If  $C_{in} \ll C_L, C_H$  then

$$\tau_{amp} \approx \frac{C_L}{g_m} \leftarrow \text{Expected Result}$$

$$\left. \begin{array}{l} \text{Speed } f_o \\ \text{settling accuracy } \propto \\ C_L \end{array} \right\} \Rightarrow f_{gm} \propto f_{un} \downarrow \downarrow I_{bias} \Rightarrow \text{Power}$$



$$f_{un} = \begin{cases} \frac{g_m}{C_L} & \text{Single stage} \\ \frac{g_{m1}}{C_C} & \text{Two stage} \end{cases}$$




↑  
Miller Compensation Cap

↳  $C_{in}$  degrades both the speed and precision of the unity-gain sampler buffer

# Slewing in opamp

$$I_L = C_L \frac{dV_{out}}{dt}$$

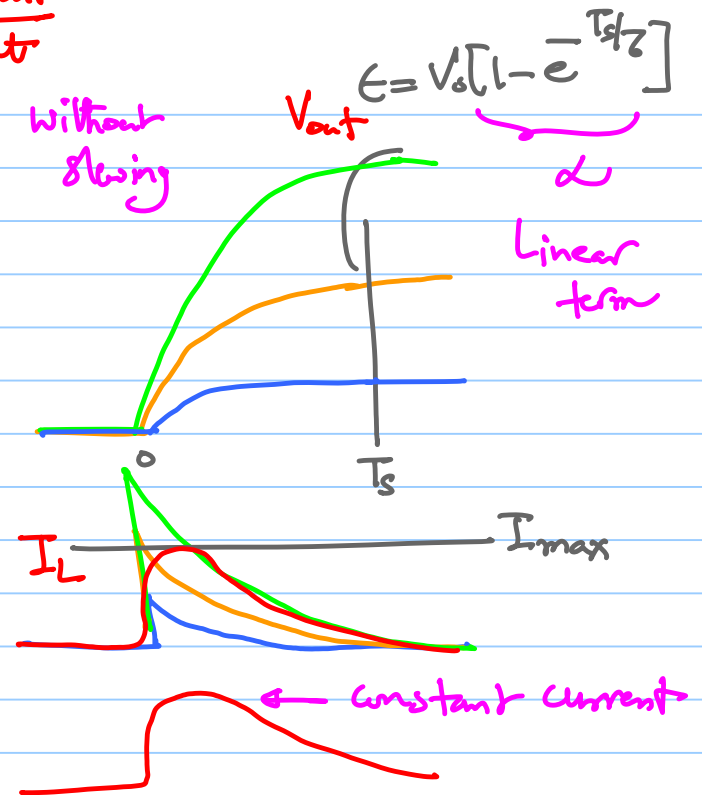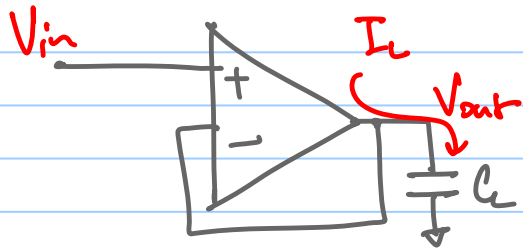

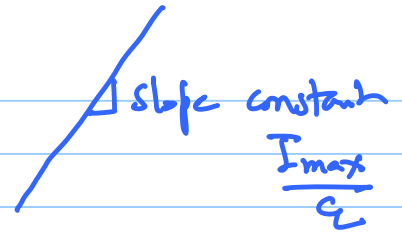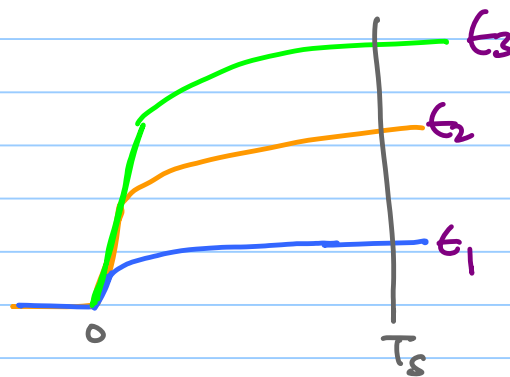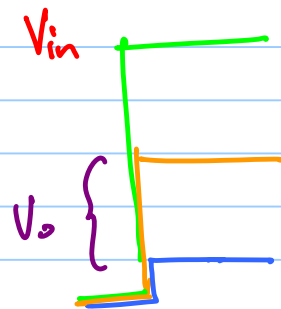

Slew


↳ settling errors  
 $t_1$ ,  $t_2$ ,  $t_3$  are  
 input dependent

↳ Non linearity!

Rule of Thumb:

The opamp should not slow for more than 25% of the settling period

→ Look at the SFDR for Non linearity

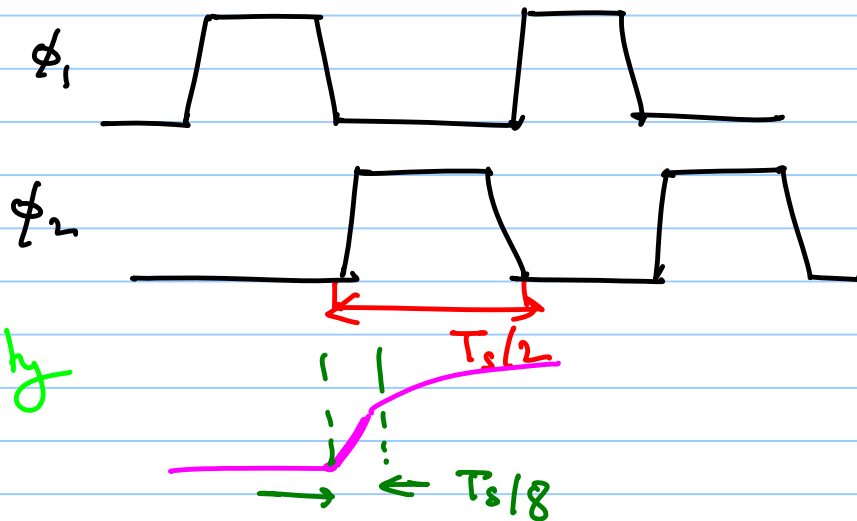

$$T_s \leq \frac{T_{CLK}}{2}$$

$$SR = \begin{cases} \frac{I_{SS}}{C_L} \\ \frac{I_{SS}}{C_C} \end{cases}$$

tail current in the diff pair

1-stage

2-stage Miller with class AB