

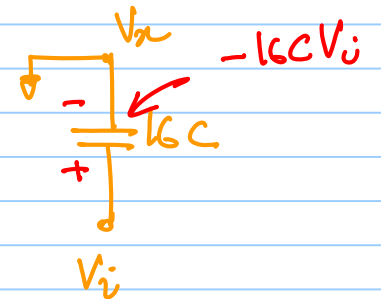


ECF 517 - Lecture 19

Note Title

3/28/2017

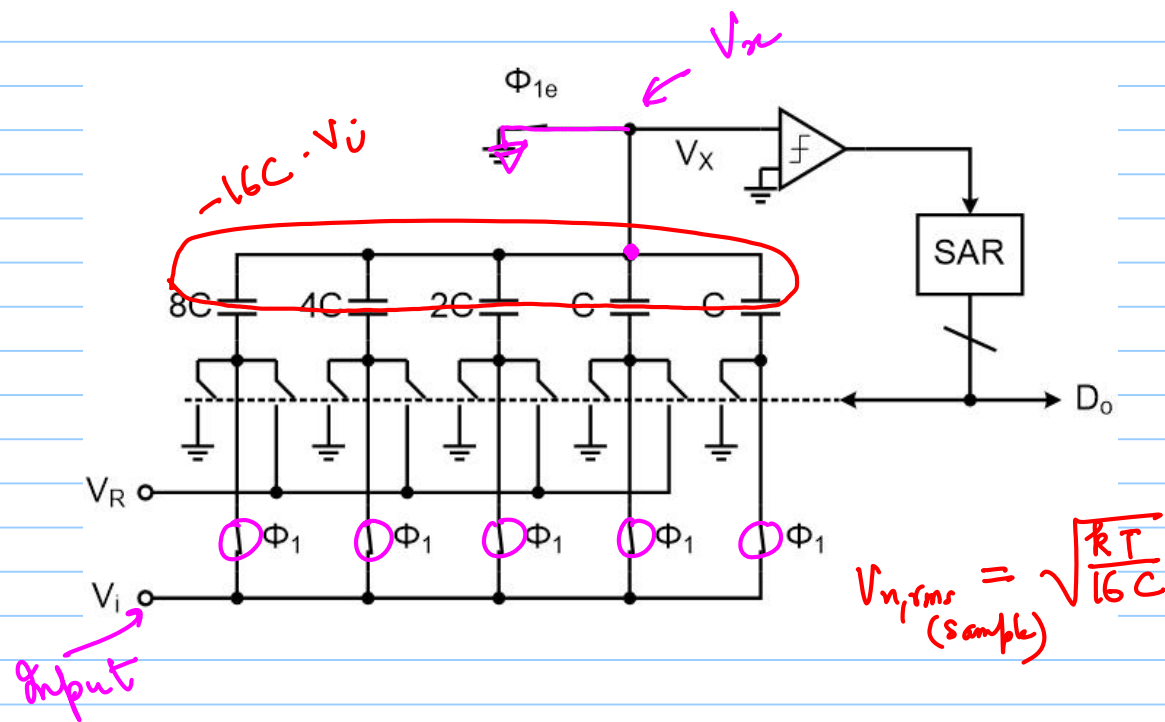

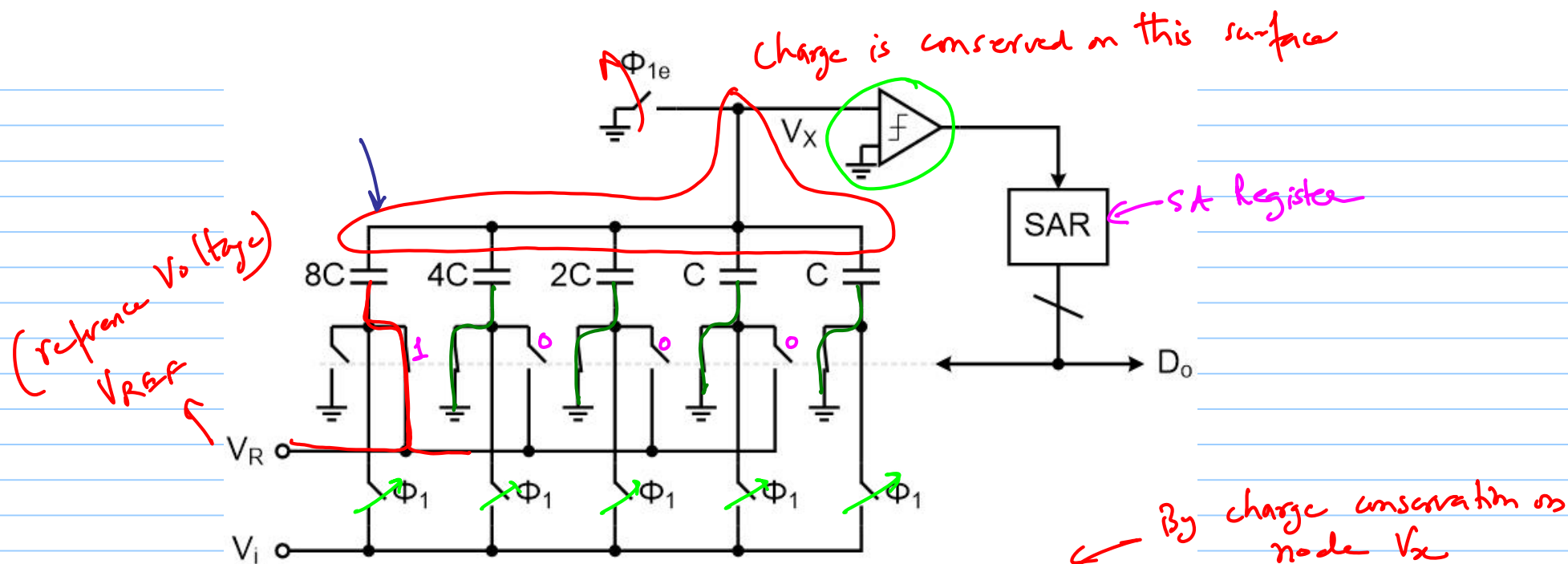

$$-8C(V_R - V_x) - (4C + 2C + C + C)(0 - V_x) = -16C V_i$$

$$-8C V_R + 16C V_x = -16C V_i$$

$$V_x = \frac{8C V_R - 16C V_i}{16C}$$


$$\Rightarrow V_x = \frac{V_R}{2} - V_i$$

zero crossing
detector


$$\underline{V_x > 0} \Rightarrow V_i < \frac{V_R}{2} \Rightarrow MSB = 0$$

$$\text{if } \underline{V_x < 0} \Rightarrow V_i > \frac{V_R}{2} \Rightarrow MSB = 1$$

$D[N-1:0]$

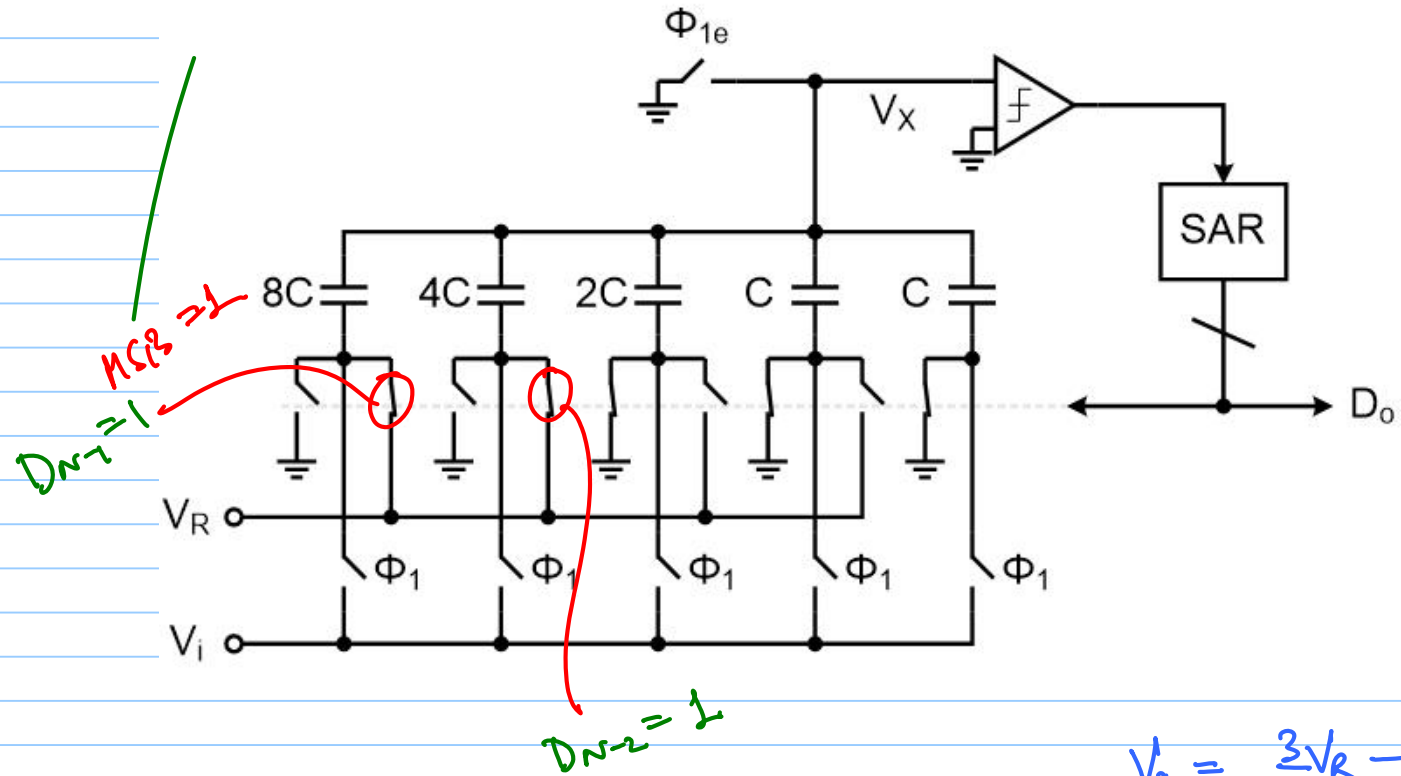


Split DAC Topology

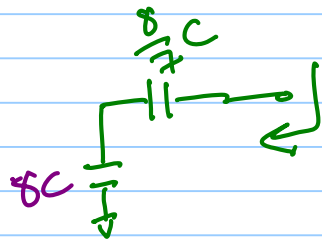

$$\frac{8 \times \frac{8}{7} C}{8 + \frac{8}{7}} = C$$

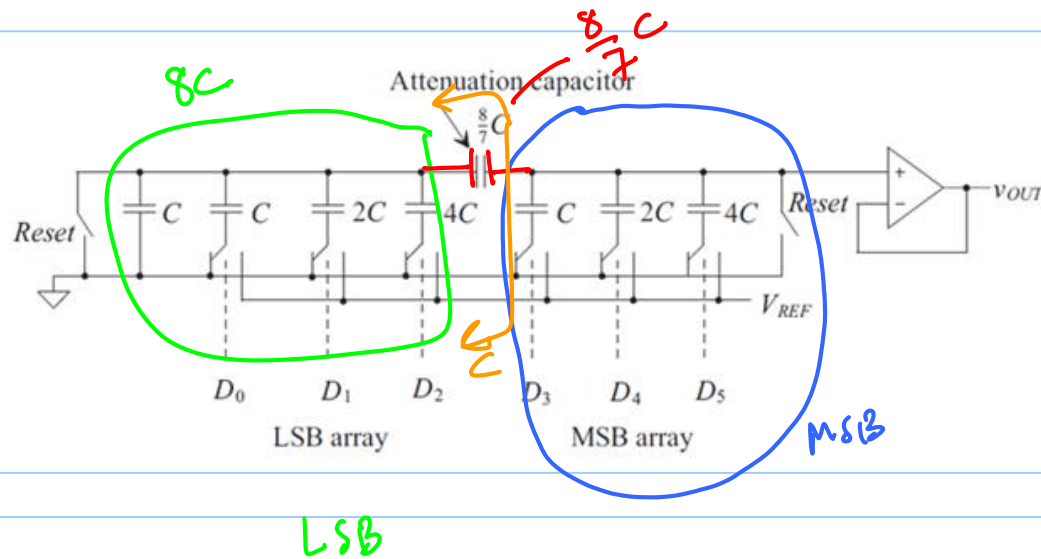6-bit SAR ADC
MSB capacitor
 $(2^{5-1})C = 32C$



C-2C
Ladder Topology

Fully Differential SAR

