


SRAM Architecture

Vishal Saxena, Boise State University
(vishalsaxena@boisestate.edu)

Outline


- ❑ Memory Arrays
- ❑ SRAM Architecture
 - SRAM Cell
 - Decoders
 - Column Circuitry
 - Multiple Ports
- ❑ Serial Access Memories

Memory Arrays

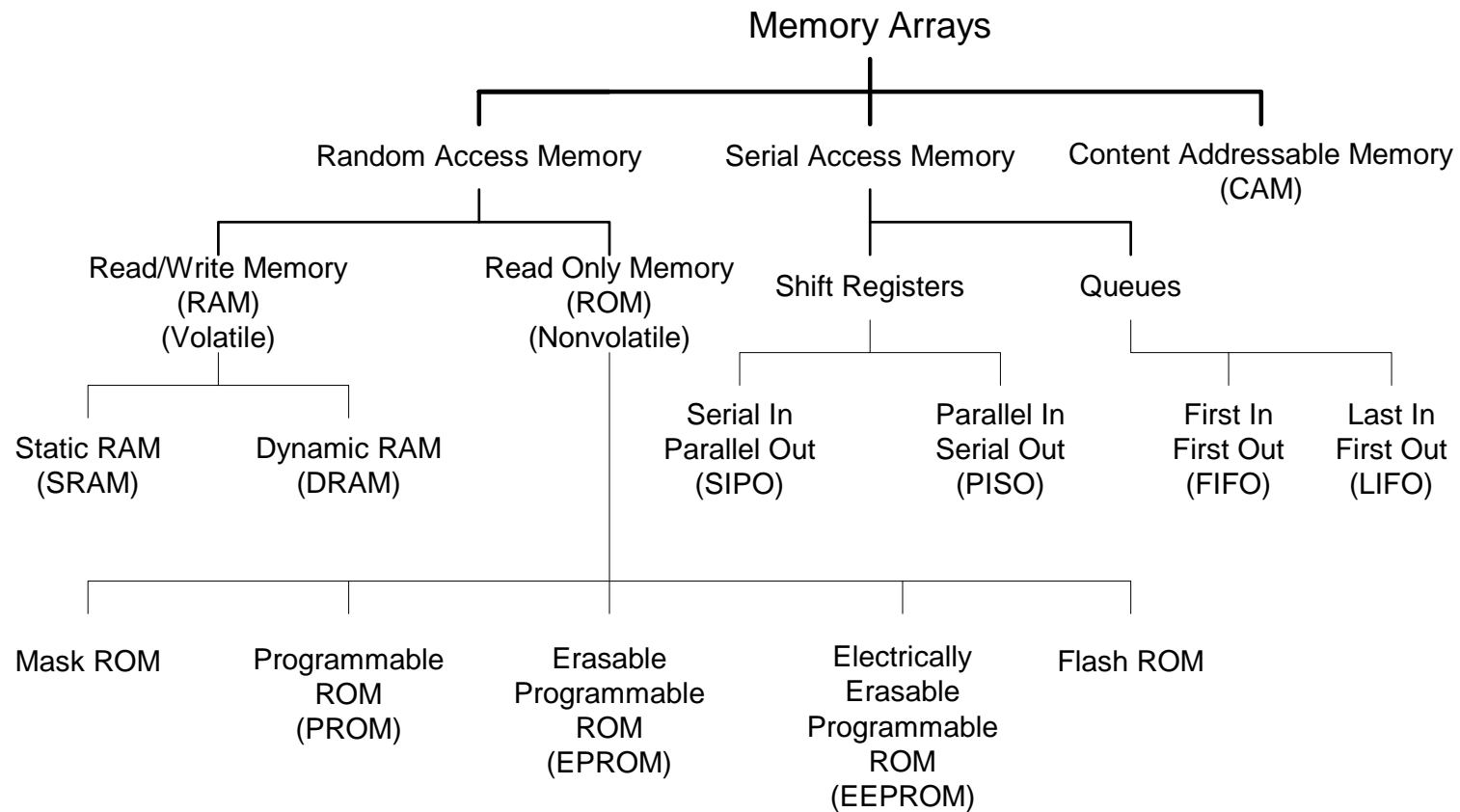


6T SRAM Cell

 - ❑ Cell size accounts for most of array size
 - Reduce cell size at expense of complexity
- ❑ 6T SRAM Cell
 - Used in most commercial chips
 - Data stored in cross-coupled inverters
- ❑ Read:
 - Precharge bit, bit_b
 - Raise wordline
- ❑ Write:
 - Drive data onto bit, bit_b
 - Raise wordline





SRAM Read

 - ❑ Precharge both bitlines high
- ❑ Then turn on wordline
- ❑ One of the two bitlines will be pulled down by the cell
- ❑ Ex: $A = 0, A_b = 1$
 - bit discharges, bit_b stays high
 - But A bumps up slightly
- ❑ *Read stability*
 - A must not flip
 - $N1 \gg N2$




SRAM Write

 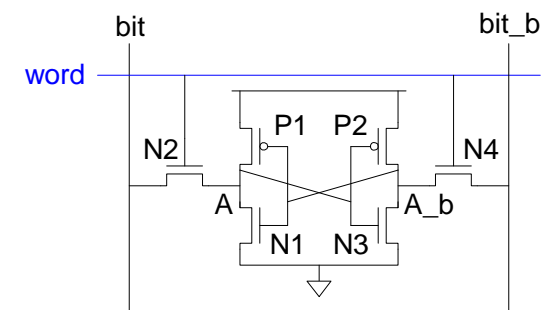- Drive one bitline high, the other low
- Then turn on wordline
- Bitlines overpower cell with new value
- Ex: $A = 0$, $A_b = 1$, $bit = 1$, $bit_b = 0$
 - Force A_b low, then A rises high
- *Writability*
 - Must overpower feedback inverter
 - $N2 \gg P1$




SRAM Sizing

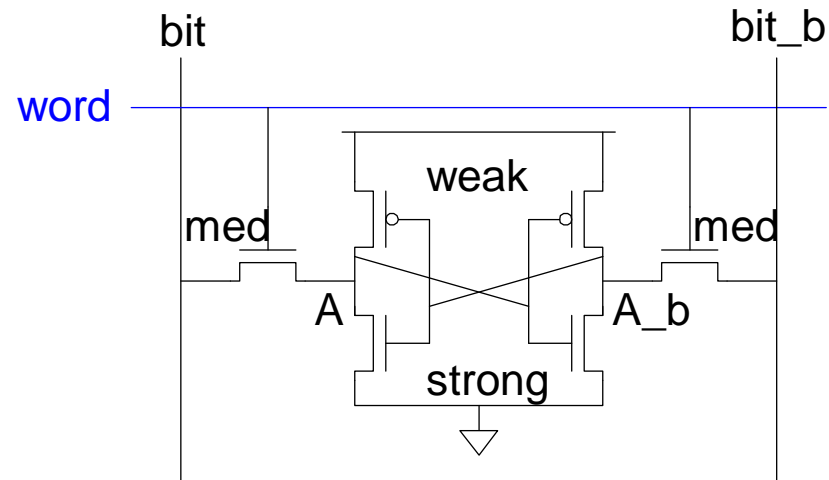- ❑ High bitlines must not overpower inverters during reads
- ❑ But low bitlines must write new value into cell




SRAM Column Example

Read


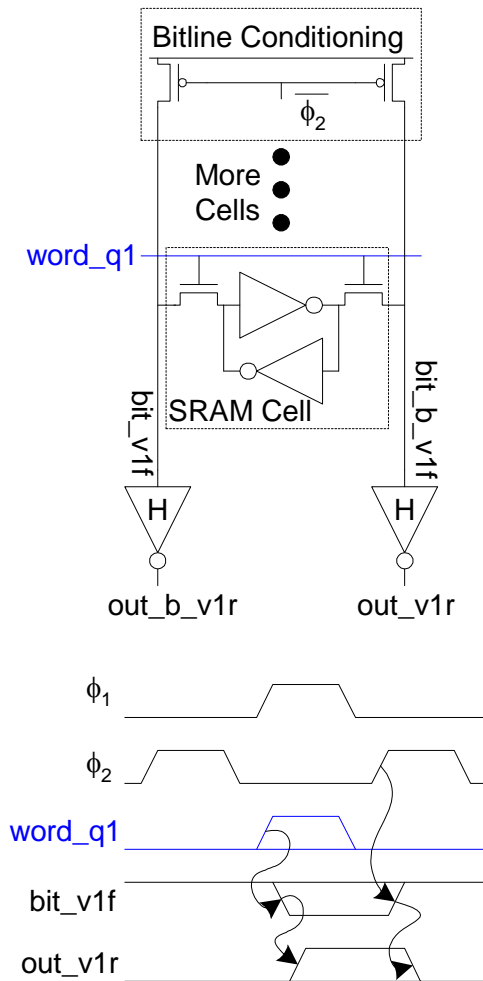


Write

 



SRAM Layout

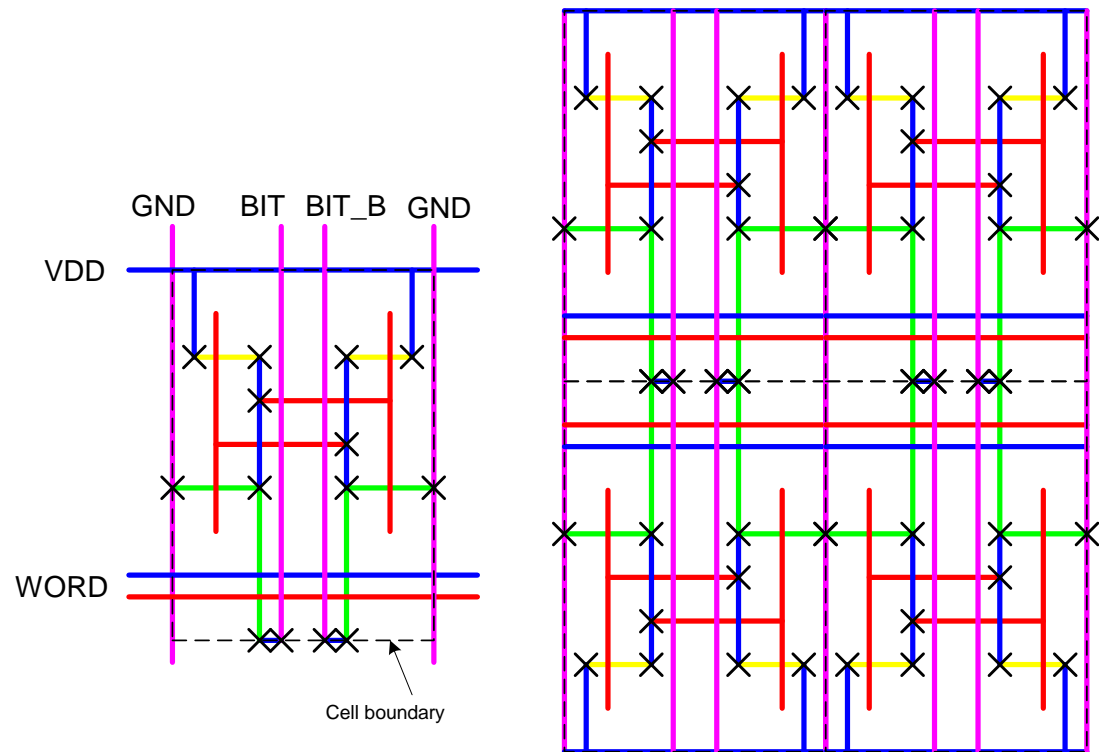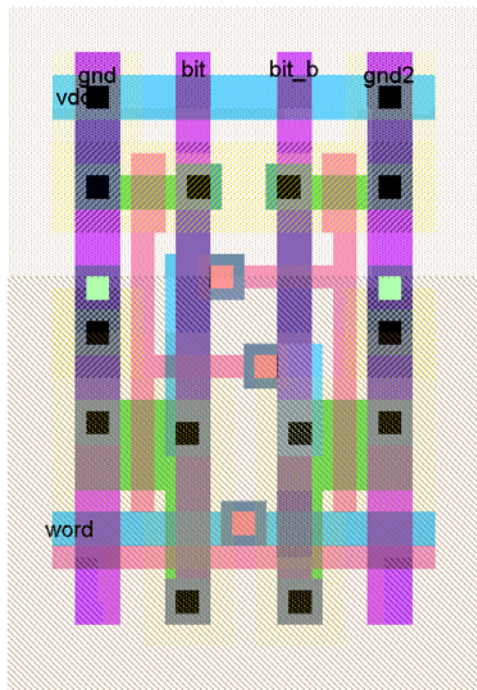- ❑ Cell size is critical: $26 \times 45 \lambda$ (even smaller in industry)
- ❑ Tile cells sharing V_{DD} , GND, bitline contacts




12T SRAM Cell

 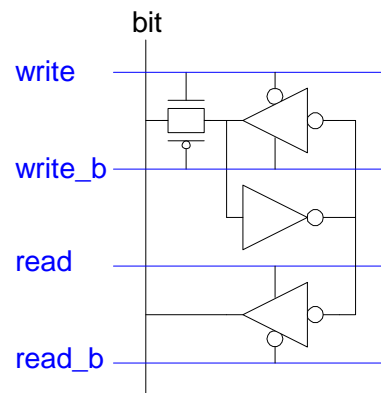- ❑ Basic building block: SRAM Cell
 - Holds one bit of information, like a latch
 - Must be read and written
- ❑ 12-transistor (12T) SRAM cell
 - Use a simple latch connected to bitline
 - $46 \times 75 \lambda$ unit cell




Thin Cell

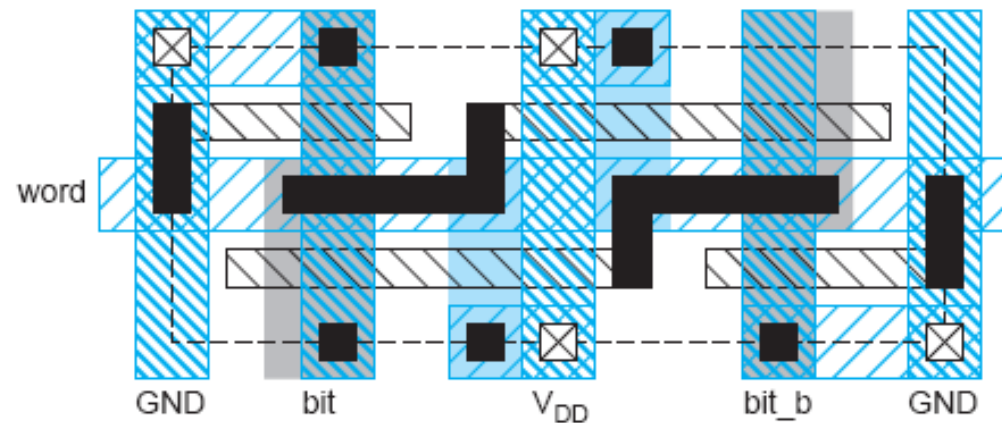- ❑ In nanometer CMOS
 - Avoid bends in polysilicon and diffusion
 - Orient all transistors in one direction
- ❑ *Lithographically friendly* or *thin cell* layout fixes this
 - Also reduces length and capacitance of bitlines



Commercial SRAMs


 
- Five generations of Intel SRAM cell micrographs
 - Transition to thin cell at 65 nm
 - Steady scaling of cell area





Decoders

- $n:2^n$ decoder consists of 2^n n -input AND gates
 - One needed for each row of memory
 - Build AND from NAND or NOR gates

Static CMOS

  


Pseudo-nMOS

  


Decoder Layout

 - ❑ Decoders must be pitch-matched to SRAM cell
 - Requires very skinny gates




Large Decoders

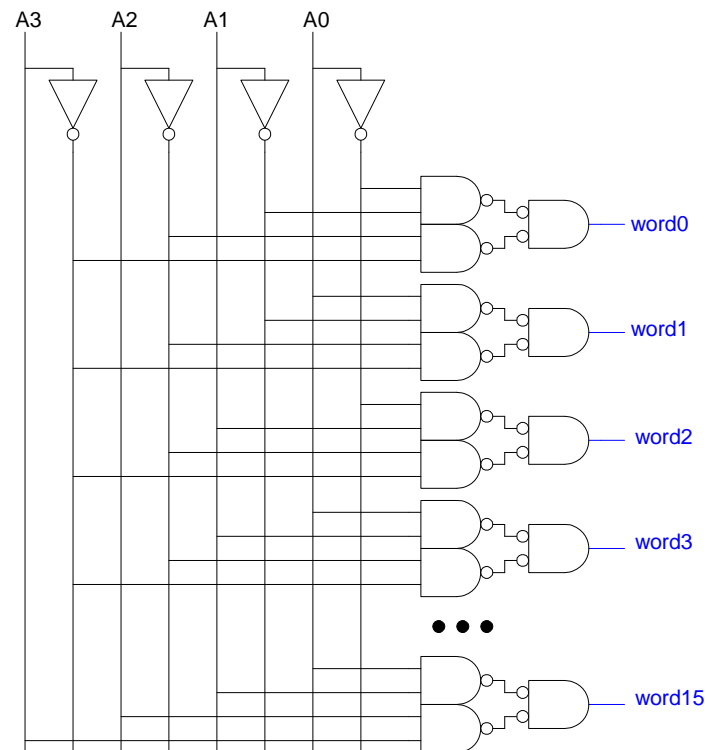- For $n > 4$, NAND gates become slow
 - Break large gates into multiple smaller gates



Predecoding

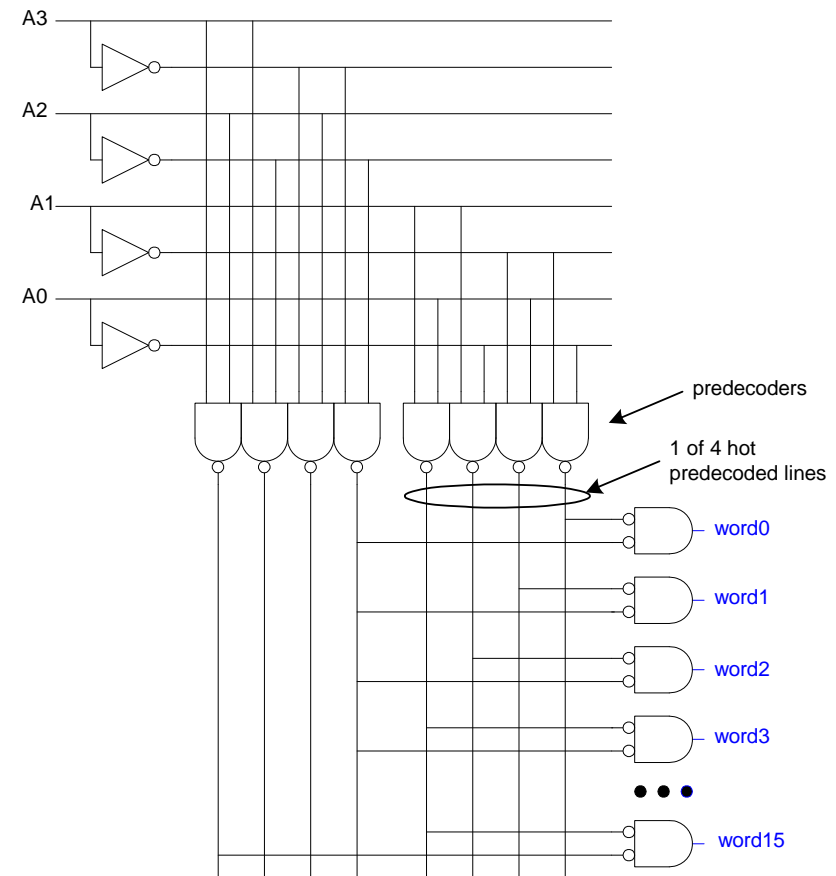- Many of these gates are redundant
 - Factor out common gates into predecoder
 - Saves area
 - Same path effort




Column Circuitry


- Some circuitry is required for each column
 - Bitline conditioning
 - Sense amplifiers
 - Column multiplexing

Bitline Conditioning

- Precharge bitlines high before reads

 

 - Equalize bitlines to minimize voltage difference when using sense amplifiers




Sense Amplifiers

- ❑ Bitlines have many cells attached
 - Ex: 32-kbit SRAM has 128 rows x 256 cols
 - 128 cells on each bitline
- ❑ $t_{pd} \propto (C/I) \Delta V$
 - Even with shared diffusion contacts, 64C of diffusion capacitance (big C)
 - Discharged slowly through small transistors (small I)
- ❑ *Sense amplifiers* are triggered on small voltage swing (reduce ΔV)


Clocked Sense Amp

 - ❑ Clocked sense amp saves power
- ❑ Requires sense_clk after enough bitline swing
- ❑ Isolation transistors cut off large bitline capacitance



Twisted Bitlines

 - Sense amplifiers also amplify noise
 - Coupling noise is severe in modern processes
 - Try to couple equally onto bit and bit_b
 - Done by *twisting* bitlines




Column Multiplexing

- Ex: 2 kword x 16 folded into 256 rows x 128 columns
 - Must select 16 output bits from the 128 columns
 - Requires 16 8:1 column multiplexers


Tree Decoder Mux

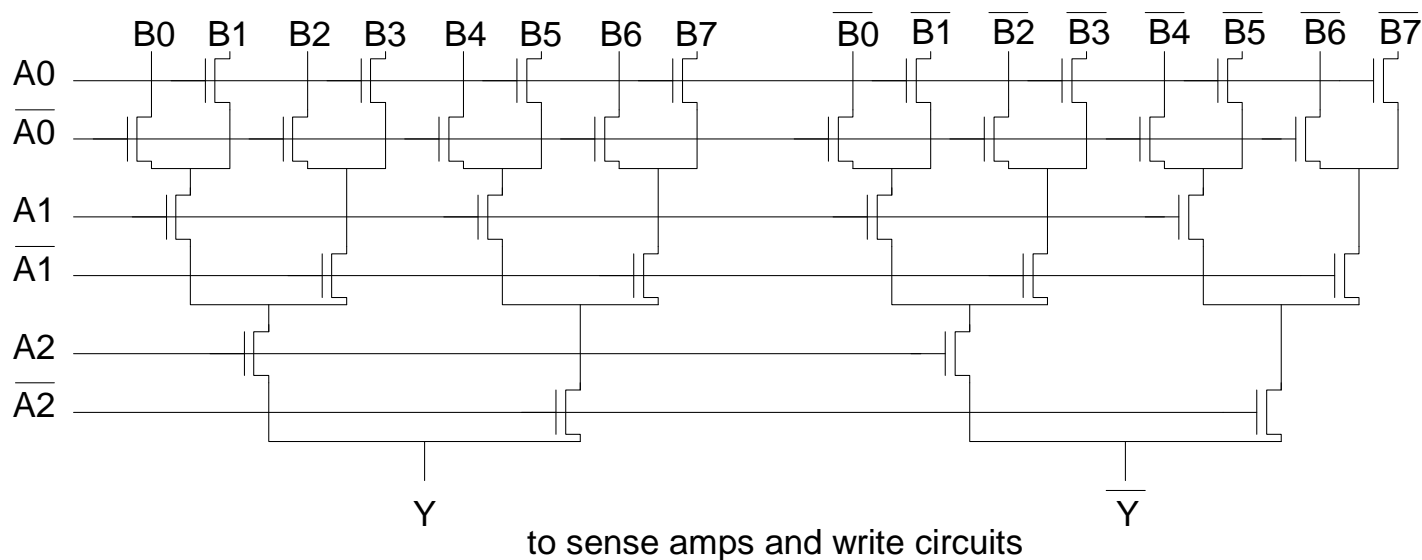- ❑ Column mux can use pass transistors
 - Use nMOS only, precharge outputs
- ❑ One design is to use k series transistors for $2^k:1$ mux
 - No external decoder logic needed




Single Pass-Gate Mux

 - Or eliminate series transistors with separate decoder



Ex: 2-way Muxed SRAM

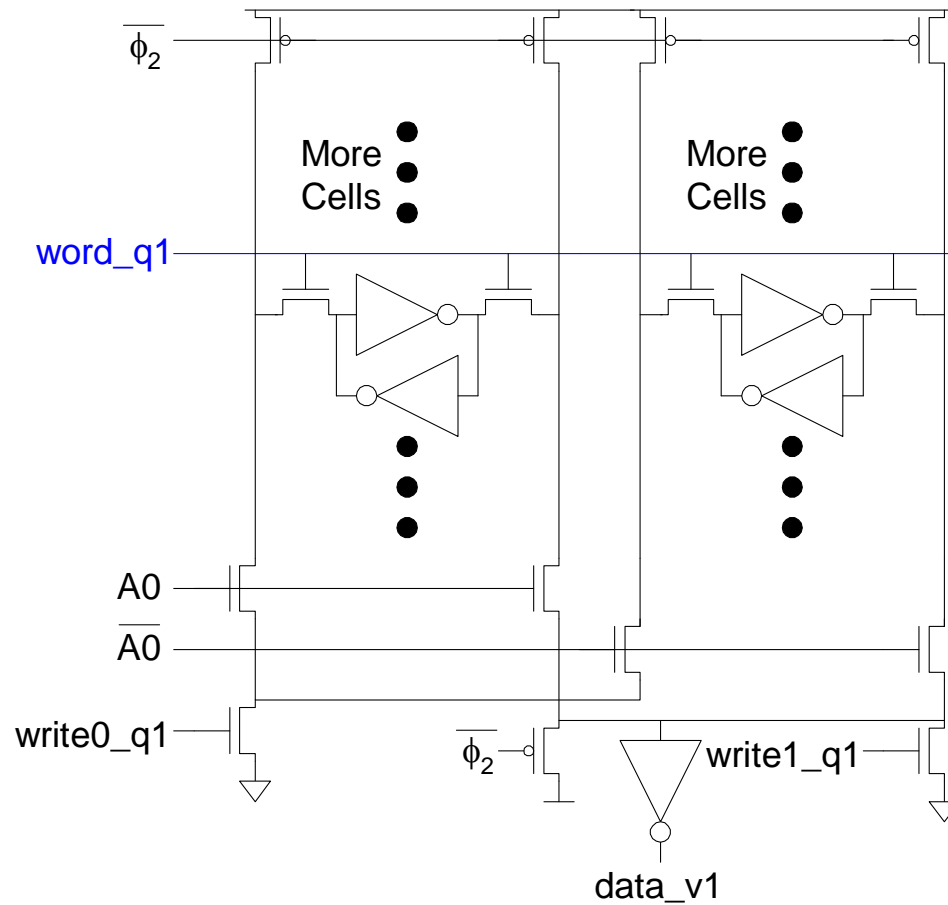


Multiple Ports

- ❑ We have considered single-ported SRAM
 - One read or one write on each cycle
- ❑ *Multiported* SRAM are needed for register files
- ❑ Examples:
 - Multicycle MIPS must read two sources or write a result on some cycles
 - Pipelined MIPS must read two sources and write a third result each cycle
 - Superscalar MIPS must read and write many sources and results each cycle

Dual-Ported SRAM

 
- Simple dual-ported SRAM
 - Two independent single-ended reads
 - Or one differential write



- Do two reads and one write by time multiplexing
 - Read during ph1, write during ph2


Multi-Ported SRAM

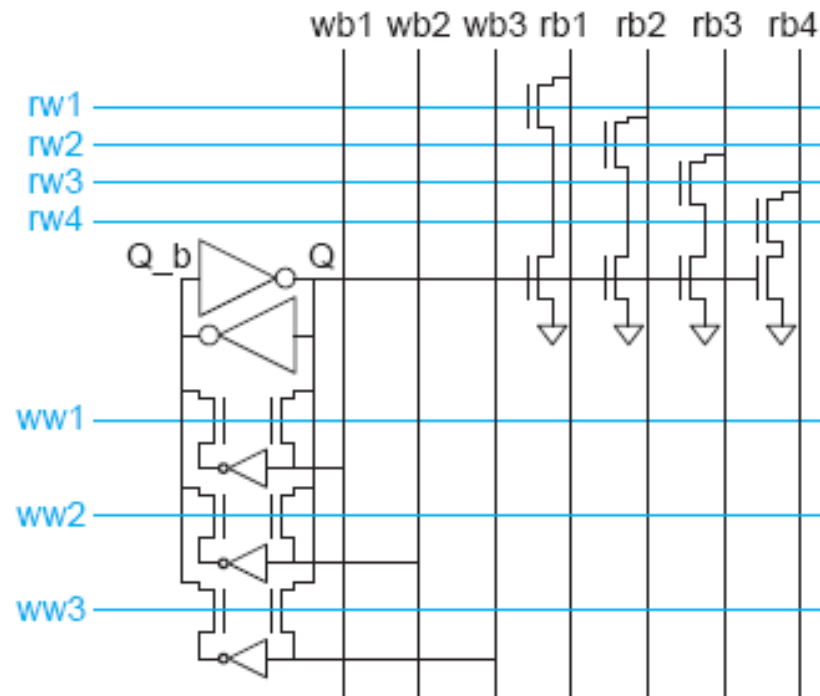- ❑ Adding more access transistors hurts read stability
- ❑ Multiported SRAM isolates reads from state node
- ❑ Single-ended bitlines save area



Large SRAMs


- ❑ Large SRAMs are split into subarrays for speed
- ❑ Ex: UltraSparc 512KB cache
 - 4 128 KB subarrays
 - Each have 16 8KB banks
 - 256 rows x 256 cols / bank
 - 60% subarray area efficiency
 - Also space for tags & control

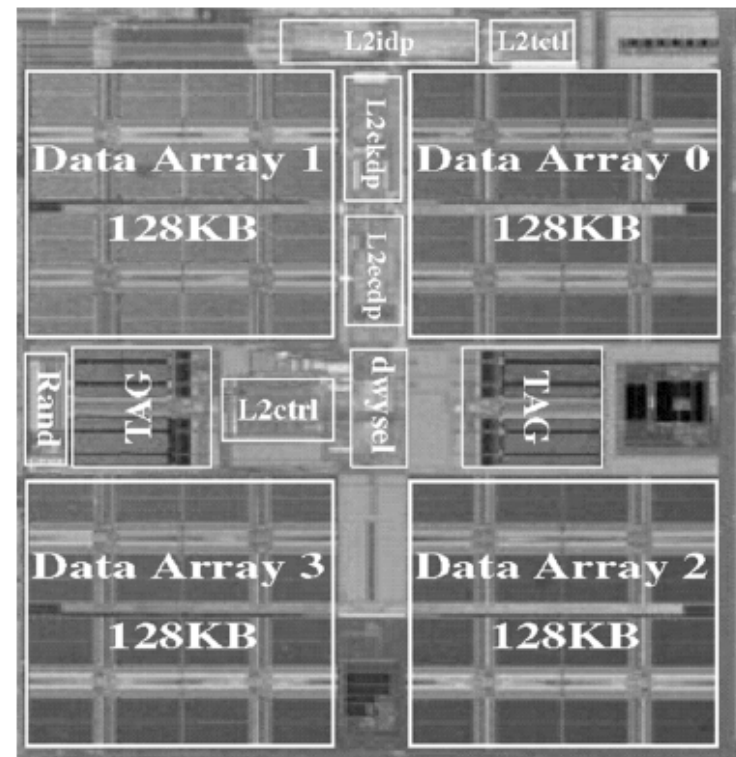

[Shin05]

ROM Example

- 4-word x 6-bit ROM
 - Represented with dot diagram
 - Dots indicate 1's in ROM

 


Word 0: 010101

Word 1: 011001

Word 2: 100101


Word 3: 101010

 

Looks like 6 4-input pseudo-nMOS NORs


ROM Array Layout

 - Unit cell is $12 \times 8 \lambda$ (about 1/10 size of SRAM)




Row Decoders

 - ROM row decoders must pitch-match with ROM
 - Only a single track per word!



Complete ROM Layout

 

References

1. Weste, Harris, "CMOS VLSI Design," 2nd Ed., Addison Wesley.