

# ECE 5/418 PLL and Memory IC Design

## Sample Midterm

Apr 14, 2015

Name: \_\_\_\_\_

Closed Book, Closed Notes, Closed Computer.


Only one page (A4 size, both sides) cheat-sheet allowed.

Show your steps clearly to get credit.

State clearly any assumptions made.

This exam has 3 questions, for a total of 100 points.

 1. Consider an alternative PLL design shown below. Here,  $K_{VCO} = 150 \frac{MHz}{V}$ ,  $I_0 = 100\mu A$ , frequencies  $f_{in} = f_{out} = 500$  MHz, and the delay of each of the elements in the VCDL is given as  $T_D = 1 \frac{ns}{V}$ .



- (a) (10 points) Draw the phase-domain small signal block diagram in steady state.

(b) (10 points) Find the expression for loop gain  $L(s)$  and determine the pole and zero locations.


(c) (10 points) Determine the value of capacitor  $C$  to achieve loop-gain phase-margin of  $45^\circ$ .

(d) (10 points) Derive the expression for closed-loop transfer function  $H_{cl}(s) = \frac{\Phi_{out}}{\Phi_{ref}}$ .

(e) (5 points) Sketch open- and closed-loop Bode magnitude and phase plots for the PLL.

(f) (Bonus 5 points) What is the main difference between the above proportional control and the conventional proportional path using a resistor.

 2. Consider the differential ring oscillator shown below. Assume that all transistors are operating in saturation.




- (a) (10 points) Find the frequency of oscillation  $\omega_{osc}$  if  $R = 1\text{ k}\Omega$  and  $C = 100\text{ fF}$ .

- (b) (10 points) What is the minimum delay-cell transistor transconductance ( $g_{m1}$ ) required for oscillation?

- (c) (10 points) A 5-stage VCO needs to be designed based upon the above schematic. Draw schematic of a delay cell to achieve this with best possible PSRR.

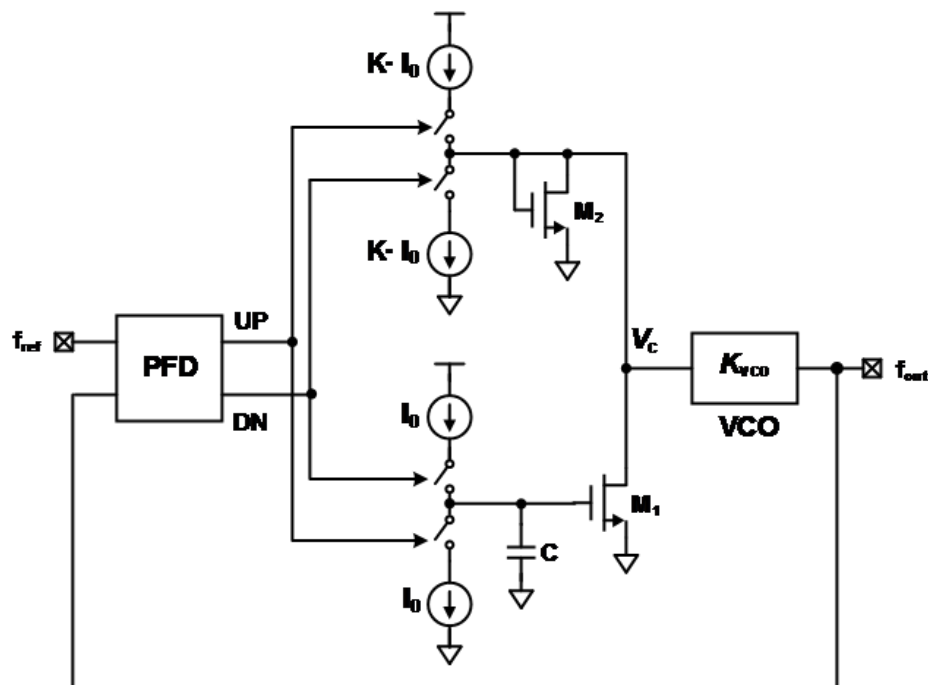3. In the resistor-less PLL shown below, assume that the VCO gain  $K_{VCO}$  is positive, all transistors operate in saturation with output resistance,  $r_o = \infty$ . Ignore the NMOS capacitance.



(a) (5 points) Draw the phase-domain *small-signal* block diagram in steady state.

(b) (5 points) What is the effective loop-filter transfer function,  $F(s) = \frac{V_c(s)}{I_0}$ ?

(c) (5 points) Find the expression for loop gain  $L(s)$  and determine the pole and zero locations.

(d) (5 points) Derive the expression for closed-loop transfer function  $H_{cl}(s) = \frac{\Phi_{out}}{\Phi_{ref}}$ .

(e) (5 points) In order to minimize the loop filter area, should  $K$  be minimized or maximized? Why?