
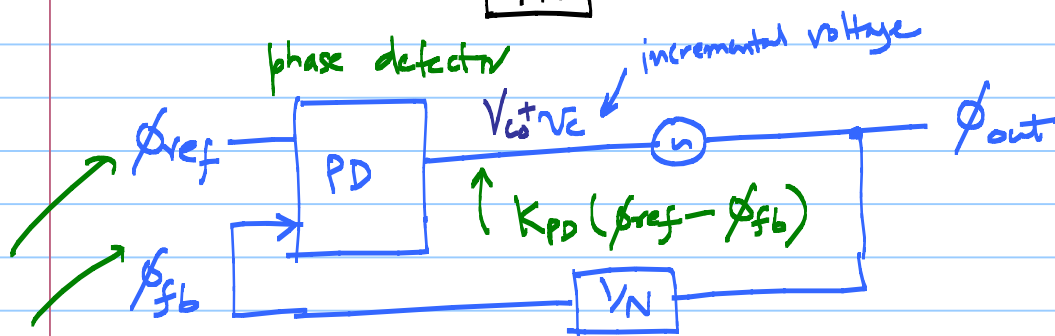


ECE 518- Lecture 10

Note Title


2/21/2013

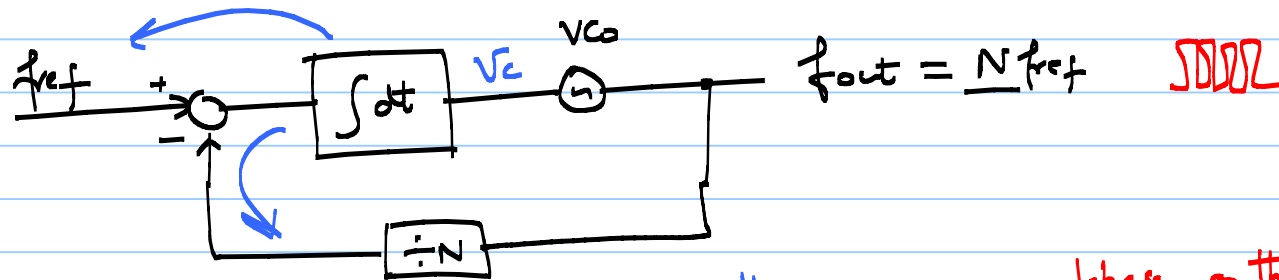

phase as the primary variable




* initially

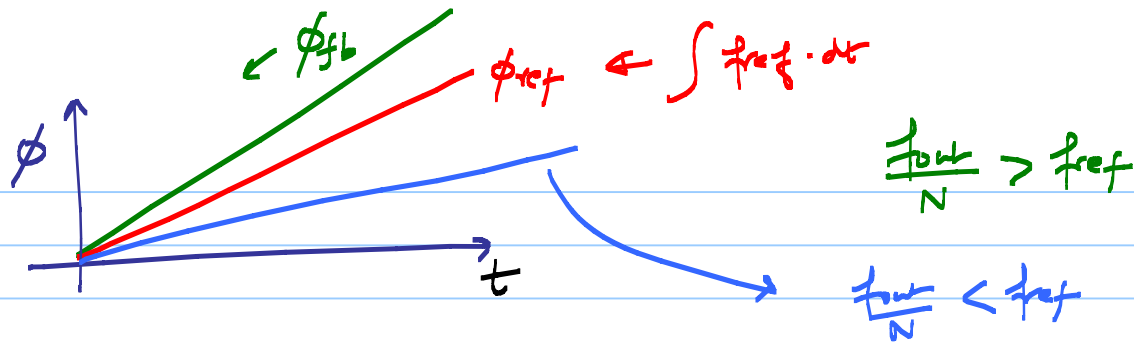

In steady-state,

$v_c \rightarrow$ becomes constant

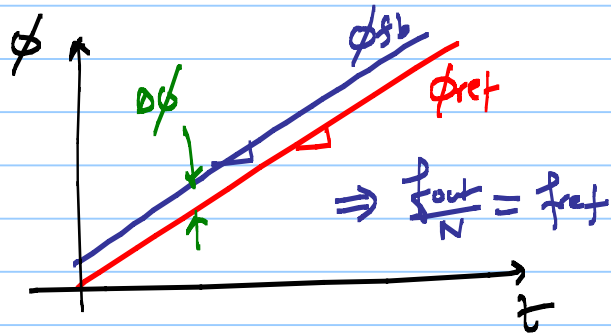When both ϕ_{ref} & ϕ_{fb} have the same slope





$\rightarrow$ they can have a constant offset

$\rightarrow$ But the $\Delta f = 0$


both the f_{ref} & feedback f_{out} are same
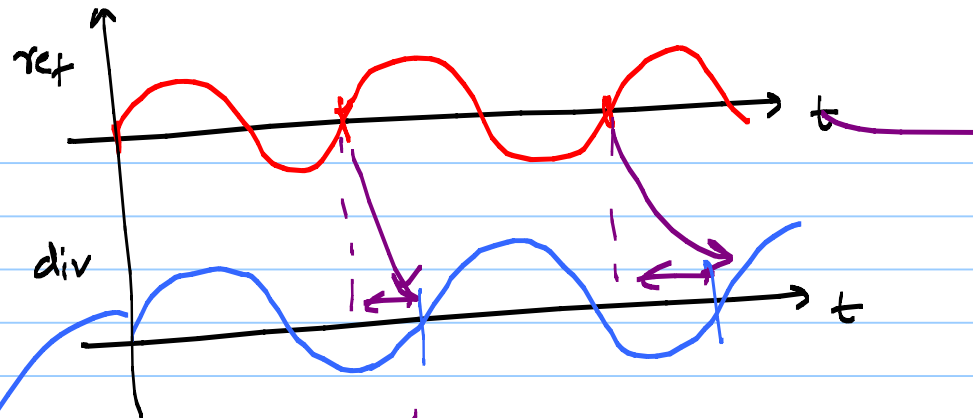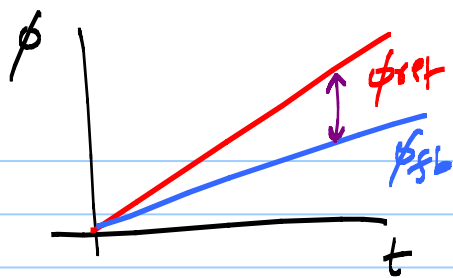
$$\Rightarrow f_{ref} = \frac{f_{out}}{N} \Rightarrow f_{out} = N f_{ref}$$



for $f_{ref} \neq \frac{f_{osc}}{N}$
 the phase difference will grow.
 the cycles are longer

"Phase locked loop"

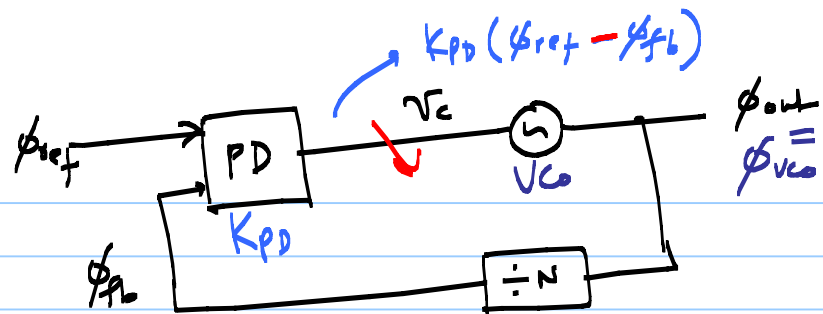

$$f_{VCO} = \underbrace{f_0}_{\text{free running frequency}} + K_{VCO} \cdot v_c$$

$$N f_{ref} > f_0 \\ v_c > 0$$

In steady-state:

$$v_c = \frac{N f_{ref} - \underbrace{f_0}_{\text{free running}}}{K_{VCO}}$$

→ ①

* Back-calculate the phase difference ($\Delta\phi = \phi_{ref} - \phi_{fb}$)

$$\phi_{ref} - \phi_{fb} = \Delta\phi = \frac{N f_{ref} - f_0}{K_{VCO} \cdot K_{PD}}$$

→ ②

Phase Detector:
gain

VCO gain

$$K_{PD} \Rightarrow \frac{V}{\text{rad}}$$

$$K_{VCO} \Rightarrow \frac{\text{Hz}}{V}$$

units are important
"2 π factor"

Phase Detector

V_c ← average output value of PD

K_{PD}

linear region



$$\phi_{ref} - \phi_{fb} = \Delta\phi$$

phase difference is inherently modulo 2π

$$\Delta\phi \in \{-\pi, \pi\}$$

* In the steady-state, we want to operate in the linear region
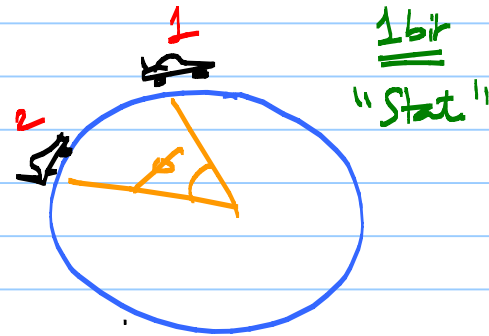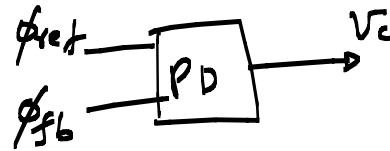
$$\Rightarrow -\pi < \Delta\phi < \pi \longrightarrow \textcircled{3}$$



⇒ If we don't keep track of the "half" cycles

↳ Can only detect 2π phase difference

from ② 4 ③

$$\underbrace{\Delta\phi}_{\text{phase error}} = \frac{N_{\text{ref}} - f_0}{K_{\text{VCO}} \cdot K_{\text{PD}}} < \pi$$

⇒



$$-\pi K_{\text{VCO}} \cdot K_{\text{PD}} < N_{\text{ref}} - f_0 < \pi K_{\text{VCO}} \cdot K_{\text{PD}} \rightarrow \textcircled{4}$$

$$\underbrace{|N_{\text{ref}} - f_0|}_{\substack{\text{fout} \\ \text{free running}}} < \underbrace{\pi K_{\text{VCO}} \cdot K_{\text{PD}}}_{\text{related to the loop-gain}}$$

output frequency range


related to the loop-gain
→ problems?
"Later"

XOR PD

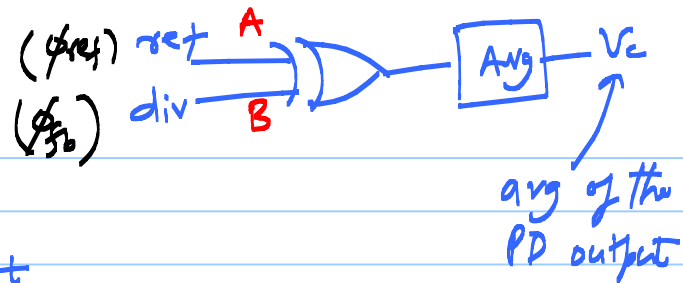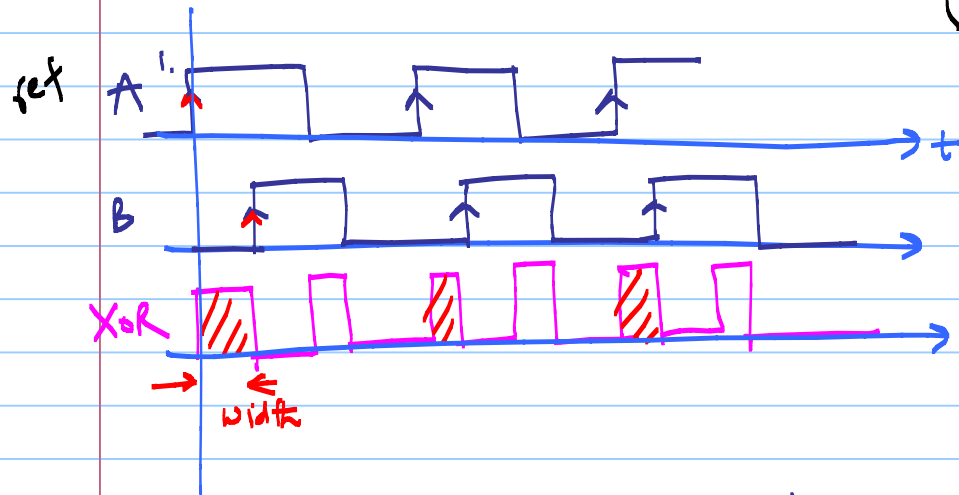

$\Delta\phi = 0$ avg = 0


$\Delta\phi = \pi$ avg = 1

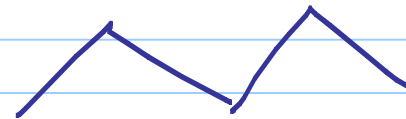


* Level sensitive

$\Rightarrow$ PD should be sensitive only to the rising edges

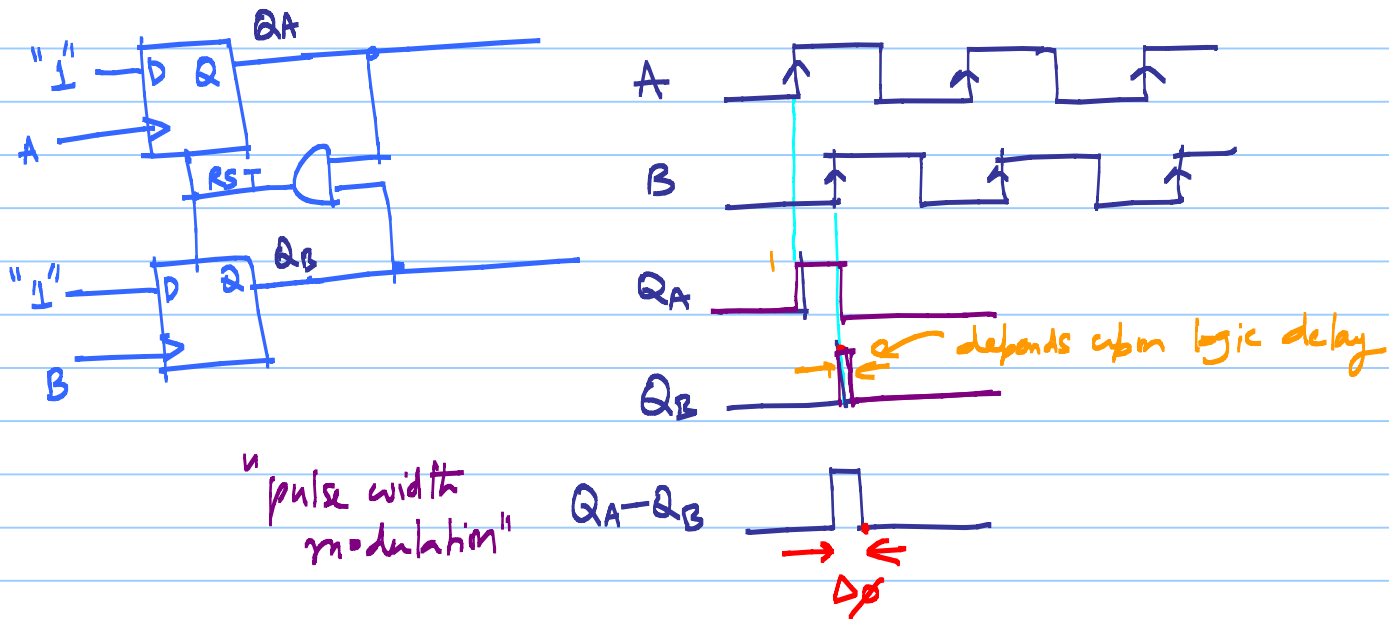We desire a PD = $\begin{cases} +ve \text{ arg output when A rises earlier than B} \\ -ve \text{ output when A rises later than B} \end{cases}$



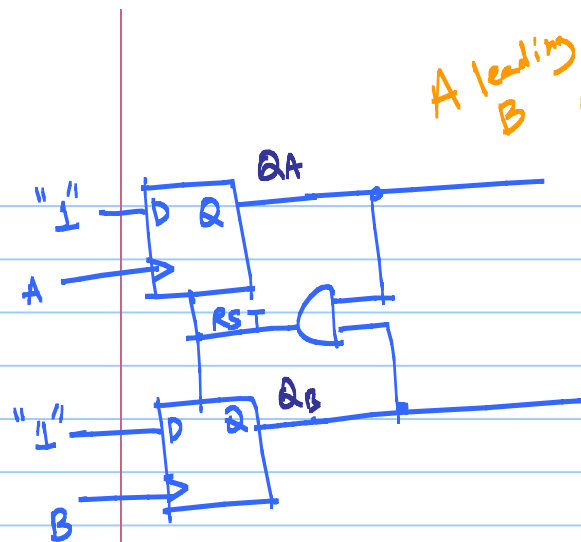

A leading B

