

 


ECE 518 - Lecture 11

Note Title


2/26/2013

 


 


$\text{avg}(Q_A - Q_B) = +\frac{V_{PD}}{2}$

 $\Delta\phi = -\pi$
 $\text{avg}(Q_A - Q_B) = -\frac{V_{PD}}{2}$



 

* PFD Input/output Characteristics

 

* Asymmetry about the origin

* Hysteresis



State Machine

[Q_A Q_B]

Tri-state Phase Detector

↳ insensitive to duty cycle

rising edge

  


if reset is fast

A↑ ⇒ move rightwards

B↑ ⇒ move leftwards

if A & B have same frequency

 

* $f_A > f_B$

↳ more A↑ than B↑

⇒ PFD will circulate


00 & 10

and often between

10 to 10

output average > 0

⇒ $A_{avg} (Q_A - Q_D) > 0$

 

* opposite will happen for $f_A < f_B$

output average will be negative

* This PFD also gives frequency detection

* if the PLL output starts at a $f_{out} \neq f_{ref}$

↳ PFD will push the PLL in one direction


* PFD is better for frequency "locking"

"PLL terminology"

Locking → for what frequency range the PLL remains locked

Capture → Apply some frequency and see if the PLL can lock
→ PFD facilitates ~ faster capture




PFD output

 



need a
 $|\Delta\phi| > 0$
 periodic error

   $f_{out} > f_0$
 Type-I PLL
 $\hookrightarrow$ # of poles at DC



Frequency content of this periodic error

↳

f_{ref} , $3f_{ref}$, $5f_{ref}$

