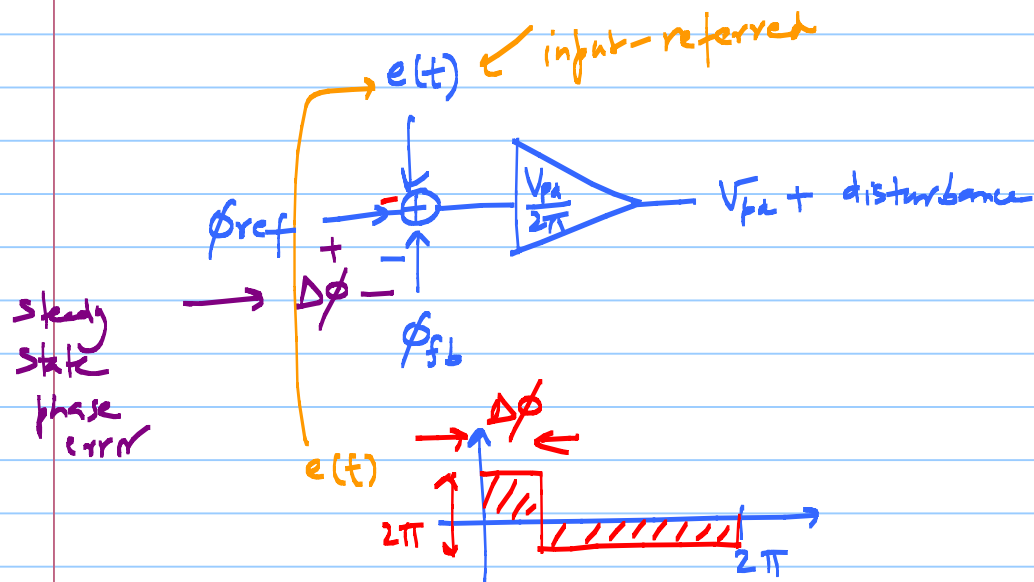


ECE 518 - Lecture 12


Note Title

2/28/2013



Skip dc

in transient
sim

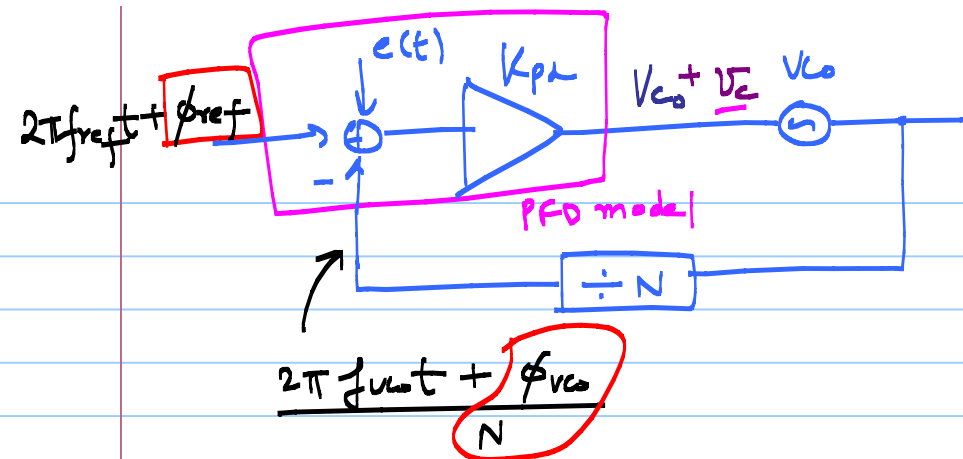



$$2\pi f_o t + \Phi_{vco} + \phi_{vco}(t)$$

output phase


* The loop has been operating in steady-state around an operating point

$\Rightarrow$ Draw the incremental (small-signal) phase equivalent circuit for this PLL


Incremental VCO Model

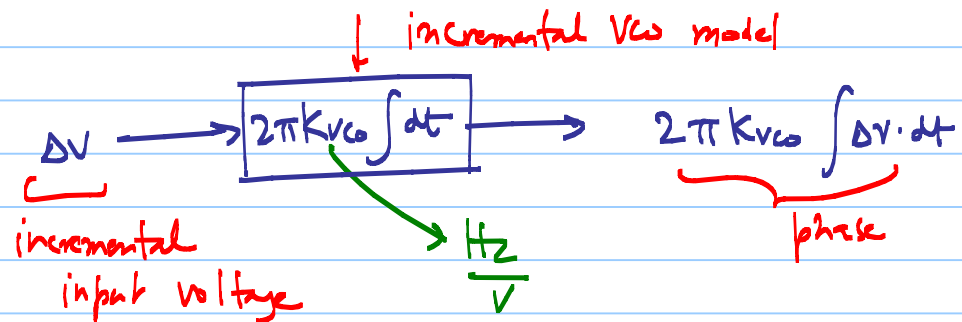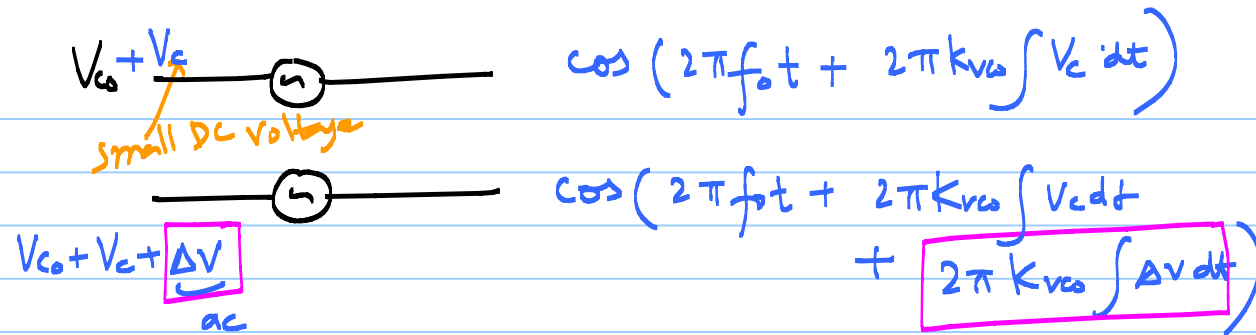

Laplace

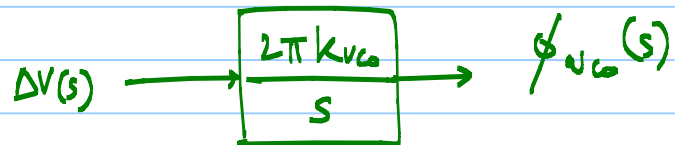


Incremental Model for the Type-I PLL

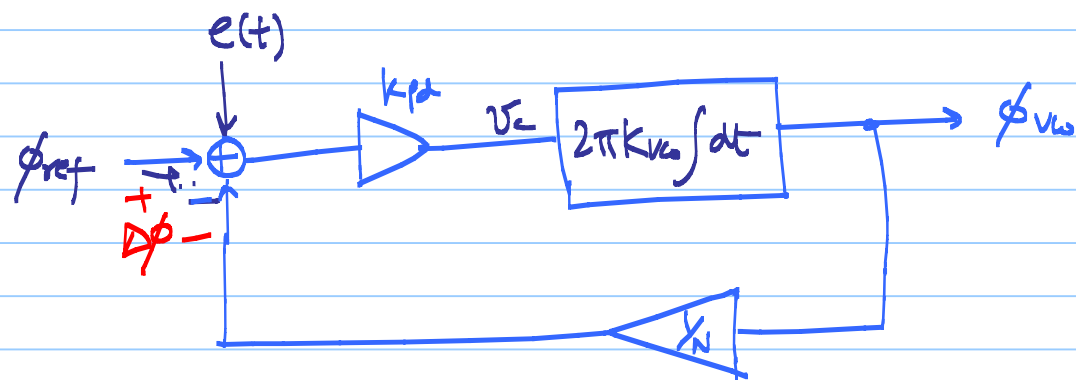

$e(t)$ depends on $\Delta\phi$

Laplace domain Model


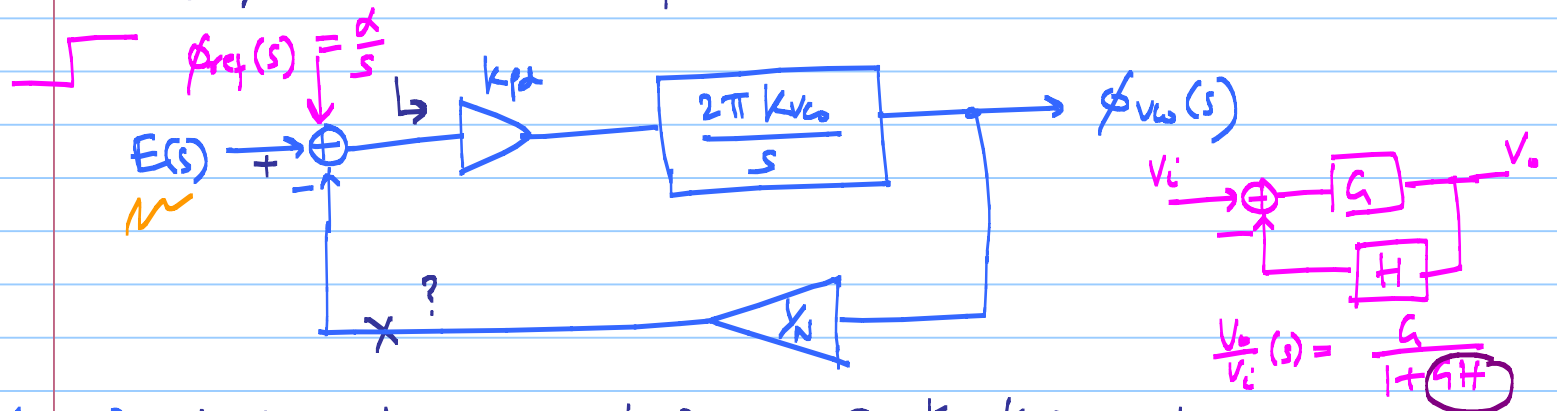


(open) Loop response = $L(s) = \frac{2\pi K_{pd} K_{vco}}{N} \cdot \frac{1}{s}$ ←

$= \frac{\omega_{u,loop}}{s}$


$$\frac{\phi_{vco}(s)}{E(s)} = \frac{N}{1 + \frac{s \cdot N}{2\pi K_{vco} \cdot K_{pd}}}$$

first-order response

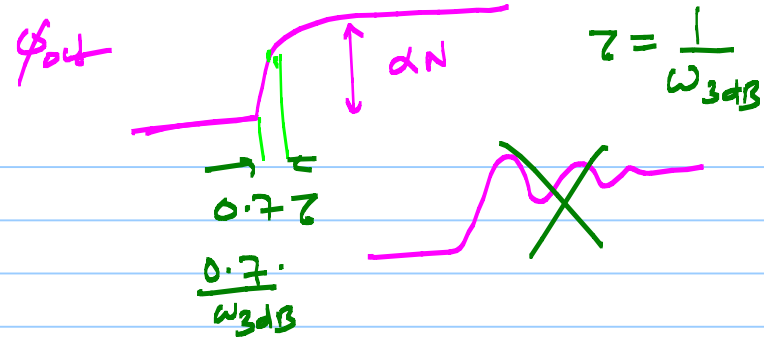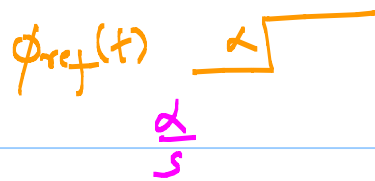

Type_n of a system

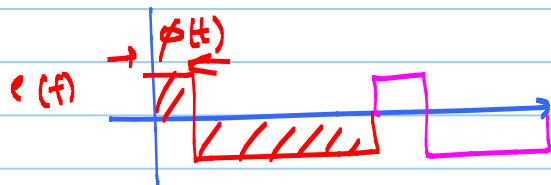
$\Rightarrow$ Loop response has # poles at DC




periodic $\Rightarrow 2\pi \cdot f_{ref} \Rightarrow \omega_{ref}$

$$T_{ref} = \frac{1}{f_{ref}}$$

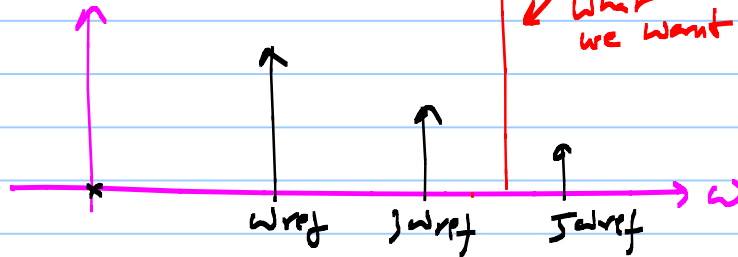$N \omega_{ref}$
 $\nwarrow$ what we want



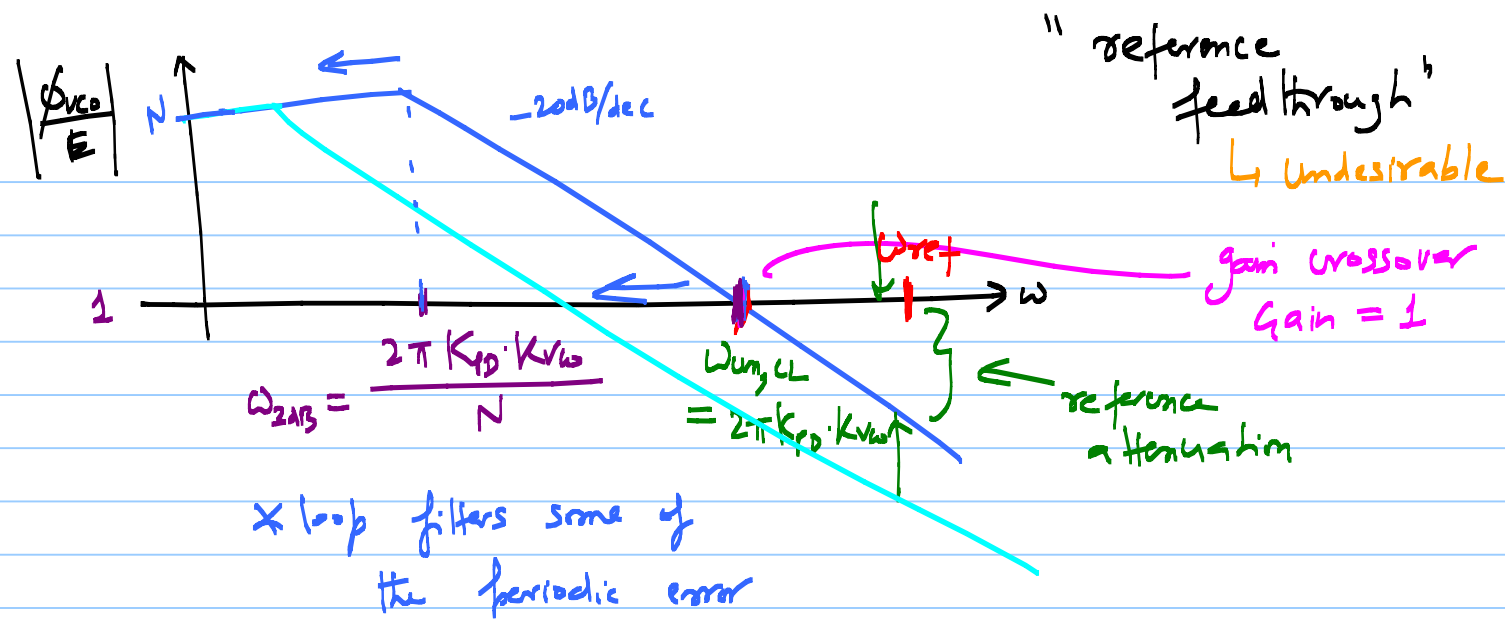

* To reduce disturbances in the o/p due to the periodic nature of the phase error

$$\boxed{\omega_{ref} \gg 2\pi K_{p0} \cdot K_{vco}} \rightarrow \textcircled{2}$$

* Constraint on the range

$$2\pi |N f_{ref} - f_o| < 2\pi K_{PD} \cdot K_{VCO} \longrightarrow \textcircled{1}$$

$$f_{ref} \gg K_{PD} \cdot K_{VCO} \longrightarrow \textcircled{2}$$

Linear region of the
PFD

$$|N f_{ref} - f_o| < K_{PD} \cdot K_{VCO} \ll f_{ref}$$

$$|N f_{ref} - f_o| \ll f_{ref}$$


$$|N f_{ref} - f_o| < \frac{f_{ref}}{10}$$

$$f_o - \frac{f_{ref}}{10} \leq f_{out} \leq f_o + \frac{f_{ref}}{10}$$

Very small tuning range


"Type-I is totally useless."

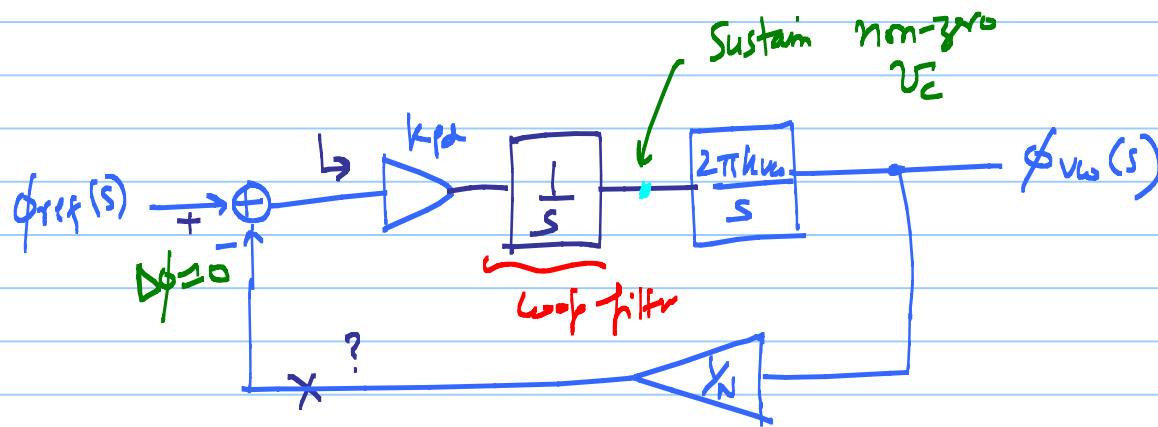Solution $\Rightarrow$ Type-II PLL $\Rightarrow$ Add a loop filter
"integrating controller"



$\Rightarrow$ 2nd-order system (Type-II)

Feedback System Review Contd.

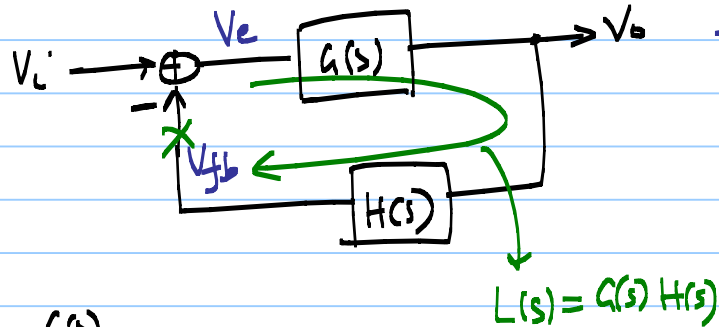


$$\frac{V_o(s)}{V_i(s)} = \frac{G(s)}{1 + G(s)H(s)}$$

$$= \frac{1}{H(s)} \cdot \frac{1}{1 + \frac{1}{G(s)H(s)}}$$

$$= \begin{cases} \frac{1}{H(s)} & \text{for } |GH| \gg 1 \\ G(s) & \text{for } |GH| \ll 1 \end{cases}$$

feedback breaks down

feedback amplifier

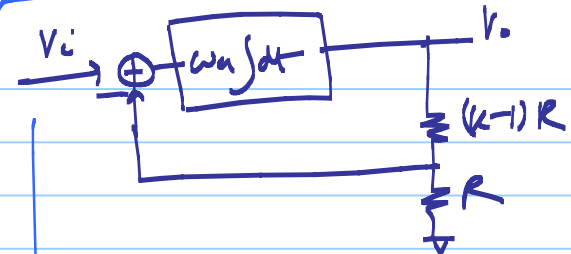


$$G(s) = \frac{\omega_n}{s}$$

$$H(s) = \frac{1}{k}$$

$$\frac{V_o}{V_i}(s) = k \cdot \frac{1}{1 + \frac{1}{\frac{\omega_n}{sk}}}$$
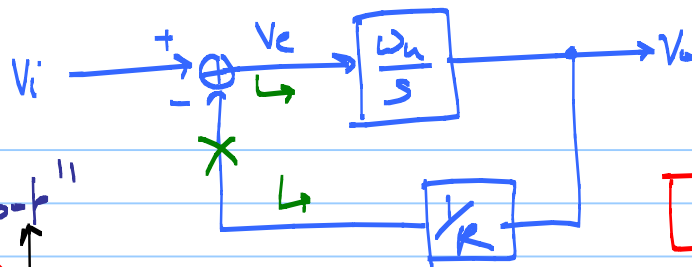
$$(\text{open}) \text{ Loop-gain} = L(s) = G(s)H(s)$$





$\omega_n \Rightarrow$ unity gain frequency for the integrator

$$L(s) = \frac{\omega_n}{s \cdot R}$$

$$R=4$$

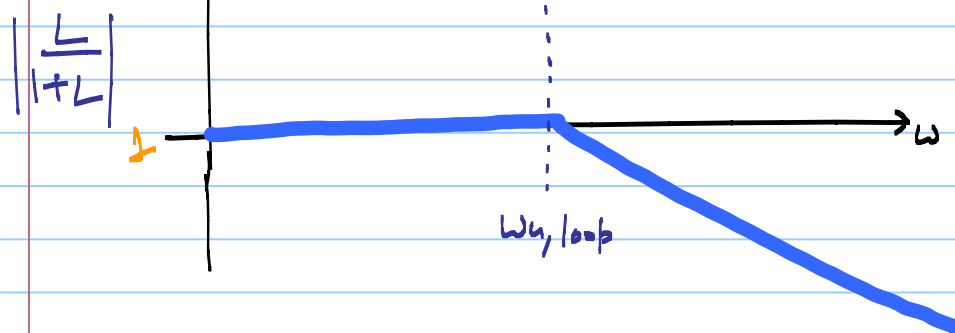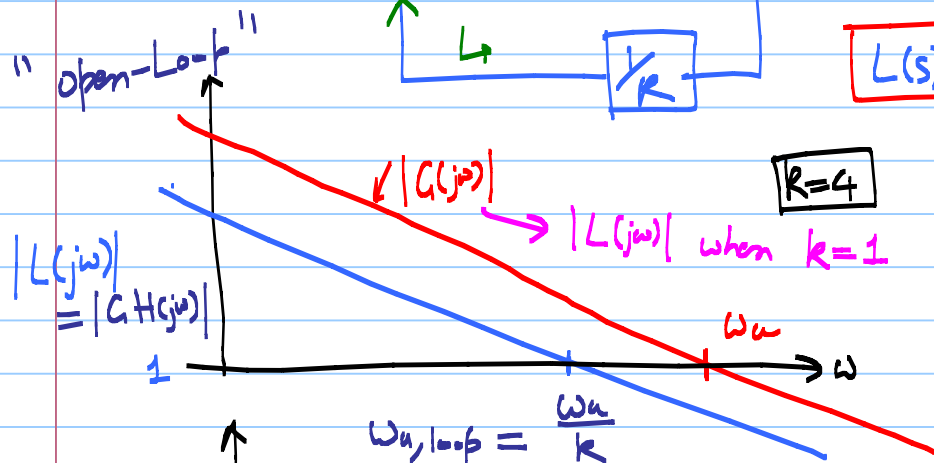$\omega_{n,loop} \Rightarrow$ UGF of the open loop



$\leftarrow$ divide by $H(s)$
 $\Rightarrow$ multiply by '1'

"closed-loop response"




In this 1st order example

$$\times \quad \omega_{u,loop} = \frac{\omega_n}{k}$$

$$\times \quad \omega_{3dB} = \omega_{u,loop} = \frac{\omega_n}{k}$$

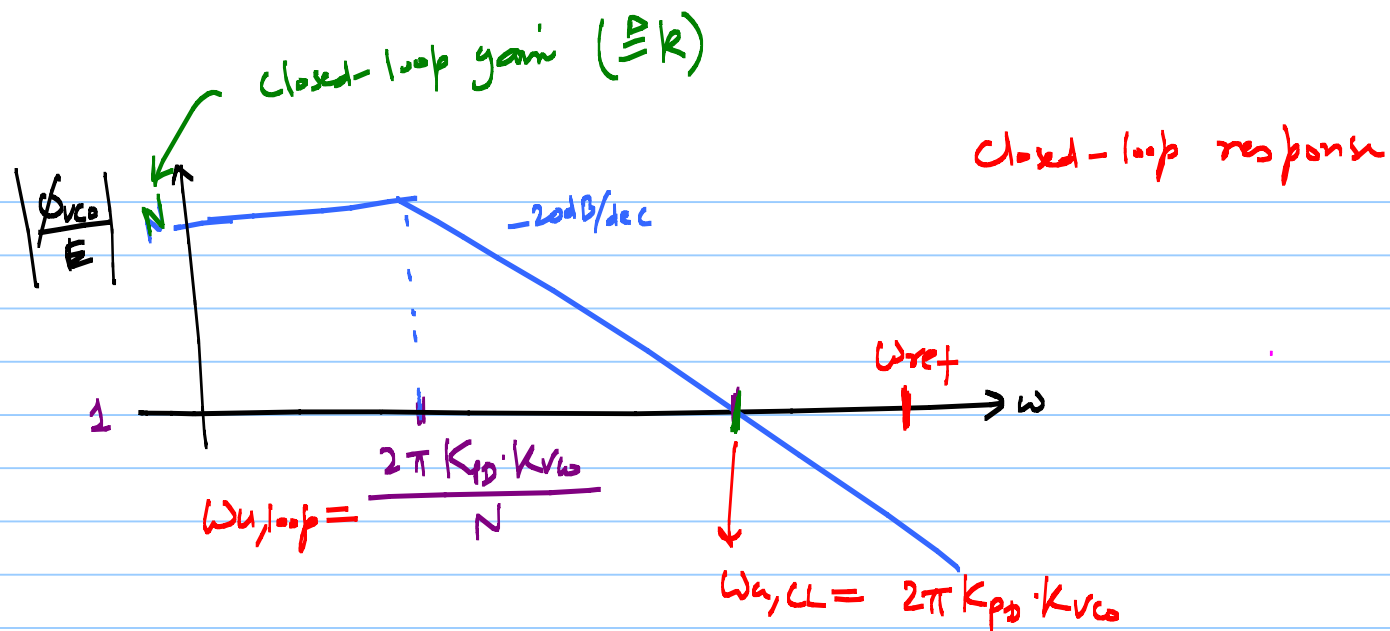$\rightarrow$ is the USF of $G(s) + (s)$
 $\times$ NOT $G(s)$



To filter ω_{ref} periodic disturbance

$\Rightarrow$ Need very small loop-bandwidth

$\hookrightarrow$ poor tuning range.