
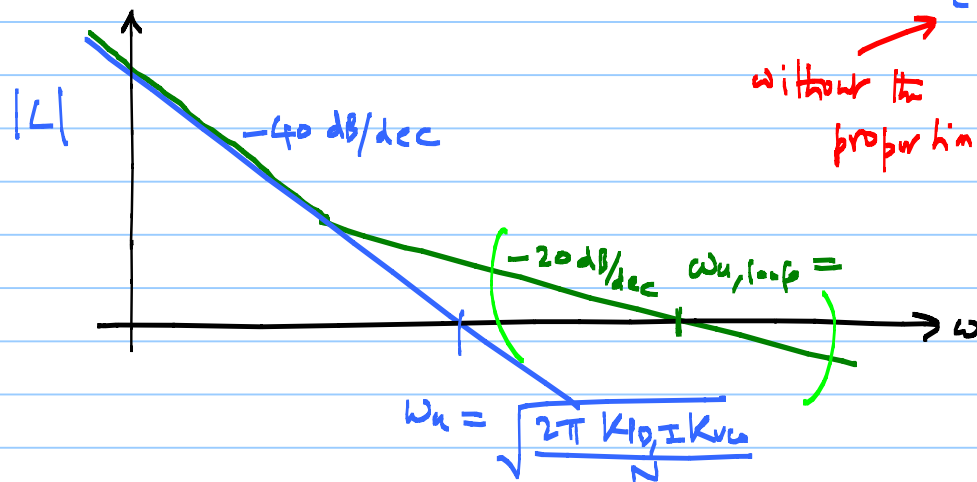


ECE 518 - Lecture 14

Note Title


3/7/2013

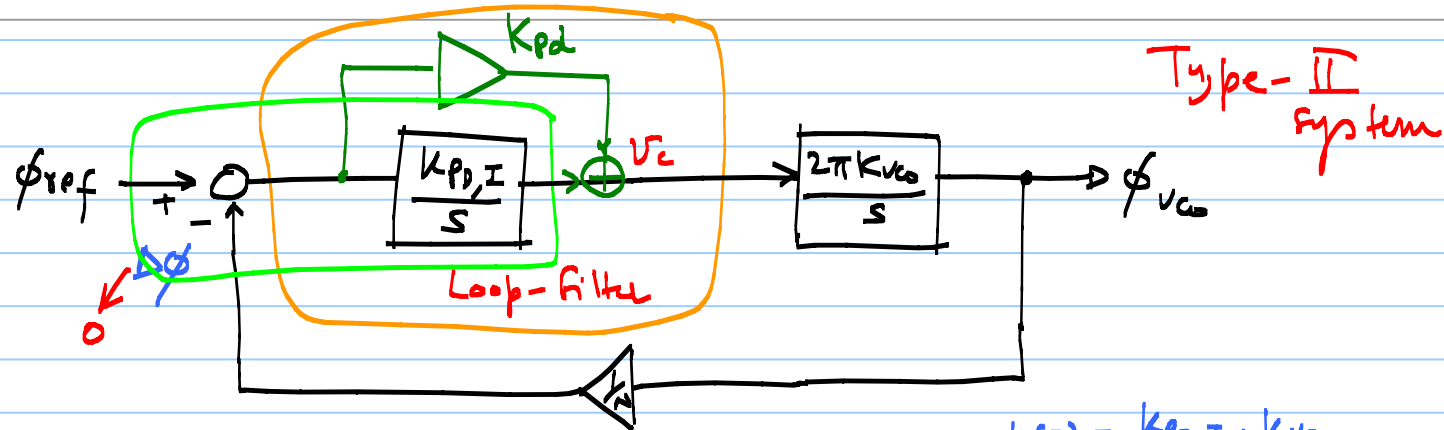

$$L(s) = \frac{2\pi K_{p,I} \cdot K_{vc}}{s^2 N}$$

without the
proportional path

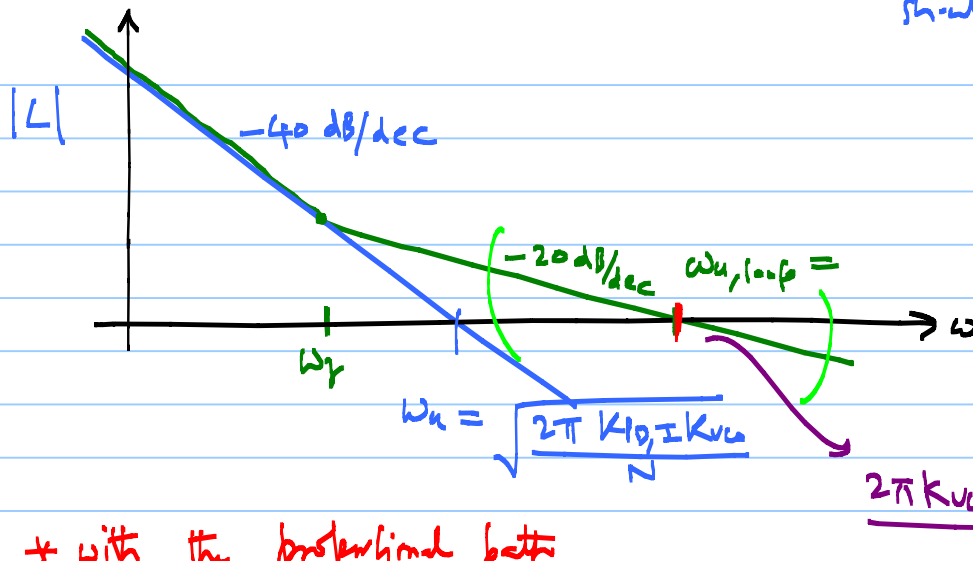* around $\omega_{u,loop}$ the system should look like -20dB/dec



* 2 poles @ DC
 * one zero earlier to $\omega_{u,loop}$
 "Type-II system"

order $\neq$ Type

$$\frac{2\pi K_{vo} \cdot k_{PD}}{N}$$

* with the proportional path

$$\begin{aligned}
 L(s) &= \left[k_{PD} + \frac{k_{PD,I}}{s} \right] \cdot \frac{2\pi k_{vo}}{s} \cdot \frac{1}{N} \\
 &= \frac{2\pi K_{vo} k_{PD,I}}{N} \cdot \frac{\left(1 + \frac{s k_{PD}}{k_{PD,I}} \right)}{s^2}
 \end{aligned}$$

@ LHP

$$1 + \frac{s}{\omega_z}$$

$$\Rightarrow \omega_z = \frac{k_{PD,I}}{k_{PD}}$$

$$= \frac{2\pi K_{v\omega} \cdot K_{PD,I}}{N} \cdot \frac{\left(1 + \frac{s}{\omega_z}\right)}{s^2}$$

around $\omega = \omega_{u,loop}$

$$1 + \frac{s}{\omega_z} \quad s \quad \frac{s}{\omega_z}$$

$\sqrt{1 + \left(\frac{\omega}{\omega_z}\right)^2}$


$$L(s) \approx \frac{2\pi K_{v\omega} K_{PD,I}}{N} \cdot \frac{s}{\left(\frac{K_{PD,I}}{K_{PD}}\right) s^2}$$

$$L(s) \approx \frac{2\pi K_{v\omega} \cdot K_{PD}}{N \omega_z} \cdot \frac{1}{s}$$


$$\omega_{u,loop} = \frac{2\pi K_{v\omega} \cdot K_{PD}}{N}$$

$$|L(s)| = \left| \frac{2\pi K_{vco} K_{PD,I}}{N} \frac{\left(1 + \frac{sK_{ra}}{K_{PD,I}}\right)}{s^2} \right| = 1 \quad s \rightarrow j\omega$$
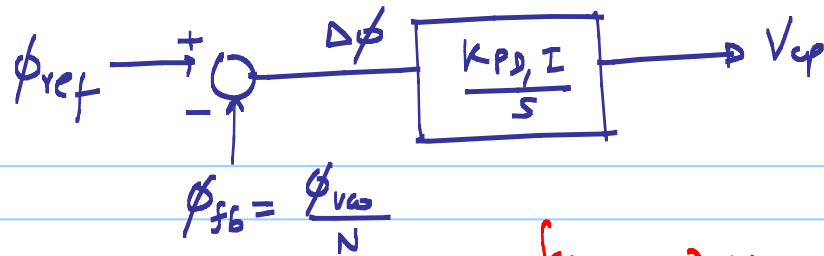
$$\Rightarrow \omega_{u,loop} = \frac{2\pi K_{vco} \cdot K_{PD}}{N}$$





$$\int (Q_A - Q_B) dt$$

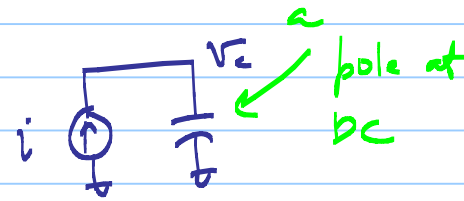


$$V_c = \frac{1}{C} \int i(t) \cdot dt$$



$$V_c(s) = \frac{1}{sC} I(s)$$

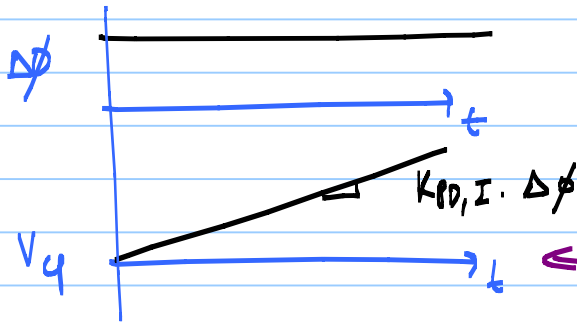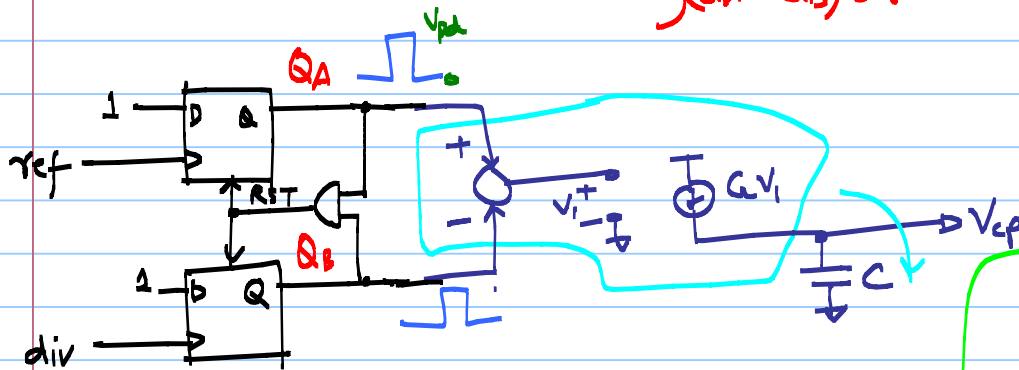

integration is CT

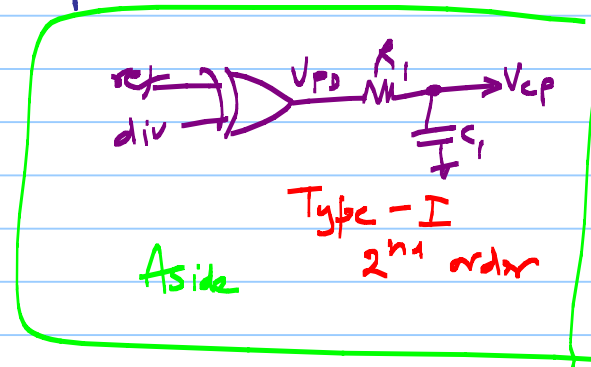

Charge Pump topology

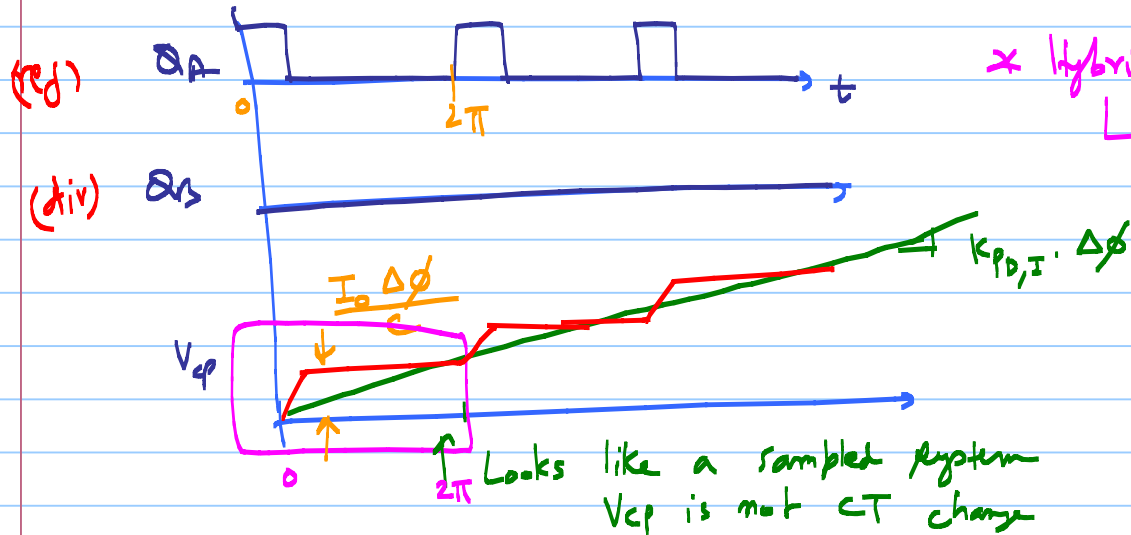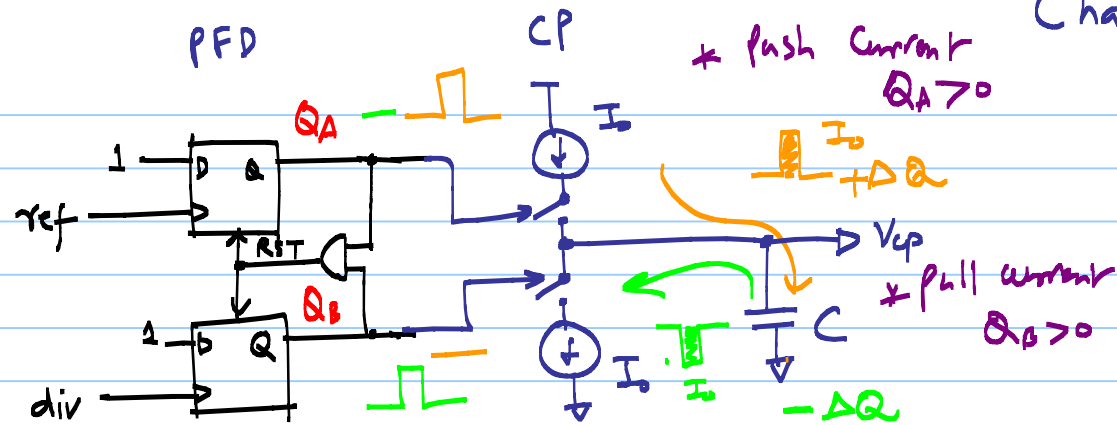


* We can approximate this system as a CT system for analysis as long as $\omega_{n,loop} \ll \omega_{ref}$

$$\omega_{n,loop} \leq \frac{\omega_{ref}}{10}$$

↑ effective rate of DT sampling

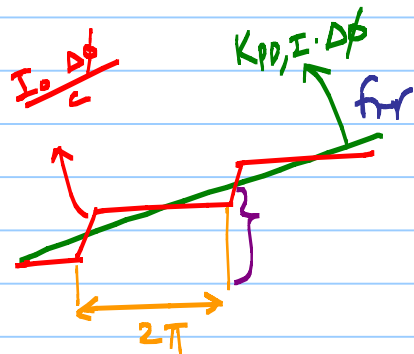
⇒ the PLL response is much slower than the frequency of phase detection (sampling)





$$\omega_{n,loop} < \frac{\omega_{ref}}{10}$$

$$K_{PD,I} \cdot \Delta\phi \cdot 2\pi = \frac{I_o \Delta\phi}{C} \Leftrightarrow V_{ref} \text{ step height}$$

$$K_{PD,I} = \frac{I_o}{2\pi C}$$

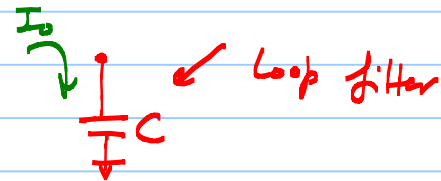


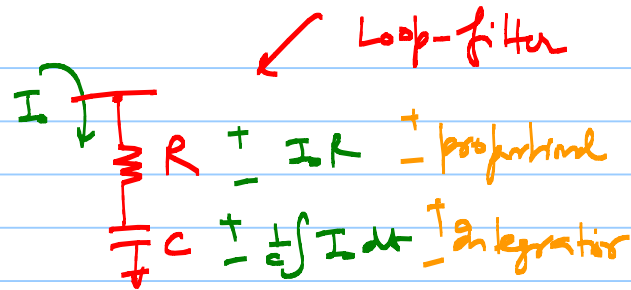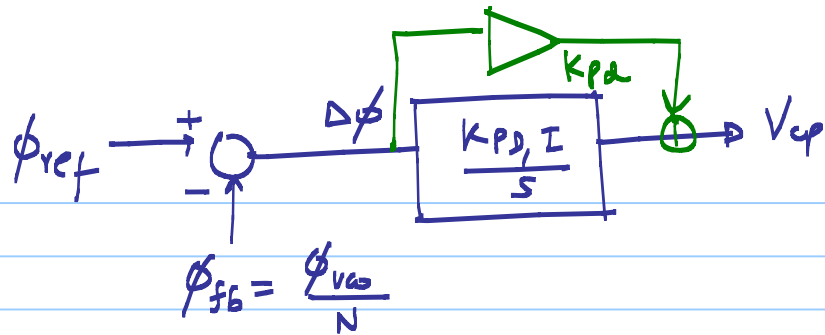

$$K_{PD} = \frac{I_0 R}{2\pi}$$

same explanation as

$$K_{PD,I} = \frac{I_0}{2\pi C}$$

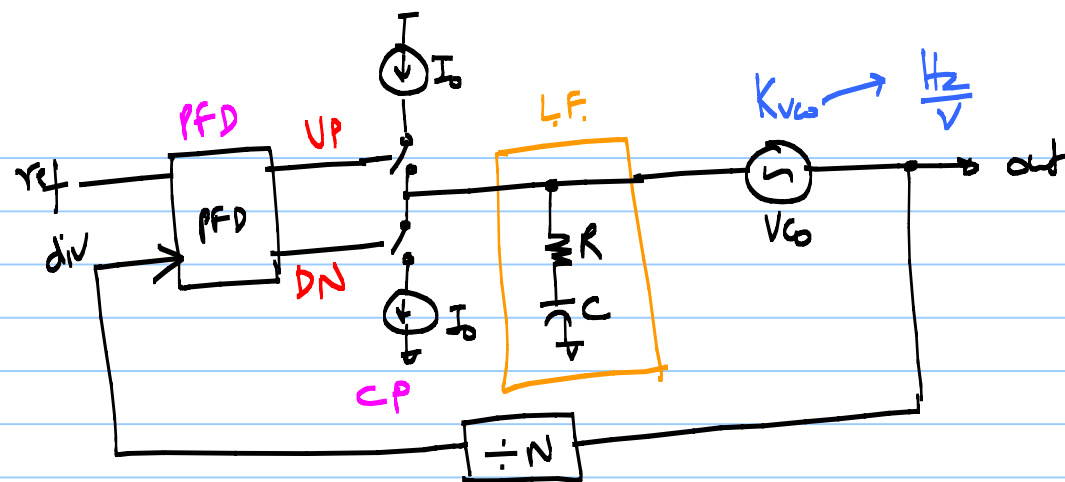

Charge Pump PLL

UP $\Rightarrow$ increase V_{co}
frequency

DN $\Rightarrow$ decrement V_{co}
frequency