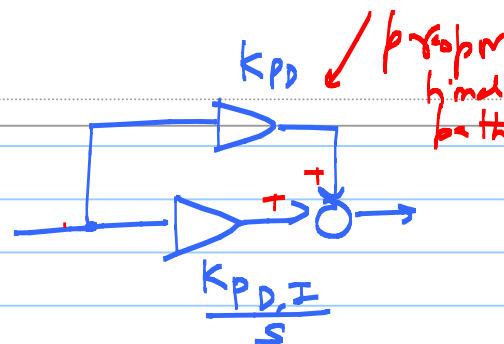


ECE 518- Lecture 15

Note Title

3/12/2013

$$L(s) = \frac{2\pi K_{VCO}}{N \cdot s} \left[\overset{I}{\frac{k_{PD,I}}{s}} + \overset{P}{k_{PD}} \right]$$



Find $|L(j\omega)| = 1$

where

$$\Rightarrow L(s) = \frac{2\pi K_{VCO}}{N \cdot s} \frac{k_{PD,I}}{s} \left[1 + \frac{s k_{PD}}{k_{PD,I}} \right]$$

$$\approx \frac{2\pi K_{VCO}}{N} \frac{k_{PD,I}}{s^2} \cdot \frac{s k_{PD}}{k_{PD,I}} \quad \text{around GX point}$$


$$= \left| \frac{2\pi K_{VCO} k_{PD}}{N s} \right| = 1$$

$$\Rightarrow \omega_{u,loop} \approx \frac{2\pi K_{VCO} \cdot k_{PD}}{N}$$

unity loop-gain frequency


Similar to the Type I PLL
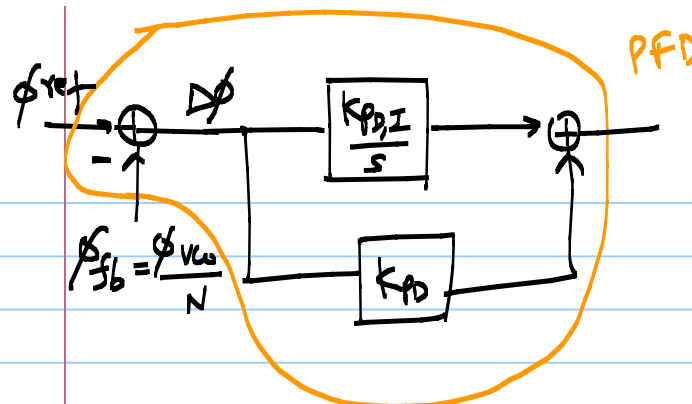
$$\left(1 + \frac{s}{\omega_z} \right) \approx \frac{s}{\omega_z} \rightarrow \frac{k_{PD,I}}{k_{PD}}$$




Phase-domain
incremental model

PFD + CP $\rightarrow$ Loop-filter

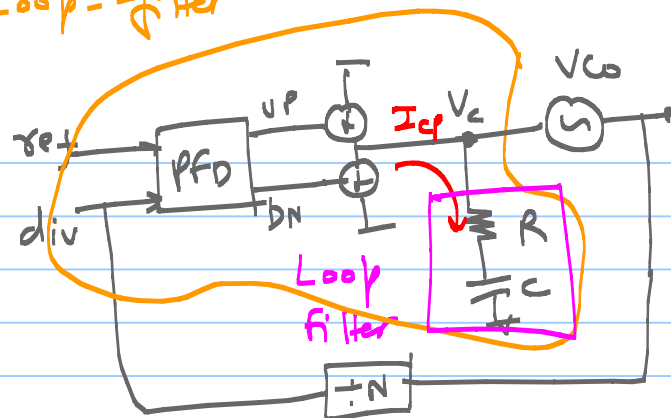

Circuit-level schematic

Type-II PLL

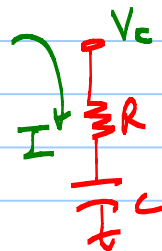

$$Z(s) = R + \frac{1}{sC}$$

$$K_{PD,I} = \frac{I_0}{2\pi C}$$

$$K_{PD} = \frac{I_0 R}{2\pi}$$

$\Delta\phi \Rightarrow$ jump in the o/p frequency

$$\Delta\phi \cdot \frac{I_o R}{2\pi} \cdot \cancel{2\pi} K_{v\omega}$$

θ_A 


θ_B 

I_{cp} 

$\Rightarrow$ jump in the divider frequency

$$\Delta\phi \left[\frac{I_o R K_{v\omega}}{N} \right]$$

$\omega_{u,loop}$

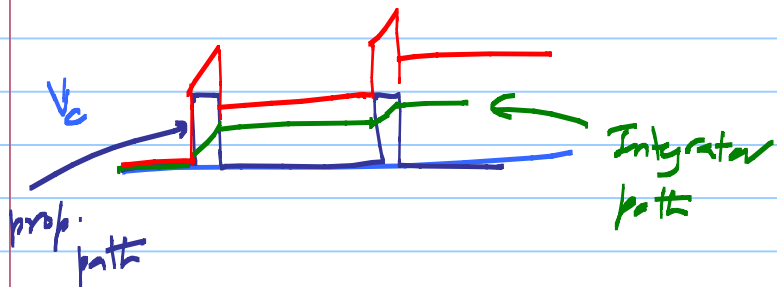

$$\omega_{u,loop} = \frac{2\pi K_{v\omega} \cdot K_{ID}}{N} \quad \leftarrow \frac{I_o R}{2\pi}$$


$$= \frac{\cancel{2\pi} K_{v\omega} I_o R}{\cancel{2\pi} N}$$

"Note 2π factor cancellation"

$K_{v\omega} \rightarrow \frac{Hz}{V}$

$$\omega_{u,loop} = \frac{K_{v\omega} \cdot I_o R}{N}$$



$$\frac{L}{1+L} = \begin{cases} 1, & |L| \gg 1 \\ |L|, & |L| \ll 1 \end{cases}$$

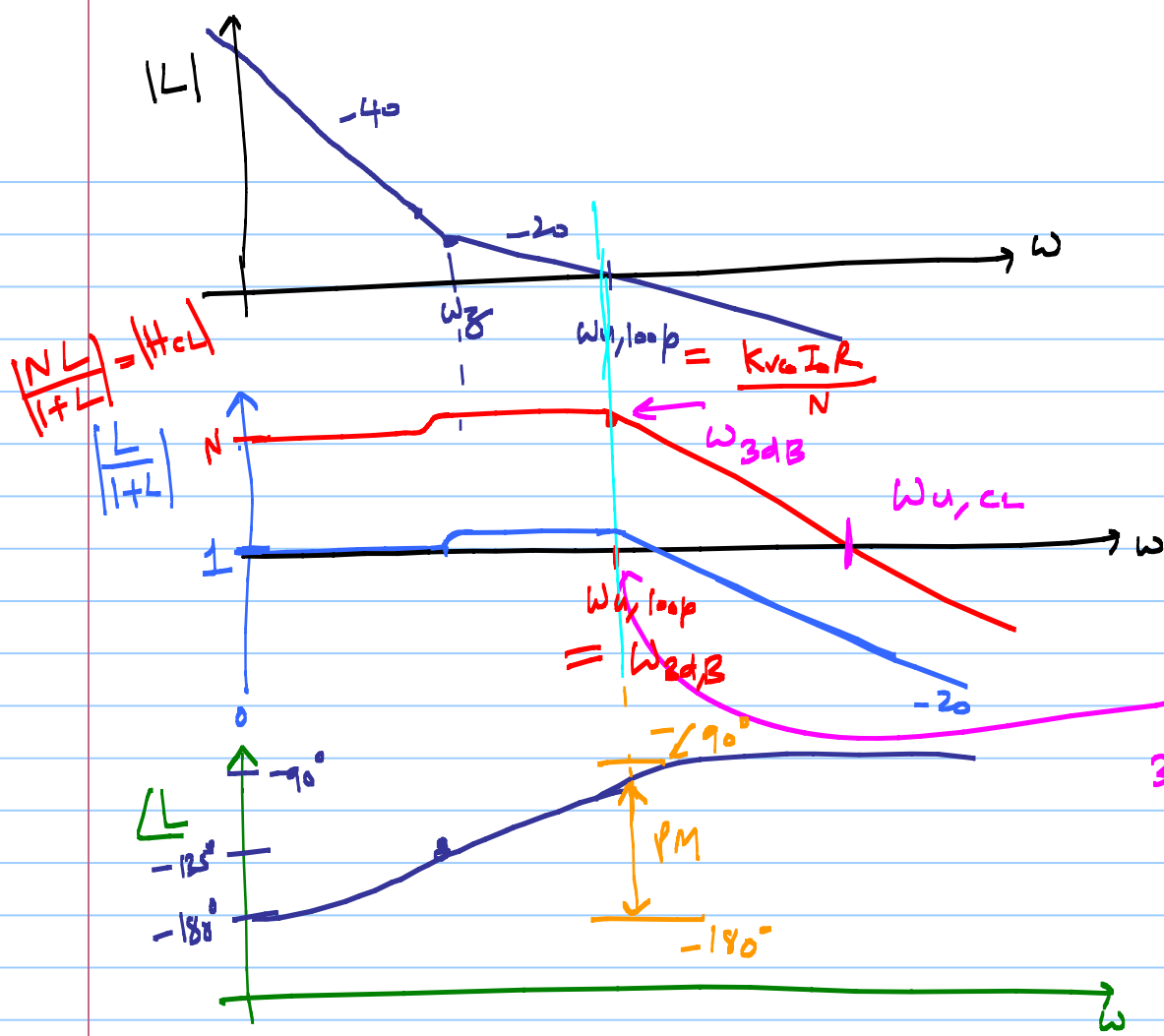


loop bandwidth
 3dB BW of the
 closed-loop

$$\omega_z = \frac{K_{PD,I}}{K_{PD}} = \frac{\frac{I_o}{2\pi C}}{\frac{I_o R}{2\pi}} = \frac{1}{RC}$$

LNA

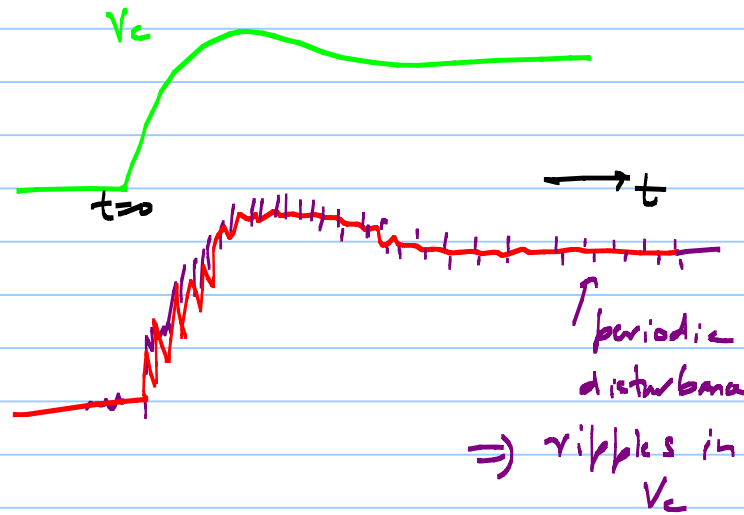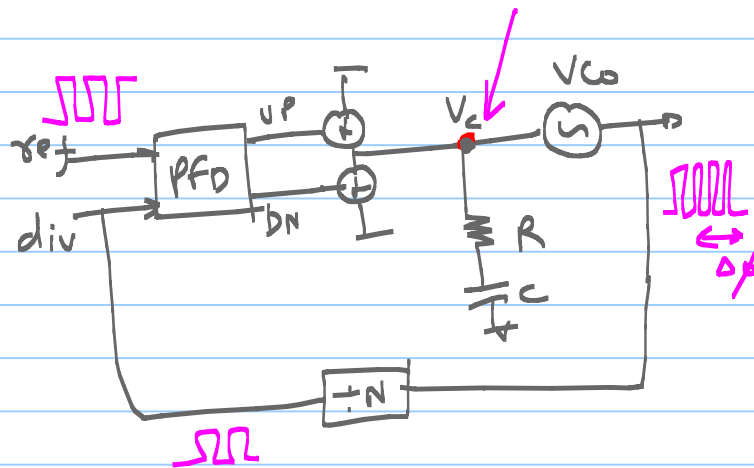

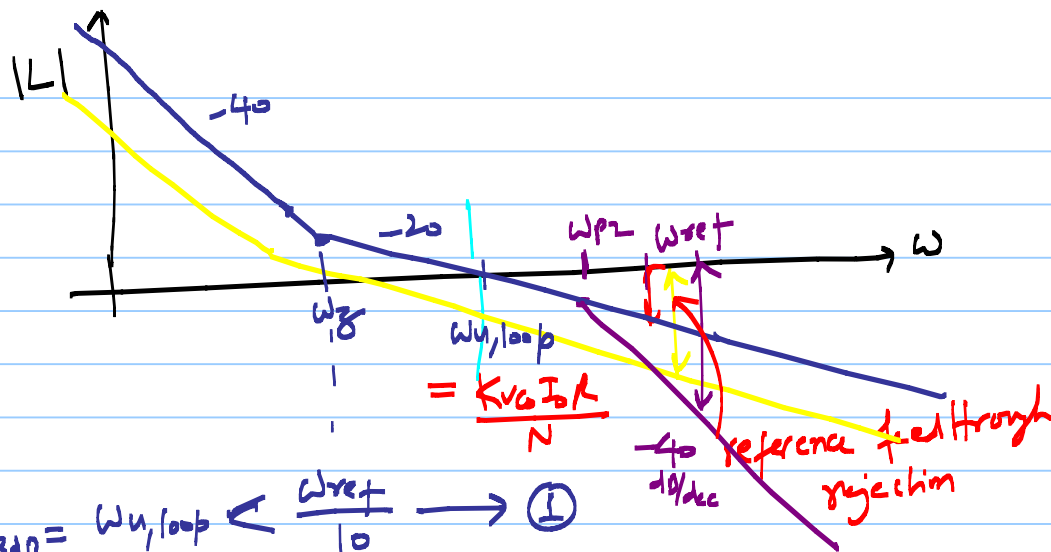

$$\omega_{3dB} = \omega_{u,loop} \leftarrow \frac{\omega_{ref}}{10} \rightarrow \textcircled{1}$$

CT approximation $\rightarrow \textcircled{2}$

Small loop BW

Type-II PLL
 $\Rightarrow \Delta\phi = 0$

* mismatch in charge pump


* Q_A & Q_B mismatch

* Add another pole for ω_{ref} rejection


* PM reduced

$\omega_{u,loop} \Rightarrow$ larger loop BW $\rightarrow$ (+) fast response
wider tracking/loading range
(-) more reference feed through

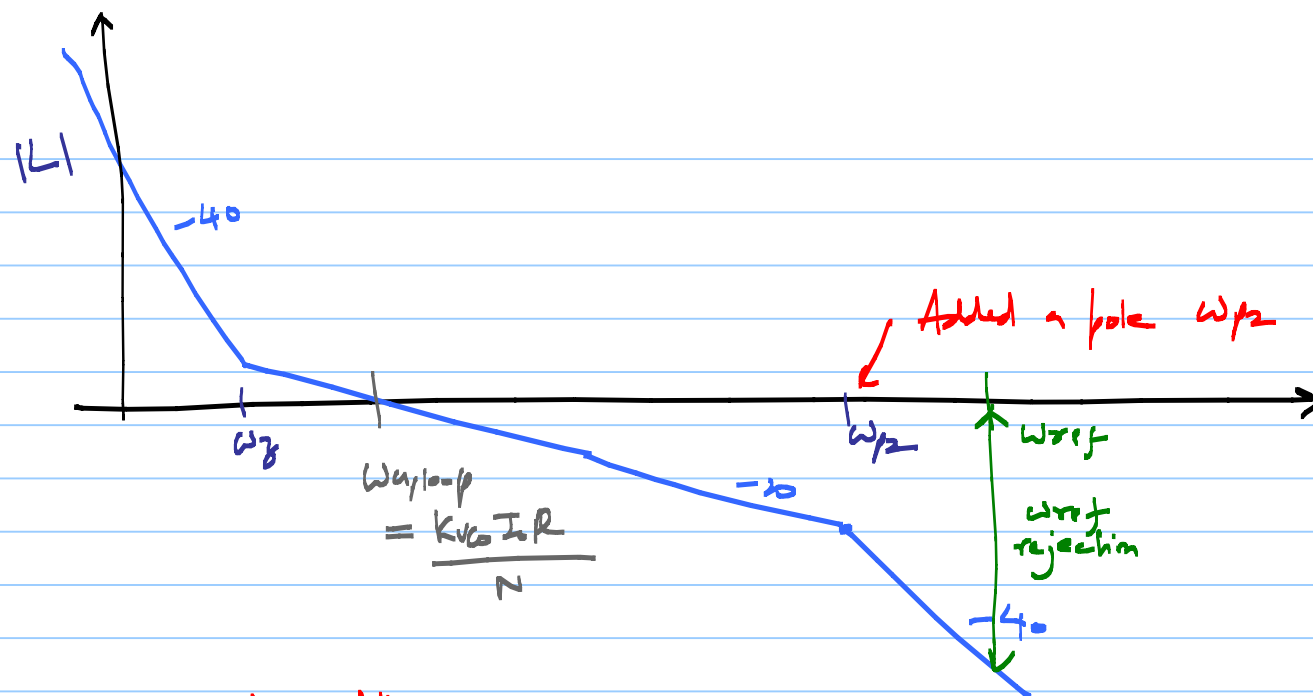$\Rightarrow$ smaller loop BW $\rightarrow$ (-) slow changes
frequencies




Loop-filter

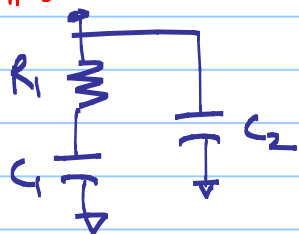


2nd-order loop filter

$$s_p = 0, -\omega_{p2}$$

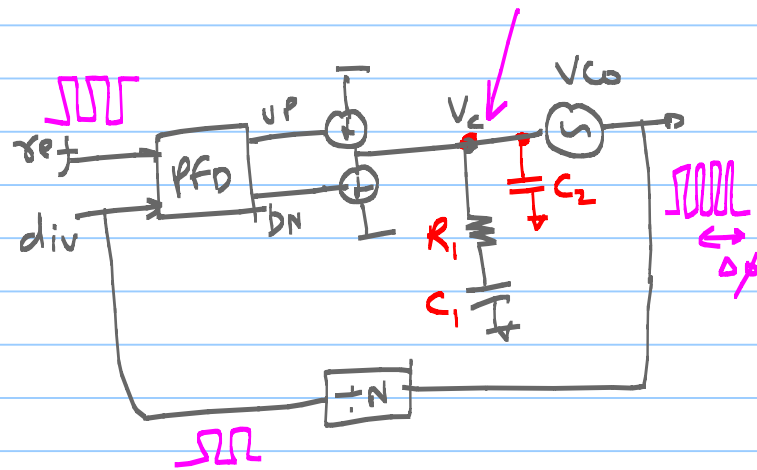Type-II Loop filter $\rightarrow 2^{nd}$ order
 $\hookrightarrow$ order $\rightarrow 3^{rd}$ order system



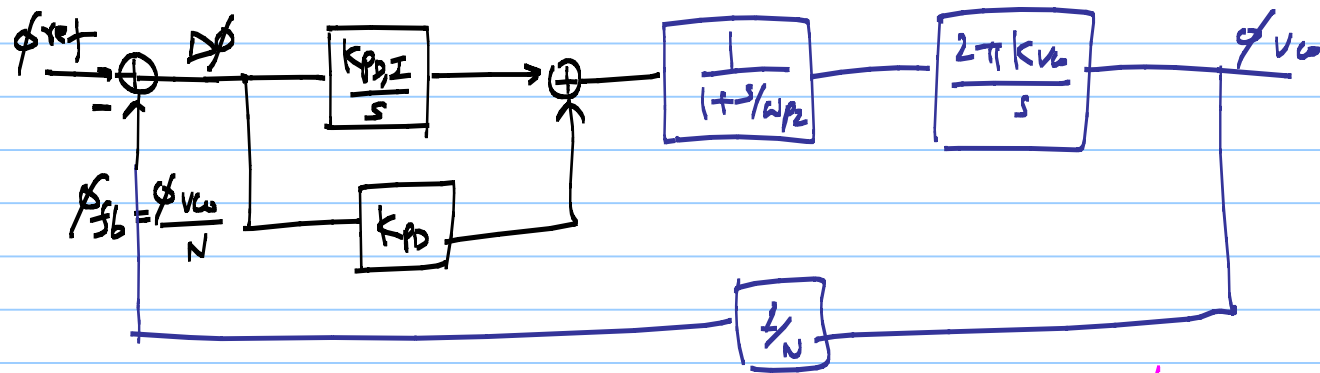* Type-II PLL with a third pole
phase domain model



$$L(s) = \frac{K_{VCO} I_0}{s^2 (C_1 + C_2) N} \frac{(1 + s R_1 C_1)}{(1 + s R_1 C_1 || C_2)}$$

$\omega_B = \frac{1}{R_1 C_1}$ (indicated by an orange arrow pointing to the zero in the numerator)
 $\omega_{p2} = \frac{1}{R_1 (C_1 || C_2)}$ (indicated by an orange arrow pointing to the pole in the denominator)
 $\frac{C_1 C_2}{C_1 + C_2}$ (indicated by a pink arrow pointing to the equivalent capacitance in the denominator)

PLL Design Example:

Spec. $f_{\text{out}} = 1 \text{ GHz}$
 $f_{\text{ref}} = 10 \text{ MHz}$
 $\Rightarrow N = 100$

$$V_{\text{co}} \Rightarrow K_{\text{vco}} = 100 \frac{\text{MHz}}{\text{V}}$$

$$V_{\text{co}} = 0.9 \text{ V}$$

$$V_{\text{DD}} = 1.8 \text{ V}$$

loop-BW: $f_{\text{u,loop}} = \frac{f_{\text{ref}}}{25} = 400 \text{ kHz}$ "chosen arbitrarily"

$$\Rightarrow \omega_{\text{u,loop}} = 2\pi \times 400 \text{ kHz}$$

$$\frac{K_{\text{vco}}(I_0 R)}{N} = 2\pi \times 400 \text{ kHz}$$

$$\frac{100 \frac{\text{MHz}}{\text{V}} \cdot (I_0 R)}{100} = 2\pi \times 400 \text{ kHz}$$

$$\Rightarrow \boxed{I_0 R \leq 2.4 \text{ V}}$$

$$I_0 = 1 \text{ mA} \Rightarrow R = 2.4 \text{ k}$$

$$\omega_z < \omega_{n, \text{loop}}$$

$$\times \quad \omega_z = \frac{1}{RC} = \frac{\omega_{n, \text{loop}}}{2} = 2\pi \times 200 \text{ kHz}$$

$$\Rightarrow \frac{1}{RC} = 2\pi \times 200 \text{ k}$$

$$\Rightarrow C = \frac{1}{2\pi \times 200 \text{ k} \times 2.4 \text{ k}}$$

$$\textcircled{\text{a}} \quad \frac{1 \text{ fF}}{\mu\text{m}^2} \Rightarrow \boxed{332 \text{ mm}^2} = 332 \text{ pF}$$

$$\Rightarrow 1 \text{ mm}^2 \Rightarrow \$60 \text{ k}$$

$$C_1 < 20 \text{ pF}$$