

ECE 518 - Lecture 16

Note Title

3/14/2013

$$f_{\text{out}} = 1 \text{ GHz}$$

$$f_{\text{ref}} = 10 \text{ MHz}$$

$$\omega_{3\text{dB}} = \omega_{\text{u/loop}} = 2\pi \cdot 400 \text{ K rad/s}$$

$$\text{settling time} \stackrel{\Delta}{=} 4.7 \tau = \frac{4.7}{\omega_{3\text{dB}}} = 12.5 \mu\text{s}$$

$$\text{How many cycles} = 12,500$$

Simulate for $> 12.5 \text{ kcycles}$

Type-II PLL loop dynamics:

$$L(s) = \frac{2\pi K_{PD,I} K_{VCO}}{Ns^2} \left(1 + \frac{sK_{PD}}{K_{PD,I}}\right)$$

* Closed-loop transfer function

$$\begin{aligned} H_L(s) &= \frac{\phi_{out}(s)}{\phi_{ref}(s)} = \frac{N \cdot L(s)}{1 + L(s)} \\ &= \frac{N \cdot \left(1 + \frac{sK_{PD}}{K_{PD,I}}\right)}{s^2 \frac{N}{2\pi K_{PD,I} K_{VCO}} + \frac{sK_{PD}}{K_{PD,I}} + 1} \\ &= \frac{N \left(1 + \frac{2\zeta}{\omega_n} s\right)}{\frac{s^2}{\omega_n^2} + \frac{2\zeta s}{\omega_n} + 1} \end{aligned}$$

$$K_{PD,I} = \frac{I_o}{2\pi C}$$

$$K_{PD} = \frac{I_o R}{2\pi}$$

"2nd-order system"



$$\triangleq \frac{N (2\zeta \omega_n s + \omega_n^2)}{s^2 + 2\zeta \omega_n s + \omega_n^2}$$

$$\Rightarrow \text{Natural frequency, } \omega_n = \sqrt{\frac{2\pi K_{PD,I} K_{V\omega}}{N}} = \sqrt{\frac{I_0 K_{V\omega}}{CN}}$$

$$\Rightarrow \text{Damping factor, } \zeta = \frac{K_{PD}}{2} \sqrt{\frac{2\pi K_{V\omega}}{N K_{PD,I}}} = \frac{R}{2} \sqrt{\frac{I_0 K_{V\omega}}{NC}}$$

$$\Rightarrow \text{Quality factor, } Q = \frac{1}{2\zeta} = \frac{1}{R} \sqrt{\frac{NC}{I_0 K_{V\omega}}}$$

$$\text{zero: } z_1 = -\frac{K_{PD,I}}{K_{PD}} = -\frac{1}{R_C} \quad @ \text{ LHP zero} \\ \omega_z = \frac{1}{R_C}$$

$$\text{poles: roots of } D(s) = s^2 + 2\zeta\omega_n s + \omega_n^2 = 0$$

$$\omega_{p1/2} = \omega_n [-\zeta \pm \sqrt{\zeta^2 - 1}]$$

Note:
that

$$\omega_d = -\frac{\omega_n}{2\zeta}$$



$\zeta < 1$

* for well separated poles (4 real) $\zeta > 1$

$$\omega_{p1} \approx \frac{\omega_n}{2\zeta}, \quad \omega_{p2} \approx 2\zeta\omega_n$$

$$\Rightarrow \omega_n = \sqrt{\omega_{p1} \omega_{p2}} \leftarrow \text{geometric Mean}$$


Root locus

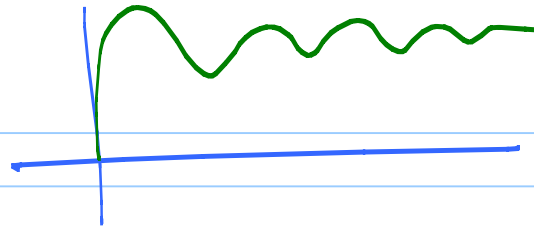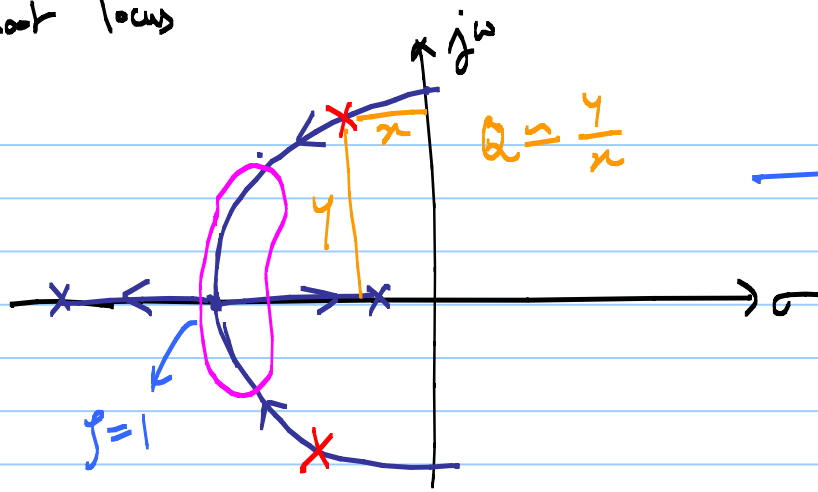

high-Q poles
 $\Rightarrow$ more transient
ringing.

$|H_{CL}(s)|$

$\frac{G_{out}(s)}{G_{ref}(s)}$

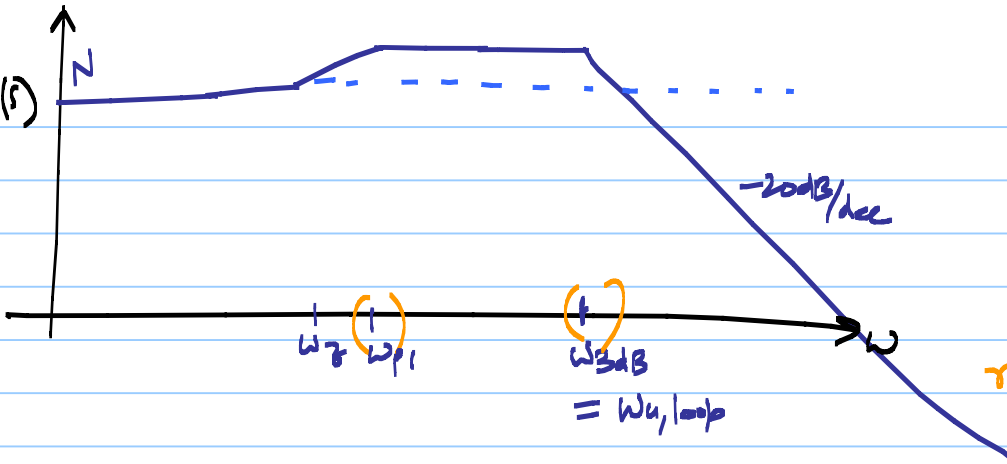


$w_z < w_{p1}$ form a doublet

$w_z > w_{p1}$

real poles

PM $\longleftrightarrow$ ξ
related

3rd-order PLL

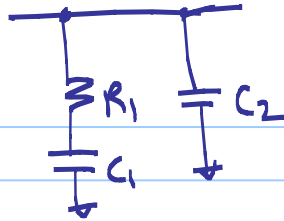


$$Z(s) = \left(\frac{b}{b+1}\right) \frac{(s/\omega_z + 1)}{s C_1 \left(\frac{s}{(b+1)\omega_z} + 1\right)}$$

$$b = \frac{C_1}{C_2}, \quad \omega_z = \frac{1}{R_1 C_1}$$

$$\omega_{p2} = \frac{1}{R_1 C_1 \parallel C_2} = \omega_z (b+1)$$

$$L(s) = \frac{K_V \omega_I}{N} \left(\frac{b}{b+1}\right) \frac{(s/\omega_z + 1)}{s^2 C_1 \left(\frac{s}{\omega_z (b+1)} + 1\right)}$$

↑ zero
↑ Type-II ↑ 3rd-pole

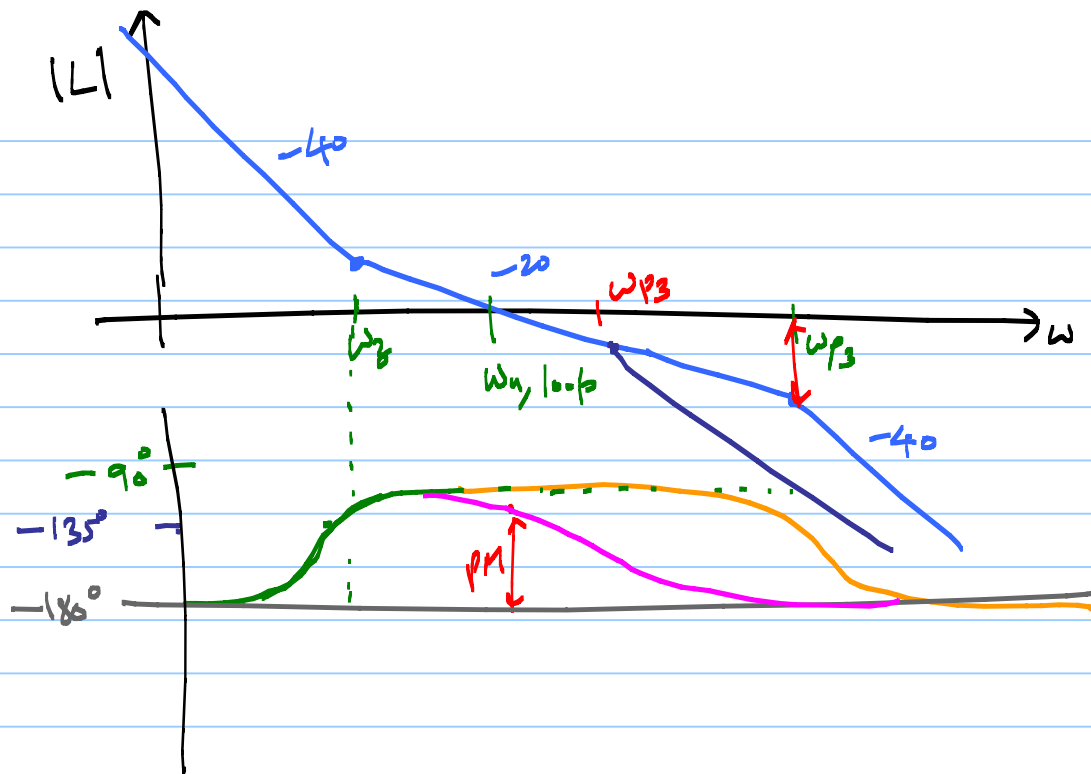

$$PM = \tan^{-1} \left(\frac{\omega_{u,loop}}{\omega_z} \right) - \tan^{-1} \left(\frac{\omega_{u,loop}}{\omega_{p3}} \right)$$

$$b = \frac{C_1}{C_2}$$

$$\Rightarrow PM = \tan^{-1} \left(\frac{\omega_{u,loop}}{\omega_z} \right) - \tan^{-1} \left(\frac{\omega_{u,loop}}{(b+1)\omega_z} \right)$$

$$b = \frac{C_1}{C_2}$$

A CMOS Frequency Synthesizer with an Injection-Locked Frequency Divider for a 5-GHz Wireless LAN Receiver

Hamid R. Rategh, *Student Member, IEEE*, Hiran Samavati, *Student Member, IEEE*, and Thomas H. Lee, *Member, IEEE*

$$PM = \tan^{-1} \left(\frac{\omega_{u,loop}}{\omega_z} \right) - \tan^{-1} \left(\frac{\omega_{u,loop}}{(b+1)\omega_z} \right)$$

$$\frac{\partial PM}{\partial \omega_{u,loop}} = 0 \Rightarrow \text{Maxima}$$

$$PM = PM_{max} \quad \text{for} \quad \omega_{u,loop} = \sqrt{b+1} \omega_z$$

$$\phi_m = PM_{max} = \tan^{-1}(\sqrt{b+1}) - \tan^{-1}\left(\frac{1}{\sqrt{b+1}}\right) = f(b)$$



$$\begin{aligned} & \tan^{-1} A - \tan^{-1} B \\ &= \tan^{-1} \left(\frac{A-B}{1+AB} \right) \end{aligned}$$

$$b = 2 \left(\tan^2 \phi_m + \tan \phi_m \sqrt{1 + \tan^2 \phi_m} \right)$$



$$PM_{max} = f(b)$$

$$* \quad \frac{C_1}{C_2} = b < 1 \Rightarrow PM = 20^\circ \\ \Rightarrow \text{ringing}$$
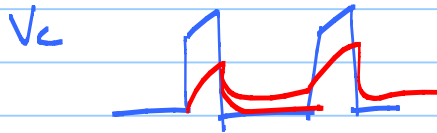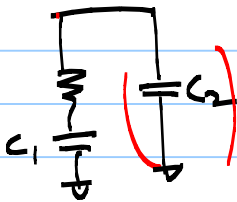
$$* \quad b = \frac{C_1}{C_2} = 5 \Rightarrow \zeta = 0.753$$




Simple Charge Pump Design

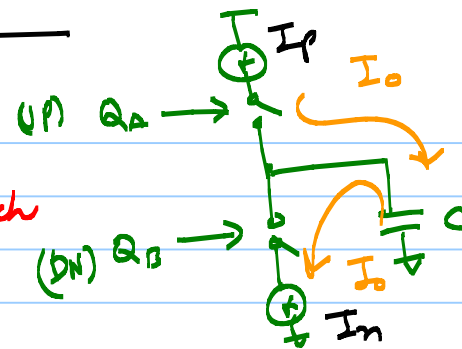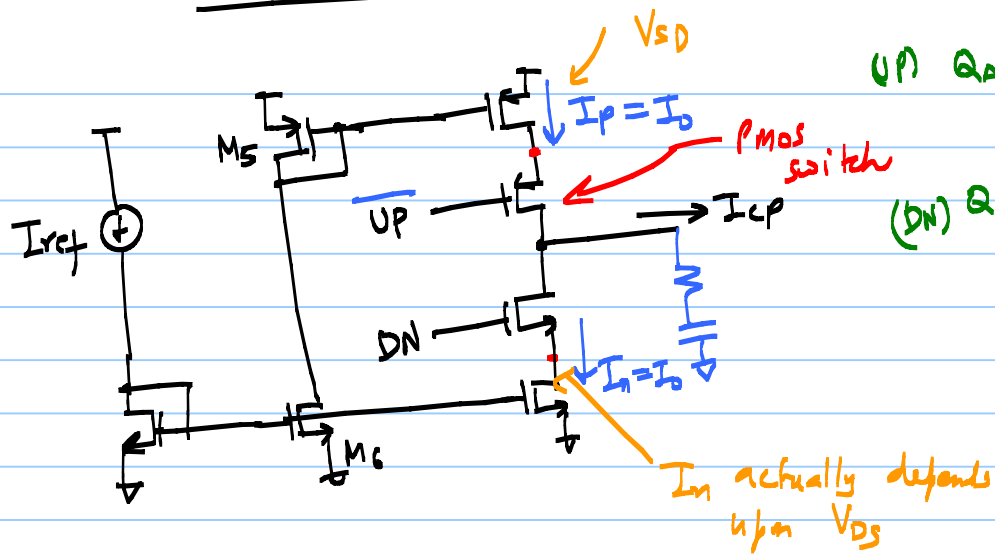


① PFD/CP dead zone


$\Delta\phi=0$, ideal case $T_{rst}=0$

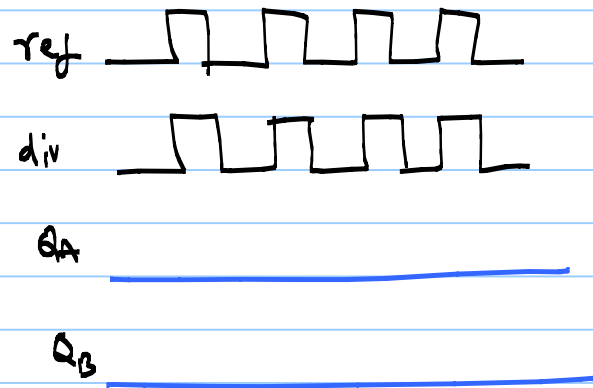

QA/QB has to turn the switch ON

$0 < \Delta\phi < \underline{\phi_0}$

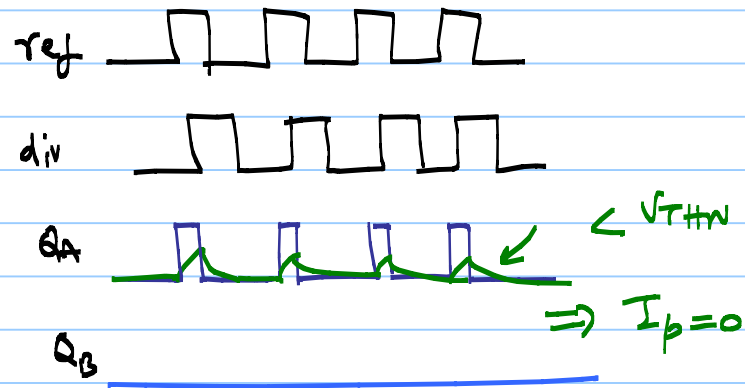

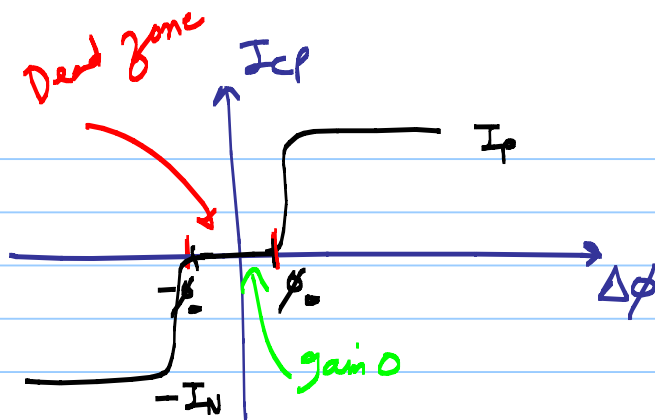


I_{cp} is no longer $\propto \Delta\phi$

$\Rightarrow |L| = 0$

$\Rightarrow$ output phase is not locked

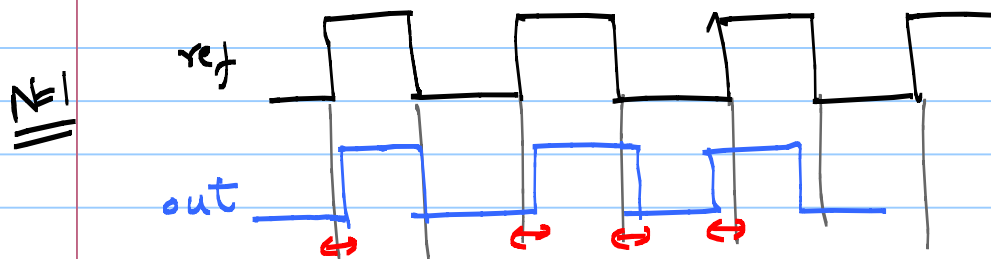$\Rightarrow$ VCO accumulates phase error



* use coincident pulses in Q_A & Q_B to eliminate the dead zone.



Select T_{rst}
that $\Delta\phi > \phi_0$

↓ Q_A & Q_B allowed
to reach full
logic-level

↳ turn the
switches on

