


ECE 518 - Lecture 17

Note Title




3/19/2013

- ① PFD/CP dead zone
- ② UP/DN skew

③ I_p, I_n (CP current mismatch)

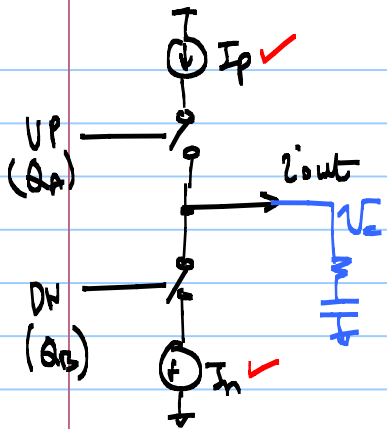

Trst
↑ Resch
pulse
width

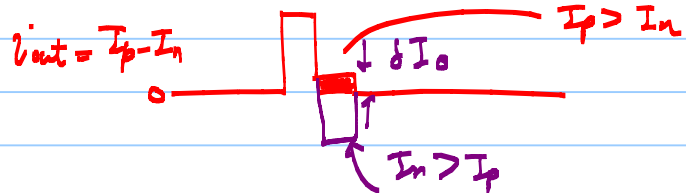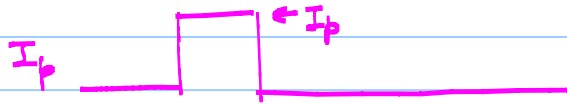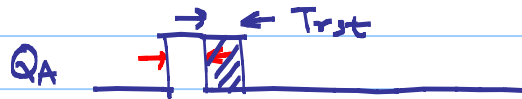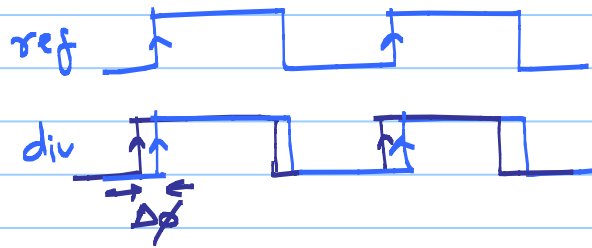

$$I_p \neq I_n$$
$$I_p > I_n$$


* Current flowing into the loop filter
due to the mismatch in the (I_{cp}) current

$$\Delta I_{cp} = I_p - I_n$$


flows for time $\Rightarrow T_{rst} > 0$

* In the steady state



$$\Delta Q = T_{rst}(I_p - I_n) = \Delta T \cdot I_n$$
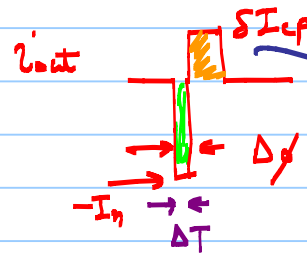
$$\Rightarrow \Delta T = T_{rst} \left(\frac{\Delta I_{cp}}{I_{cp}} \right)$$




Areas are forced to be equal by the -ve feedback loop

→ $\Delta \phi = \left(\frac{\Delta T}{T_{ref}} \right) \cdot 2\pi$
radians

$$\Delta \phi = 2\pi \cdot \left(\frac{T_{rst}}{T_{ref}} \right) \cdot \left(\frac{\Delta I_{cp}}{I_{cp}} \right)$$

$> 0 \Rightarrow$ reference feed through

④ Charge Sharing

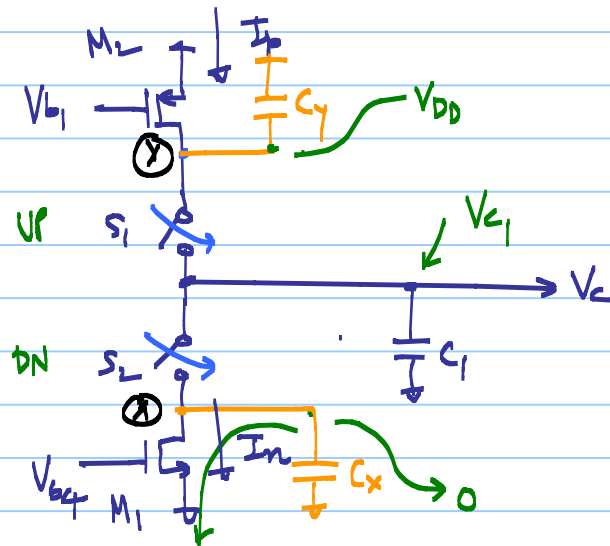


* Initially s_1 & s_2 are off

$X \rightarrow$ discharged to ground

$Y \rightarrow$ charged to V_{DD}

* Now, the switches are turned on

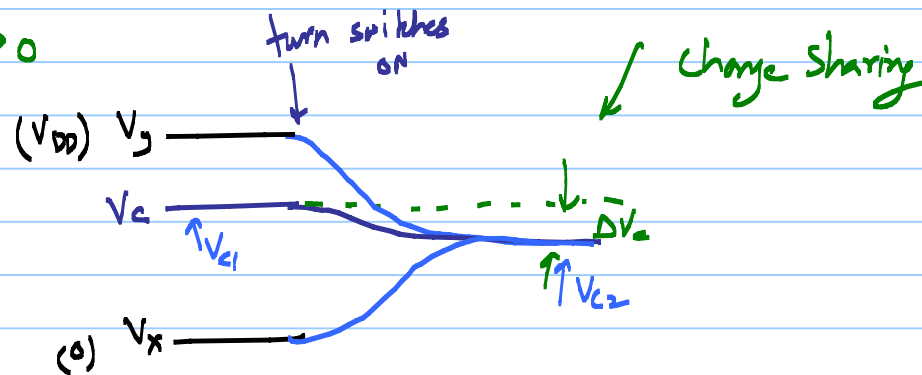

* When the switches S_1 & S_2 turn ON

V_x rises, & V_y falls

and eventually $V_x = V_y = V_c$

⇒ charge sharing occurs b/w

C_x , C_y & C_1

$$V_{c, \text{final}} = \frac{C_x V_x^0 + C_y V_y^{V_{DD}} + C_1 V_{c1}}{C_x + C_y + C_1} \neq V_{c1}$$

* Due to charge sharing

⇒ V_c "jumps" ⇒ VCO phase error ⇒ ^{output} jitter


* This amount of disturbance depends upon the steady state value of V_c

⇒ desired f_{out}

⇒ disturbance/jitter in the output depends
upon $f_{out} = \underline{N} \cdot f_{ref}$


"Big problem!"

⑤ Channel length Modulation

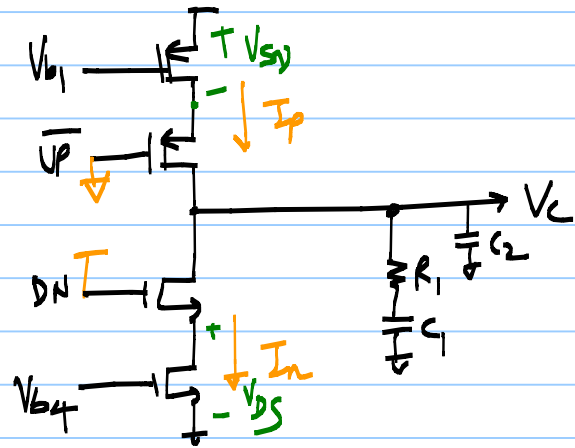

* different output voltages will lead to different $V_{DS} \leftarrow V_{SD}$ for the current sources

⇒ mismatch between I_p & I_n

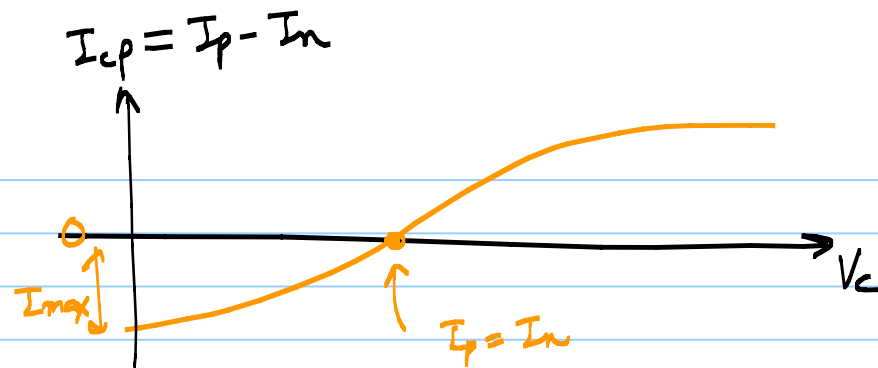

$$\frac{I_{max}}{I_o} \approx 30 - 45\%$$


∴ mismatch depends upon $\rightarrow V_{ce}$
 $\Rightarrow f_{out}$

⑥ Charge Injection and clock feed through


Charge pump with improved matching

$$UP = DN = 1$$

$$UP = DN = 0$$

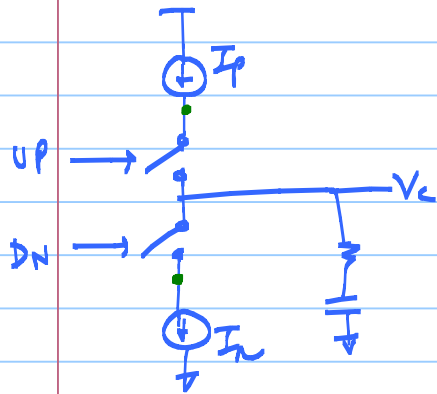


Current sources
shut off and
turned on

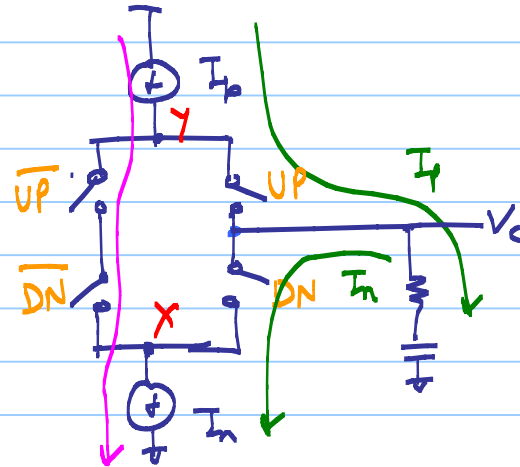

* Charge sharing solution $\Rightarrow$ keep the current sources turned on and simply steer the currents.

x

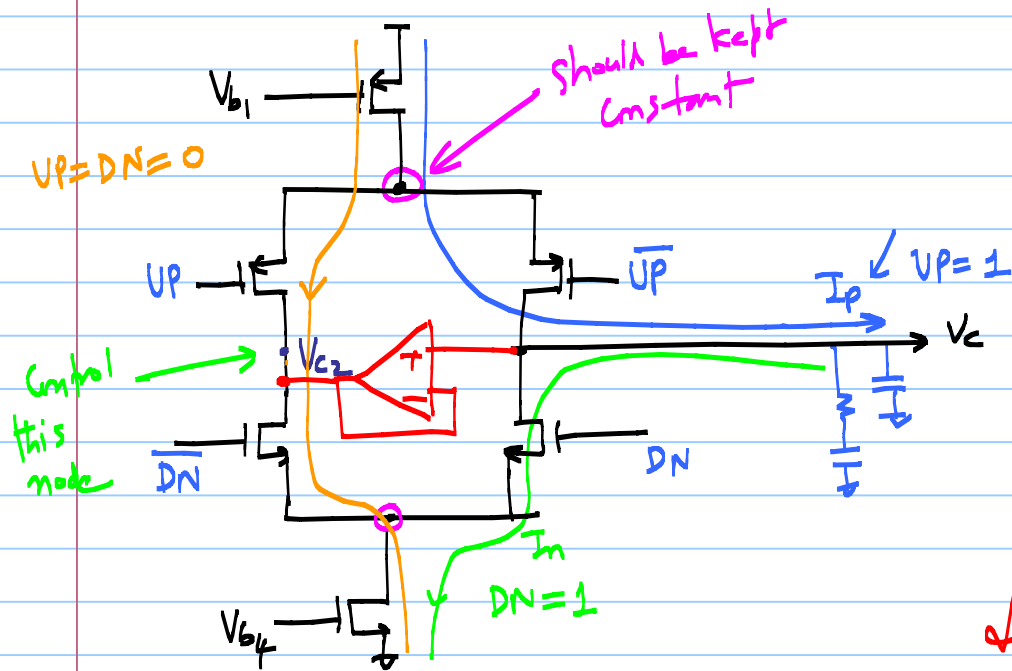* Need to keep the V_{DS} ($\sim V_{SD}$) of the current sources constant.



* To keep the V_{SD} & V_{DS} of the current sources constant

V_{c2} must mirror V_c

(in project, use ideal opamp)

reduced transient current mismatch

Professional CP Design :

