

ECE 518- Lecture 6


Note Title

2/7/2013


$$\overset{\text{NMOS}}{\beta_{\text{pull-down}}} > \beta_{\text{access}} > \overset{\text{PMOS}}{\beta_{\text{pull-up}}}$$

readable writable


SRAM Cell Noise Margin

 


"Butterfly curves"

 


"Storage Mode"

 

"Read Mode"

 


"Monte Carlo"

 


Read Butterfly curve

BL's are precharged at $\frac{V_{DD}}{2}$, Read

WL @ V_{DD}

 


4T Cell SRAM

 


(-) leakage current

Storage Mode

 


"Read mode"

 

Noise margin is less

Floating Gate Memory :

 

* poly 1 is floating $\rightarrow$ not electrically connected

* poly 2 $\Rightarrow$ controlling gate of this transistor

$\hookrightarrow$ we can store information (memory) by changing, adding or removing charge stored in the floating gate

