

ECE 518 - Lecture 8



HW is posted

Phase Locked Loops (PLLs)

→ memories, μ Ps, FPGAs, HDDs, RF, wireline & fiber optic
TRx, Cell phones,
XBOX, Displays.

Applications:

① Frequency Synthesis

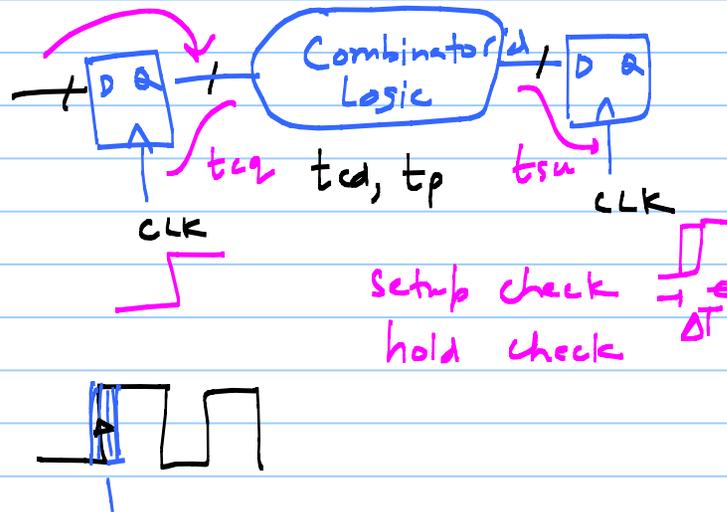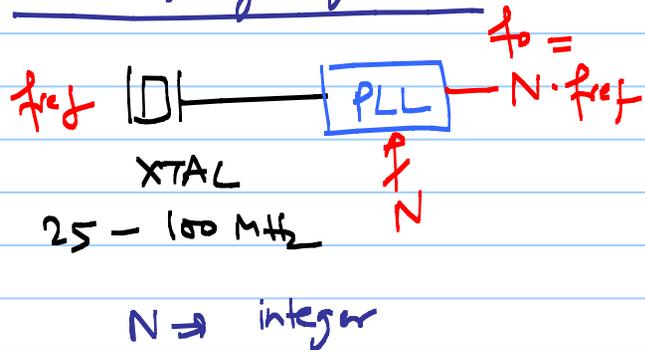


$$N \rightarrow \text{fraction} = \frac{n}{m}, n, m \in \mathbb{I}$$



"STA"


↳ ASIC Design

Cell phone → GSM

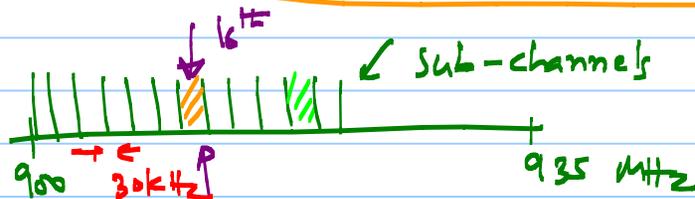

↳ "frequency synthesizer"


② Skew Reduction

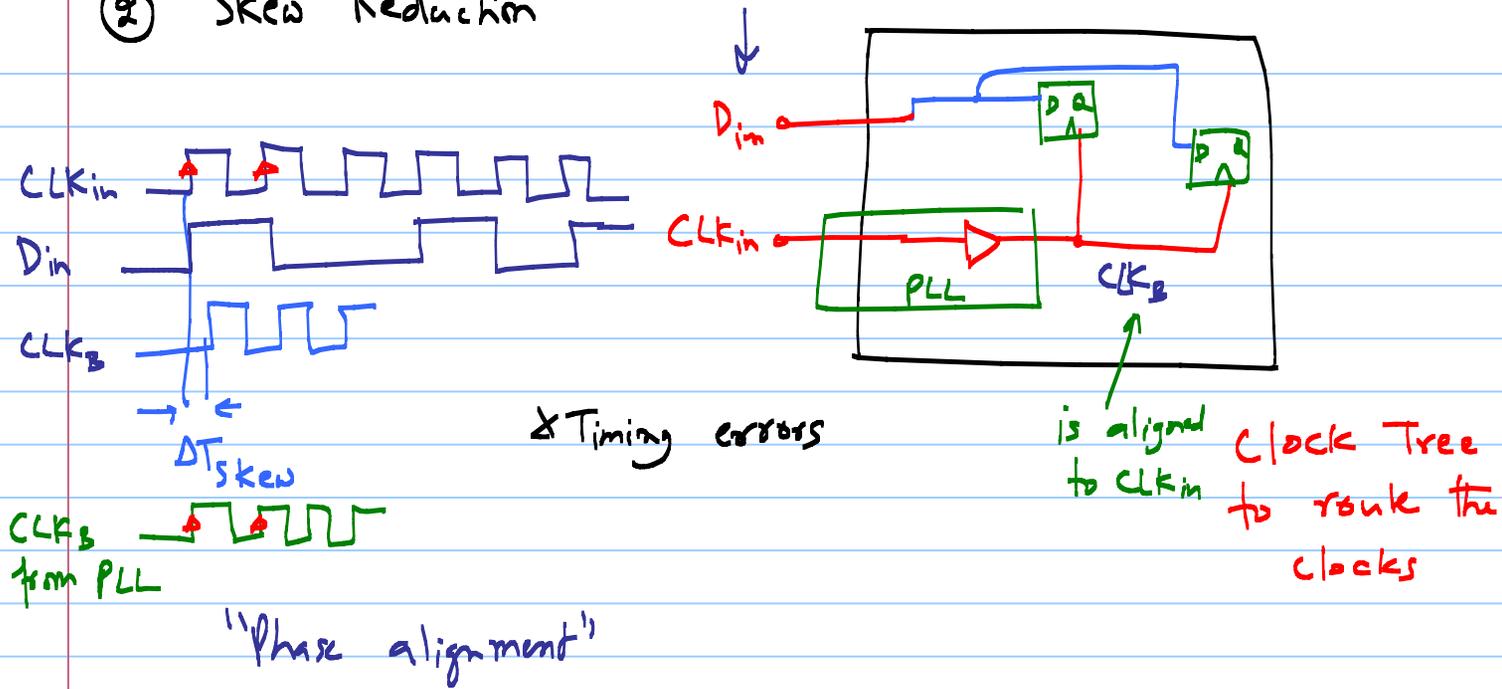


③ Clock/Data Recovery (CDR)

SERDES, Serial links

Vias, connectors
↳ reflection

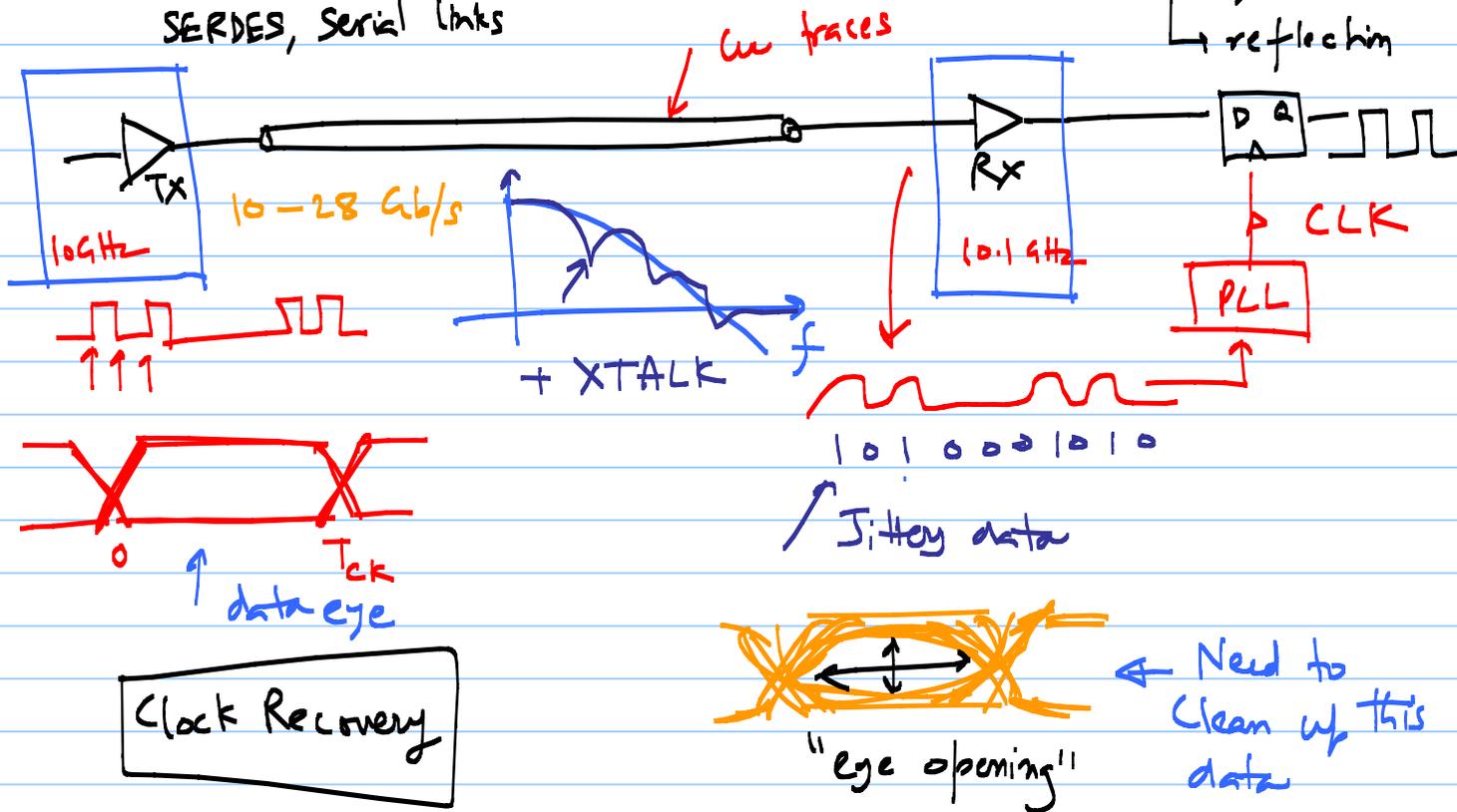


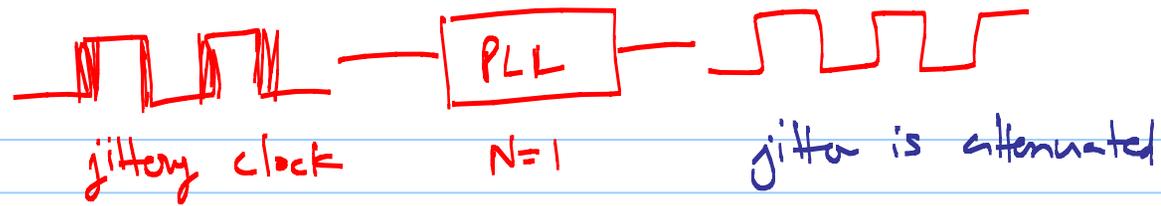

- ④ Modulation & Demodulation
↳ FM radio receiver

"DLL" → skew reduction → adjust delays
↳ simpler → application is limited
no freq multiplication

Negative feedback Systems


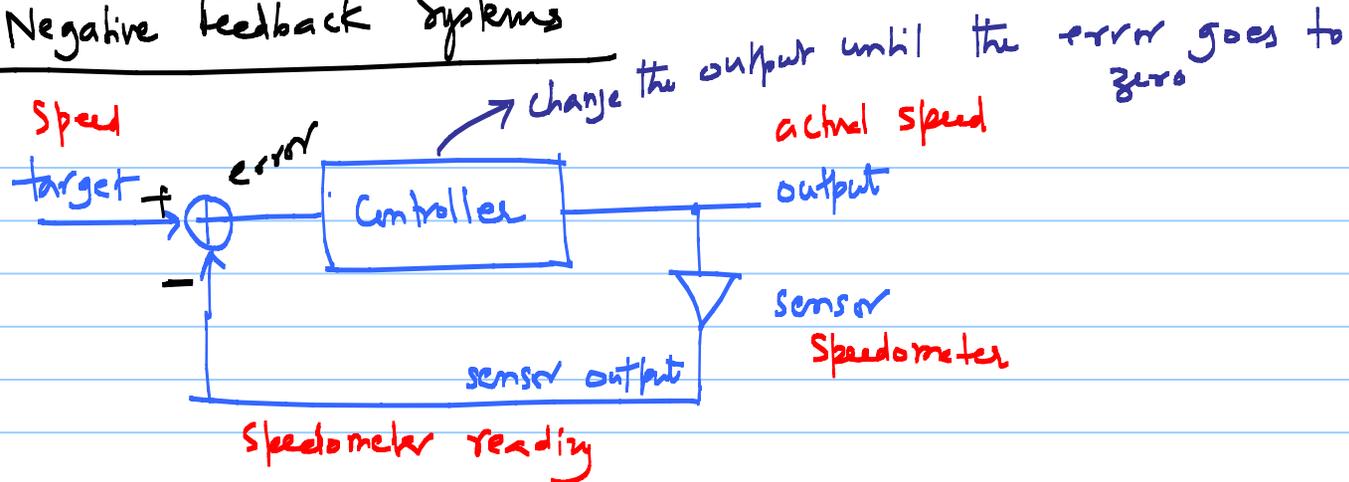


* continuously adjusting the o/p until the desired output is achieved.


* Can't set the o/p to the correct value instantaneously.




* What is the nature of the controller?

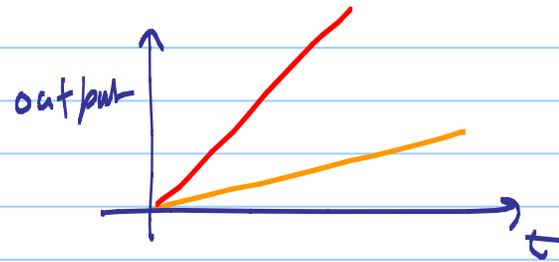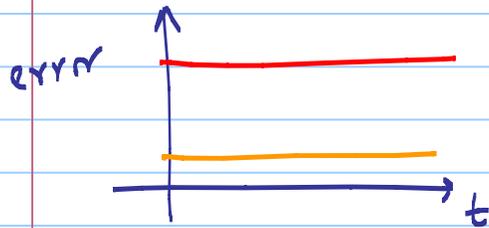

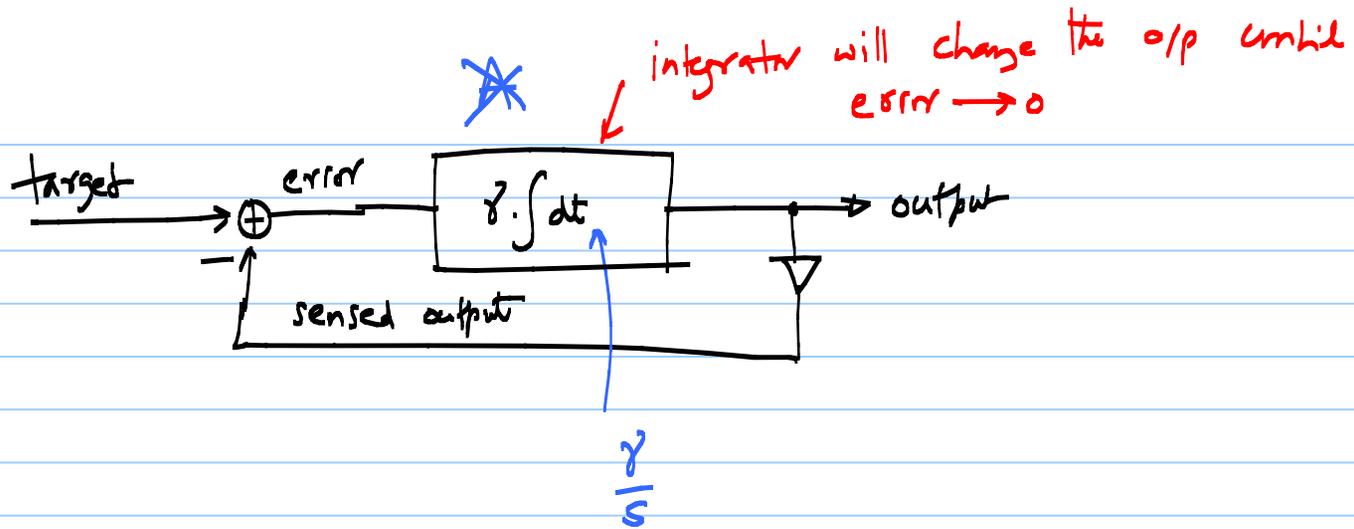
* an integrator is used as the controller.



Example: Negative feedback amplifier

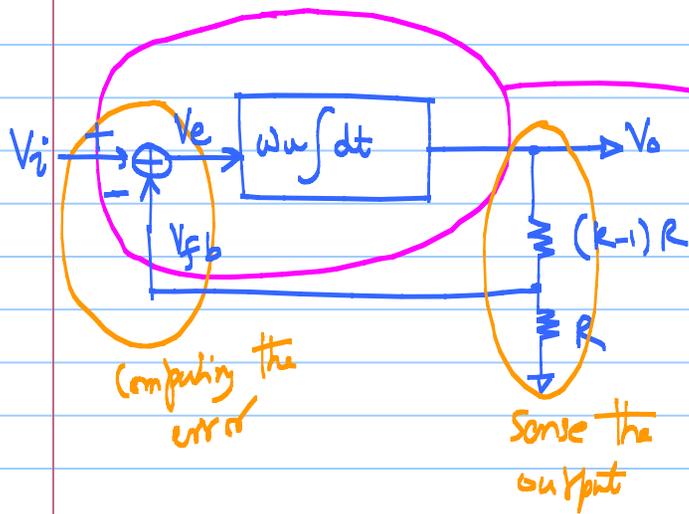

Desired output
 $V_o = k V_i$

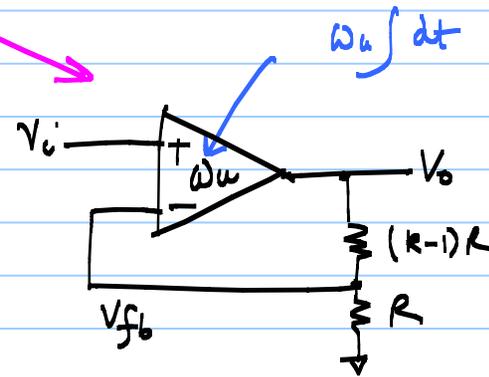



target $\rightarrow V_i$



sensed output = $\frac{V_o}{k}$

error: $V_e = V_i - \frac{V_o}{k}$


* in steady-state

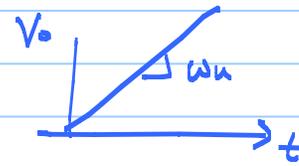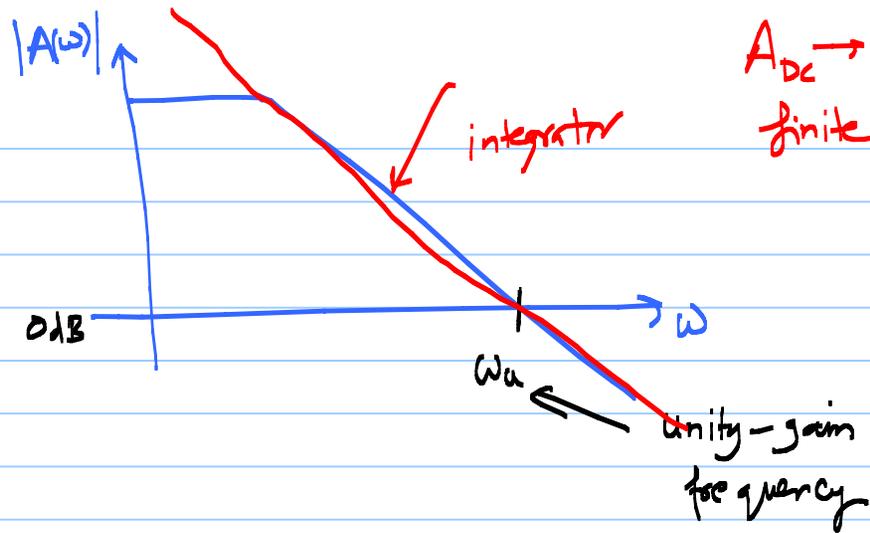$V_e \rightarrow 0 \Rightarrow V_o = k \cdot V_i$



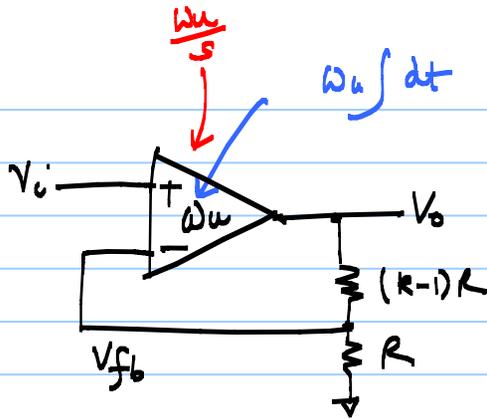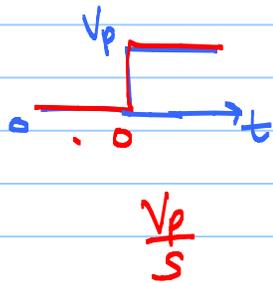

$$\frac{k}{1+s\tau}$$

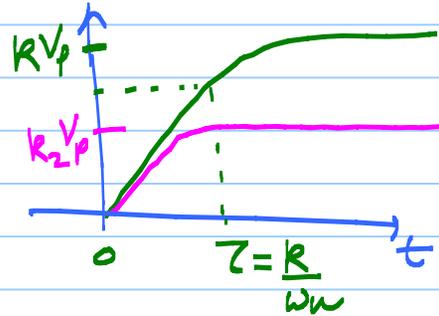

$$\frac{V_o}{V_i}(s) = \frac{k}{1 + \frac{s}{(\omega_u/k)}}$$

time constant $\tau = \frac{k}{\omega_u}$



for large 'k' \Rightarrow τ is larger

$$V_{out}(s) = \frac{V_p}{s} \cdot \frac{k}{1 + \frac{s}{\omega_u/k}} \xrightarrow{\mathcal{L}^{-1}} kV_p [1 - e^{-t\omega_u/k}] u(t)$$

$f_{in} \leftarrow$ input

generate $f_o = N \cdot f_i$

" $k=N$ "

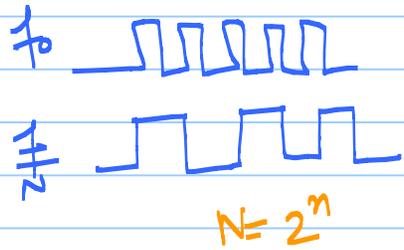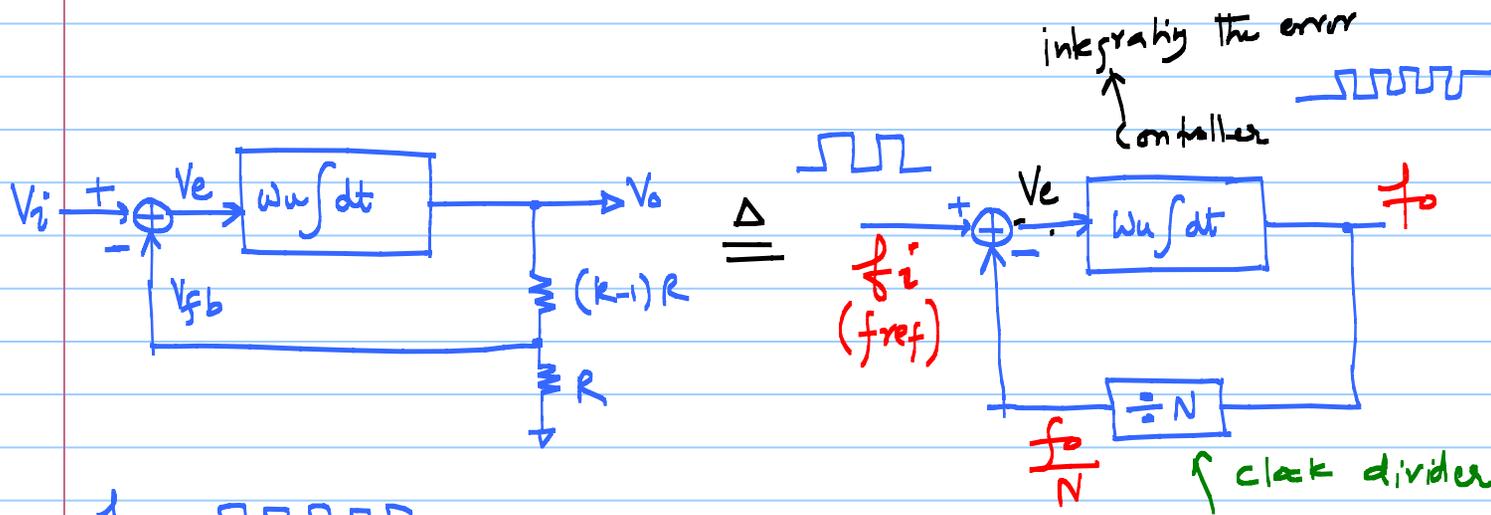

in steady-state $\Rightarrow f_o = N f_{ref}$

⊗ we need a controlled frequency source
⊕ Vary the frequency of oscillation using an electrical signal

⊗ VCO