
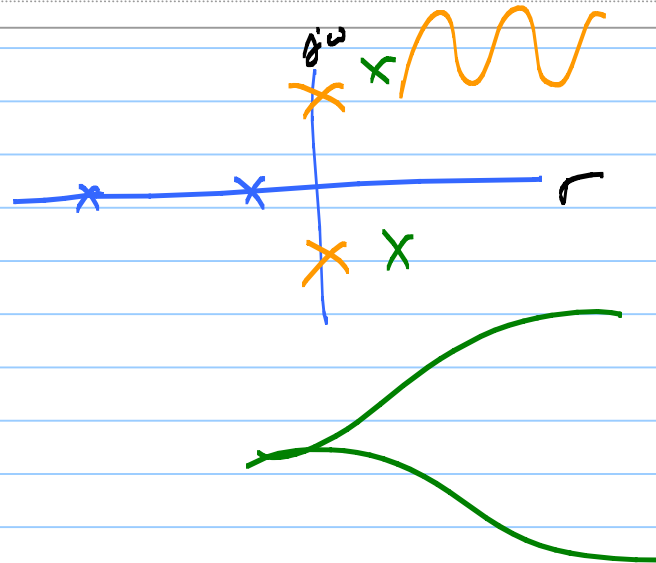


ECE 518- Lecture 9

Note Title

2/19/2013

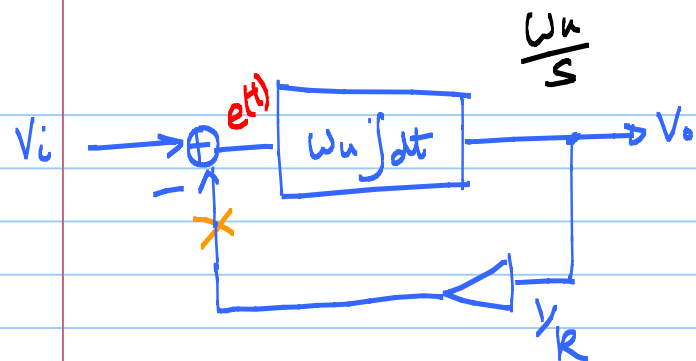




in steady-state

$$V_o = \underline{k} V_i$$

$$e(t) = V_i - \frac{V_o}{k} \rightarrow 0$$

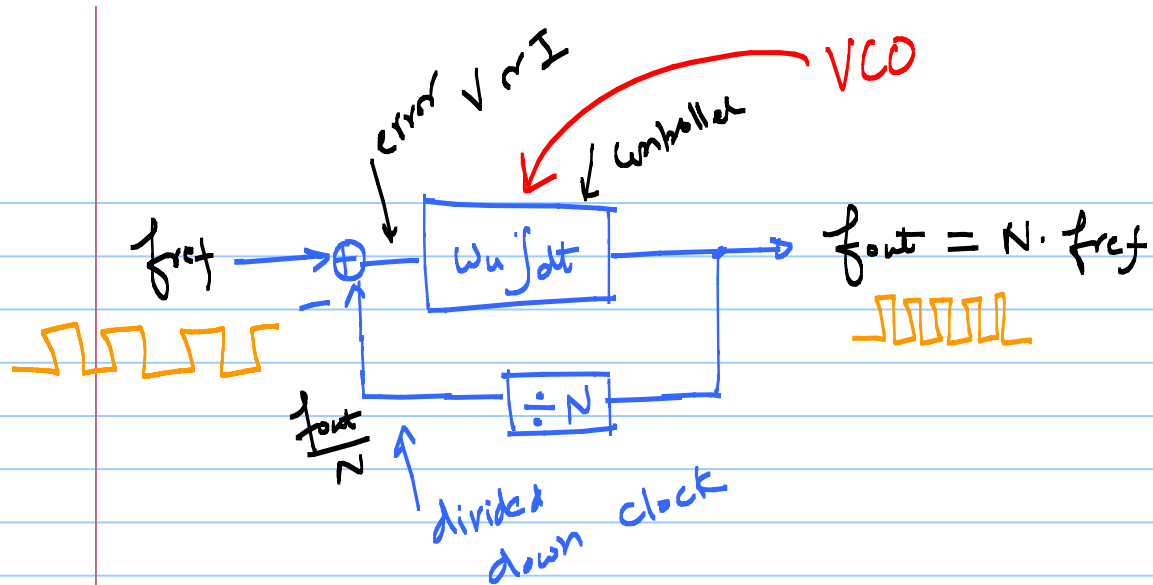
precise gain set by 'k'
as the DC loop-gain is ∞ .






$$f_{out} = \underline{N} f_{ref}$$

frequency synthesizer




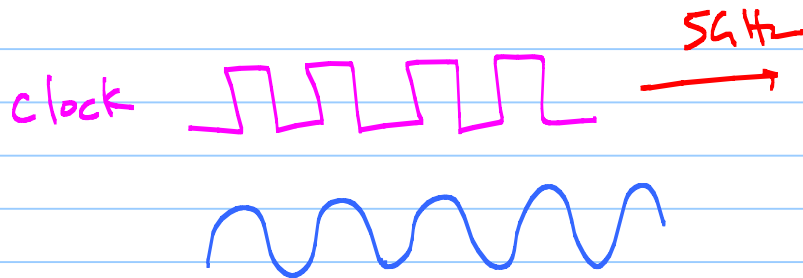


$$1 \cdot \cos(\omega \cdot t)$$

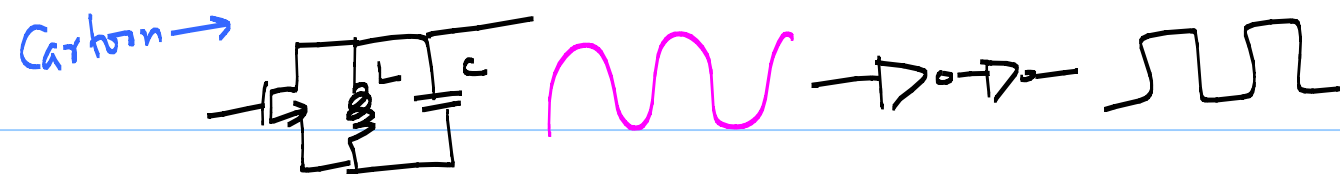any periodic pulse shape $\rightarrow$ clock



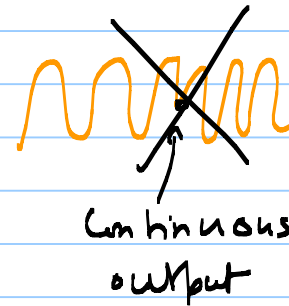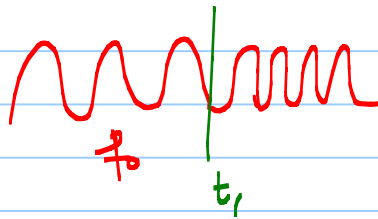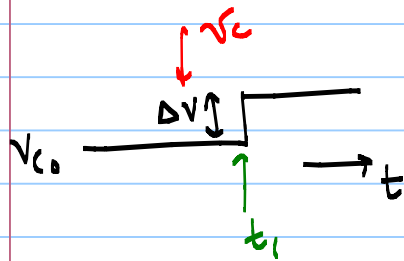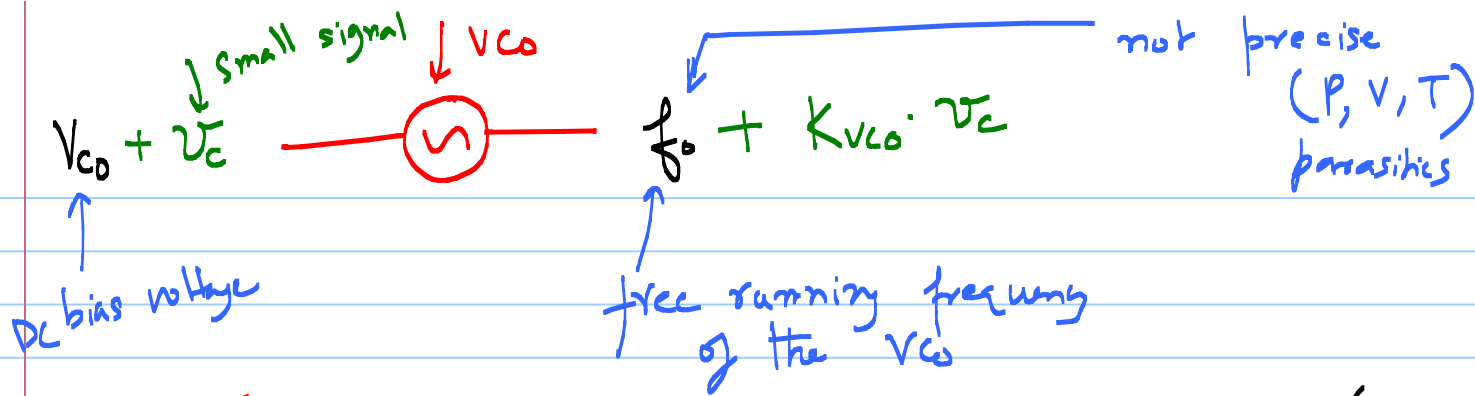* we need a voltage controlled oscillator (VCO)



VCO output = ~~$\cos(2\pi f_0 t + 2\pi K_{VCO} v_c t)$~~

free running

$\cos(2\pi f_0 t + 2\pi K_{VCO} \int_0^t v_c(t) dt)$ ✓


* the frequency change doesn't happen
instantaneously


$$\cos \left(\overbrace{2\pi f_0 t}^{\text{free running}} + \overbrace{2\pi K_{VCO} \int_0^t v_c(t) dt}^{\text{increment part}} \right)$$

$\phi(t) \leftarrow$ phase of the output

$$v_c(t) = V_c$$



$$2\pi K_{VCO} \cdot V_c \underline{t}$$

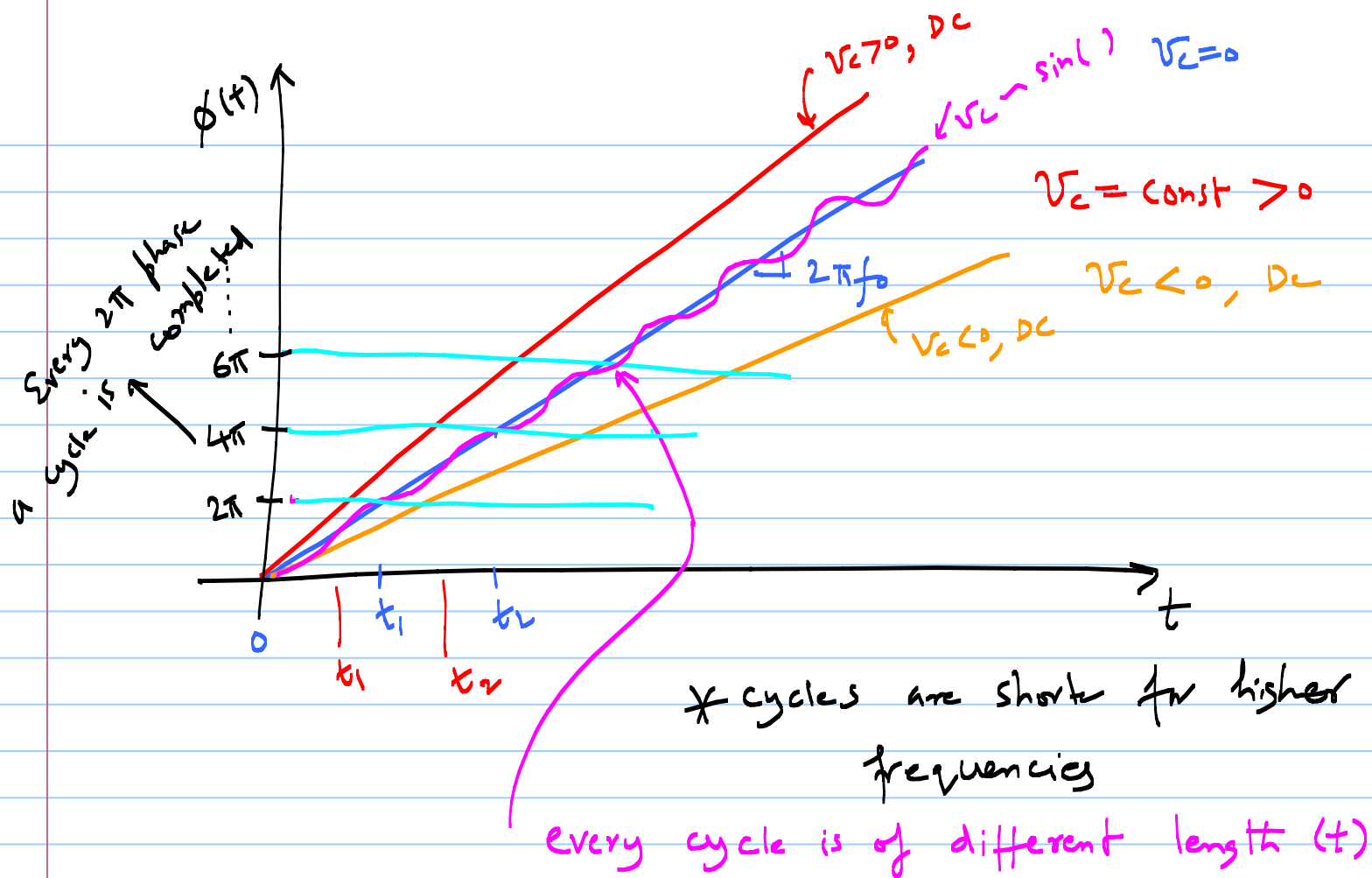

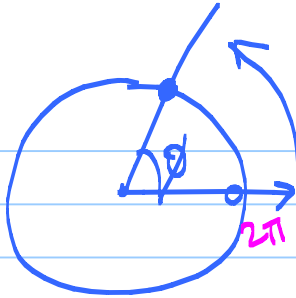

1 Hz $\rightarrow$ 1 sec cycle

10 Hz $\rightarrow$ 100 msec cycle

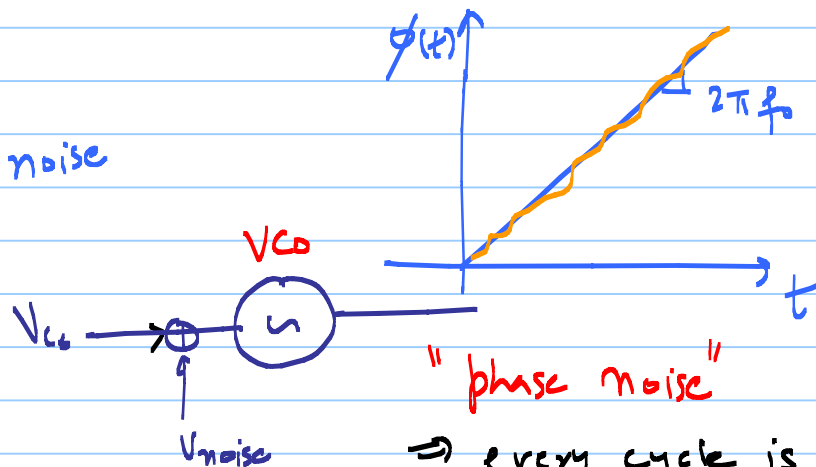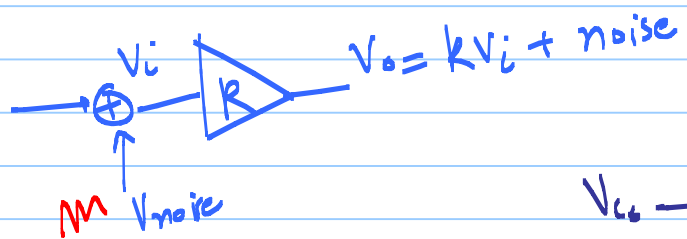

"phase noise"

$\Rightarrow$ every cycle is not perfectly the same


$$\cos \left(\underbrace{2\pi f_0 t + 2\pi K_{v\omega} \cdot \int_0^t v_c(t) dt}_{\phi(t)} \right)$$

instantaneous frequency $f_i(t) = \frac{1}{2\pi} \frac{d\phi(t)}{dt}$


refer to
FM

$$f_i(t) = \underline{f_0} + \underline{K_{v\omega} \cdot v_c(t)}$$

frequency divider

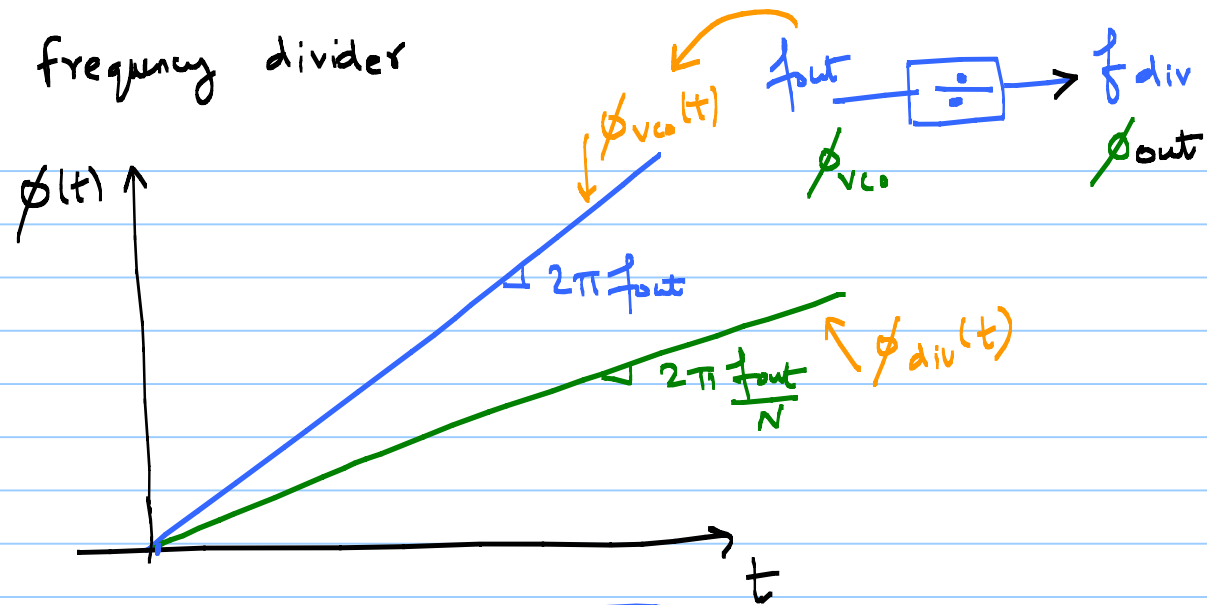

↑ gain of $1/N$ in "phase domain"

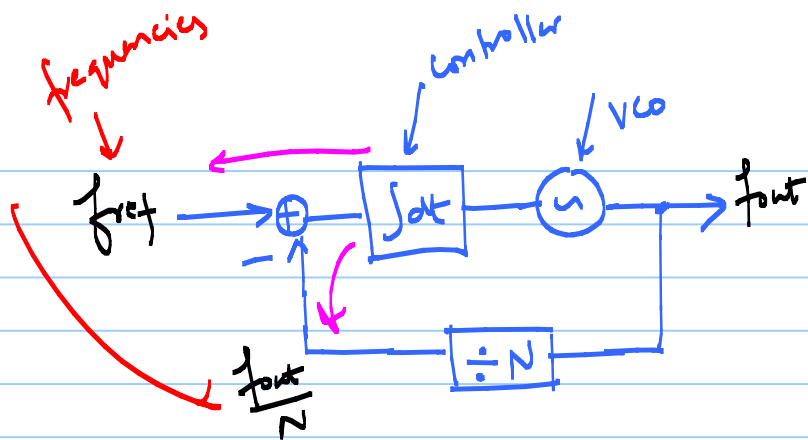

pull the integrator out

