

Homework 5

ECE 5/418 – PLL and Memory IC Design

Note: Use Cadence schematic capture and Spectre simulation tools, available on the AMS servers for the homework problems. Use TSMC 180 nm models with $V_{DD} = 1.8\text{ V}$.

Problem 1- Ring VCO Design

Design a voltage-controlled oscillator (VCO) to generate frequencies in the range $f_{out} = 100 - 500\text{ MHz}$. Use any suitable ring-based topology for your design.

1. Show the VCO voltage tuning curve (f_{out} vs $V_{control}$) and find the linearized VCO gain K_{VCO} .
2. Simulate the changes in the VCO tuning curve as the voltage supply (V_{DD}) is varied.
3. Plot the phase noise contribution of the VCO.