

Noise in PLLs

Noise sources

Deterministic




- Supply noise
- Coupling
- Substrate noise

Random

- Thermal
- flicker



Also, we have reference feedthrough

Thermal Noise

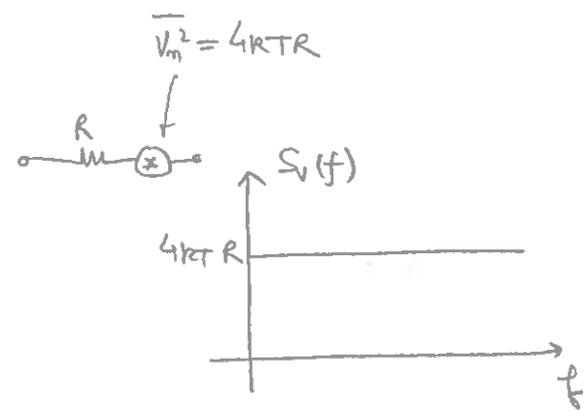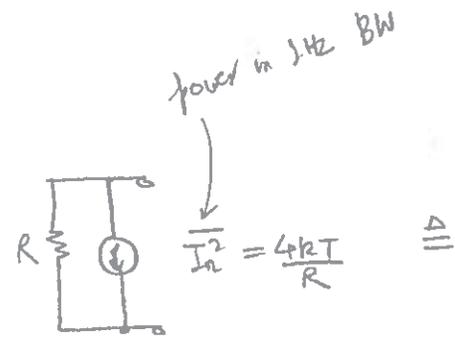
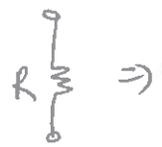


Boltzmann's constant $k = 1.38 \times 10^{-22} \text{ J/K}$

SAT

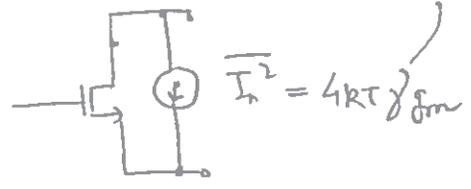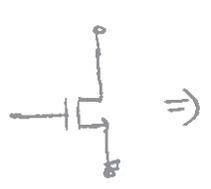

$\gamma = 2/3$ for long-channel

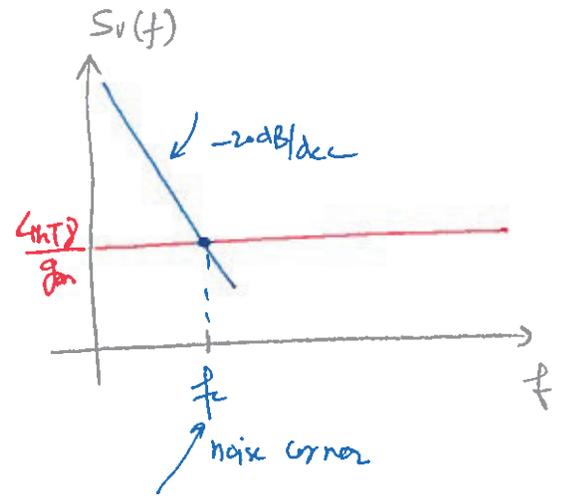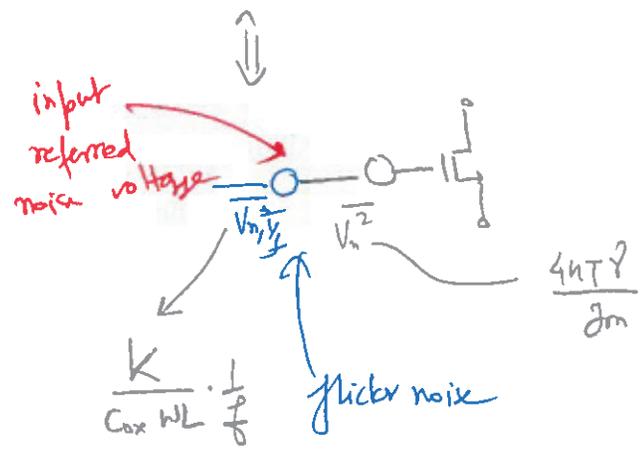

Generic Noise Analysis

(2)

* Small-signal analysis with several noise sources


Procedure:

- ① Identify all noise sources
- ② Calculate (estimate by simulation), PSD of each noise source $S_i(f)$
- ③ Evaluate TF from each of the noise sources to the output ($H_i(f)$)
- ④ Determine the contribution of each noise source to the output $|H_i(f)|^2 S_i(f)$

Result: $S_i(f) \rightarrow [H(f)] \rightarrow S_{out}(f) = S_i(f) |H(f)|^2$
from Comm Theory

- ⑤ Sum all the contributions $\sum_i |H_i(f)|^2 \times S_i(f)$ to find the total output noise

Noise in PLLs

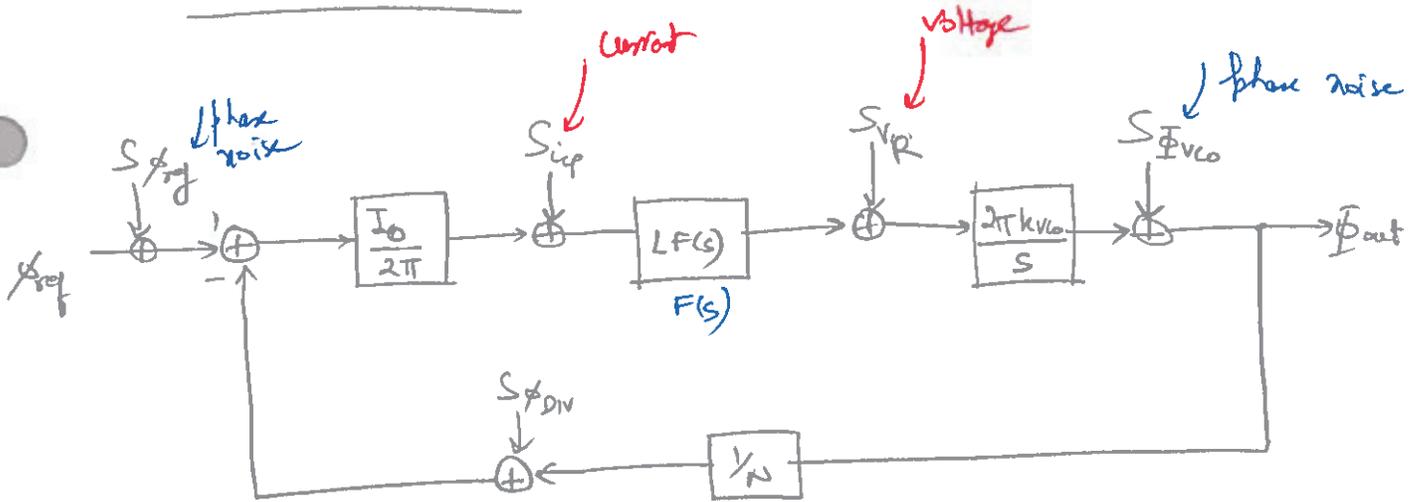

$S_{\phi_{ref}} \Rightarrow$ Reference clock noise PSD

$S_{i_{cp}} \Rightarrow$ PFD/CP noise PSD (CP dominates)

$S_{V_R} \Rightarrow$ Loop filter resistor noise PSD

$S_{\phi_{vco}} \Rightarrow$ VCO phase noise PSD

$S_{\phi_{div}} \Rightarrow$ Divider noise PSD

Noise Transfer function:

loop gain $\Rightarrow L(s) = \frac{I_0 k_{vco}}{N} \frac{F(s)}{s}$

$NTF_{ref}(s) = \frac{\phi_{out}(s)}{\phi_{ref}(s)} = \frac{N \cdot L(s)}{1 + L(s)}$ **LPF**


AB LPF $NTF_{div}(s) = NTF_{ref}(s)$ ← Same entry point as ϕ_{ref}

LPF $NTF_{cp}(s) = \frac{\phi_{out}(s)}{i_{cp}(s)} = \frac{2\pi}{I_{cp}} \cdot NTF_{ref}(s)$ ← divide by the gain of CP to refer to the input


BPF $NTF_R(s) = \frac{\phi_{out}(s)}{V_R(s)} = \frac{\left(\frac{2\pi k_{vco}}{s}\right)}{1 + L(s)}$ ← "Notice same Denominator"


HPF $NTF_{vco}(s) = \frac{\phi_{out}(s)}{i_{vco}(s)} = \frac{1}{1 + L(s)}$

→ feedback system TF property

 

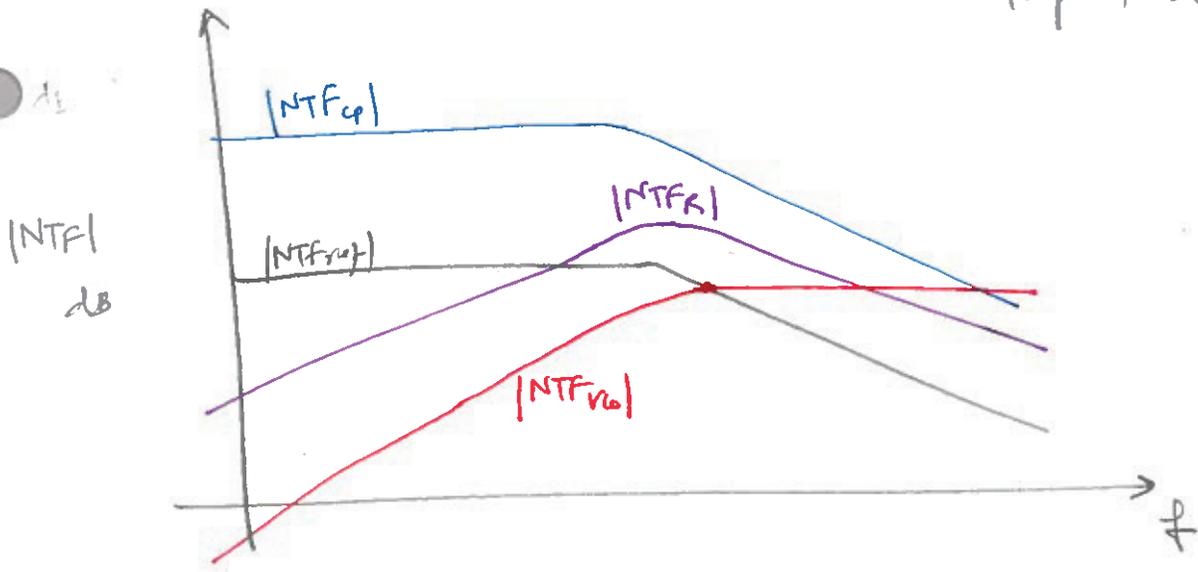* Note, these are closed loop transfer functions (4)



 

output phase Noise Contribution

5


$$S_{\phi_{out}}^{\phi_{ref}} = S_{\phi_{ref}} \cdot |NTF_{ref}(j\omega)|^2$$

$$S_{\phi_{out}}^{i_q} = S_{i_q} \cdot |NTF_{cp}(j\omega)|^2$$

$$S_{\phi_{out}}^{VR} = S_{VR} \cdot |NTF_R(j\omega)|^2$$

$$S_{\phi_{out}}^{\phi_{vco}} = S_{\phi_{vco}} \cdot |NTF_{vco}(j\omega)|^2$$
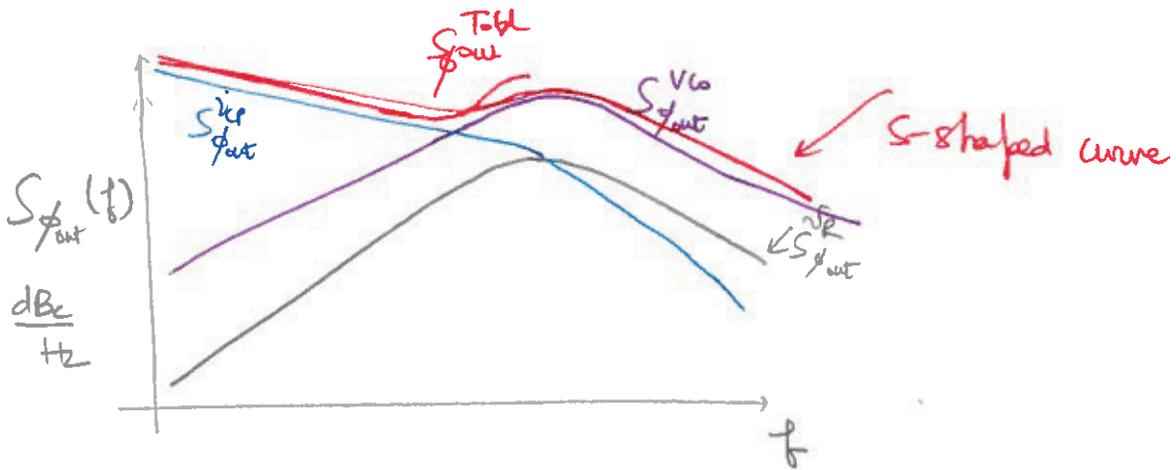
$$S_{\phi_{out}}^{Total} = S_{\phi_{out}}^{\phi_{ref}} + S_{\phi_{out}}^{i_q} + S_{\phi_{out}}^{VR} + S_{\phi_{out}}^{\phi_{vco}} + S_{\phi_{out}}^{\phi_{div}}$$



Calculating Jitter from Phase Noise :

$$\text{Total phase noise} = \sigma_{\Delta\phi}^2 = \int_0^{\infty} S_{\phi_{out}}^{\text{Total}}(f) df$$

↑
variance of phase noise
(in radians)

$$\sigma_{\Delta\phi} = \sqrt{\int_0^{\infty} S_{\phi_{out}}^{\text{Total}}(f) \cdot \frac{360^{\circ}}{2\pi}} \quad (\text{degrees})$$

$$\sigma_{\Delta T} = \sqrt{\int_0^{\infty} S_{\phi_{out}}^{\text{Total}}(f) \cdot \frac{T_{V_{10}}}{2\pi}} \quad (\text{sec})$$

* Use trapz function in MATLAB to evaluate discrete integration

Jitter usually represented as some
ps rms

Noise Optimization :

(7)

* optimal PLL bandwidth to minimize overall noise

Procedure :

- ① Start with an estimate of PLL BW (ω_{3dB})
 $\omega_{3dB} \ll \frac{\omega_{ny}}{10}$
- ② find loop parameters
- ③ Simulate/Calculate PSD of all the "noise" sources
- ④ find the total output phase noise
- ⑤ If the output phase noise doesn't meet the specification, adjust ω_{3dB} or lower noise
- ⑥ If spec met, check if power can be reduced further
- ⑦ Repeat 1-6 until you achieve phase noise spec with lowest power.

Use Matlab or PLL assistant from cypsim.com

