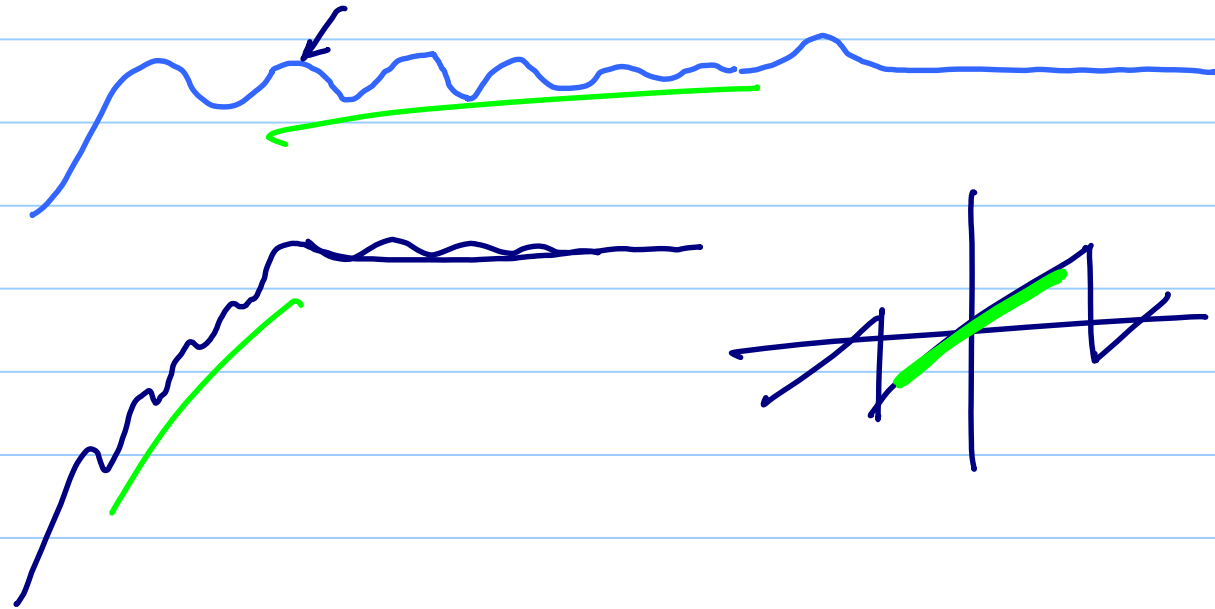


ECE 518 - Lecture 13


Note Title

2/26/2015




PFD + CP, Loop filter

VCO
Divider

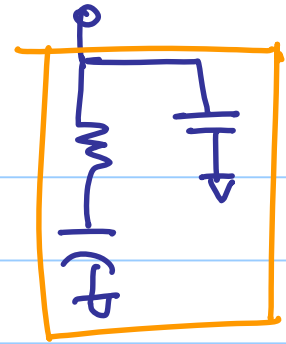

Oscillators Basics

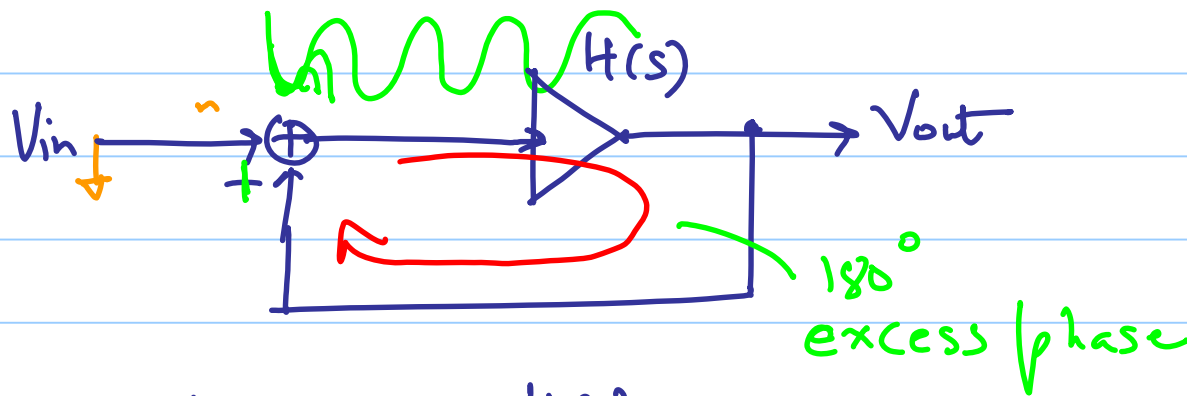

$$\beta = 1$$

$$L(s) = \beta H(s)$$

$$H_{cl}(s) = \frac{V_{out}(s)}{V_{in}} = \frac{H(s)}{1 + L(s)}$$

for oscillation at $s = j\omega_0$, we require

$$L(j\omega_0) = -1$$

$$\Rightarrow |L(j\omega_0)| = 1 \text{ \& } \angle L(j\omega_0) = -180^\circ$$

$$|H_{cl}(j\omega_0)| \rightarrow \infty$$

*


$$\text{Loop-gain} \quad |L(j\omega)| \cong 1$$

$$\& \quad \angle L(j\omega) = -180^\circ$$

↳ conditions are necessary but not sufficient

↳ typically we choose the loop gain to be 2-3

①

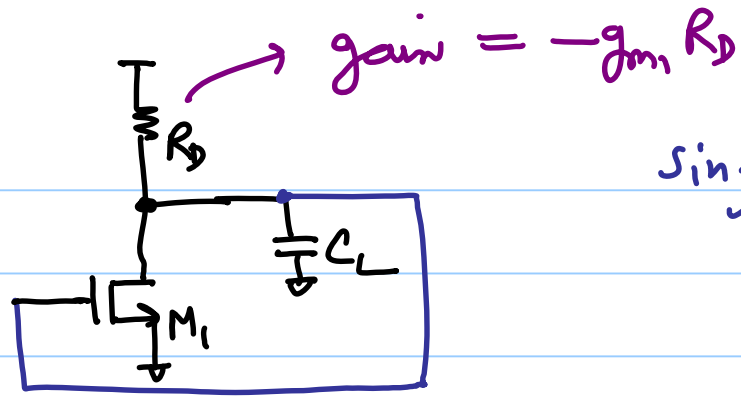


single-pole

$$L(s) = \frac{-g_{m1} R_D}{(1 + s R_D C_L)}$$

max phase shift $\Rightarrow 90^\circ$




②

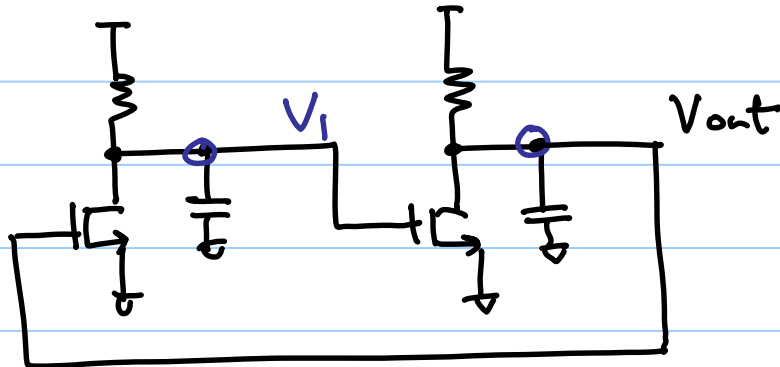

two-poles

$$L(s) = \frac{(g_{m1} R_{D1})^2}{(1 + s R_{D1} C_L)^2}$$


max exten phase shift

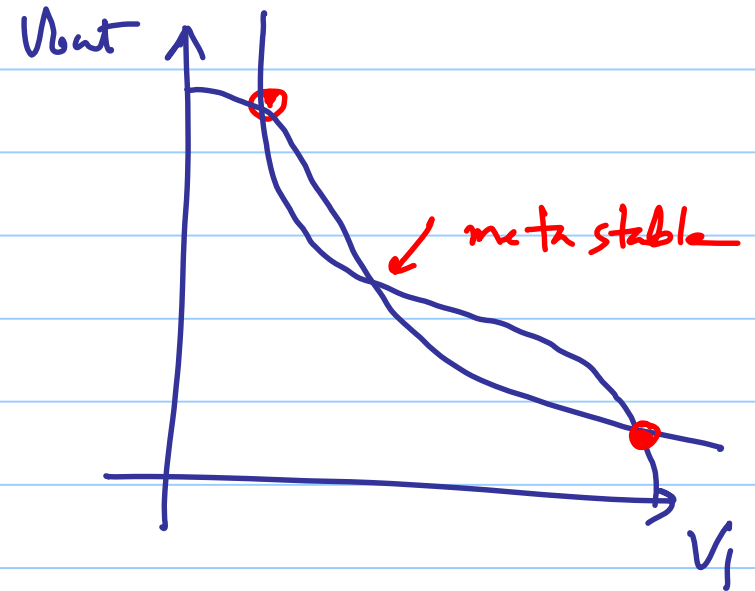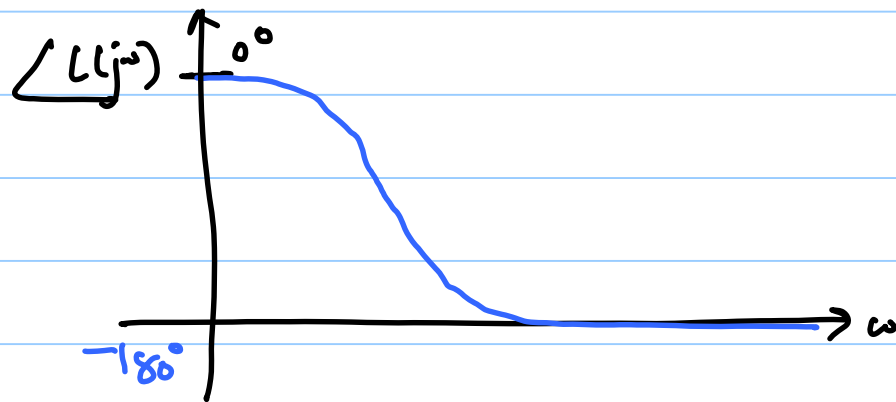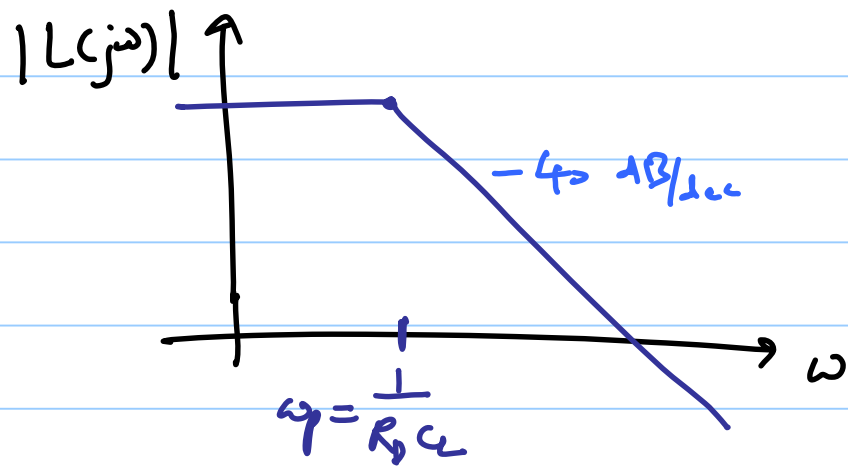



3


$$\omega_0 = \frac{1}{R_D C_L}$$

Ignore C_{gs} caps
3-poles

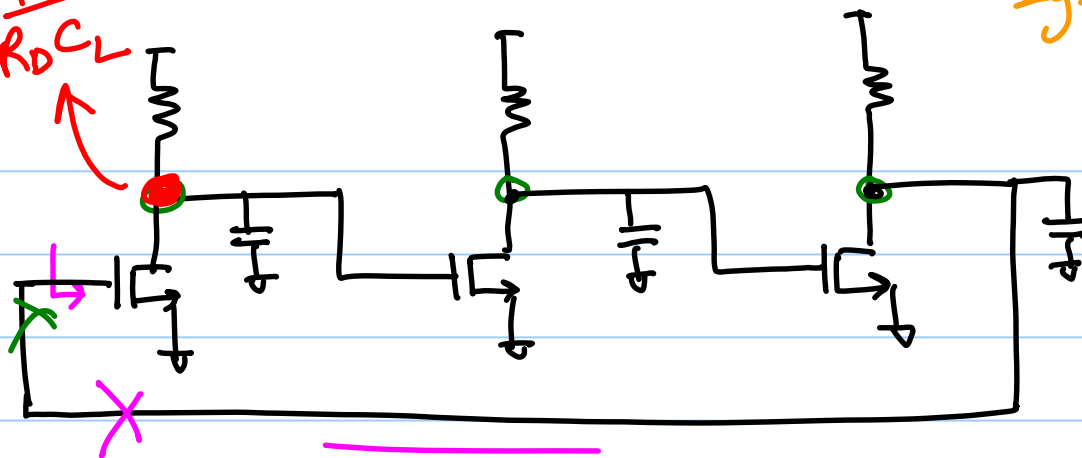
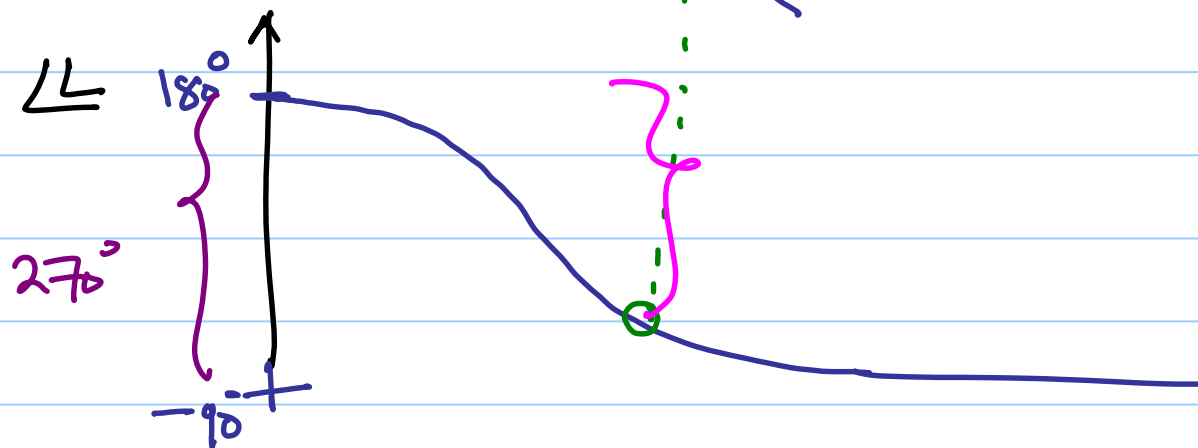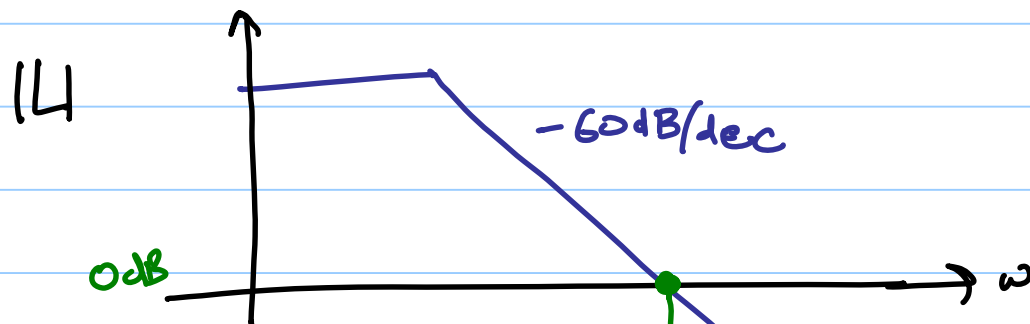
$$L(s) = \frac{-(g_m R_D)^3}{(1 + s R_D C_L)^3}$$



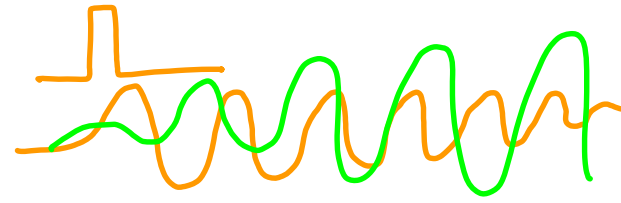

at $\omega = \omega_0$

The circuit oscillates only if the excess phase
 $= 180^\circ$
 $\Rightarrow$ each stage is contributing 60°

$$\omega_0 = \frac{1}{R_0 C_L}$$

$$\tan^{-1} \left(\frac{\omega_{osc}}{\omega_0} \right) = 60^\circ$$

$$\frac{\omega_{osc}}{\omega_0} = \tan(60^\circ) = \sqrt{3}$$

$$\Rightarrow \boxed{\omega_{osc} = \omega_0 \sqrt{3}}$$



$\Rightarrow$ Also, the min voltage gain per stage must
be such that $\omega_{osc} = \omega_0 \sqrt{3}$

Single gain stage

$$L(s) = \frac{-g_m R_D}{(1 + s/\omega_0)}$$

$$\omega_0 = \frac{1}{R_D C_L}$$

need
gain ≥ 1

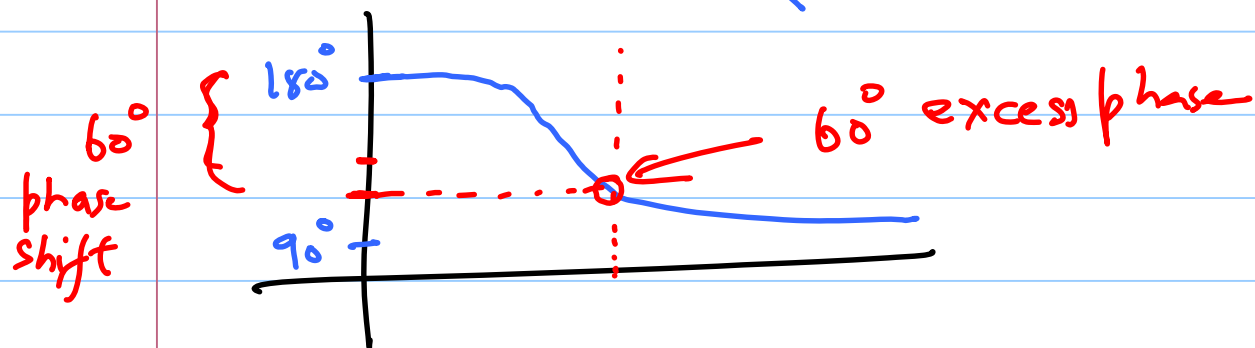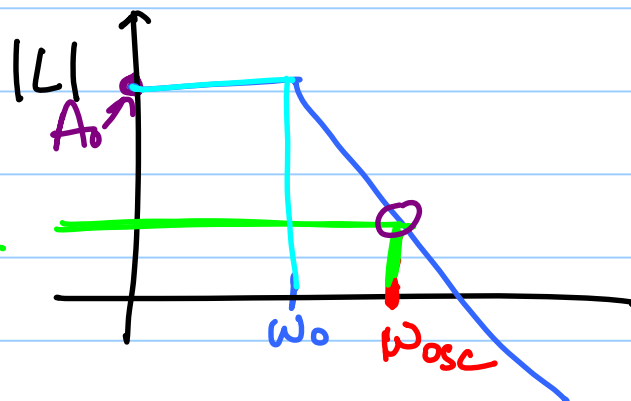

$$\angle \tan^{-1}\left(\frac{\omega}{\omega_0}\right) = \angle 60^\circ$$

$$\omega_{osc} = \omega_0 \sqrt{3}$$

need a loop-gain of 1 at $\omega_{osc} = \omega_0\sqrt{3}$

$$|L(j\omega_{osc})| = 1$$

$$\Rightarrow \frac{A_o^3}{\left(\sqrt{1 + \left(\frac{\omega_{osc}}{\omega_0}\right)^2}\right)^3} = 1$$

$$\Rightarrow \frac{A_o}{\sqrt{1 + \left(\frac{\omega_{osc}}{\omega_0}\right)^2}} = 1$$

$$\Rightarrow \frac{A_o}{\sqrt{1+3}} = 1$$

$$\Rightarrow A_o = \sqrt{4} = 2$$

DC gain per stage

$$A_o^3 = 2^3 = 8$$

DC gain of the loop

$\Rightarrow$ We need a DC gain of 2 per stage in a 3-stage oscillator


$$\frac{A_0}{\left(1 + \frac{s}{\omega_0}\right)} \leftarrow |g_m R_D| \geq 2$$

Two conditions

$$A_0 \geq 2$$

$$\omega_{osc} = \omega_0 \sqrt{3}$$
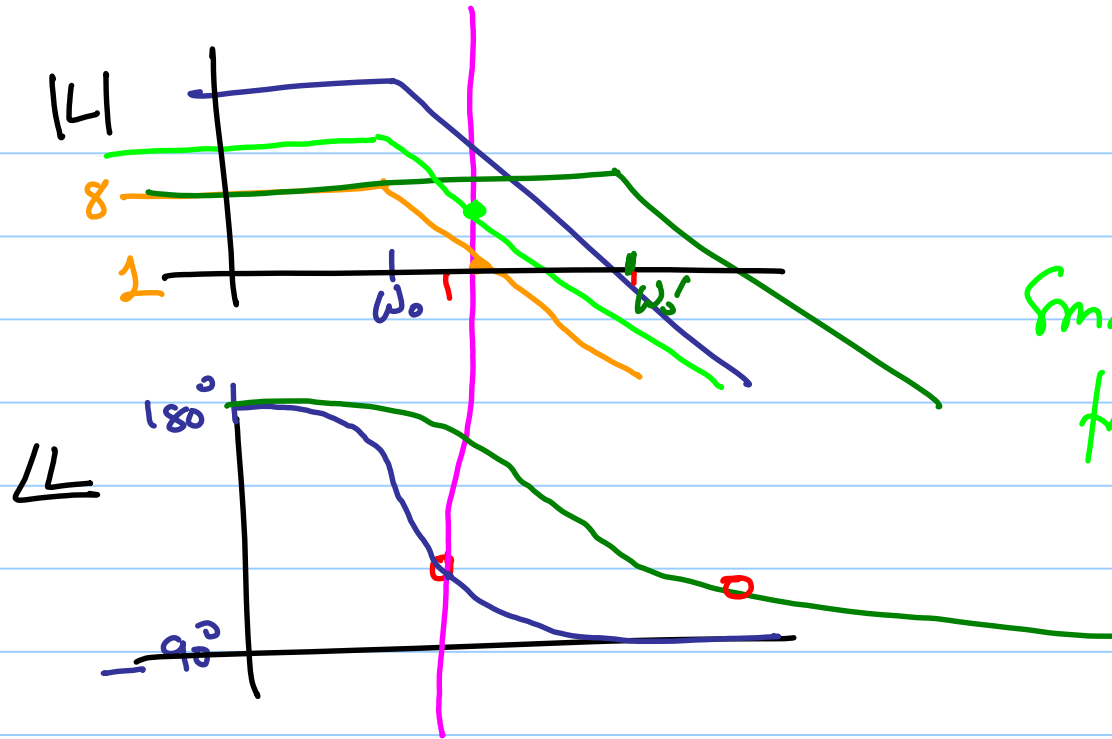
$$L(s) = \frac{-A_0^3}{\left(1 + \frac{s}{\omega_0}\right)^3}$$



Small signal
transfer function

* what happens when $A_0 \neq 2$

- for $A_0 < 2$, the circuit fails to oscillate
- for $A_0 > 2$??
..

$$L(s) = \frac{-A_0^3}{(1+s/\omega_0)^3}$$

$$H_{CL}(s) = \frac{V_{out}}{V_{in}}(s) = \frac{\frac{-A_0^3}{(1+s/\omega_0)^3}}{1 + \frac{A_0^3}{(1+s/\omega_0)^3}}$$

$$= \frac{-A_0^3}{\left(1 + \frac{s}{\omega_0}\right)^3 + A_0^3} \leftarrow D(s) = 0$$

closed-loop poles?

$$\left(1 + \frac{s}{\omega_0}\right)^3 + A_0^3 = 0$$

3 roots of the
polynomial

$$s = \begin{cases} -(A_0 + 1)\omega_0 \\ \left(\frac{A_0(1 \pm j\sqrt{3})}{2} - 1\right)\omega_0 \end{cases}$$

*

$$e^{-(A \pm j)\omega_0 t}$$



exponentially decaying term.

*


the complex conjugate poles.

$$\omega_{p_{2,3}} = \omega_0 \left[\frac{A_0 (1 \pm j\sqrt{3})}{2} - 1 \right]$$



steady-state response


→ for $A_0 = 2$
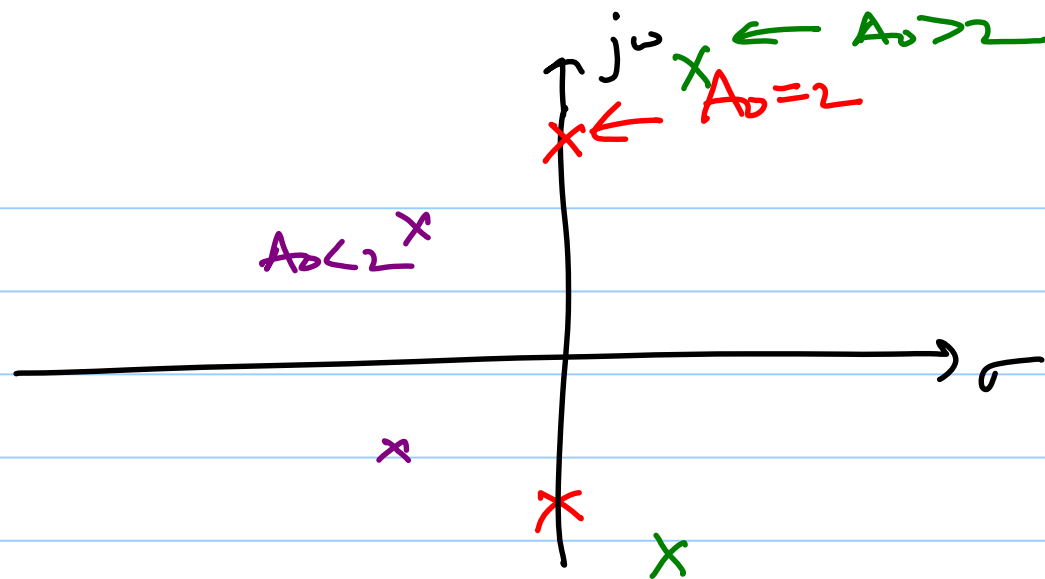
$$\omega_{p_{2,3}} = \omega_0 [1 \pm j\sqrt{3} - 1] = \pm j\omega_0\sqrt{3}$$



$f_w \quad A_0 > 2$

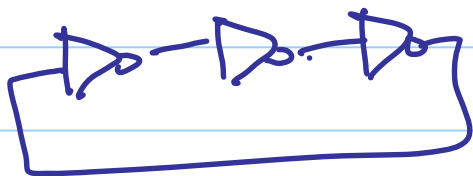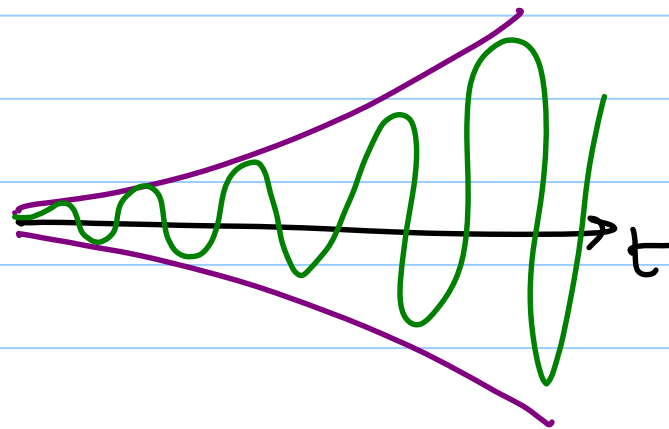

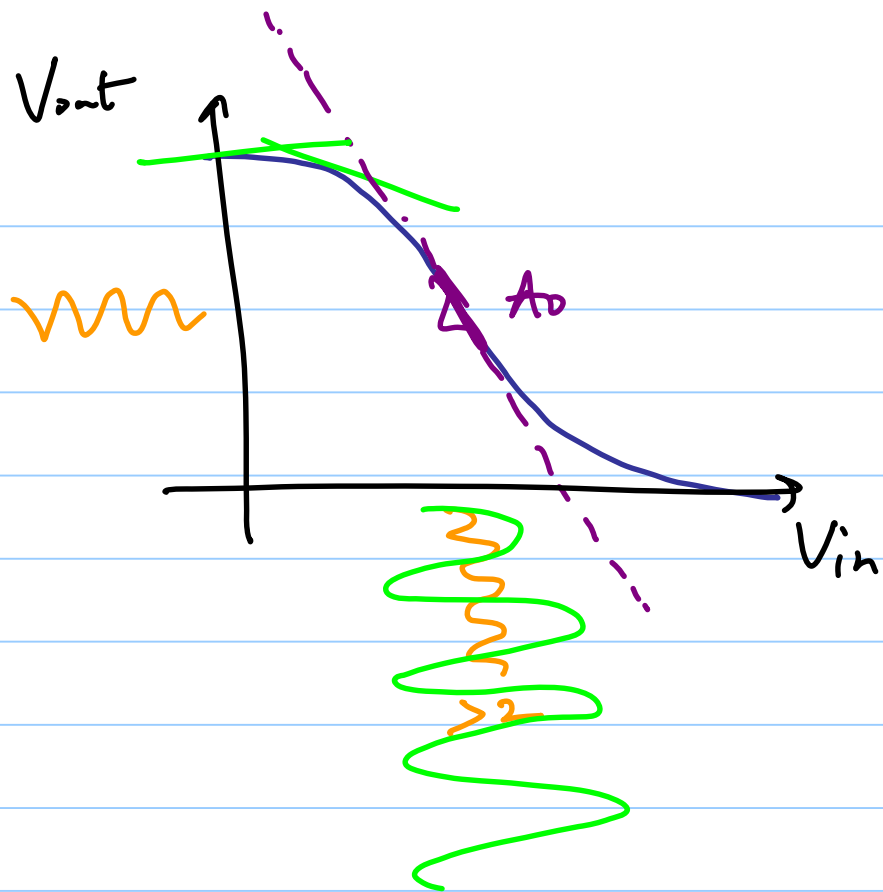

* In practice, as the oscillation amplitude increases

↳ gain stages experience nonlinearity

↳ limits the maximum amplitude

↳ "average loop gain" drops

↳ eventually the conjugate poles move to the $j\omega$ axis



$A_0 > 2$

