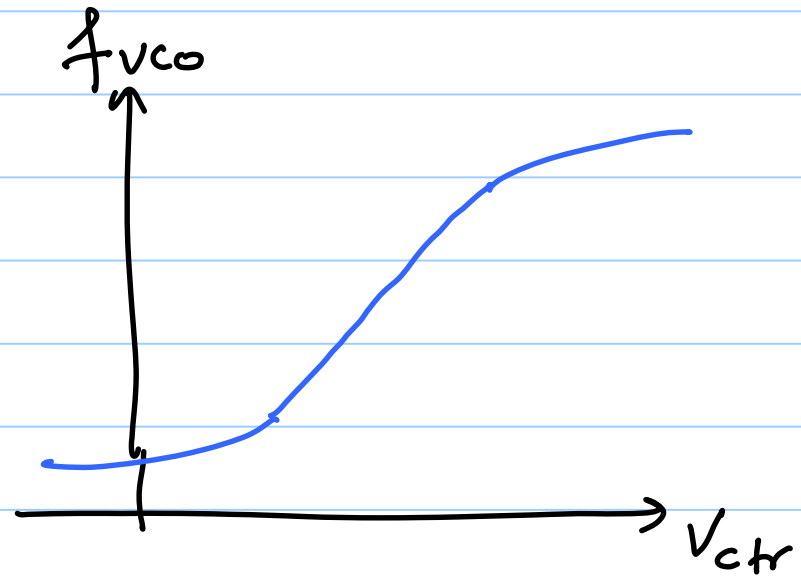


ECE 518 - Lecture 15

Note Title


3/5/2015

VCO tuning curve



See slides on PSS analysis
in Spectre RF

Ring oscillator

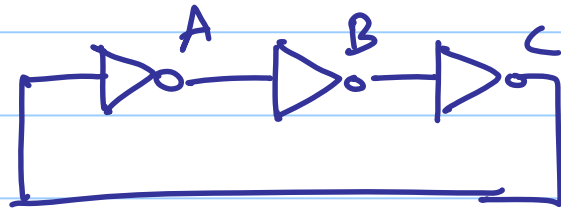


$$A_0 \geq 2$$

$$\omega_{osc} = \omega_0 \sqrt{3}$$

$$\omega_0 = \frac{1}{RC}$$

3-stage
Ring oscillator

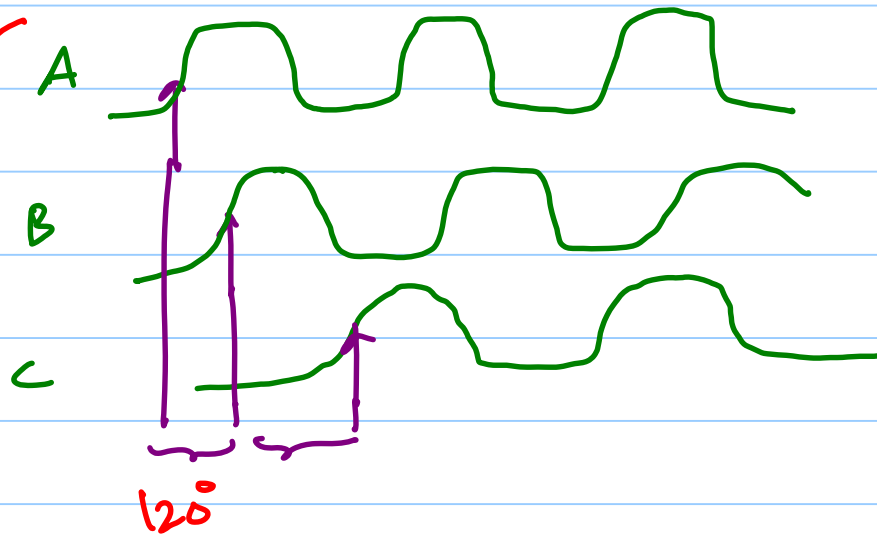


each stage has $\Rightarrow$ 180° phase shift
 60° excess phase shift


$$240^\circ = 360^\circ - 120^\circ$$

$$2 \times 3 \times T_d = T_{ck}$$

$$T_{ck} = 6T_d \stackrel{D}{=} 2N T_d$$
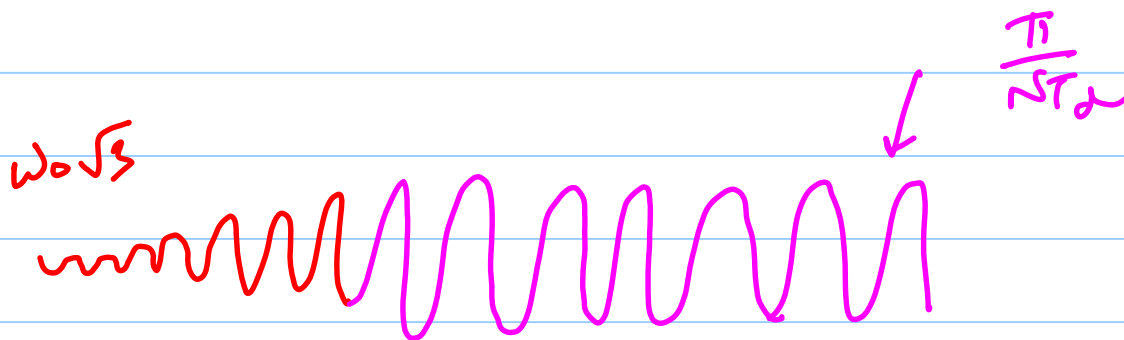
$$\omega_{sc} = \frac{2\pi}{T_{ck}} = \frac{2\pi}{2N T_d} = \boxed{\frac{\pi}{N T_d}}$$



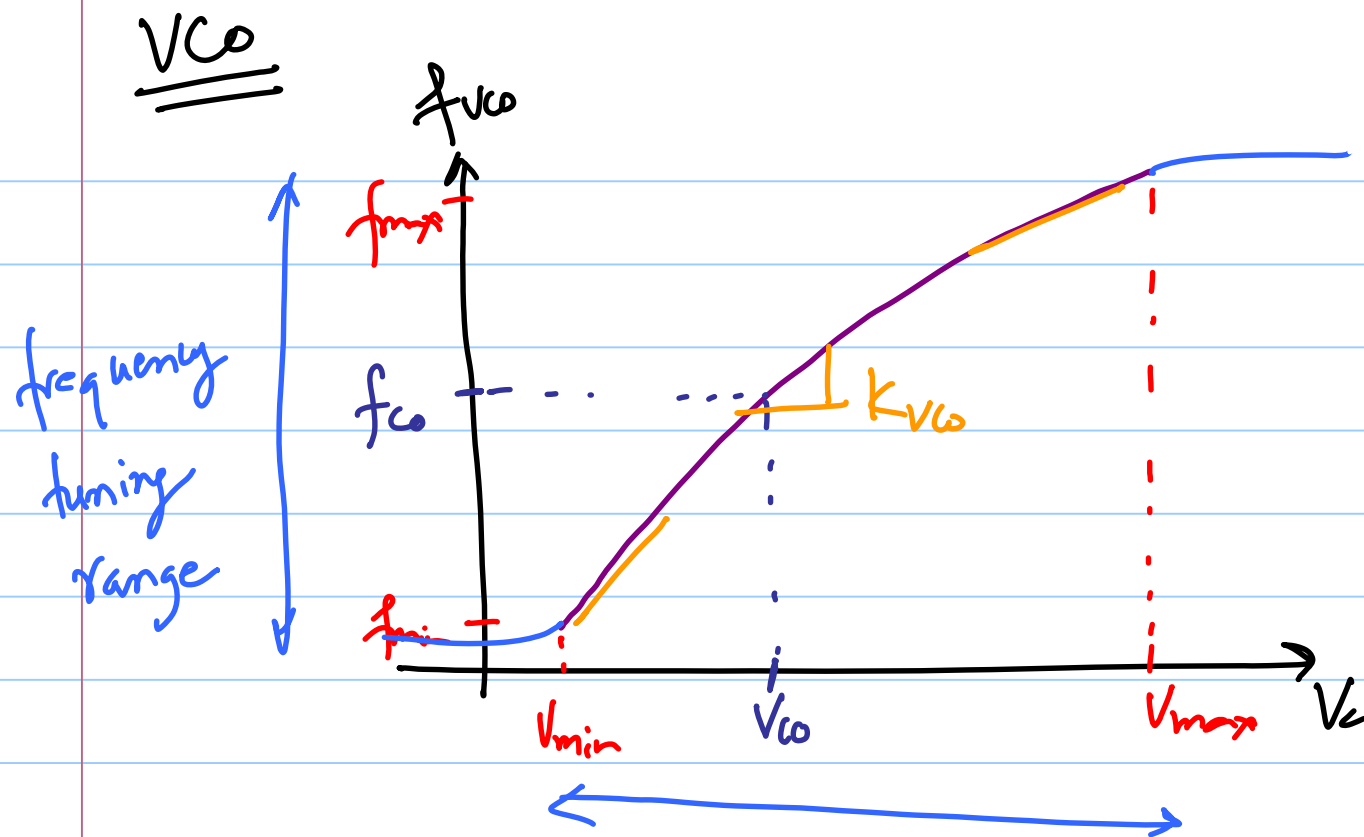

$$f_{vco} = f_0 + 2\pi K_{vco}(V_c - V_0)$$

incremental phase

$$\phi_{out} = 2\pi K_{vco} \int_{-\infty}^t V_c dt$$


$$\rightarrow \phi_{out}(s) = \frac{2\pi K_{vco} \cdot V_c(s)}{s}$$

Performance Metrics:

* Tuning Range


$\rightarrow$ Need wide-enough tuning range to cover all the PVT variations

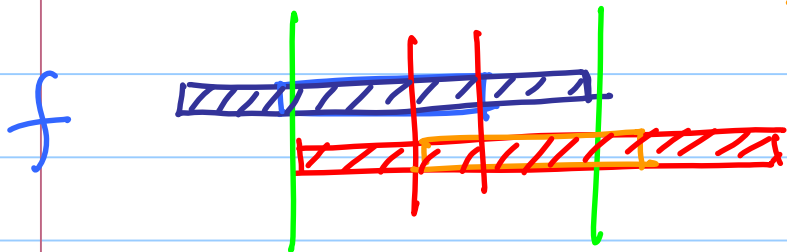$\rightarrow$ PVT can cause 750% freq variation



Digital ASIC clock gens $\rightarrow$ 5x tuning range
Ex. 100 MHz - 500 MHz

* Tuning linearity

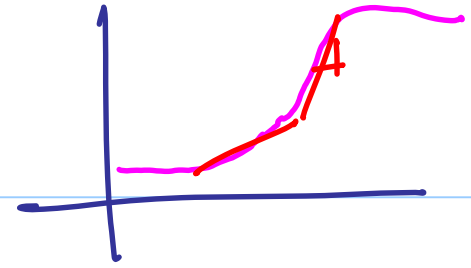

↳ Affects loop dynamics $\rightarrow$ BW & ϕ_m

↳ 2x - 3x Variation in K_{VCO} if not linearized

* Can "linearize" V_{CO}

* Power:




↳ Meet jitter specs with
lowest possible power



$$\propto N C V^2 f$$

Power Supply rejection:

↳ critical in ASIC PLLs

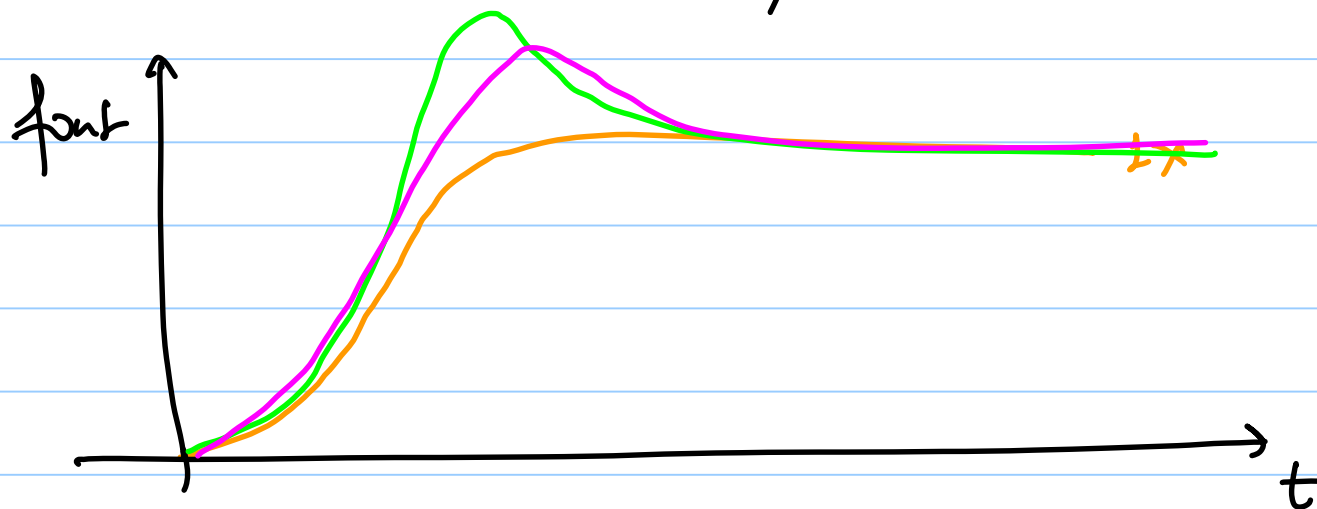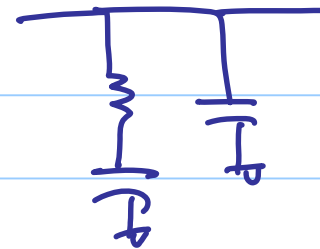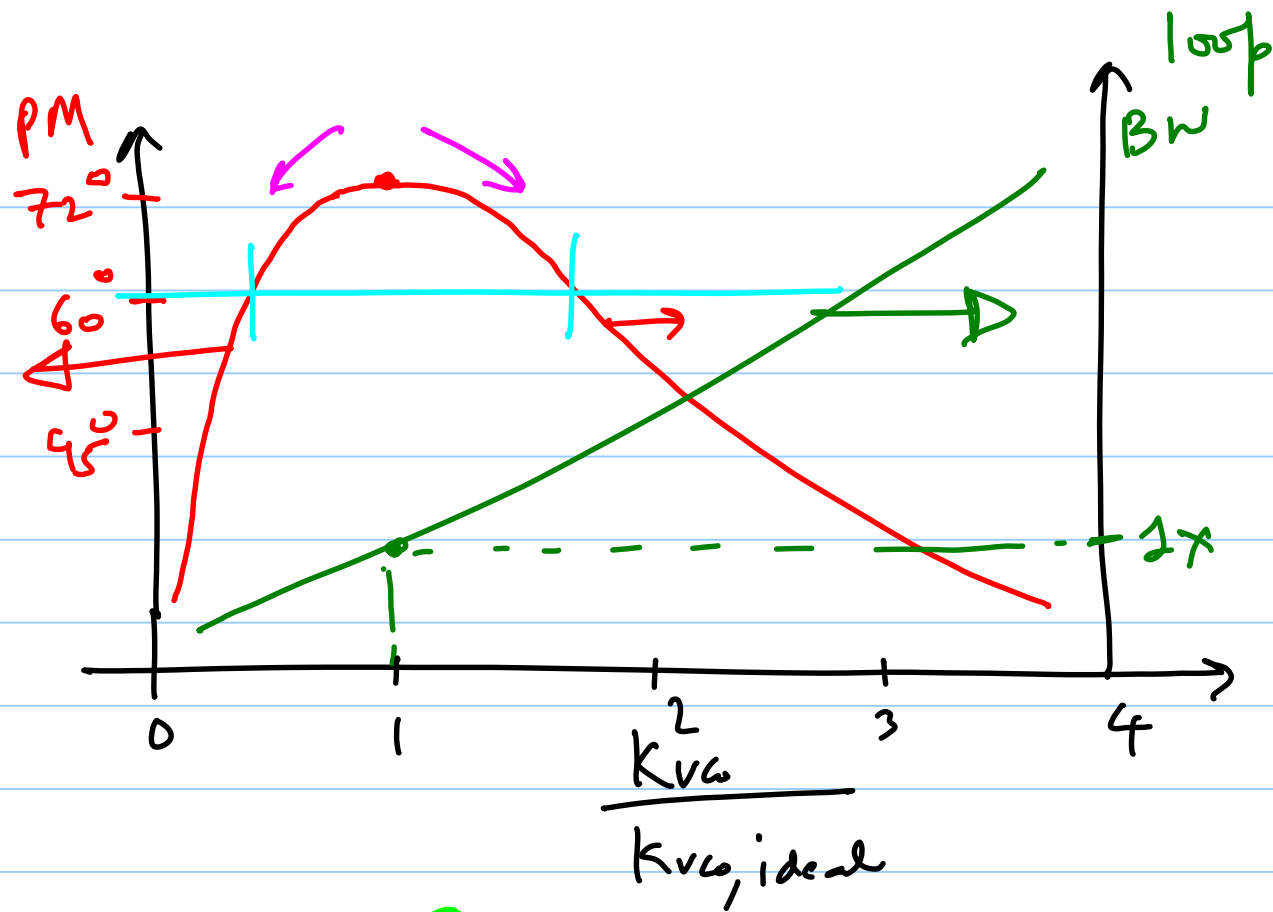
↳ Typically limits the jitter performance




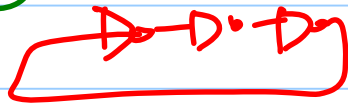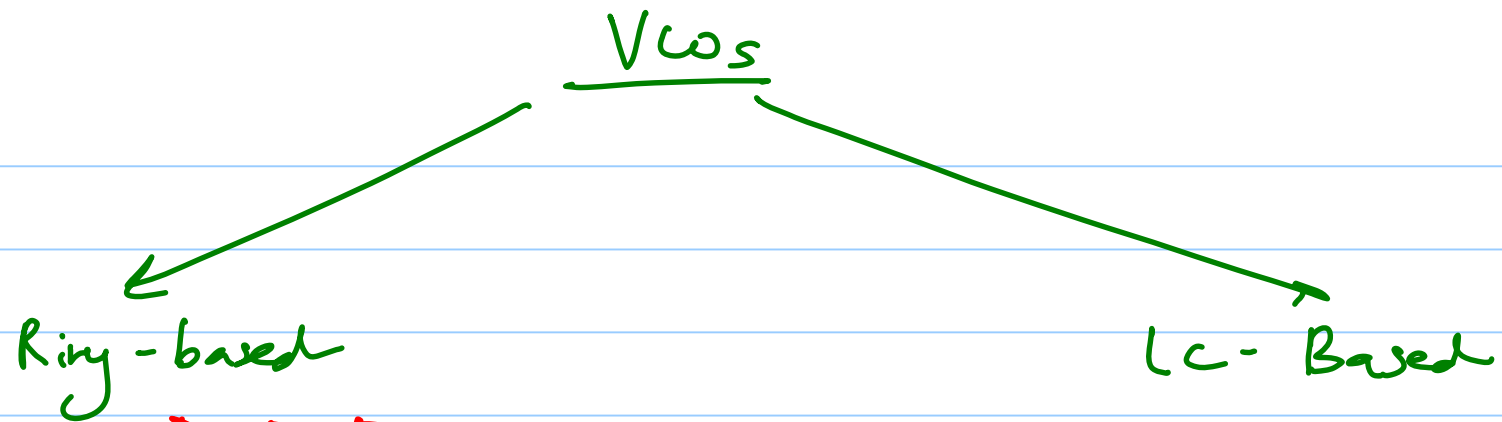


low swing

full- V_{DD} swing

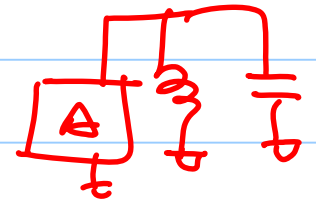


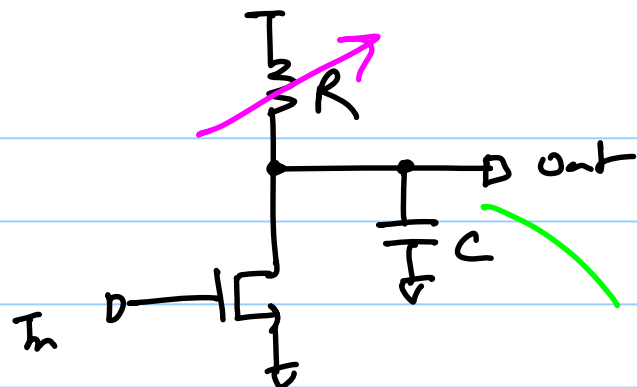
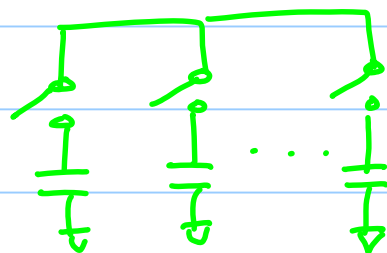
$$\omega_{osc} = \frac{\sqrt{3}}{R_C} \quad \text{for 3-stages}$$



Digital control

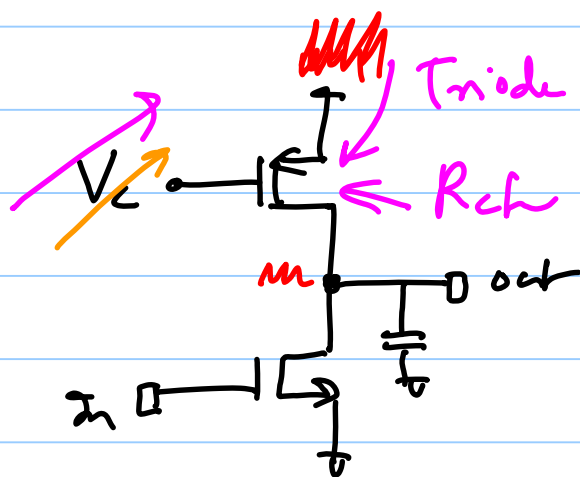


Single-ended stage

$$R_{ch} = \frac{1}{\beta [(V_{SG} - V_{THP}) - V_{SD}]}$$

$V_{DD} - V_c$

V_{SD}
deep triode

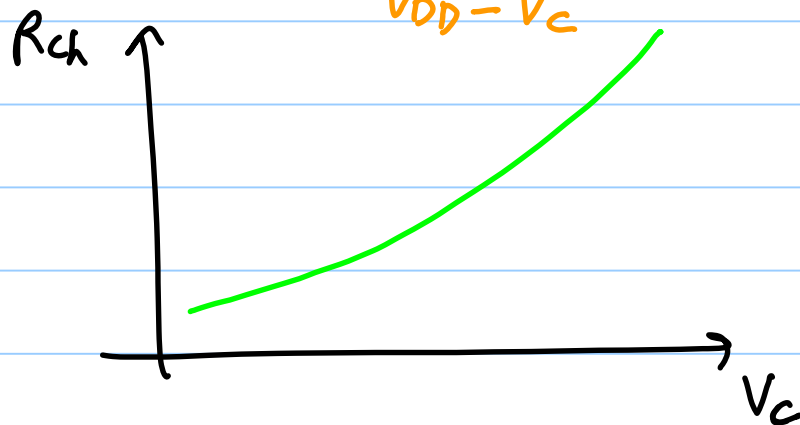

Differential Stage

