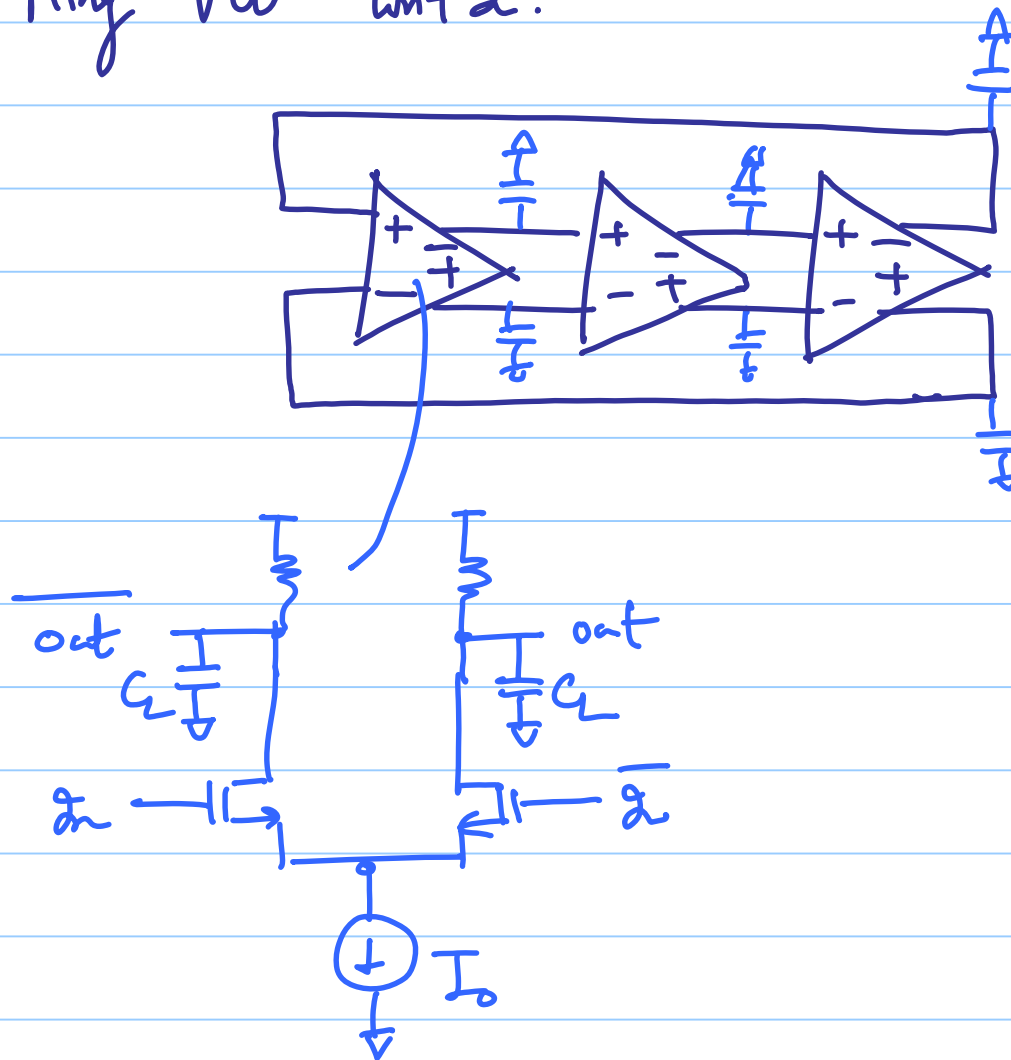


ECE 518- Lecture 16




Note Title


3/10/2015

Ring VCO int'd.



Low swing
Large swing

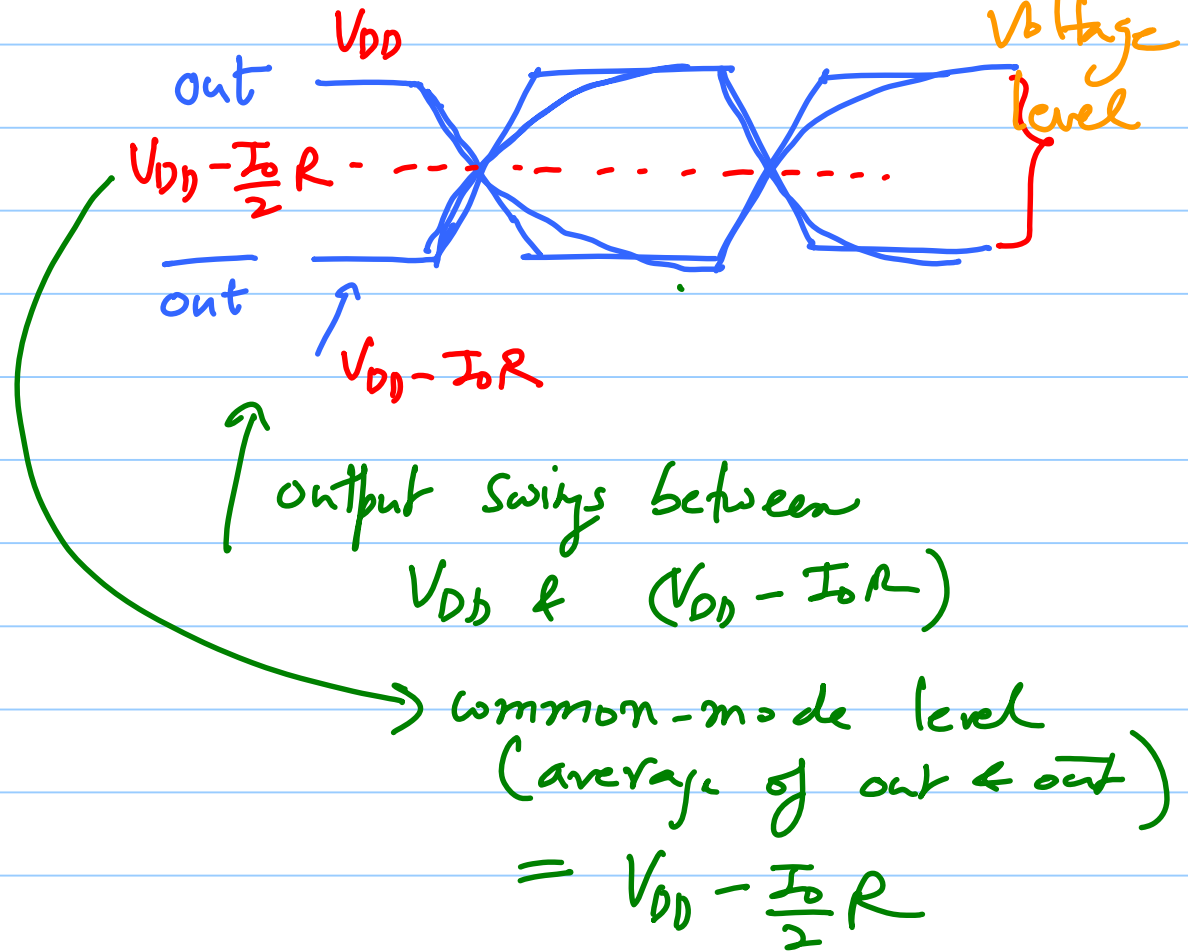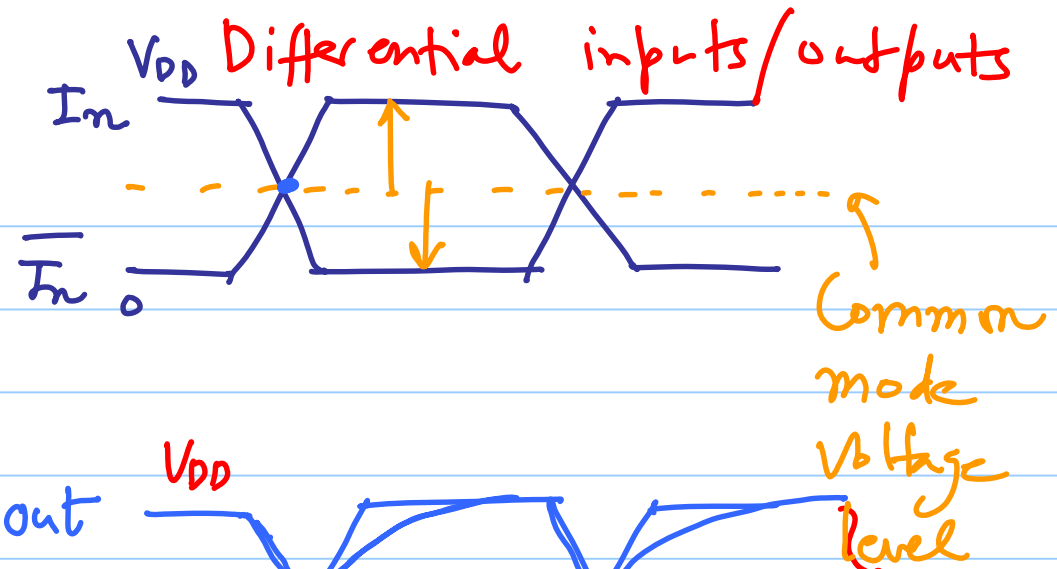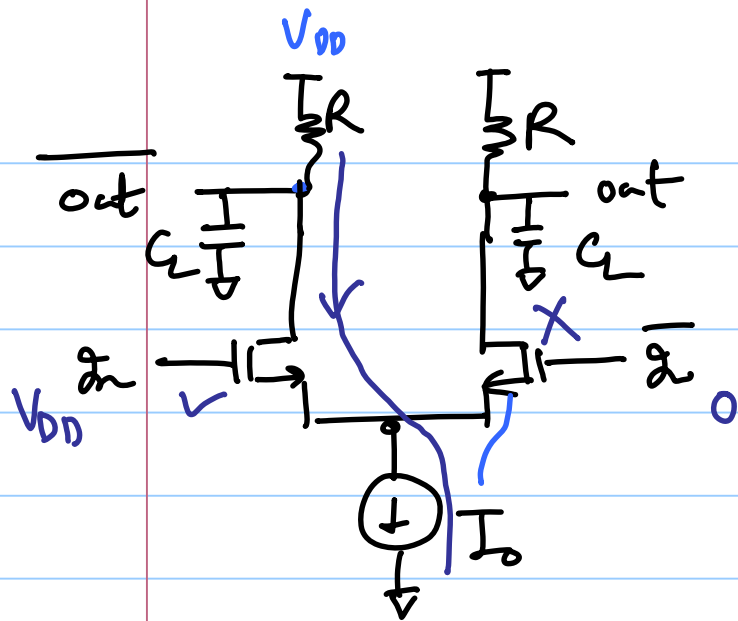

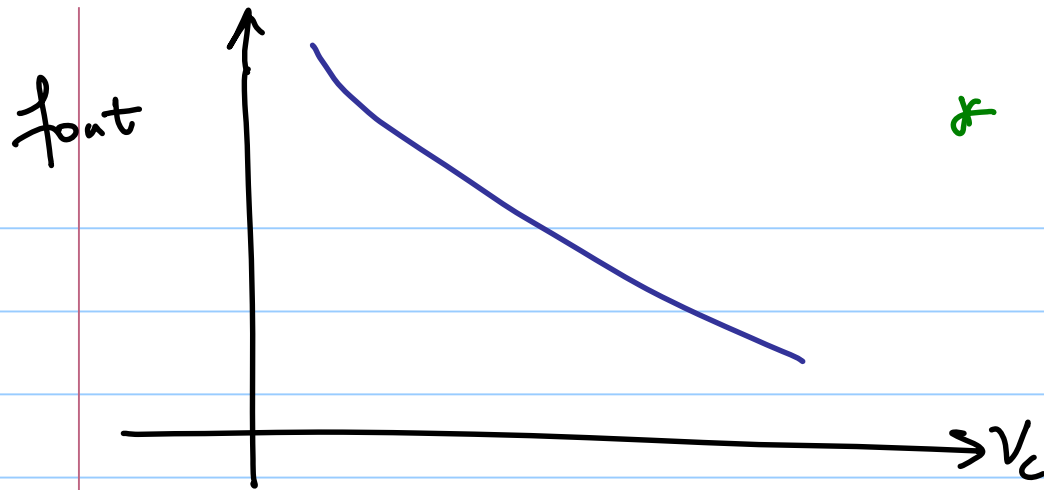

* Valid only when the load transistors are in triode

$$V_{SD} < V_{SD, sat}$$

$$V_{SD} = I_0 R_{on} = \frac{I_0}{K_{Pn} \frac{W}{L} (V_{DD} - V_L - V_{THP})} < \overbrace{V_{DD} - V_L - V_{THP}}^{V_{SD, sat}}$$

$$(V_{DD} - V_L - V_{THP}) > \sqrt{\frac{I_0}{K_{Pn} \cdot \frac{W}{L}}}$$

If this is not satisfied, then the load transistors enter saturation

$\rightarrow$ VCO characteristics saturate
 $\rightarrow$ output common mode voltage is undefined.

$*$ $V_{\text{swing}} = I_0 R_{\text{on}} \propto \frac{I_0}{f_{\text{out}}} \propto \frac{1}{f_{\text{out}}}$


Frequency dependent
 swing

$R_{\text{on}} \rightarrow$




$f_{\text{out}} \propto \frac{1}{R_{\text{on}} C}$

$R_{\text{on}} \propto \frac{1}{f_{\text{out}}}$


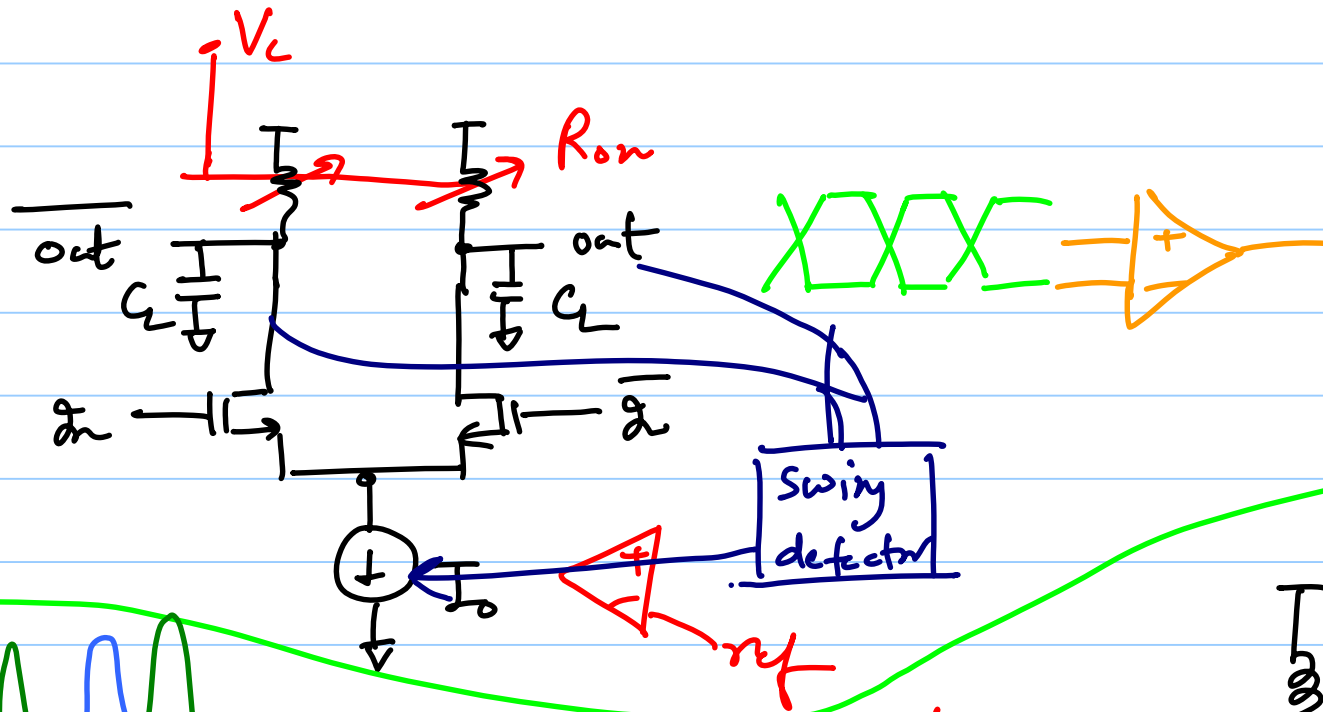
$V_c \uparrow \Rightarrow R_{on} \uparrow$
 $f_{out} \downarrow$
 $Swing \uparrow$




ASIDE

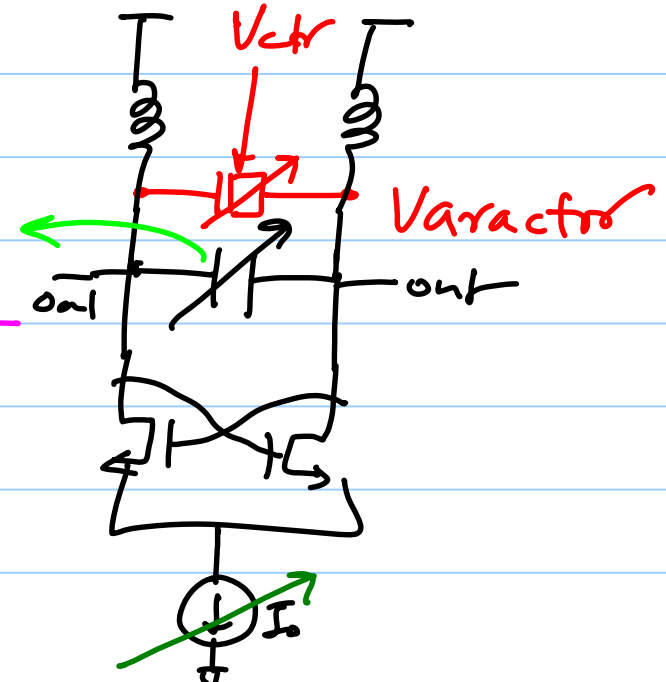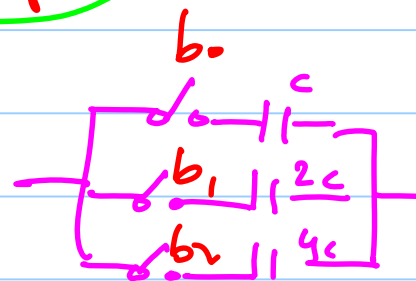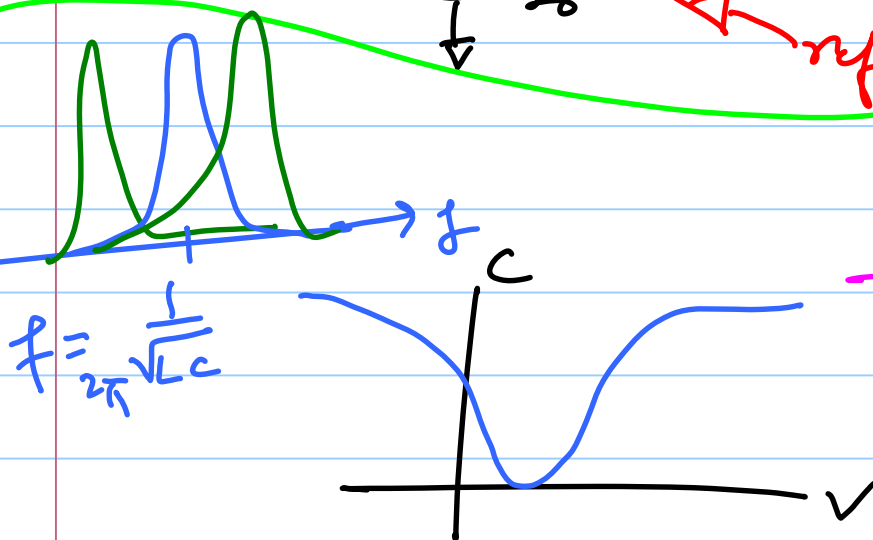


$$f_{osc} = \frac{1}{2\pi \sqrt{LC}}$$

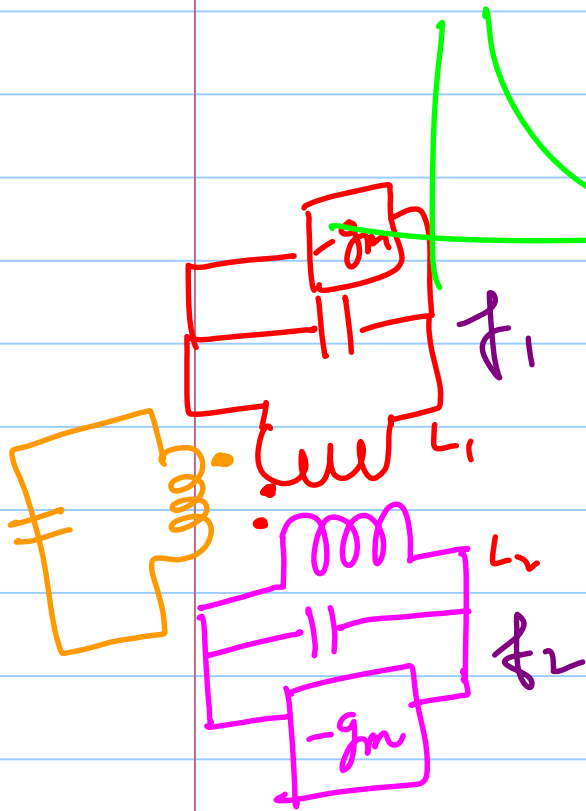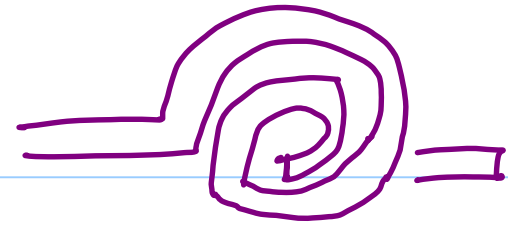

SDR
0-6 GHz

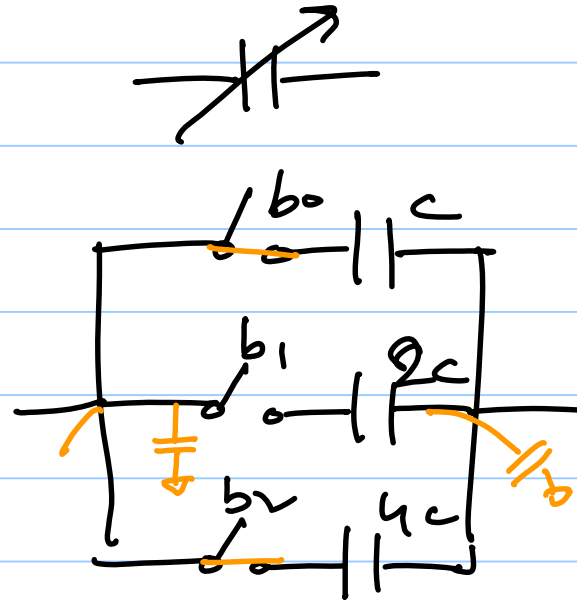



C_{con}
C_{off}

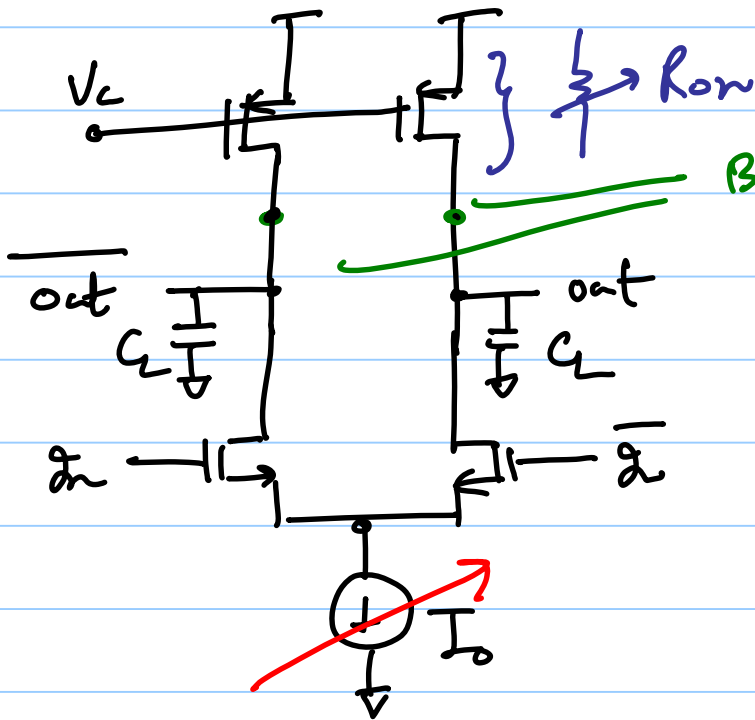


Better fix the CM-level

→ control the current for tuning the frequency

Replica Biasing

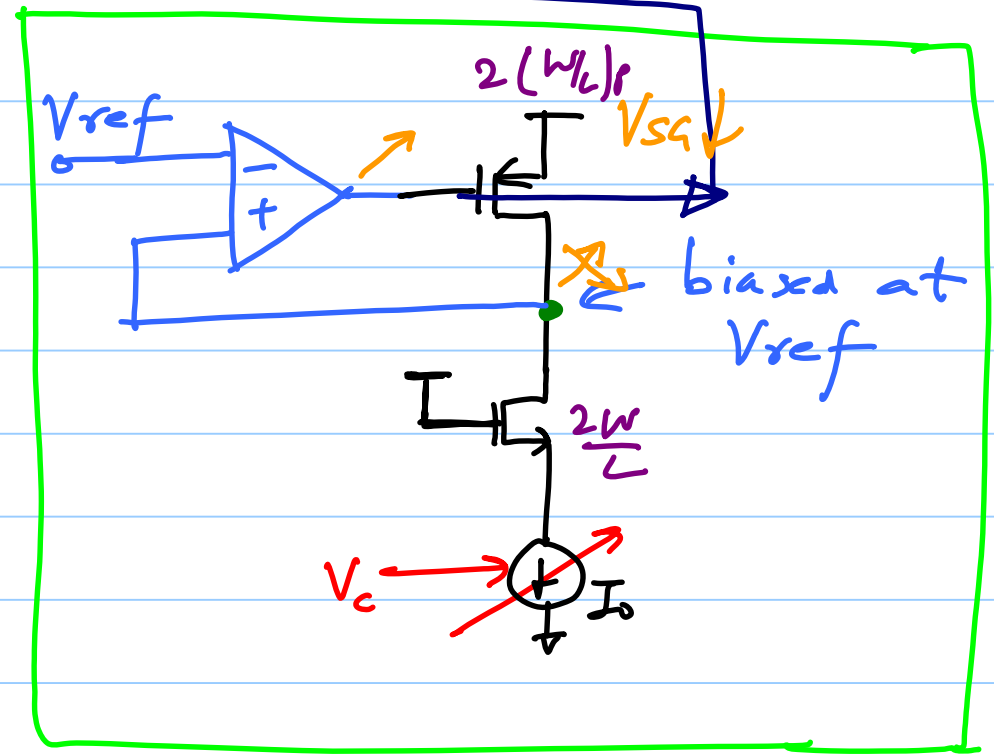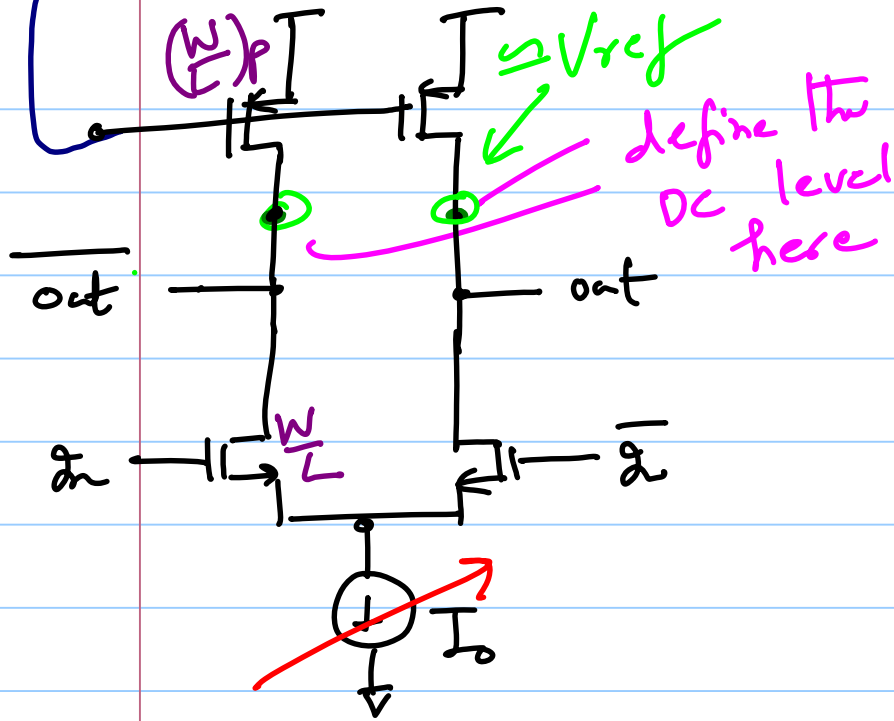


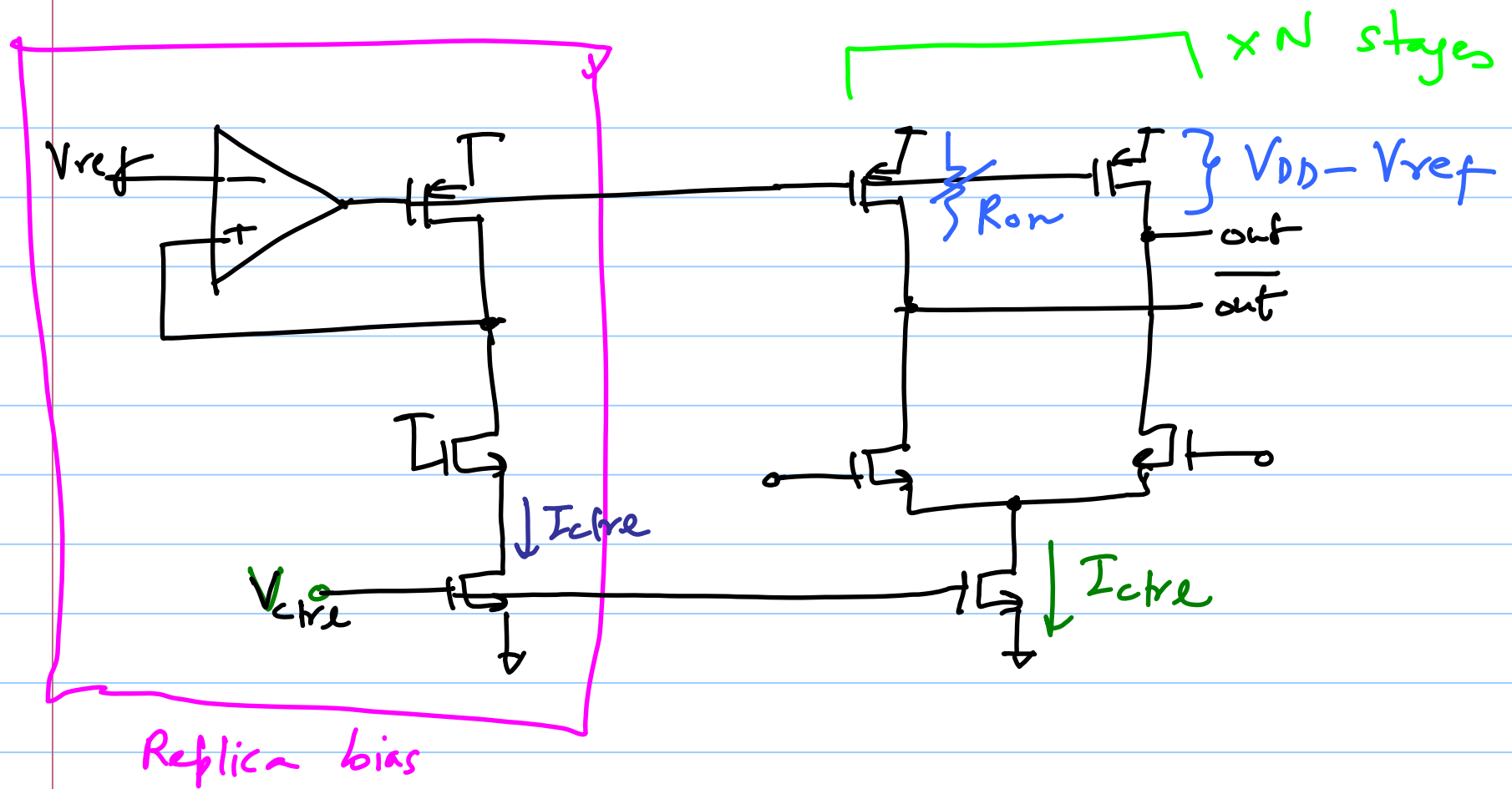




The Replica bias forces $R_{on} = \frac{(V_{DD} - V_{ref})}{I_{ckre}}$

$$f_{out} \propto \frac{1}{R_{out} C} \propto \frac{I_{cfr}}{(V_{DD} - V_{ref}) C}$$

$$I_{cfr} = f(V_{cfr}) = \beta \frac{(V_{cfr} - V_{th})^2}{2}$$
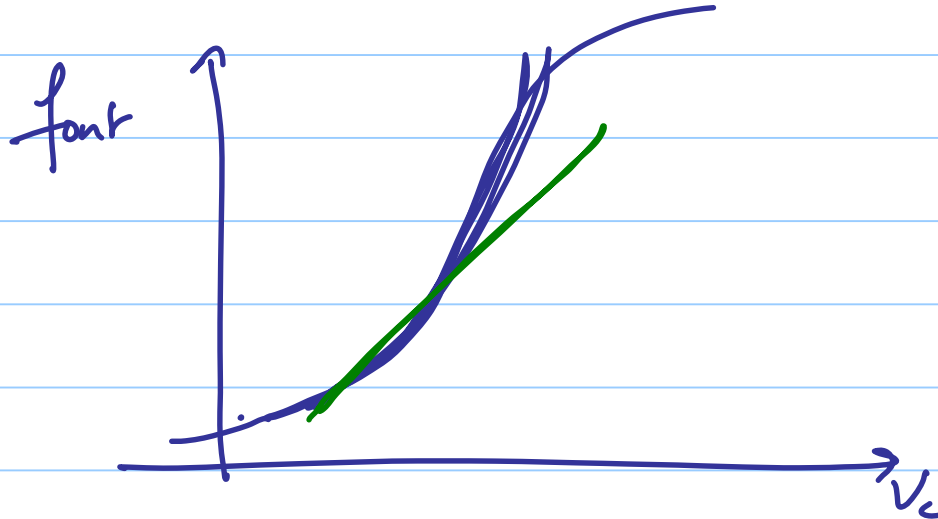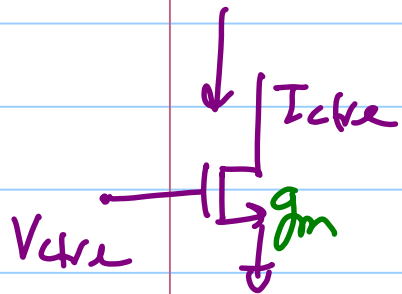
$$\approx g_m V_{cfr} \text{ for small signal}$$



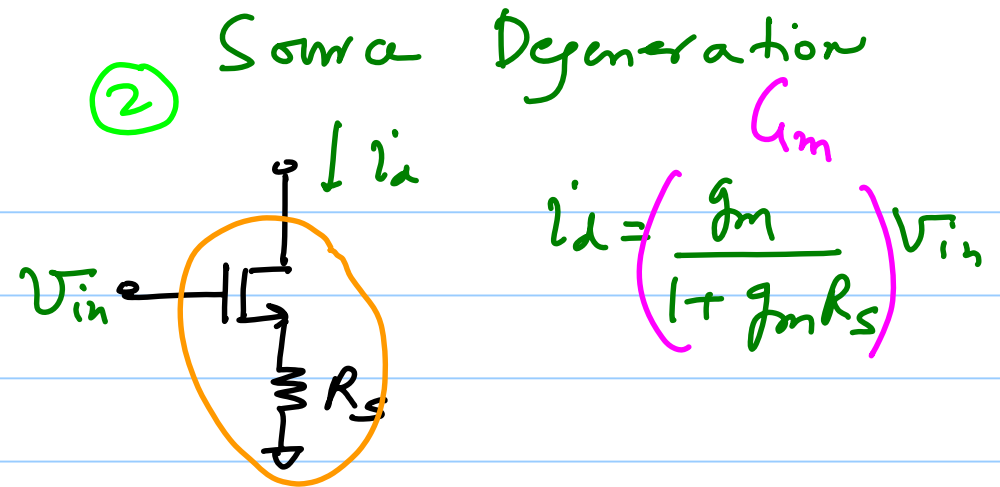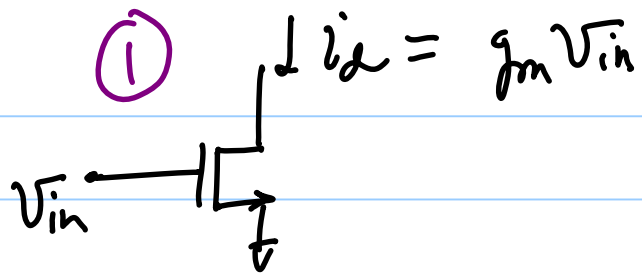


$$g_m = \frac{g_m}{1 + g_m R_s}$$

$$= \frac{g_m}{g_m R_s} \approx \frac{1}{R_s}$$

For $g_m R_s \gg 1$

$$\Rightarrow g_m \gg \frac{1}{R_s}$$

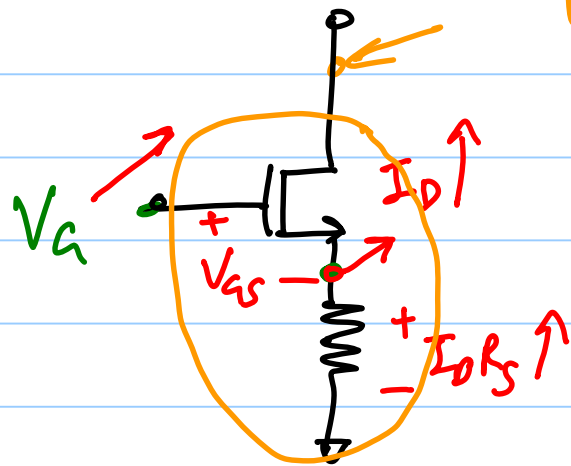


$$V_D > (V_{GS} - V_{THN}) + I_D R_S$$

$$V_{DS} > V_{GS} - V_{THN}$$



$$V_D - I_D R_S > V_G - I_D R_S - V_{THN}$$

$$V_D > V_G - V_{THN}$$

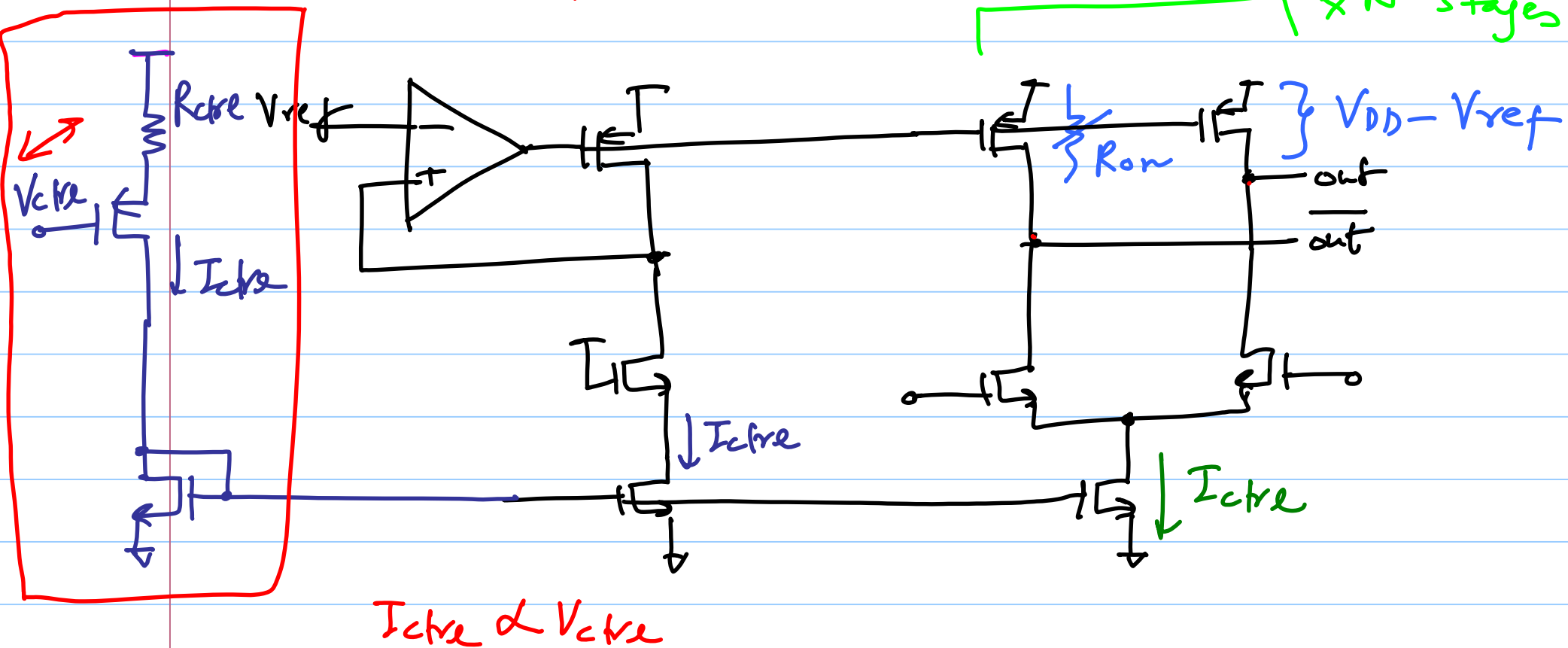
$V2I \leftarrow$ linear voltage to current converter circuit



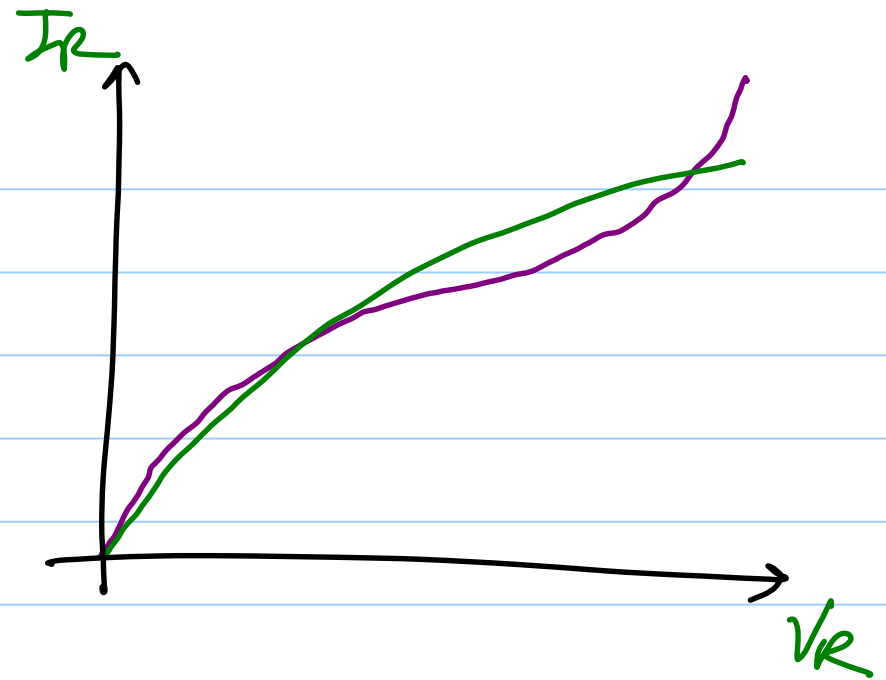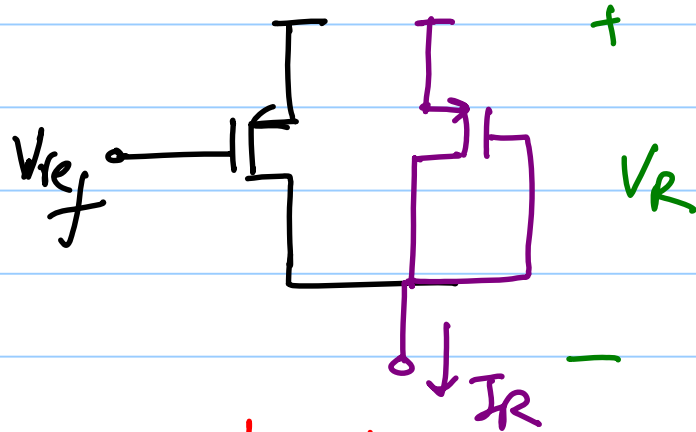* non-linear resistor converts supply noise to differential noise output
↳ poor PSRR



Symmetric loads

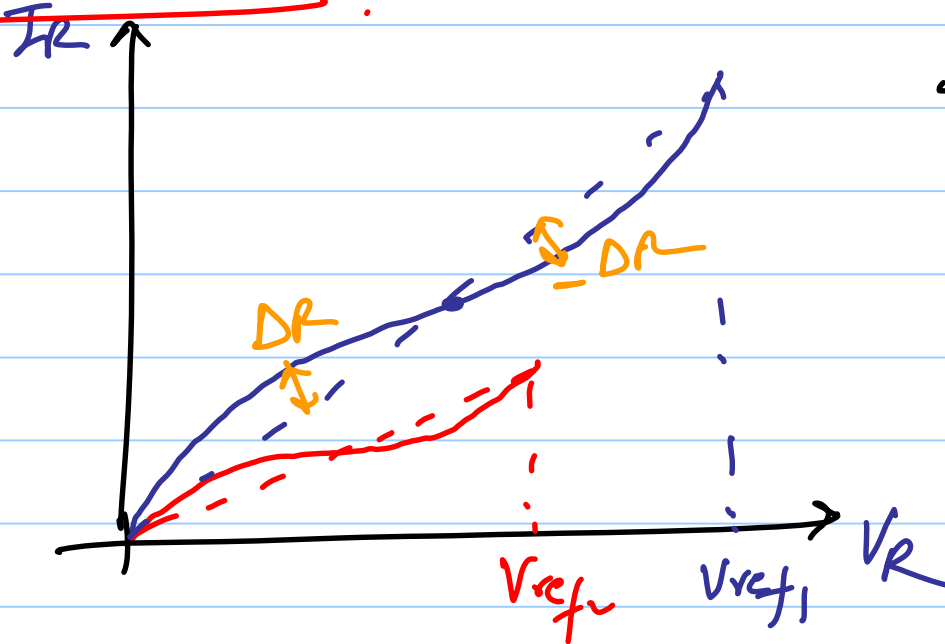

Symmetric I-V char

↳ Symmetric resistor

↳ Better PSRR