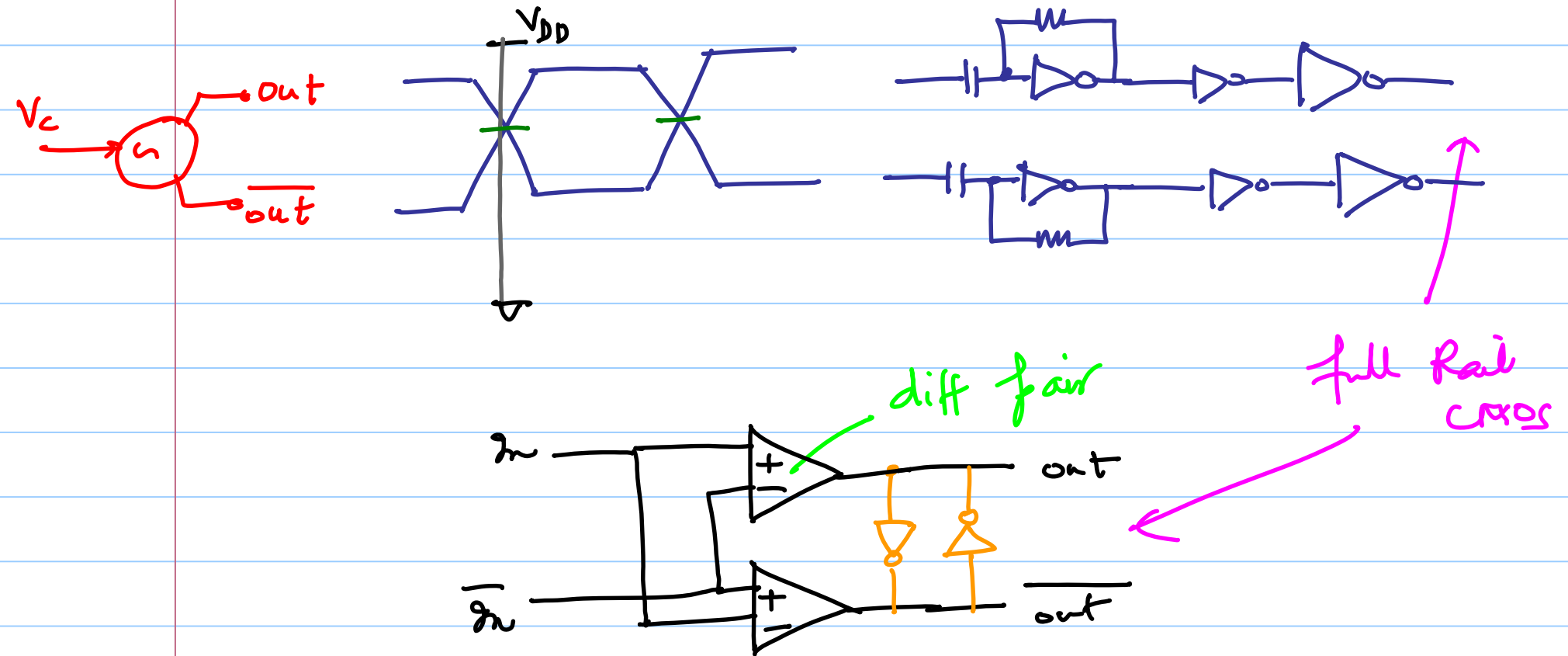



ECE 518 - Lecture 18

Note Title

3/17/2015

VCO Buffers :




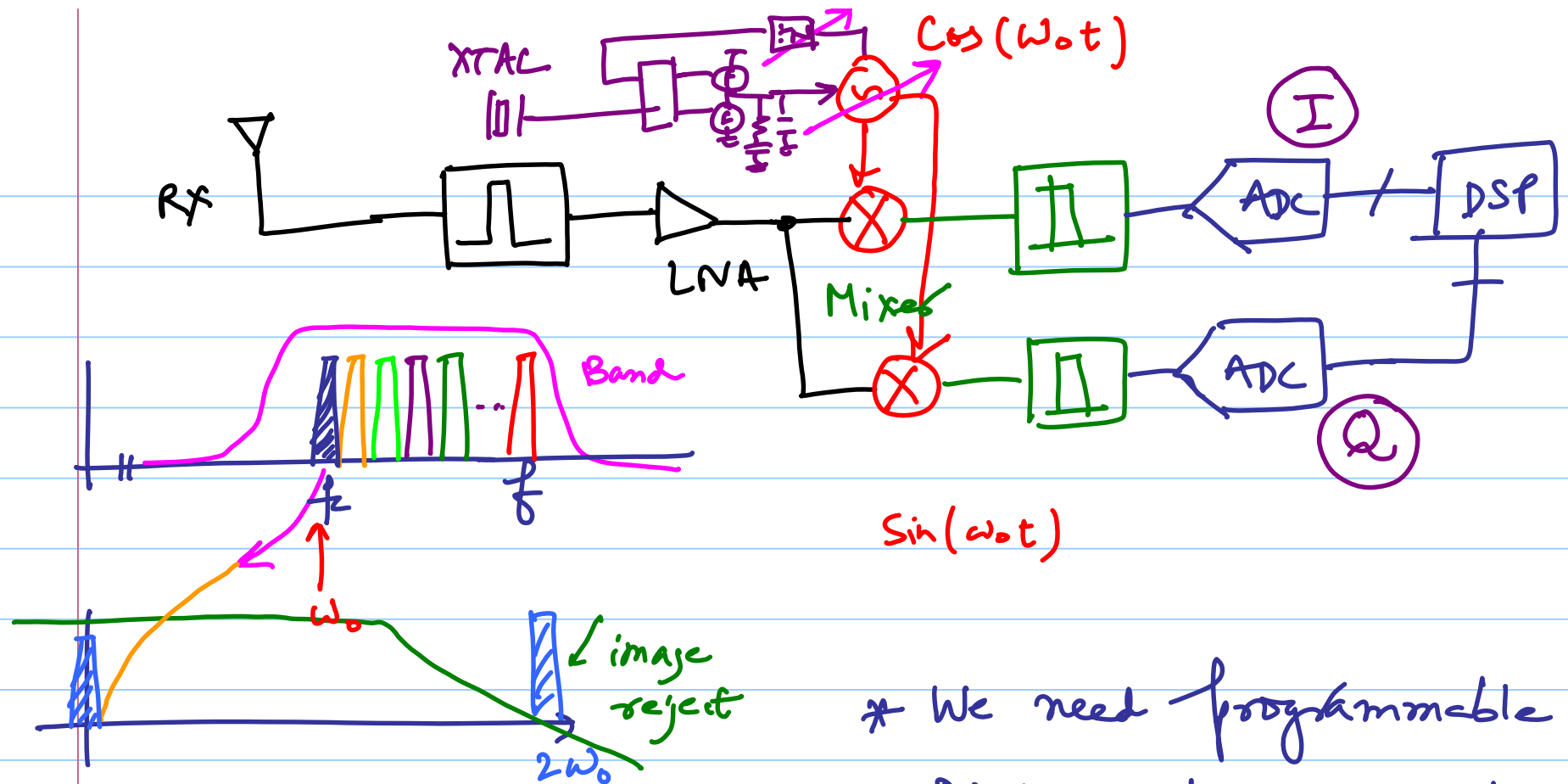

* We need programmable Dividers to cover all channels with a given frequency spacing & within specified switching time.

16

$\div 16$

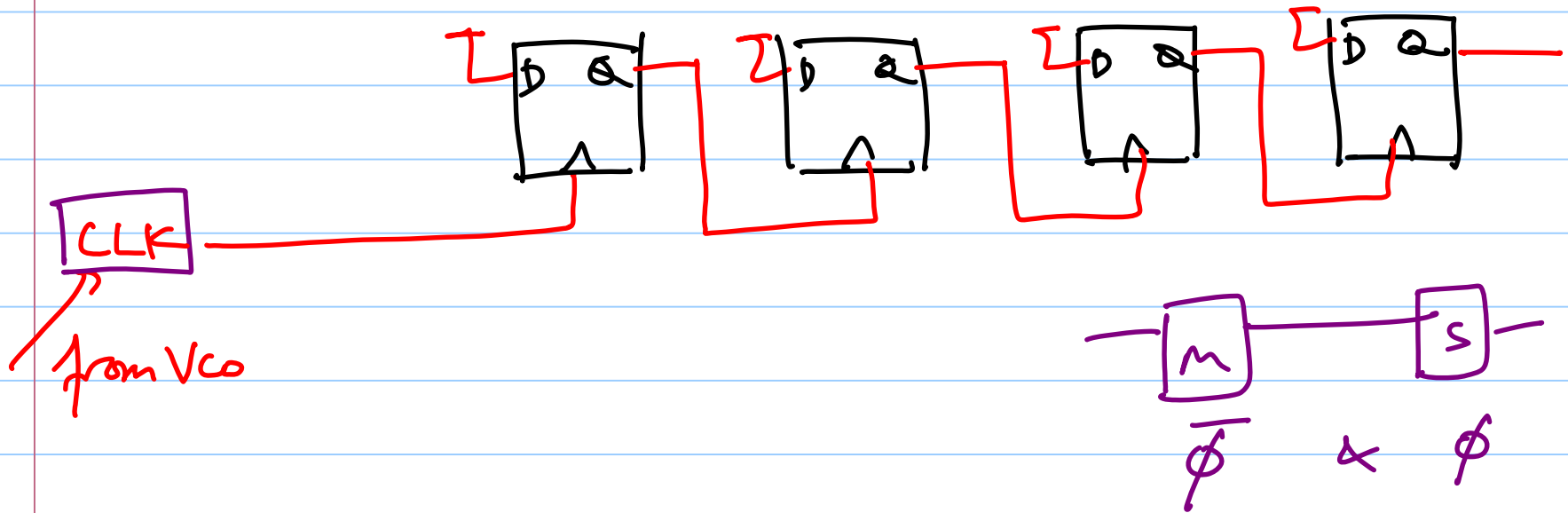


TSPC Latch

↳ True Single phase clock
(Dynamic Logic)

Oscillator Phase Noise Overview

Ideal
Oscillator


$$A \cos \omega_c t$$

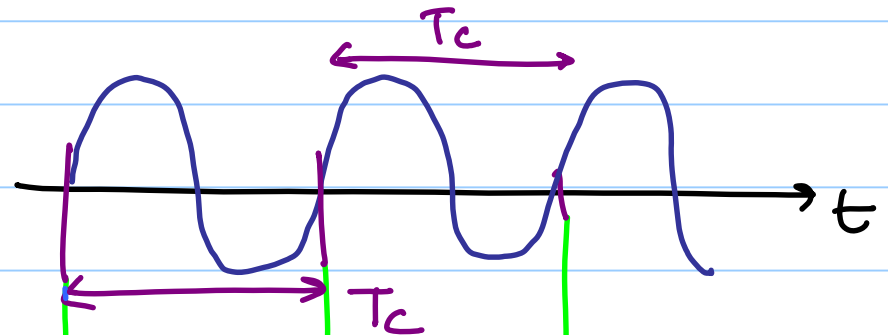


Noisy
Oscillator

$$A \cos(\omega_c t + \phi_n(t))$$

↑
phase noise

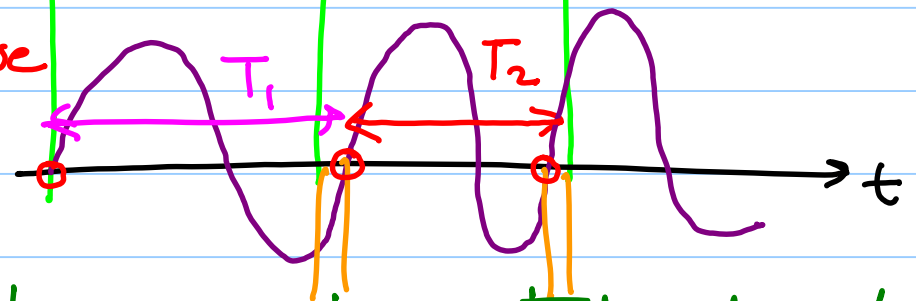

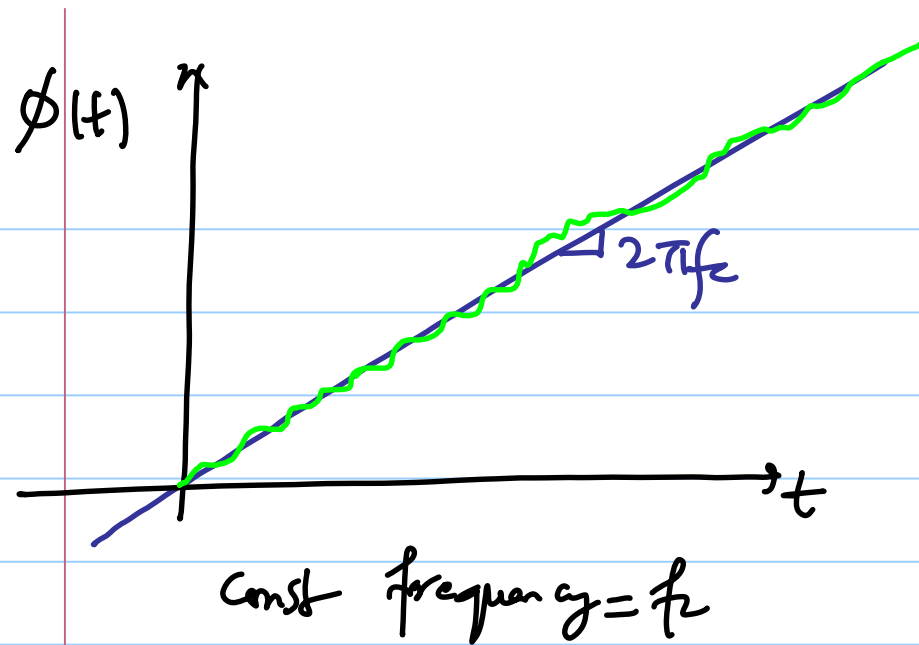* $\phi_n(t)$ is a random phase quantity that deviates
zero crossings from multiples of T_c



$\phi_n(t) \rightarrow$ random noise
(random process)


zero mean
 σ^2

$\Rightarrow$ Gaussian

power spectral density
PSD




Ideal

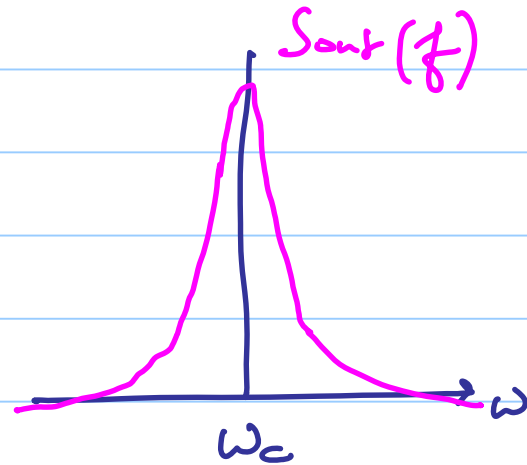

Real

impulse is 'broadened' due to phase noise

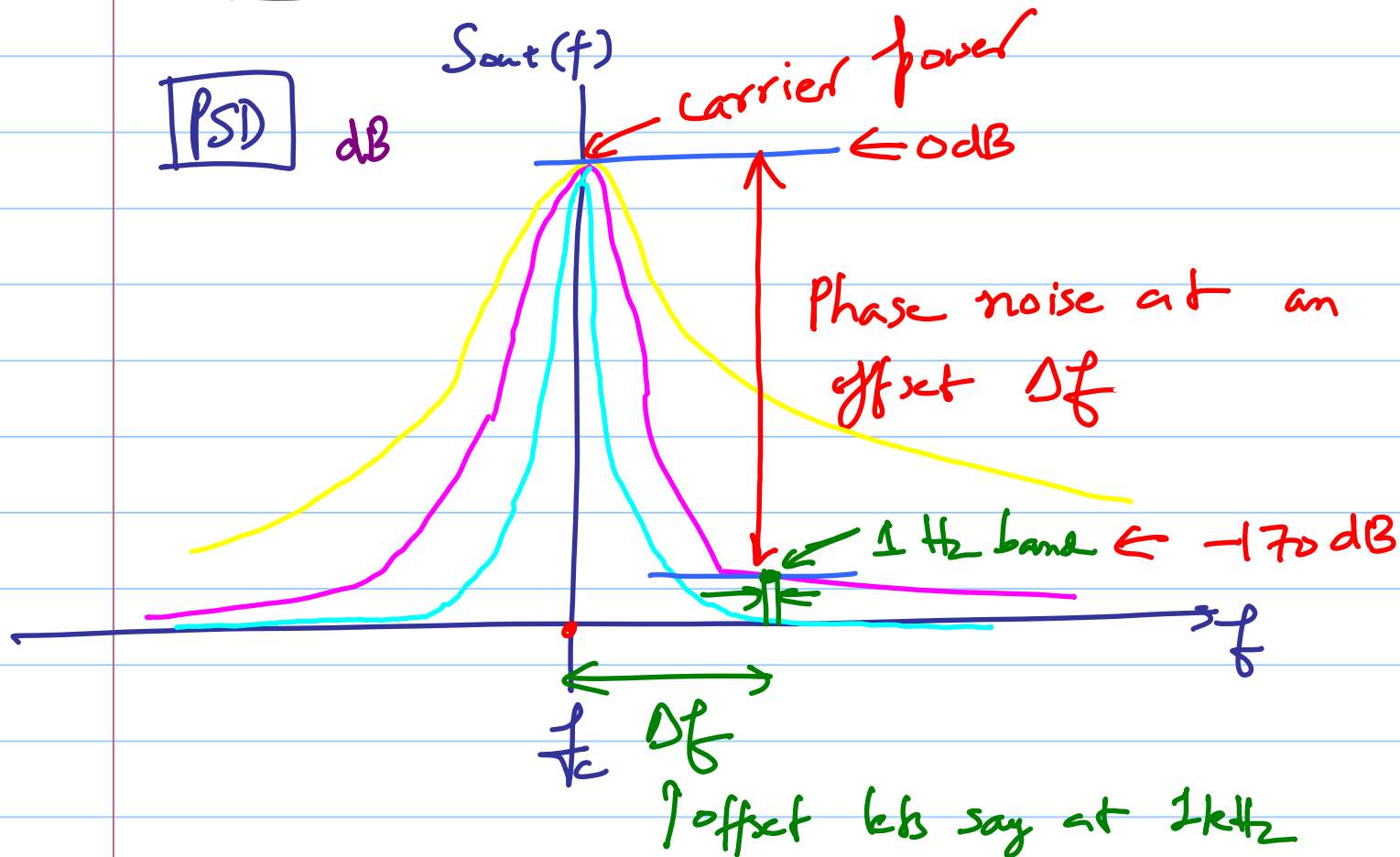specification of the oscillator phase noise



Normalize the power at $f_c + \Delta f$ in 1 Hz BW
w.r.t. to the power of the carrier peak

Ex.

* -170 dBc/Hz at an offset of
1 kHz


Ex GSM:

$< -115 \text{ dBc/Hz}$ at 600 kHz offset

spectrum analyzer measures power of

$$A \cos(2\pi f + \phi_n(t))$$

Oscillator

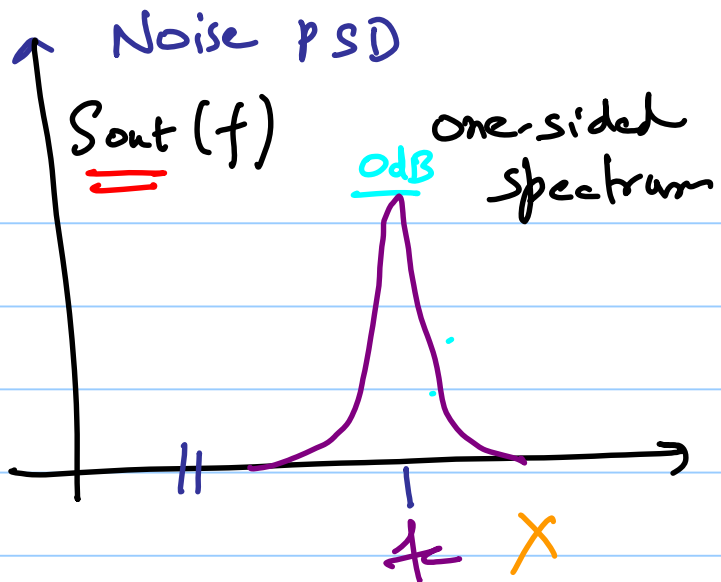

VOLTAGE DOMAIN

