
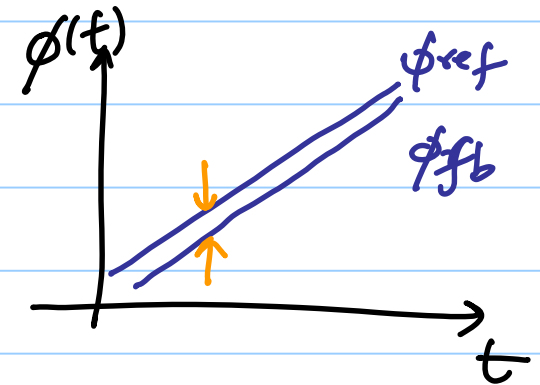


ECE 518 - Lecture 3

Note Title

1/20/2015

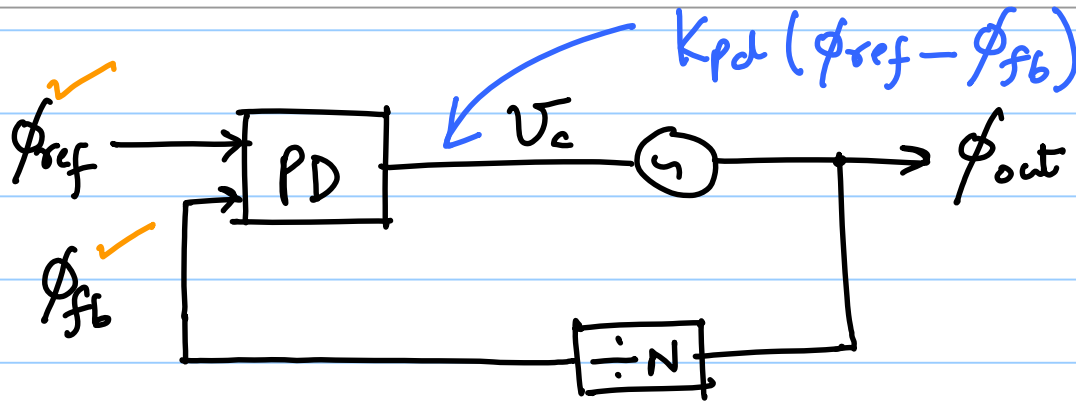

In steady state $\Rightarrow V_c \rightarrow \text{constant}$

$$f_{vco} = f_0 + K_{vco} V_c$$


$$f_{vco} = N f_{ref}$$

$$V_c = \frac{f_{vco} - f_0}{K_{vco}}$$

In steady-state $V_c = \frac{N f_{ref} - f_0}{K_{vco}} \longrightarrow \textcircled{1}$

$$V_c = K_{pd} (\phi_{ref} - \phi_{fb}) \longrightarrow \textcircled{2}$$

from ① & ②, we get

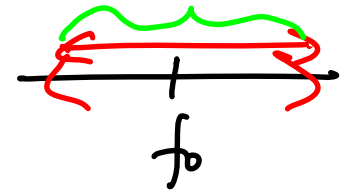

$$\underbrace{\phi_{ref} - \phi_{fb}}_{\Delta\phi} = \frac{\overbrace{N_{ref} - f_0}^{f_{vco}}}{\underbrace{K_{vco} \cdot K_{pd}}_{\text{Combined gain of PD \& VCO}}}$$

→ ②


phase offset

Combined gain of PD & VCO

PD gain	$K_{pd} \Rightarrow \frac{V}{\text{rad}}$	} units are important!
VCO gain	$K_{vco} \Rightarrow \frac{\text{Hz}}{V}$	

PD characteristics
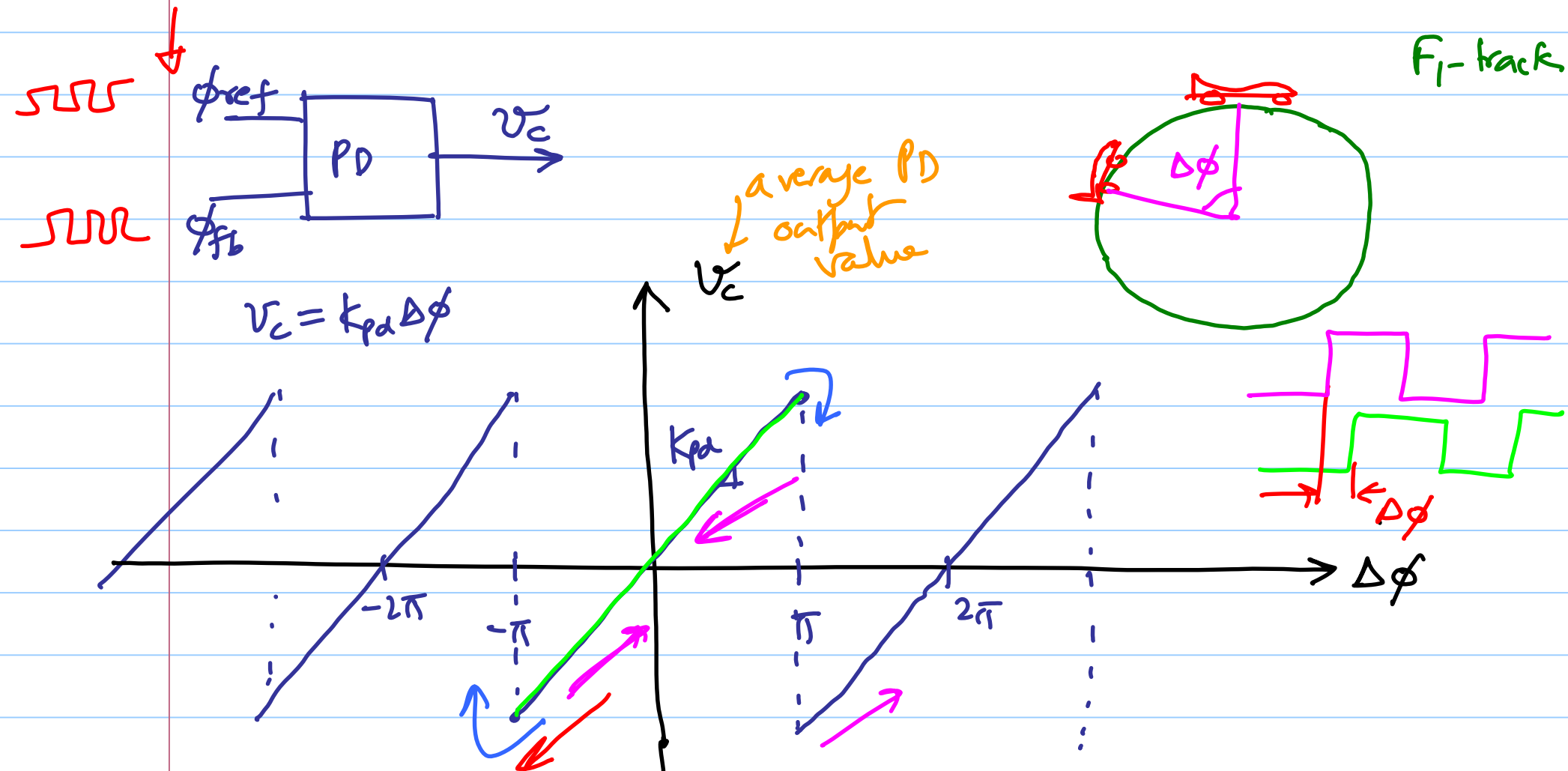
$$v_c \propto \Delta\phi = K_{pd} \Delta\phi$$



if you don't track the "lap difference"
↳ can only find $\{-\pi, \pi\}$ phase difference

phase difference is inherently
modulo 2π

$-\pi < \Delta\phi < \pi$: linear characteristics

$$-\pi < \frac{N_{ref} - f_0}{K_{vo} \cdot K_D} < \pi$$

$\Rightarrow$

$$-\pi K_D K_{vo} < N_{ref} - f_0 < \pi \cdot K_D \cdot K_{vo}$$

$$\Rightarrow \boxed{|N_{ref} - f_0| < \pi K_D \cdot K_{vo}} \text{ with a finite } \Delta\phi$$

for a wide range of output frequency

$K_D \cdot K_{vo}$ should be large
 $\hookrightarrow$ forward path gain

very large frequency range $\Rightarrow$ large gain

Any problems due to this?
"Later"

* If the reference frequency is lowered, such that $\Delta\phi < -\pi$, the PLL will not remain locked


If this frequency range is outside $\pi K_p K_{vco}$ value, the PLL will not lock.

Also if $f_{ref} \neq \frac{f_{vco}}{N} \Rightarrow \Delta\phi$ will be time varying


$\Rightarrow v_c$ will be time

$\Rightarrow$ the output will not be a fixed ^{Varying} frequency.

XOR ID:

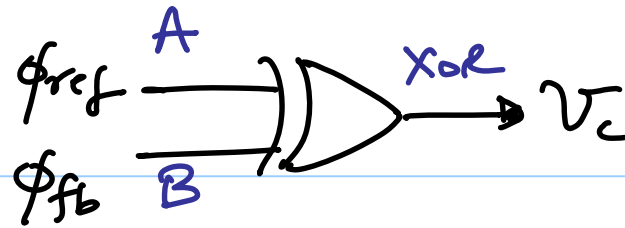

Level sensitive

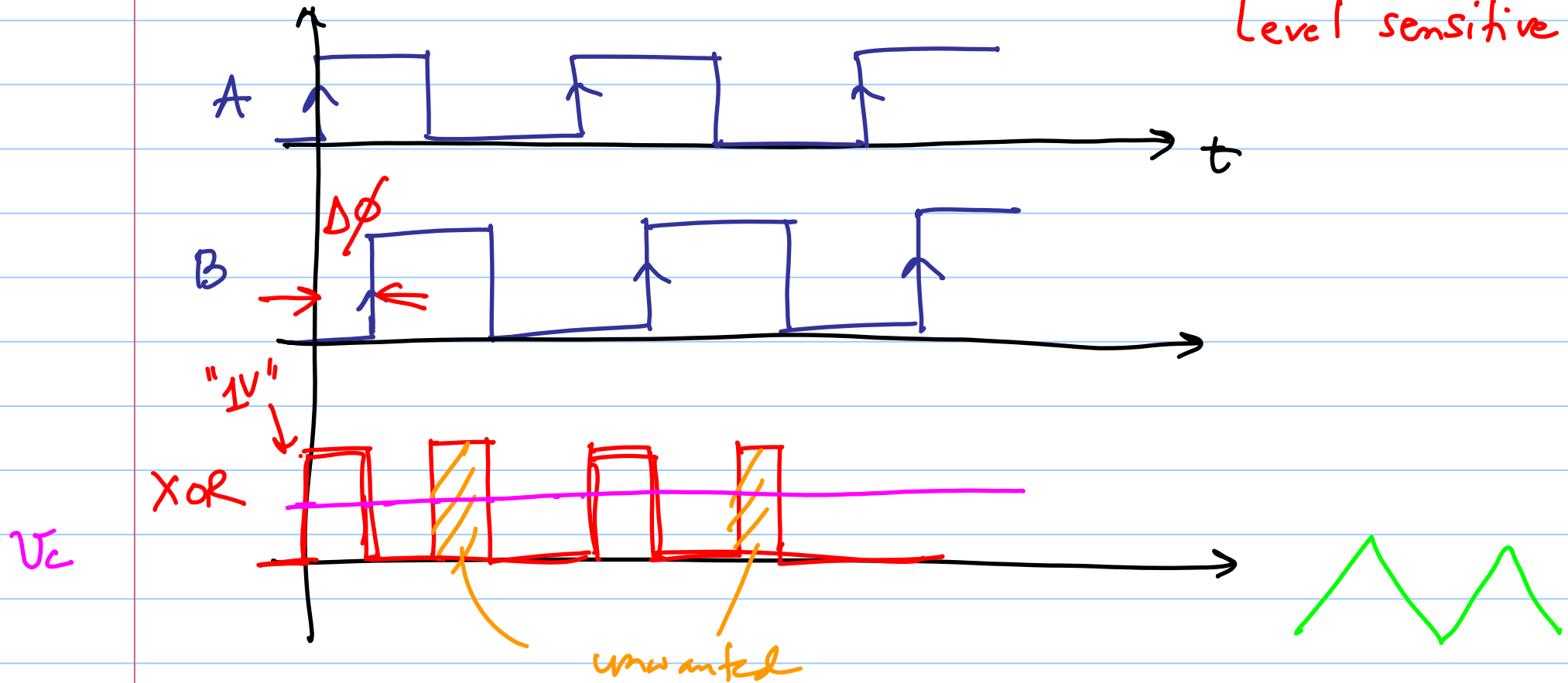


XOR is duty cycle sensitive

↳ sensitive to logic levels, not edges.

We want a PD output

$\left\{ \begin{array}{l} +ve \text{ when } A \text{ rises earlier than } B \\ -ve \text{ when } A \text{ rises later than } B \end{array} \right.$


Rising edge of $A \Rightarrow Q_A = 1$

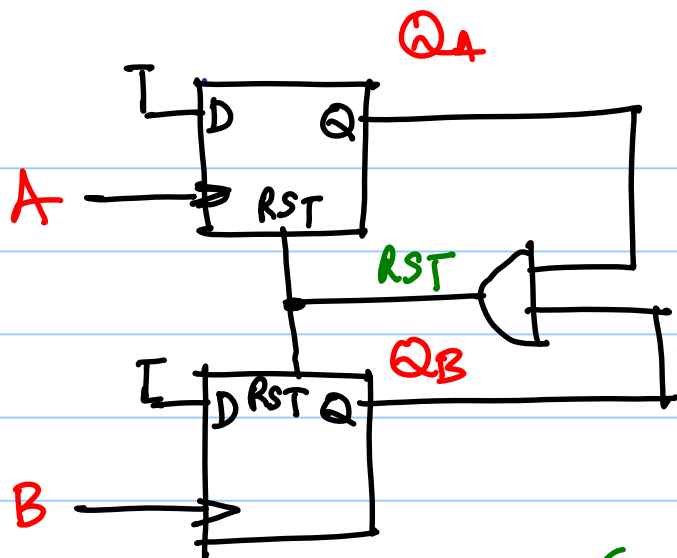


A is leading B

Let $V_c = \underbrace{Q_A - Q_B}_{\text{Analog difference}}$

A is lagging B

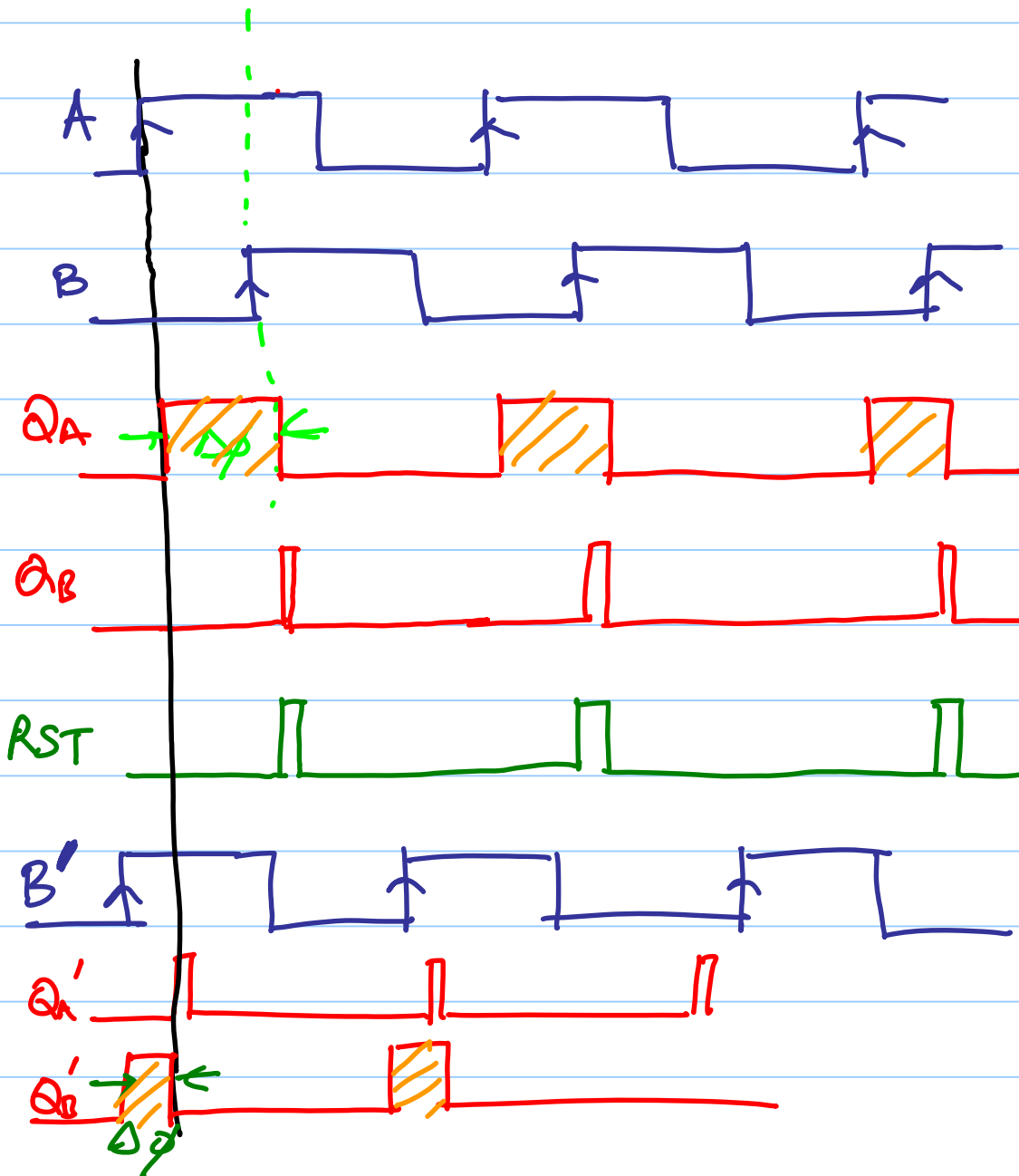


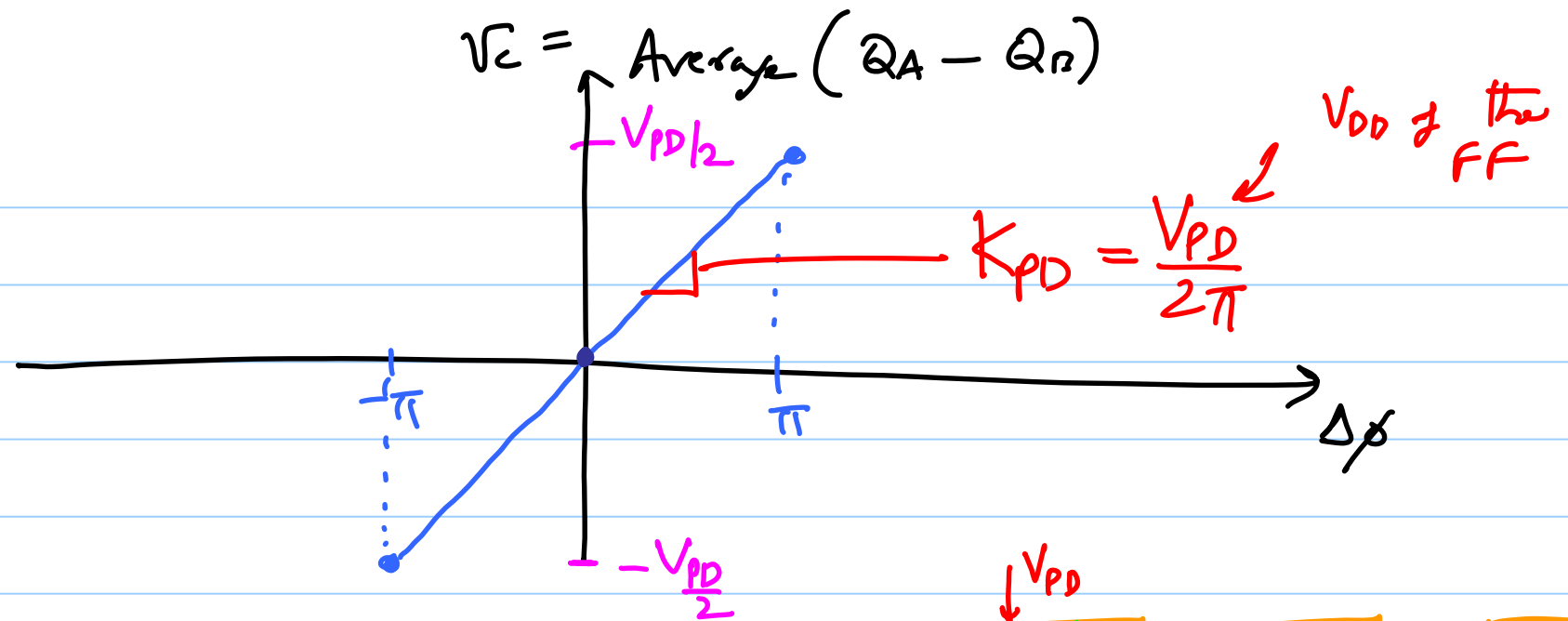

① $\Delta\phi = 0 \Rightarrow 0$

② $\Delta\phi = \pi \longrightarrow$

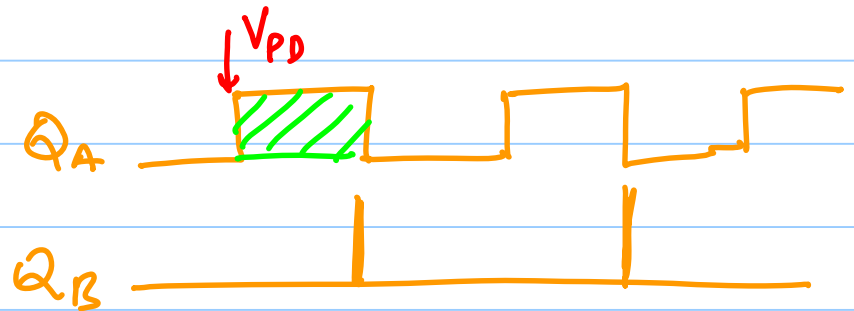$\text{avg}(Q_A - Q_B) = \frac{V_{PD}}{2}$




③ $\Delta\phi = -\pi$

$\text{avg}(Q_A - Q_B) \Rightarrow -\frac{V_{PD}}{2}$


$$\arg(Q_A - Q_B) \quad K_{PD} = \frac{V_{PD}}{2\pi}$$



full $\pm 2\pi$ range

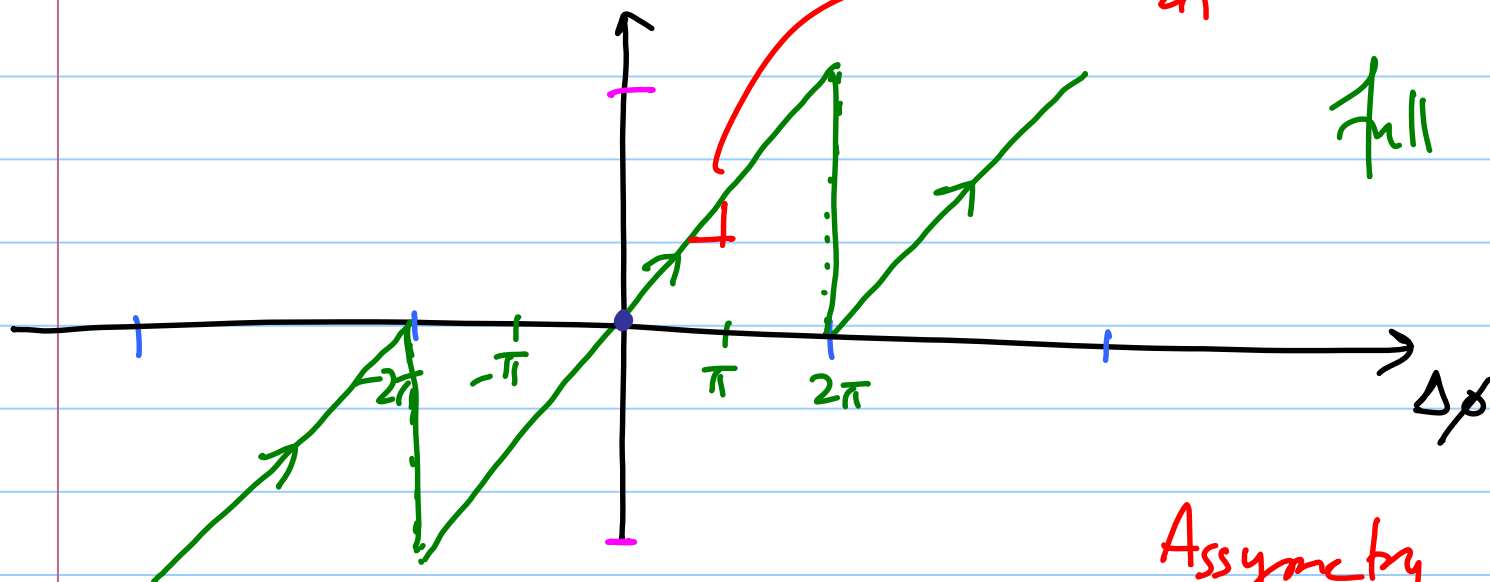

Asymmetry about y-axis
 $\Rightarrow$ hysteresis

Let's say B is slowing its frequency

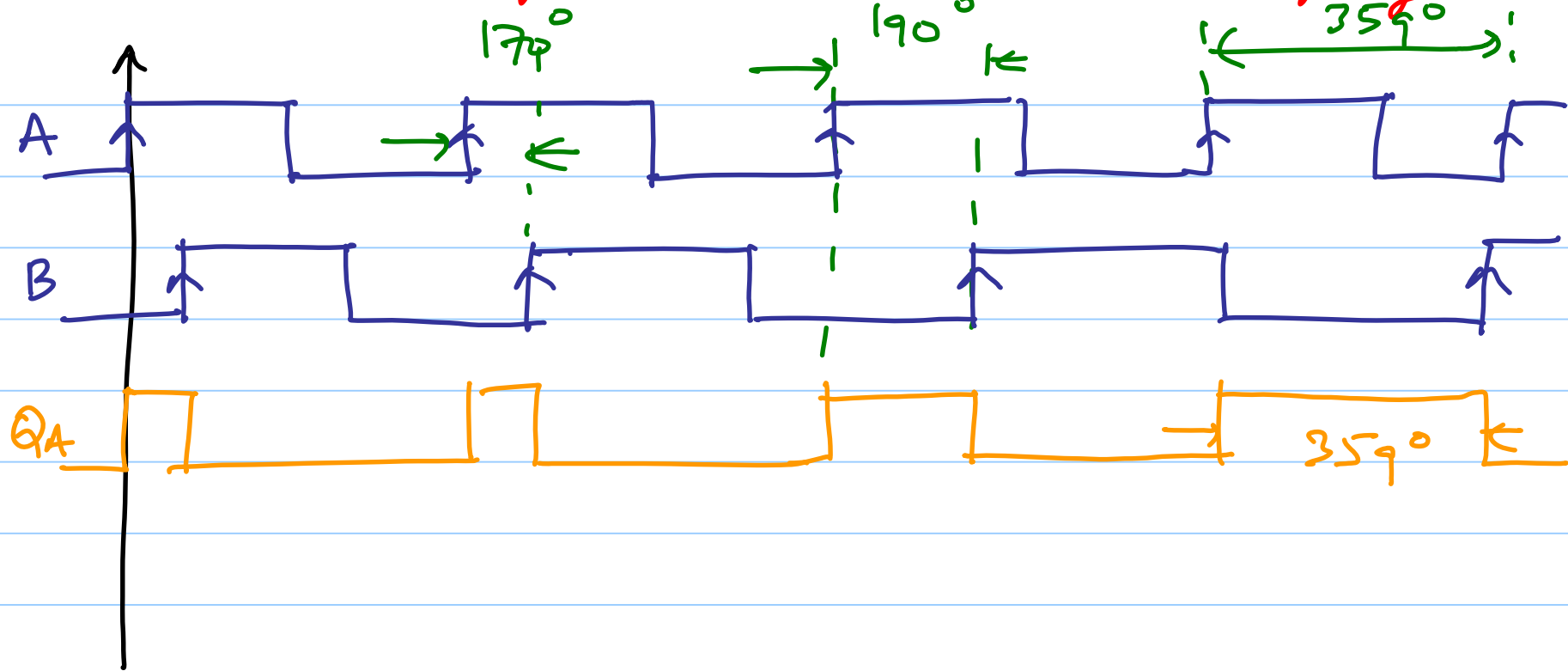

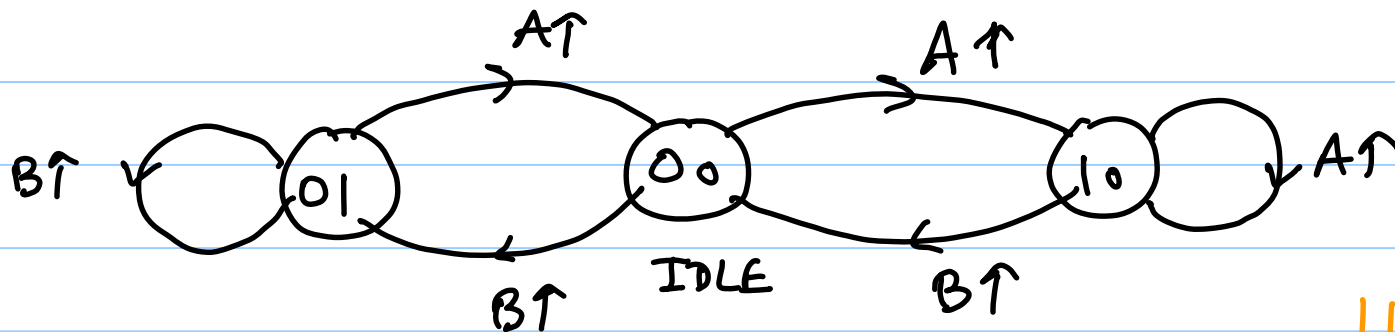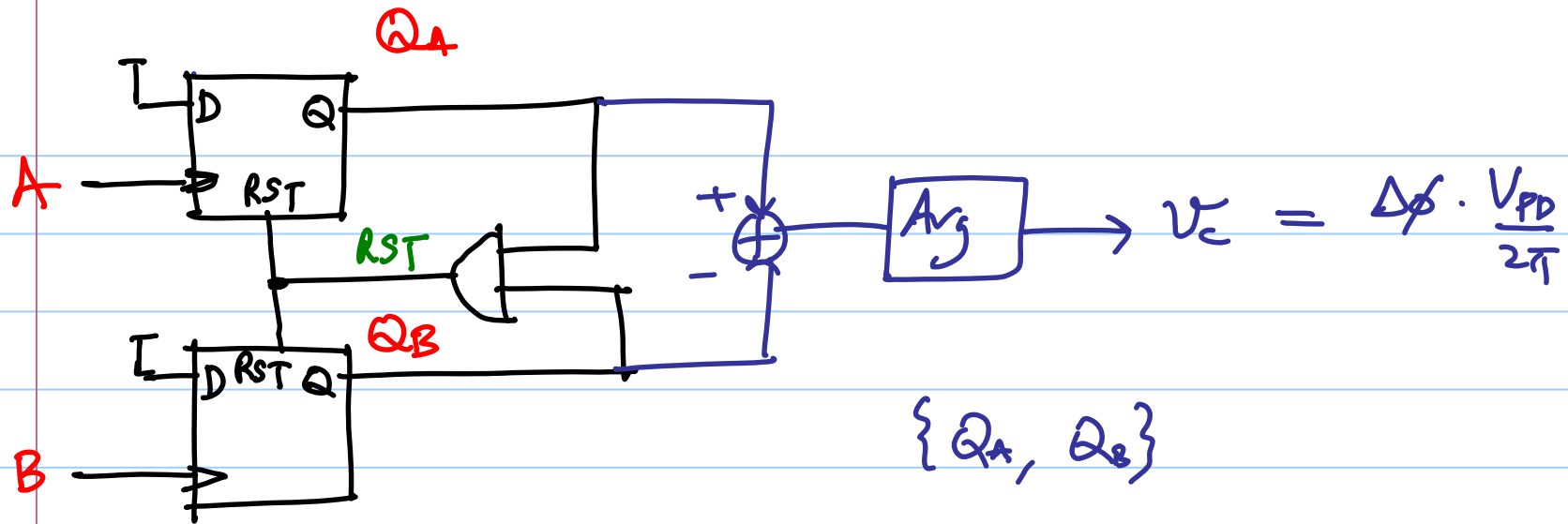

3-state Phase Frequency detector

11 is not a valid state