


ECE 518- Lecture 4.

Note Title

1/22/2015

Phase-frequency Detector

$\{Q_A, Q_B\}$

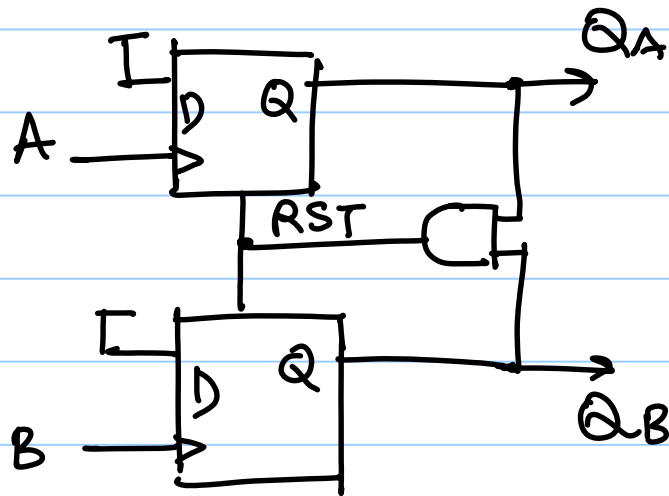



A

B

$$V_c = \text{avg}(Q_A - Q_B) > 0$$

invalid
state
X

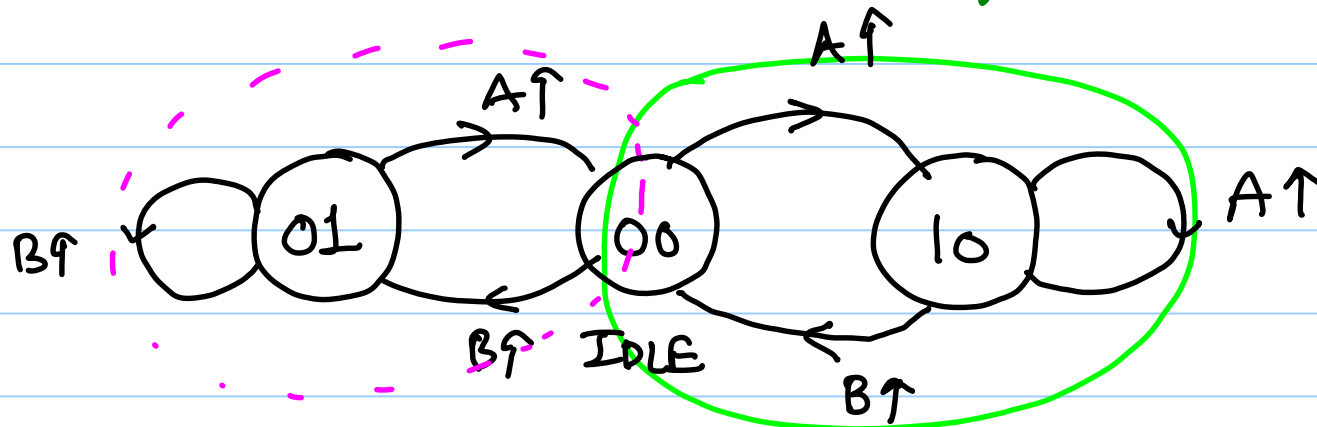



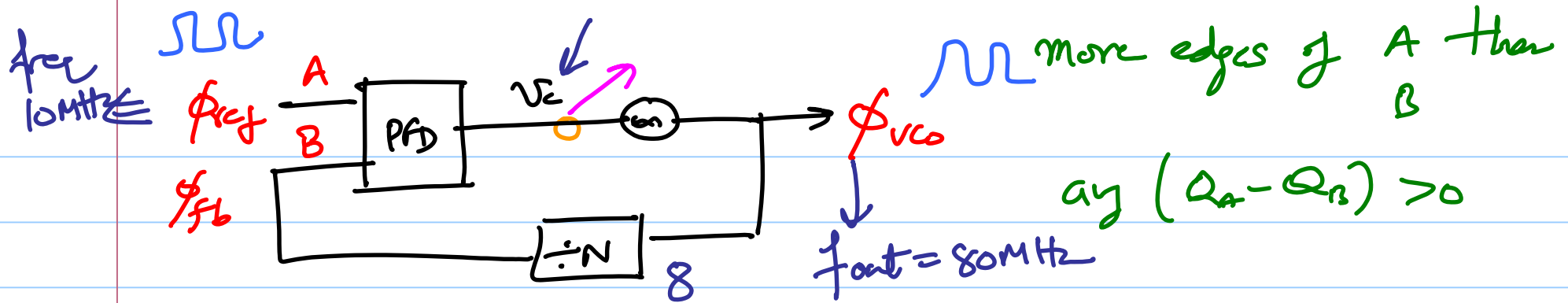


* This PFD also gives frequency detection


↳ better for PLL as the PLL will start at a different frequency

↳ PFD ensures that the PLL moves in the right direction

"Locking" $\Rightarrow$

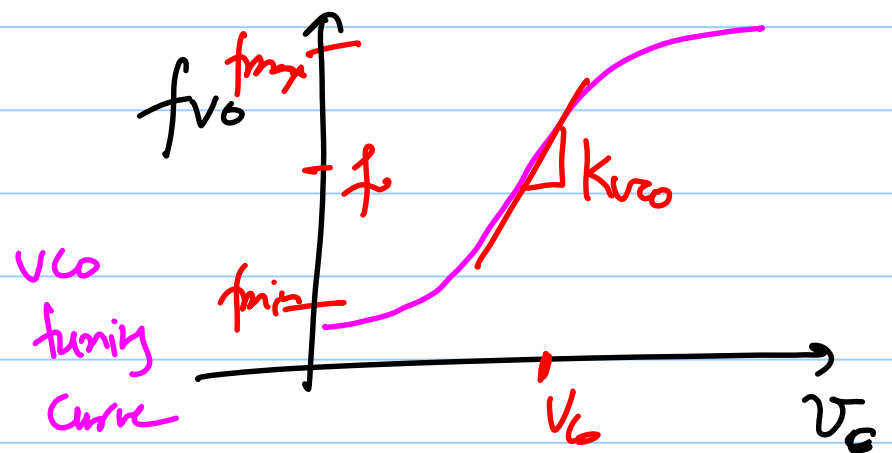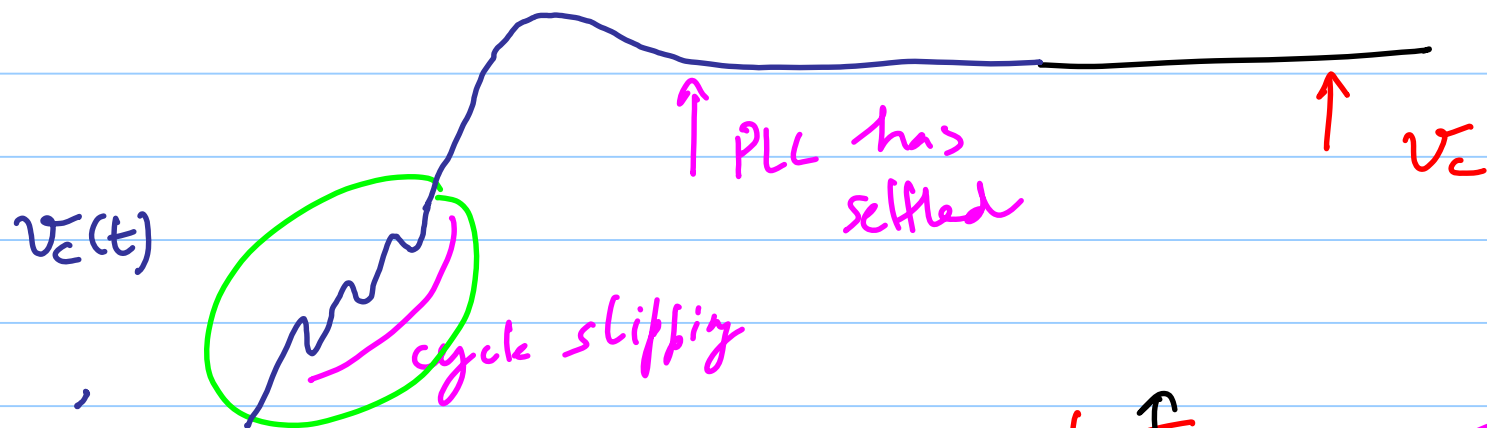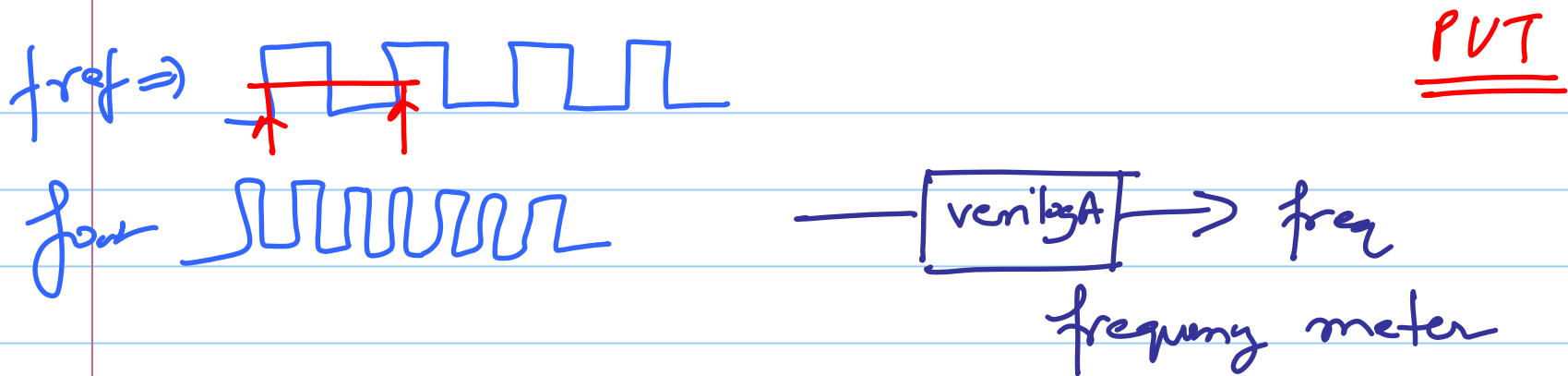

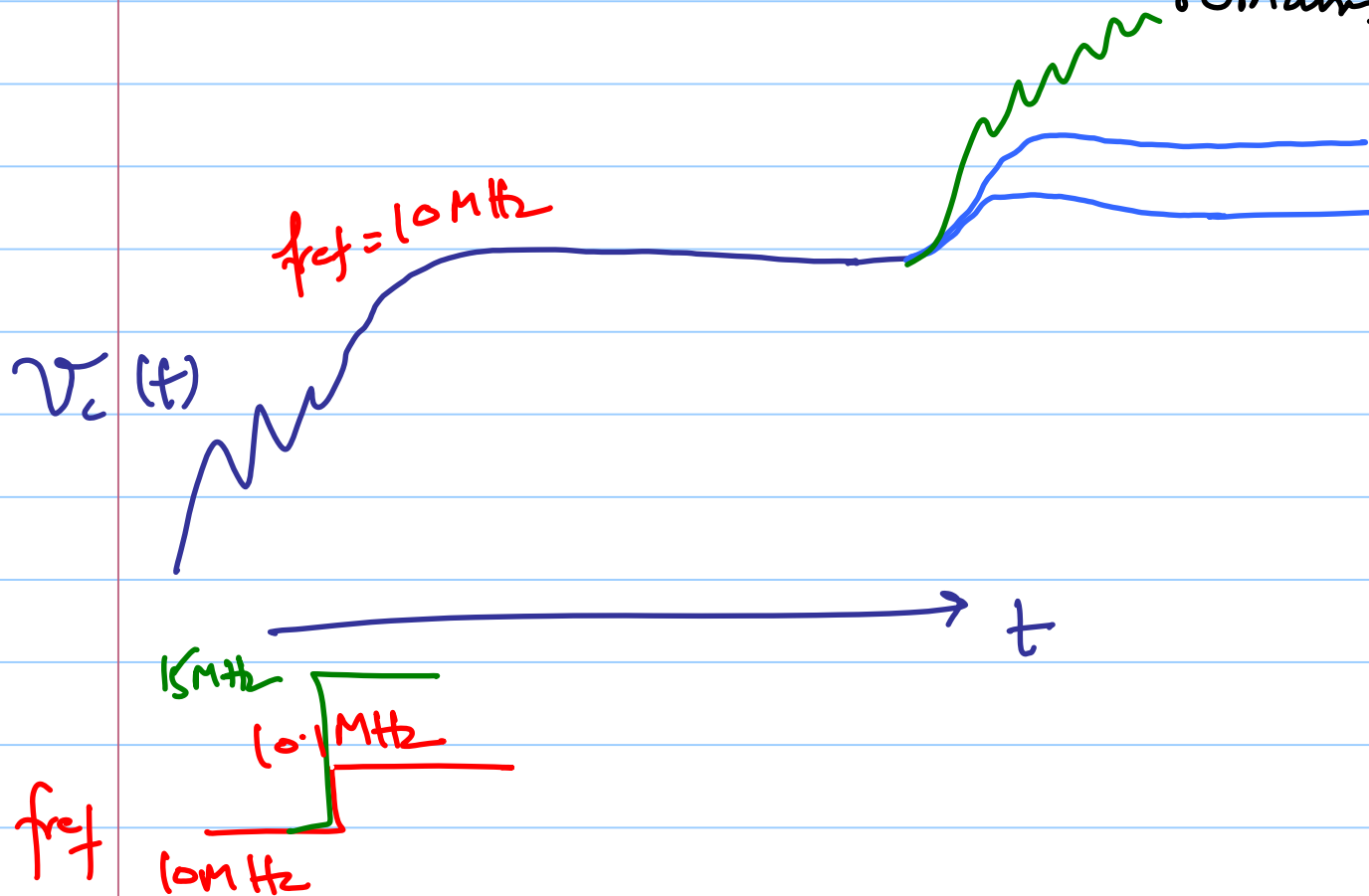Lock-range $\Rightarrow$ for what frequency range the PLL remains locked




"Capture" $\Rightarrow$ apply some frequency and see if the PLL can lock.

$$V_c = \beta \Delta\phi$$







$\downarrow$ frequency of this error ??

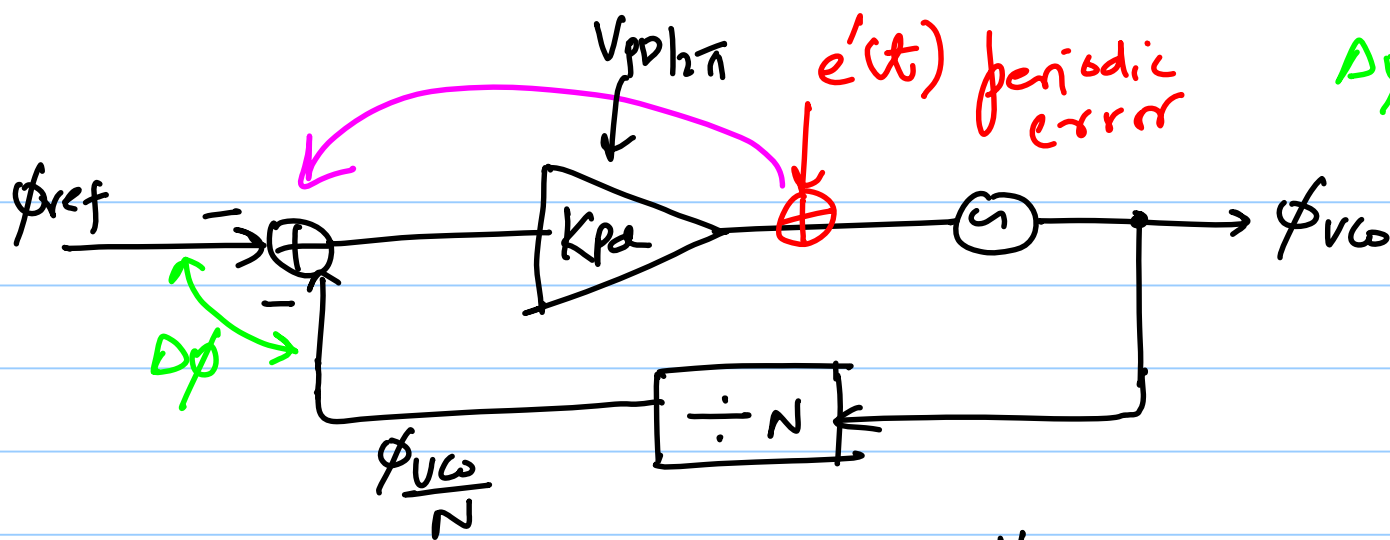


$$\Delta\phi = \frac{f_{VCO} - f_0}{K_{pd} K_{VCO}}$$

$\Delta\phi \gg 0$

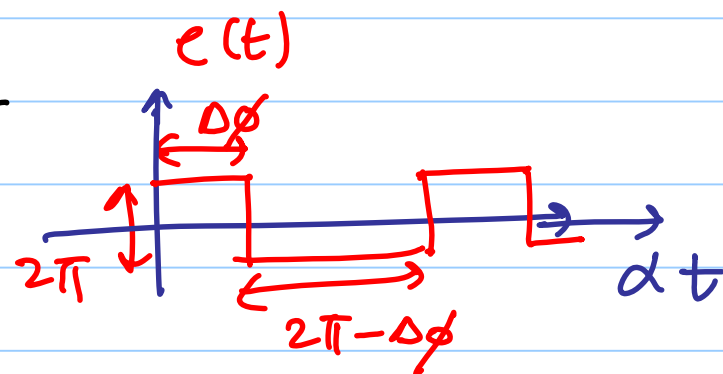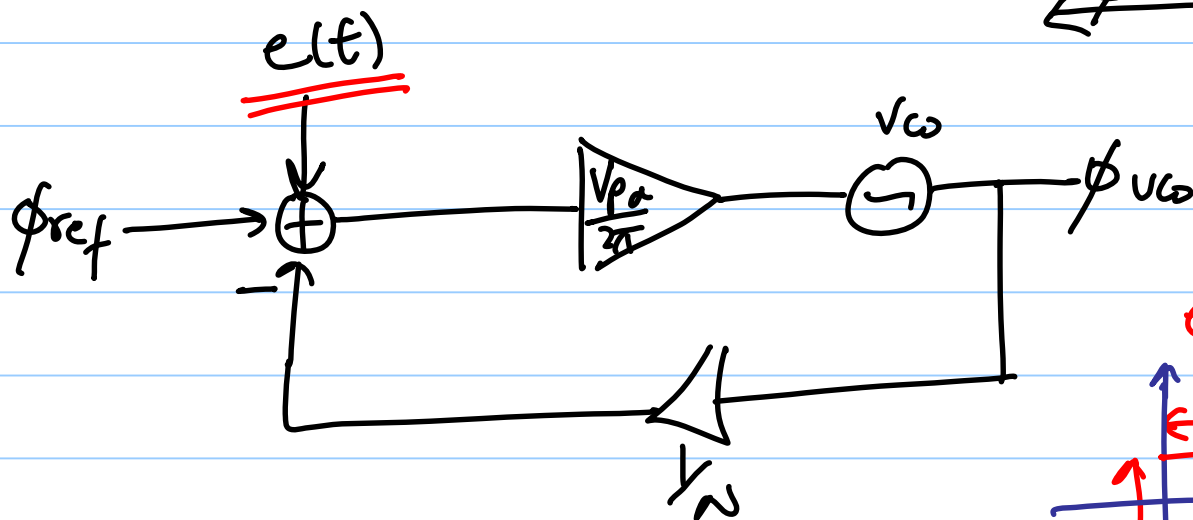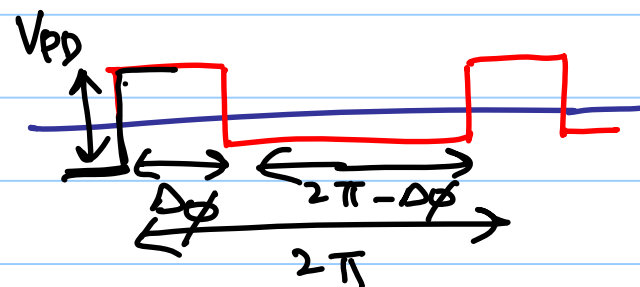

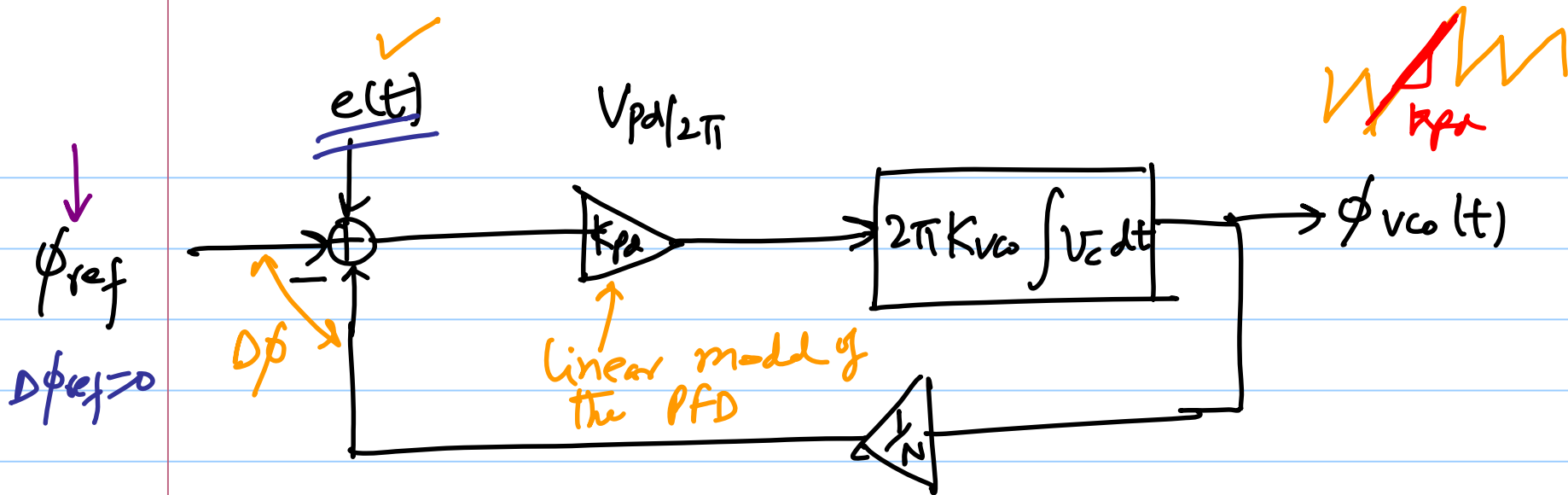

Laplace Model: 

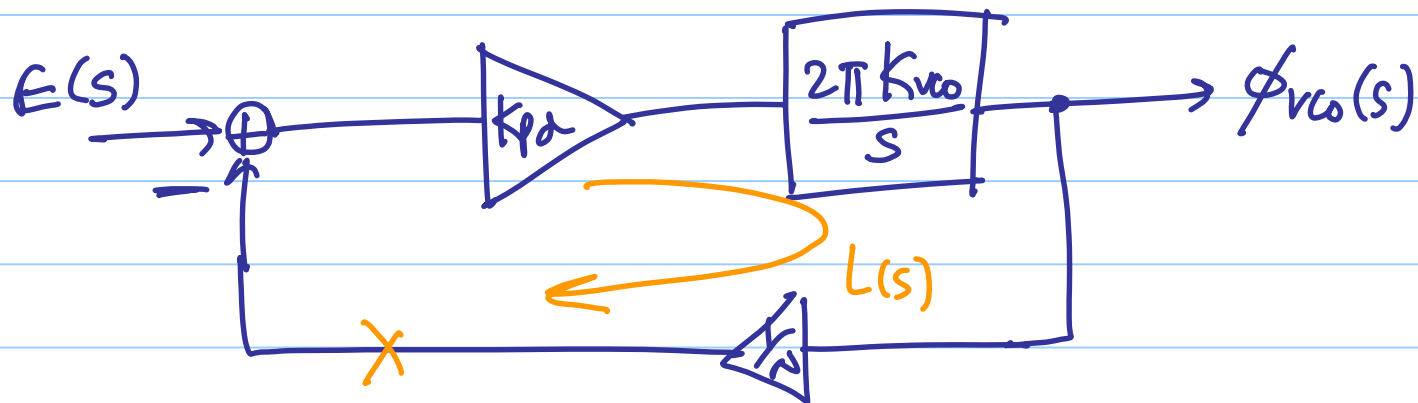

$$(E(s) - \frac{\phi_{vco}(s)}{N}) K_{pd} \times \frac{2\pi K_{vco}}{s} = \phi_{vco}(s)$$


$$\text{loop gain } L(s) = \frac{2\pi K_{pd} K_{vco}}{N \cdot s}$$

$$\frac{\phi_{VCO}(s)}{E(s)} = \frac{N}{1 + \frac{s \cdot N}{2\pi K_{VCO} \cdot K_{PD}}}$$

if the loop gain
 $|L| \gg 1$,
 closed-loop
 gain = $\frac{1}{1/N}$
 $= N$

gain
 $(1 + \frac{s}{\omega_{3dB}})$

low-pass filter
 $\Rightarrow$ 1st-order

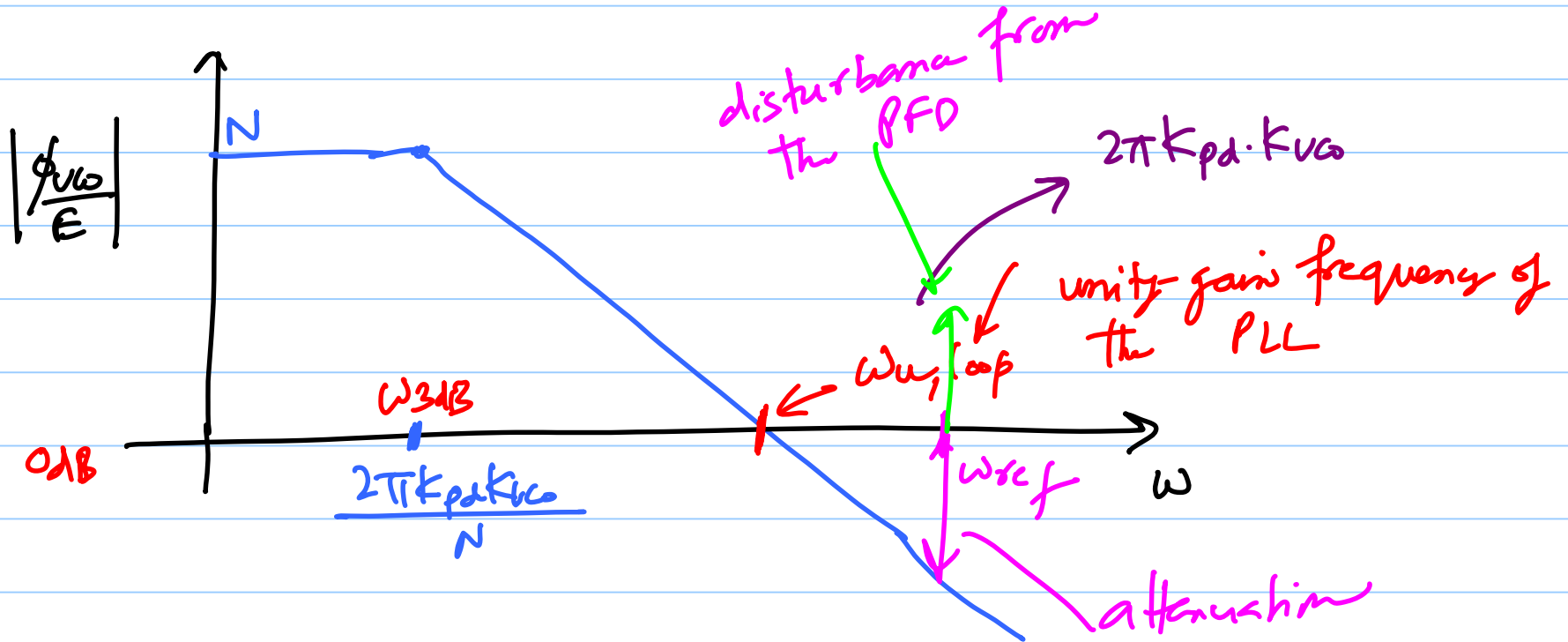

we want frequency content of the periodic disturbance
to be attenuated

$$\Rightarrow \omega_{ref} \gg \omega_{u,loop}$$

$$\omega_{ref} \gg 2\pi K_{po} \cdot K_{vco}$$

to reduce disturbances due to the
periodic nature of the
PFD.

Constraint 1:

$$|N f_{ref} - f_0| < 2\pi K_{pd} K_{vco} \longrightarrow \textcircled{1}$$

Constraint 2:

$$\cancel{\omega_{ref}} \gg \cancel{2\pi} K_{pd} \cdot K_{vco}$$

$$f_{ref} \gg K_{pd} K_{vco} \longrightarrow \textcircled{2}$$

$$|N f_{ref} - f_0| < 2\pi K_{pd} \cdot K_{vco} \ll 2\pi \cdot f_{ref}$$

$$\underline{\underline{\implies}} \quad |f_{out} - f_0| \ll 2\pi f_{ref}$$

$\Rightarrow$ range is much less than f_{ref} , but we want the
o/p frequency to be much larger than f_{ref}

↳ very limited tuning range $\approx \frac{f_{ref}}{f_{\infty}}$

* We want $\Delta\phi$ to be zero to have a useful design

↳ we need an "integrator" in the loop to support the non-zero VCO input, $V_c(t)$, with $\Delta\phi=0$.

* DC phase error of zero is what we desire

