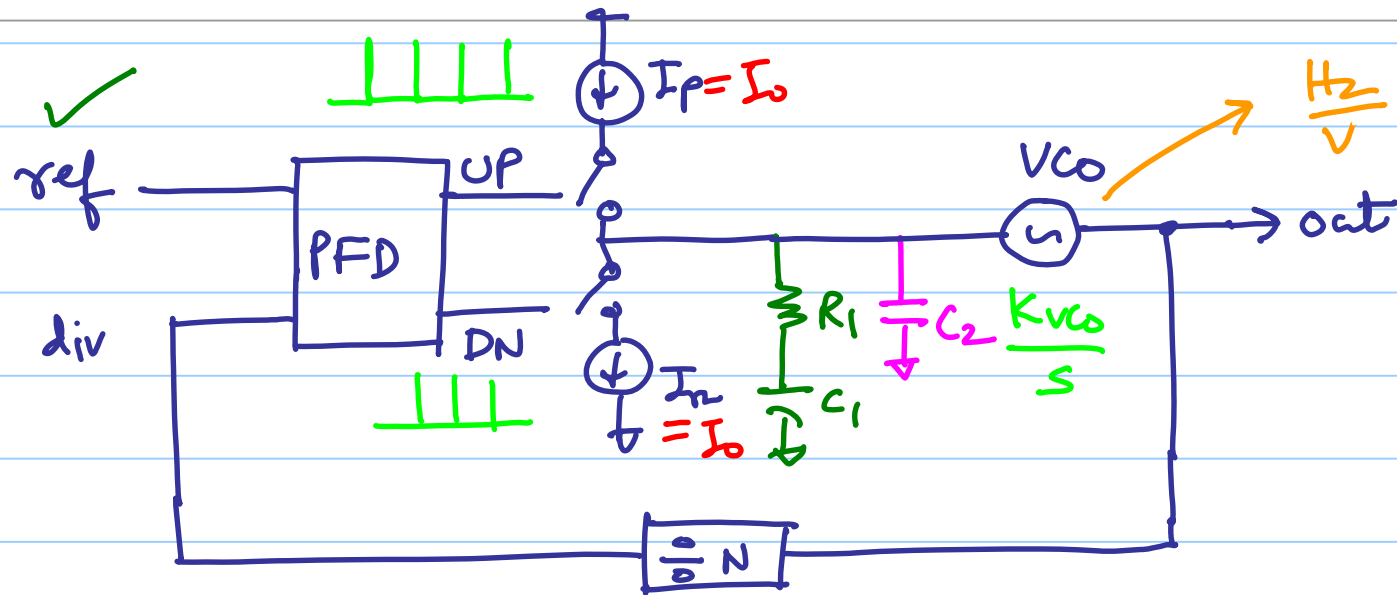


ECE 518- Lecture 8

Note Title

2/10/2015



Type-II
~~2nd order~~
 3rd order



$$K_{PD, I} = \frac{I_o}{2\pi C_1}$$

$$K_{PD} = \frac{I_o R_1}{2\pi}$$

$$\omega_{u, \text{loop}} \approx \frac{2\pi K_{VCO} \cdot K_{PD}}{N} = \frac{K_{VCO} \cdot I_o R}{N}$$


Single-pole approximation

Type-II PLL loop dynamics

$$K_{pd,I} = \frac{I_0}{2\pi C}$$

$$K_{pd} = \frac{I_0 R}{2\pi}$$

2nd-order:

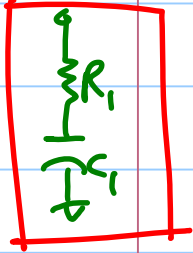

$$L(s) = \frac{2\pi K_{pd,I} \cdot K_{vco}}{s^2} \left(1 + \frac{s K_{pd}}{K_{pd,I}} \right)$$

open-loop response

$$H_{CL}(s) = \frac{\phi_{out}(s)}{\phi_{ref}(s)} = \frac{G(s)}{1 + \underbrace{G(s)H(s)}_{L(s)}} = \frac{1}{H(s)} \cdot \frac{L(s)}{1 + L(s)} = \frac{N \cdot L(s)}{1 + L(s)}$$

$\uparrow$
 $1/N$

$$= \frac{N \cdot \left(1 + \frac{s K_{pd}}{K_{pd,I}} \right) \xrightarrow{\text{zero}}}{s^2 \frac{N}{2\pi \cdot K_{pd,I} K_{vco}} + \frac{s K_{pd}}{K_{pd,I}} + 1}$$

$\underbrace{\hspace{10em}}_{\text{2 poles}}$

$$= \frac{N \left(1 + \frac{2\zeta}{\omega_n} s \right)}{\frac{s^2}{\omega_n^2} + \frac{2\zeta s}{\omega_n} + 1}$$

Standard form

$$H_{CL}(s) = \frac{N(1 + \frac{2\zeta}{\omega_n}s)}{\frac{s^2}{\omega_n^2} + \frac{2\zeta s}{\omega_n} + 1} \Leftrightarrow \frac{N(2\zeta\omega_n s + \omega_n^2)}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

Standard form

Natural frequency, $\omega_n = \sqrt{\frac{2\pi K_{PD,I} K_{VCO}}{N}} = \sqrt{\frac{I_0 K_{VCO}}{C \cdot N}}$

Damping factor, $\zeta = \frac{K_{PD}}{2} \sqrt{\frac{2\pi K_{VCO}}{N K_{PD,I}}} = \frac{R}{2} \sqrt{\frac{I_0 K_{VCO} C}{N}}$

$K_{VCO} \rightarrow \frac{Hz}{V}$
 2π discrepancy

Quality factor $Q \triangleq \frac{1}{2\zeta} = \frac{1}{R} \sqrt{\frac{NC}{I_0 \cdot K_{VCO}}}$

ω_z

zero;

$$\omega_z = \frac{k_{p, I}}{k_{pD}} = \frac{1}{R_C}$$

"LHP zero"

closed
loop

poles:

$$= \frac{s^2}{\omega_n^2} + \frac{2\zeta s}{\omega_n} + 1$$

roots of $D(s) = s^2 + 2\zeta\omega_n s + \omega_n^2 = 0$

$$\omega_{p1/2} = \omega_n \left[-\zeta \pm \sqrt{\zeta^2 - 1} \right]$$

$$\omega_z = \frac{\omega_n}{2\zeta}$$

* for well separated poles $\zeta \gg 1$

$$D(s) \stackrel{0}{=} \left(\frac{s}{\omega_{p1}} + 1 \right) \left(\frac{s}{\omega_{p2}} + 1 \right) = \frac{s^2}{\omega_{p1}\omega_{p2}} + s \left(\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}} \right) + 1$$

$$\omega_n = \sqrt{\omega_{p1}\omega_{p2}} \leftarrow \text{geometric mean}$$

$$\frac{2\zeta}{\omega_n} = \frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}}$$

← harmonic mean

→

$$\omega_{p1} = \frac{\omega_n}{2\zeta}$$


$$\omega_{p2} = 2\zeta \omega_n$$

$$\omega_z = \frac{\omega_n}{2\zeta}$$

$$A_m \Rightarrow \frac{x_1 + x_2}{2}$$

$$\zeta_m = \sqrt{x_1 x_2}$$


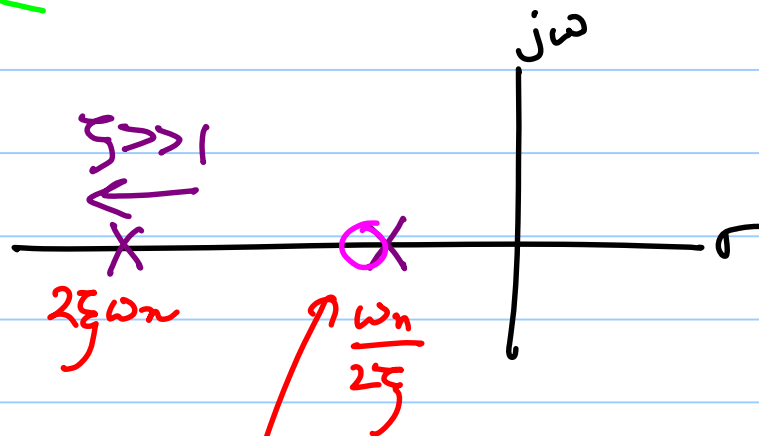
$$\frac{1}{4m} = \frac{1}{x_1} + \frac{1}{x_2}$$



pole-zero doublet

one-pole approximation
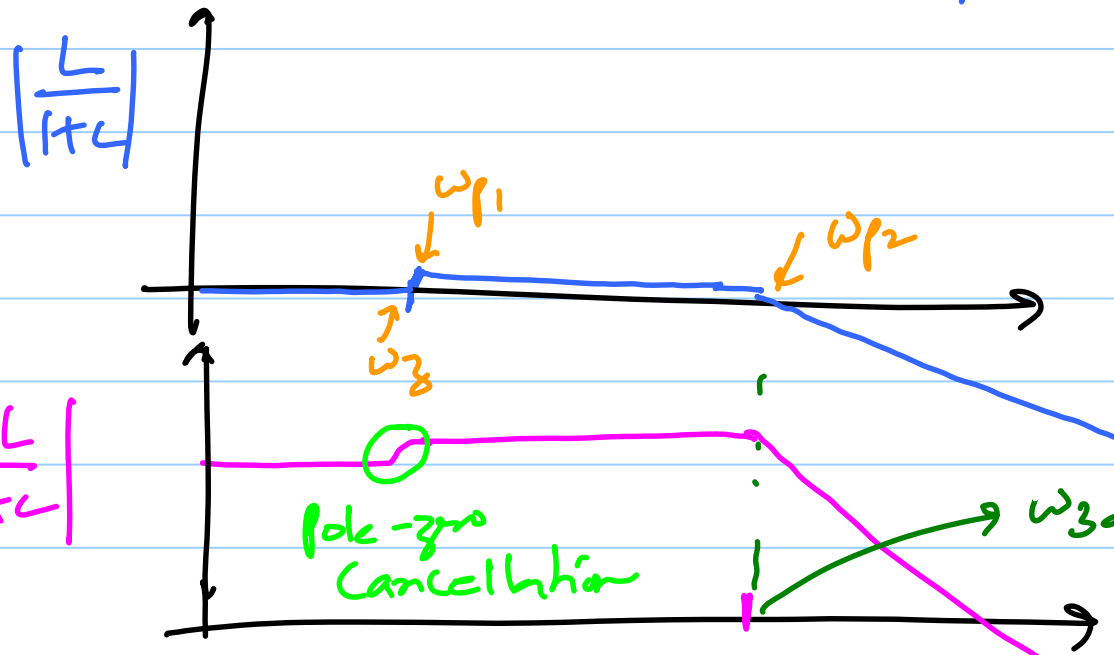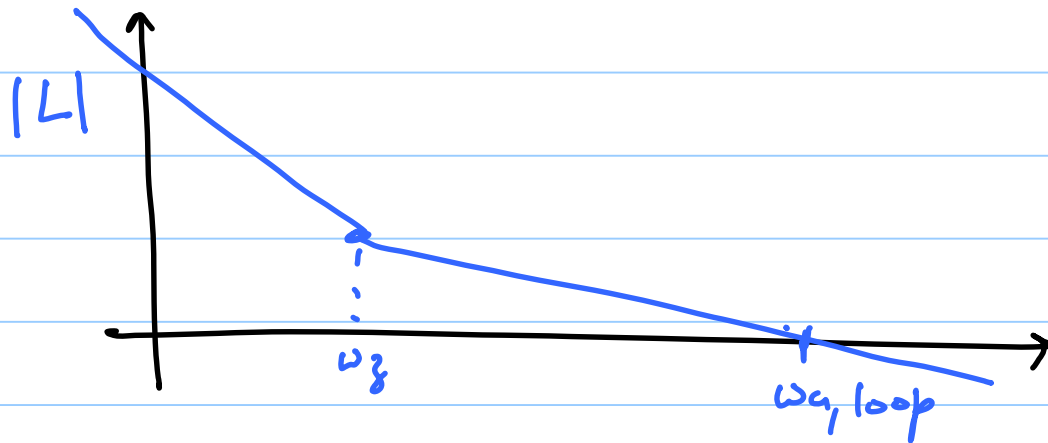
$$\omega_{3dB} = 2\xi\omega_n \leftarrow \text{closed-loop BW}$$



$$\frac{\phi_{out}}{\phi_{ref}}(s) = \left| \frac{NL}{1+L} \right|$$

Phase Margin of a Type-II PLL

a) 2nd-order PLL

$$L(s) = \frac{K_{VCO} \cdot I_o R_1}{2\pi} \frac{(1 + sR_1C_1)}{s^2}$$

$$\Rightarrow \omega_{u,loop} \approx \frac{K_{VCO} \cdot I_o R_1}{N}$$

$$\phi = -180^\circ + \underbrace{\tan^{-1}\left(\frac{\omega}{\omega_z}\right)}_{\text{LHP zero}}$$

$$\begin{aligned} \text{Phase Margin} &= \tan^{-1}\left(\frac{\omega_{u,loop}}{\omega_z}\right) \leftarrow \text{phase added by the LHP zero at } \omega = \omega_{u,loop} \\ &= \tan^{-1}\left(\frac{K_{VCO} I_o R_1^2 C_1}{N}\right) \end{aligned}$$

