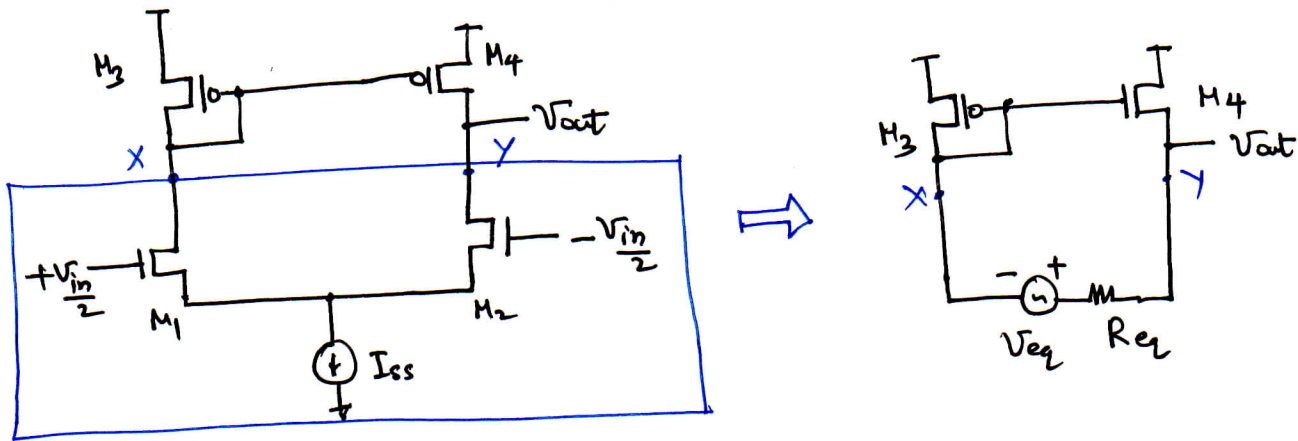


Current Mirror Load Diff-Amp


①

* Exact Analysis for small-signal gain:


• Substitute the input diff-pair by its Thevenin Equivalent.



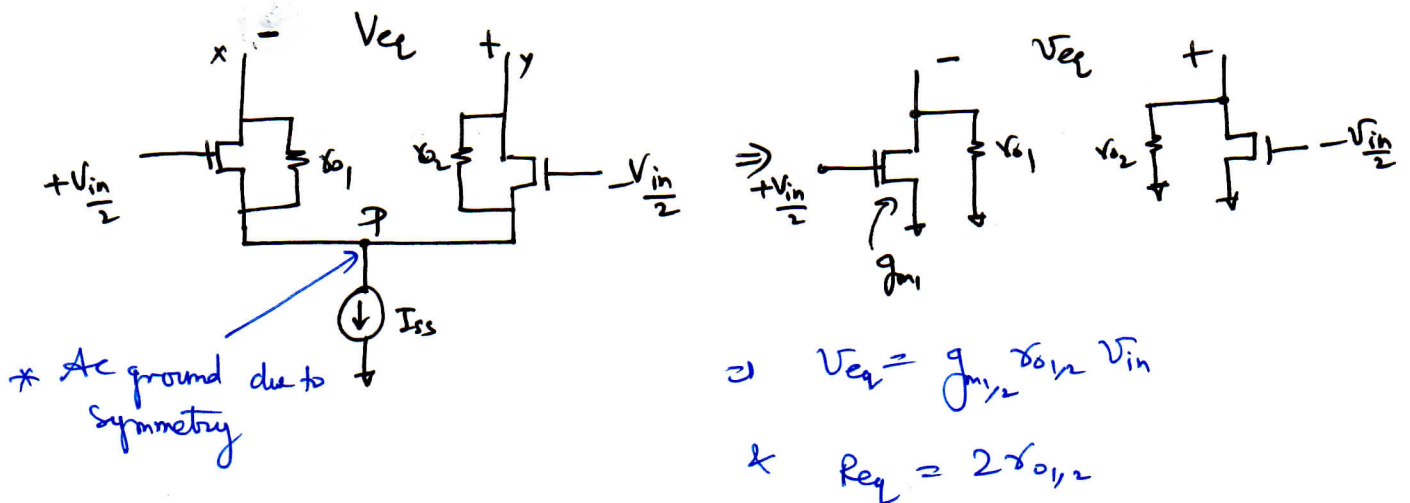→ Calculation of the Thevenin equivalent circuit.



(2)

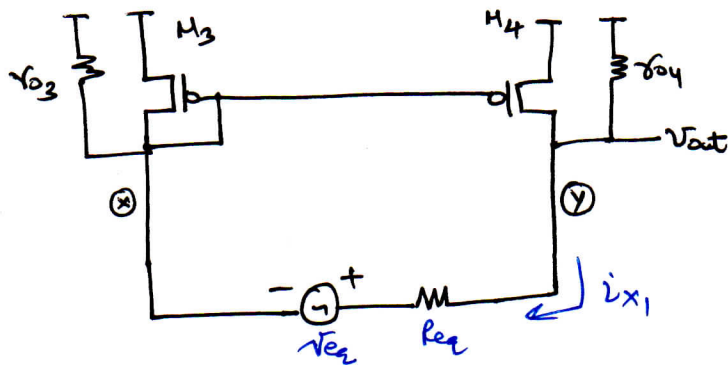

* Assuming ideal tail current source.

↳ Current through R_{eq} is

$$i_{x1} = \frac{V_{out} - V_{eq}}{R_{eq} + \frac{1}{g_{m3}} \parallel r_{o3}}$$

$$\Rightarrow i_{x1} = \frac{V_{out} - g_{m1,2} r_{o1,2} V_{in}}{2r_{o1,2} + \frac{1}{g_{m3}} \parallel r_{o3}}$$

* The fraction of this current which flows through $\frac{1}{g_{m3}}$ is mirrored into M_4 with unity gain

⇒ @ node y

$$2 i_x \left(\frac{r_{o3}}{r_{o3} + \frac{1}{g_{m3}}} \right) = - \frac{V_{out}}{r_{o4}}$$


$$\Rightarrow 2 \frac{V_{out} - g_{m1,2} r_{o1,2} V_{in}}{2r_{o1,2} + \frac{1}{g_{m3}} \parallel r_{o3}} \cdot \frac{r_{o3}}{r_{o3} + \frac{1}{g_{m3}}} = - \frac{V_{out}}{r_{o4}}$$

Assuming $2r_{o1,2} \gg \left(\frac{1}{g_{m3,4}} \parallel r_{o3,4} \right)$, we get

$$\frac{V_{out}}{V_{in}} = \frac{g_{m1,2} r_{o3,4} \cdot r_{o1,2}}{r_{o1,2} + r_{o3,4}} = g_{m1,2} (r_{o1,2} \parallel r_{o3,4})$$

$$\approx +g_{mn} (r_{op} \parallel r_{on}).$$

Common Mode Properties:

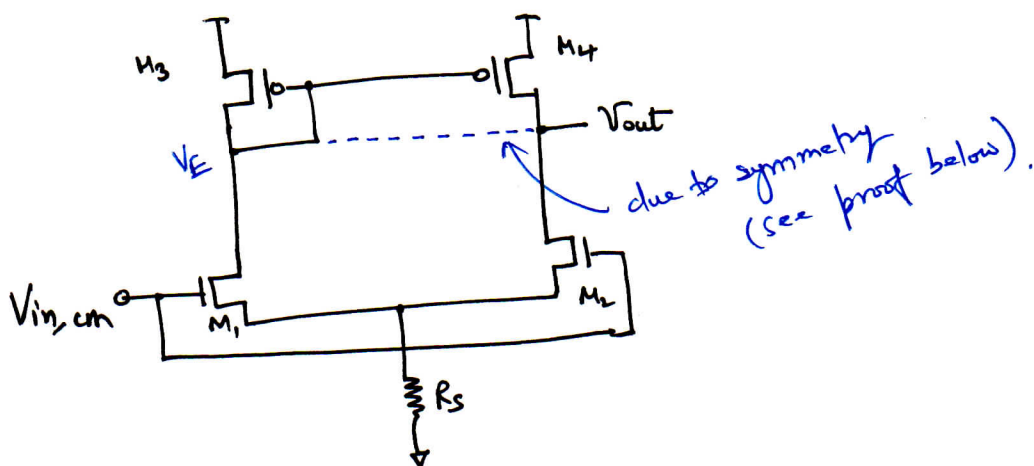

We first require to prove that the circuit is symmetric for CM analysis, i.e. V_{out} tracks V_E .


Proof by Contradiction:

let $V_{out} < V_E$
 $\rightarrow$ then due to channel length modulation, M_1 must carry greater current than M_2 ($\Rightarrow I_{D1} > I_{D2}$)
 $\Rightarrow M_4$ carries greater current than M_3 ($I_{D4} > I_{D3}$)
 $\Rightarrow I_{D2} > \frac{I_{SS}}{2}$
 $\Rightarrow I_{D1} > \frac{I_{SS}}{2} \Rightarrow I_{D3} > \frac{I_{SS}}{2}$
 $\Rightarrow I_{D4} < \frac{I_{SS}}{2} \Rightarrow I_{D2} < \frac{I_{SS}}{2}$ ← contradiction
 $\Rightarrow I_{D1}$ must be equal to I_{D2}
 $\Rightarrow V_{out} = V_E = \underline{V_{DD} - V_{GS3}}$

* However, asymmetries in circuit may result in a large deviation in V_{out} .

$\rightarrow$ circuit is rarely used in open-loop.

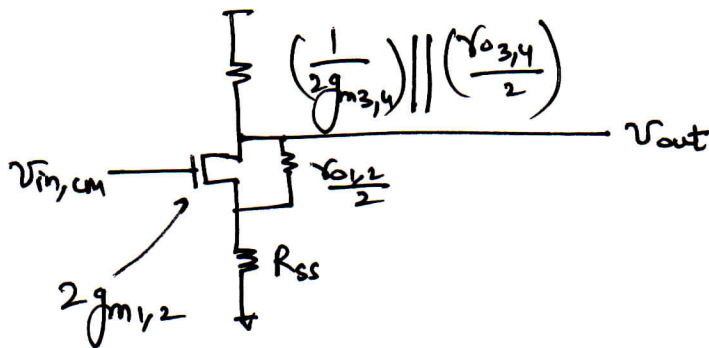⇒ CM Half ~~the~~ Circuit is shown below!



$$\Rightarrow A_{v,cm} = \frac{-\frac{1}{2g_{m3,4}} \parallel \frac{r_{o3,4}}{2}}{\frac{1}{g_{m1,2}} + R_{SS}}$$

$$= \frac{-1}{1 + 2g_{m1,2}R_{SS}} \cdot \frac{g_{m1,2}}{g_{m3,4}}$$

$$\approx -\frac{1}{2g_{m3,4}R_{SS}}$$


$$\Rightarrow CMRR = \left| \frac{A_{v,dm}}{A_{v,cm}} \right| = g_{m1,2}(r_{o1,2} \parallel r_{o3,4}) \cdot 2g_{m3,4} \cdot R_{SS}$$

⇒ Even with perfect symmetry in devices The output signal is corrupted by input CM variations.


↳ This drawback doesn't exist in fully-differential devices.

Diffamp Frequency Response

Differential mode circuit

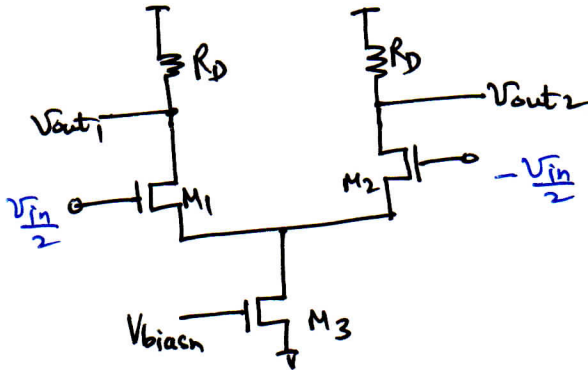

DM Half Circuit

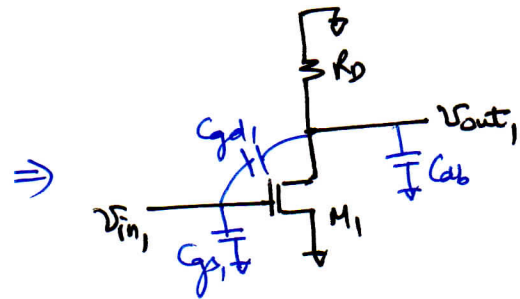

⇒ frequency response is same as the CS amplifier (with $R_s = 0$).

* Both the signal paths get multiplied by the same transfer-function


⇒ poles in $\frac{v_{out}}{v_{in}}$ are same as in each of the signal paths

$$\Rightarrow \frac{v_{out}}{v_{in}}(s) = - \frac{A_{v0} (1 - s/\omega_z)}{(1 + s/\omega_{p1})}$$

$$\omega_{p1} = \frac{1}{(C_{gs1} \parallel R_D) C_L}, \quad \omega_z = + \frac{g_{m1,2}}{C_{db2}}$$

(6)

Common Mode Response!

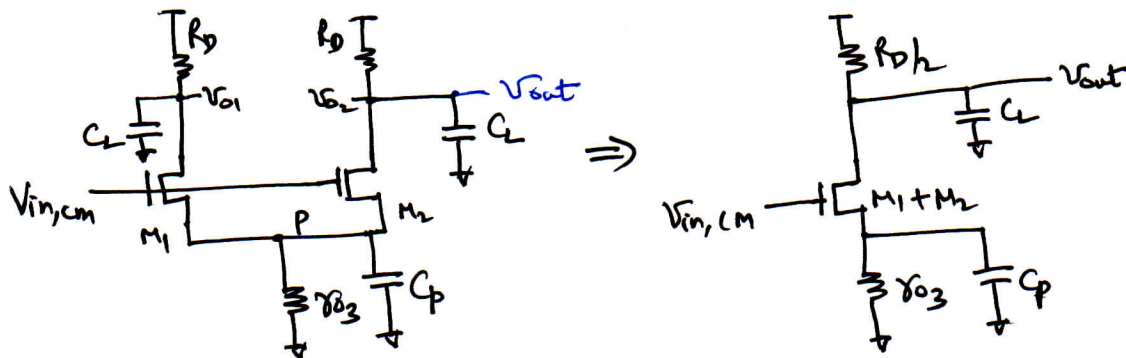


$$\Rightarrow A_{v,cm}(s) = - \frac{\frac{R_D}{2} \parallel \frac{1}{sC_L}}{\frac{1}{g_{m1+2}} + (r_{o3} \parallel \frac{1}{sC_p})}$$

$\Rightarrow$ if the ^{output} pole due to P is at lower frequency than ω_{p1}

$\hookrightarrow$ common mode rejection degrades at high-frequencies.

Current Mirror load Diffamp :


⑦

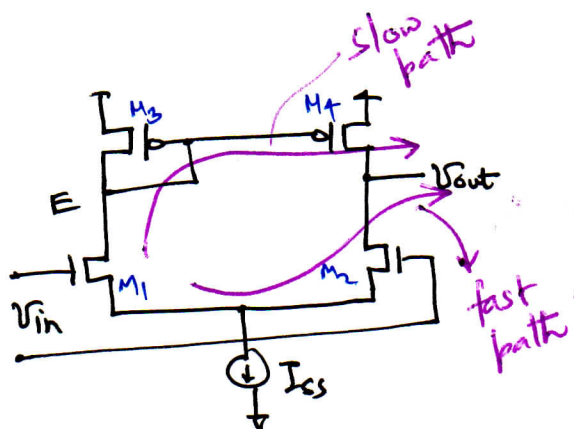

* The topology contains two signal paths to the output with different transfer functions.

* path $M_3-M_4 \rightarrow$ pole at node E $\Rightarrow \omega_{p2} \approx \frac{g_{m3}}{C_E} \leftarrow$ "Mirror pole"

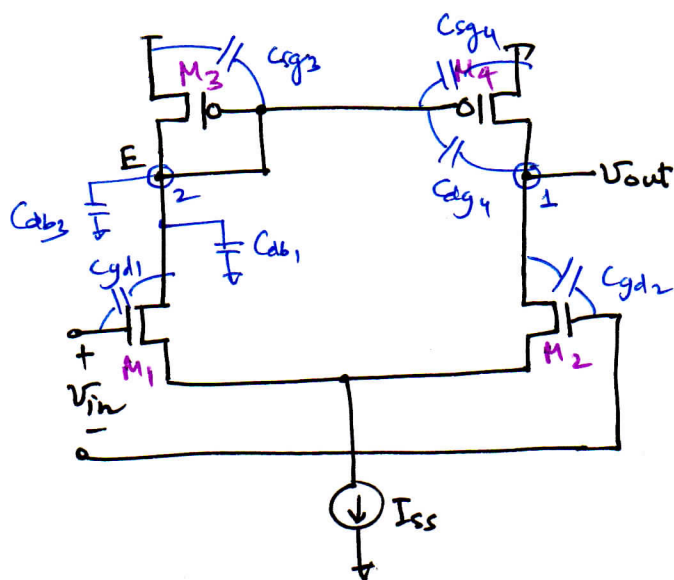Hence $C_E = C_{gs3} + C_{gs4} + C_{db3} + C_{db4} +$
+ Miller contributions from C_{gd1} & C_{gd4}



$\Rightarrow$ Both signal paths contain a pole at the output node ①
 $\hookrightarrow$ the slow path contains extra pole at ②

$\Rightarrow$ Two zeros due to both the paths. RHP or LHP ??


⑧

* In order to estimate frequency response of this Diff-amp


↳ 1) Replace V_{in} , M_1 & M_2 by a Thevenin Equivalent

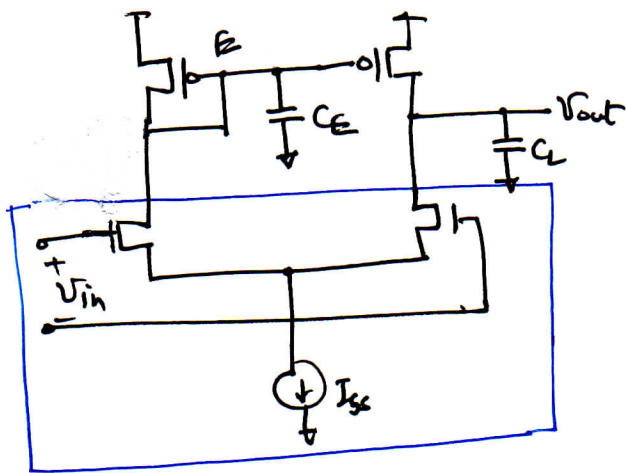2) All other caps than C_E are ignored.

↳ The RHP zero due to $C_{g1,2}$ is not captured in this model.



⇒

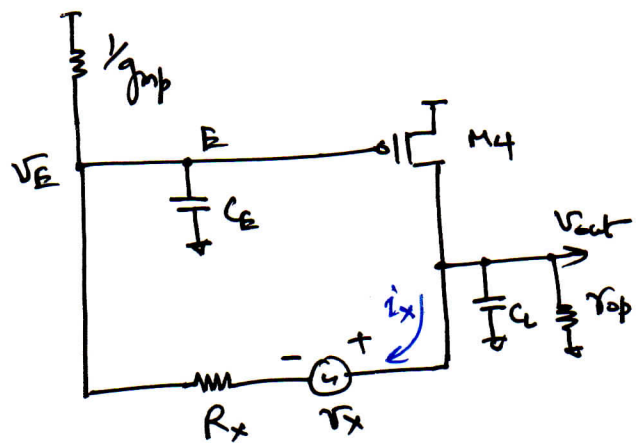

Assume $1/g_{mp} \ll r_{op}$.

Here, $V_x = g_{m1} r_{on} V_{in}$
 $R_x = 2r_{on}$

$$\Rightarrow V_E = (V_{out} - V_x) \frac{\frac{1}{sC_E + g_{mp}}}{\frac{1}{sC_E + g_{mp}} + R_x}$$

$$\Rightarrow i_{d4} = g_{m4} V_E$$

Using $-g_{m4} V_E - i_x = V_{out} [sC_L + 1/r_{op}]$, we get.

(9)

$$\Rightarrow \frac{V_{out}(s)}{V_{in}} = \frac{g_{mn} r_{on} (2g_{mp} + sC_E)}{2r_{op} r_{on} C_E C_L s^2 + [(2r_{on} + r_{op}) C_E + r_{op} (1 + 2g_{mp} r_{on}) C_L] s + 2g_{mp} (r_{on} + r_{op})}$$

* Since the mirror pole is typically quite higher in magnitude than the output pole (i.e. $|\omega_{p2}| \gg |\omega_{p1}|$), we get

$$\omega_{p1} \approx \frac{1}{\text{Coeff}^n \text{ of } s} = \frac{2g_{mp} (r_{on} + r_{op})}{(2r_{on} + r_{op}) C_E + r_{op} (1 + 2g_{mp} r_{on}) C_L}$$

neglecting the first term and assuming $2g_{mp} r_{on} \gg 1$,

$$\omega_{p1} \approx \frac{1}{(r_{on} \parallel r_{op}) C_L}$$

$$\omega_{p2} \approx \frac{g_{mp}}{C_E}$$

$$\omega_{z2} = + \frac{g_{mn}}{C_{gdn}} \quad (\text{RHP zero})$$

$$\omega_{z1} = - \frac{2g_{mp}}{C_E} \quad (\text{LHP zero}) \quad \text{interesting!}$$

* The origin of the LHP can be seen as follows:

The transfer functions of the slow and fast paths are given by

$$A_{\text{slow}}(s) = \frac{A_0}{(1+s/\omega_{p1})(1+s/\omega_{p2})}$$

$$A_{\text{fast}}(s) = \frac{A_0}{(1+s/\omega_{p1})}$$

$$\Rightarrow \frac{V_{\text{out}}}{V_{\text{in}}}(s) = A_{\text{slow}}(s) + A_{\text{fast}}(s)$$


$$= \frac{A_0}{(1+s/\omega_{p1})} \left[\frac{1}{(1+s/\omega_{p2})} + 1 \right]$$

$$= \frac{A_0 (2+s/\omega_{p2})}{(1+s/\omega_{p1})(1+s/\omega_{p2})}$$

$\Rightarrow$ The resulting system exhibits an ^{LHP.} zero at $2\omega_{p2}$

$$\omega_{z1} = -2\omega_{p2} = -\frac{2g_{\text{mb}}}{C_E}$$

Zero Discussion !

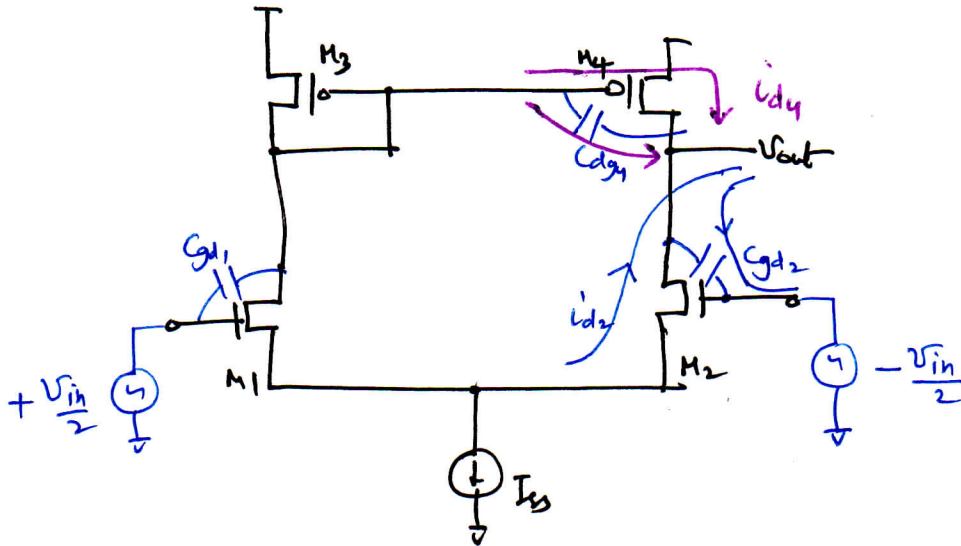

fast path: Currents adding in opposite polarity at the output
 $\Rightarrow$ RHP zero

slow path: Currents adding in the same polarity at the output
 $\Rightarrow$ LHP zero!

