
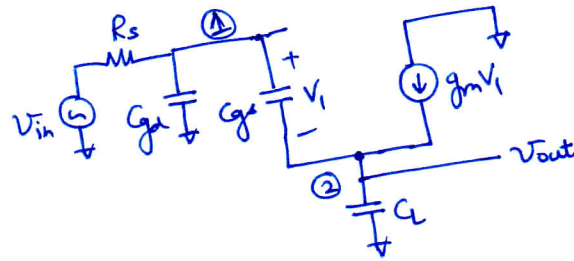


Source follower frequency response

①

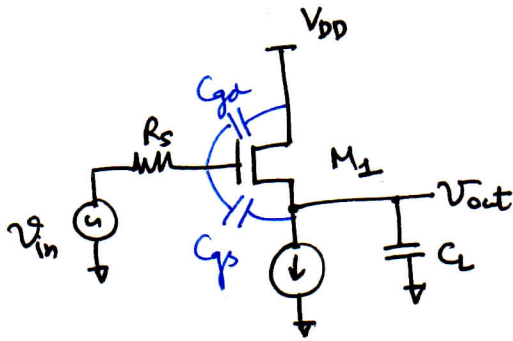

* strong interaction between nodes ① & ② through C_{gs} .
 ↳ can't associate a pole with each node

node ②

$$V_1 C_{gs} s + g_m V_1 = V_{out} C_L s$$

$$\Rightarrow V_1 = \frac{C_L s}{g_m + C_{gs} s} V_{out}$$

* KVL beginning from V_{in}

$$V_{in} = R_s [V_1 C_{gs} s + (V_1 + V_{out}) C_{gd} s] + V_1 + V_{out}$$

Substitute V_1

$$\Rightarrow \frac{V_{out}(s)}{V_{in}} = \frac{(g_m + C_{gs} s)}{R_s [C_{gs} C_L + C_{gs} C_{gd} + C_{gd} C_L] s^2 + [g_m R_s C_{gd} + C_L + C_{gs}] s + g_m}$$

⇒ LHP zero

$$\omega_z = - \frac{g_m}{C_{gs}}$$

⇒ signal conducted by C_{gs} , adds to the signal carried by the main transistor with the same polarity.


Assuming $|\omega_{p1}| \ll |\omega_{p2}|$

Dominant pole is at

$$\omega_{p1} \approx \frac{g_m}{g_m R_s C_{gd} + C_L + C_{gs}}$$

$$= \frac{1}{R_s C_{gd} + \frac{C_L + C_{gs}}{g_m}} = \frac{g_m}{C_L + C_{gs}} \text{ iff } R_s = 0.$$

Input impedance of SF:

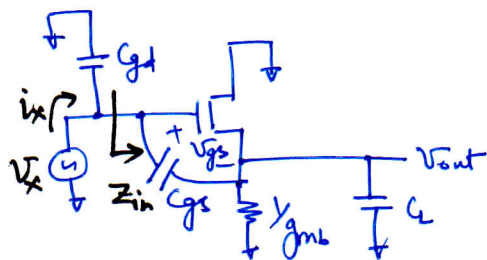

* C_{gd} shunts the input

$$v_{gs} = \frac{i_x}{sC_{gs}} \Rightarrow i_d = g_m v_{gs} = \frac{g_m i_x}{sC_{gs}}$$

$$\Rightarrow v_x = \frac{i_x}{sC_{gs}} + \left(i_x + \frac{g_m i_x}{sC_{gs}} \right) \left(\frac{1}{g_{mb}} \parallel \frac{1}{sC_L} \right)$$

$$\Rightarrow Z_{in1} = \frac{1}{sC_{gs}} + \left(1 + \frac{g_m}{sC_{gs}} \right) \frac{1}{g_{mb} + sC_L}$$

@ low-frequencies

$$g_{mb} \gg |sC_L|$$

$$\Rightarrow Z_{in1} \approx \frac{1}{sC_{gs}} \left(1 + \frac{g_m}{g_{mb}} \right) + \frac{1}{g_{mb}} = \frac{1}{sC_{gs} \left(1 + \frac{g_m}{g_{mb}} \right)} + \frac{1}{g_{mb}}$$

$\Rightarrow$ Input cap is a fraction of $C_{gs} + C_{gd}$.

At higher frequencies

$$g_{mb} \ll |sC_L|$$

$$\Rightarrow Z_{in_1} = \frac{1}{sC_{gs}} + \frac{1}{sC_L} + \frac{g_m}{C_{gs}C_L s^2}$$


$\Rightarrow$ for same $s = j\omega$

$$Z_{in_1} = \underbrace{\frac{1}{j\omega} \left[\frac{1}{C_{gs}} + \frac{1}{C_L} \right]}_{\text{Capacitance}} - \underbrace{\frac{g_m}{C_{gs}C_L \omega^2}}_{\text{negative resistance}}$$

$$Re(Z_{in_1}) = R_{in_1} = \frac{-g_m}{C_{gs}C_L \omega^2} \leftarrow \text{useful in oscillators.}$$

Output impedance:

neglecting g_{mb} & C_{gd}

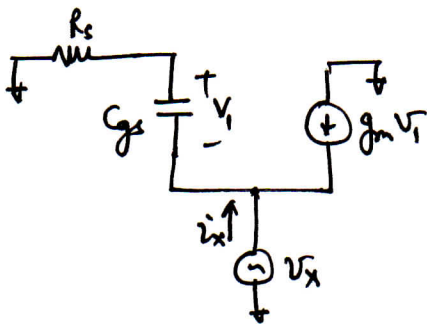

$$V_i C_{gs} s + g_m V_i = -i_x \rightarrow (1)$$

$$V_i C_{gs} s R_s + V_i = -V_x \rightarrow (2)$$


$$\frac{(2)}{(1)} \Rightarrow$$

$$Z_{out} = \frac{V_x}{i_x} = \frac{R_s C_{gs} s + 1}{g_m + s C_{gs}}$$

④

@ low frequencies $\Rightarrow Z_{out} \approx 1/g_m \rightarrow$ Expected from a SF

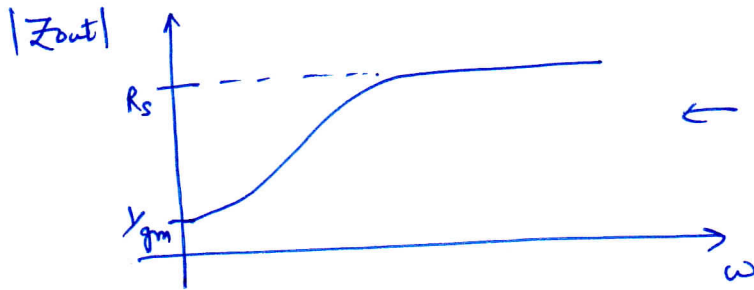@ very high frequencies $\Rightarrow Z_{out} \approx R_s$ ($\because C_{gs}$ shorts gate & source)




← realistic scenario as in a buffer
 $1/g_m \ll R_s$

* Since the $Z_{out} \uparrow$ with frequency

$\hookrightarrow$ should contain an inductive component!
($j\omega L$)

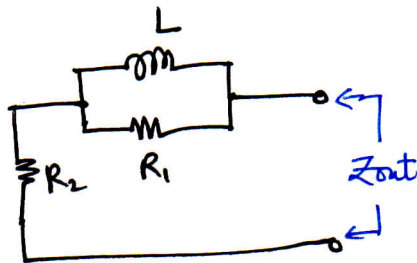Equivalent impedance can be derived to be !



$$R_2 = 1/g_m$$

$$R_1 = R_s - 1/g_m$$


$$L = \frac{C_{gs}}{g_m} (R_s - 1/g_m)$$

$$\therefore L = \frac{C_{gs}}{g_m} (R_s - 1/g_m)$$

$\Rightarrow$ If the SF is driven by a large R_s

$\Rightarrow$ then it exhibits substantial inductive behavior

$\hookrightarrow$ manifests as ringing

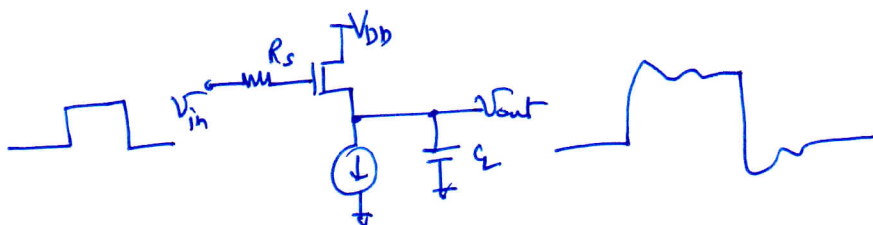


* Useful as gain peaking loads!

Common Gate Frequency Response

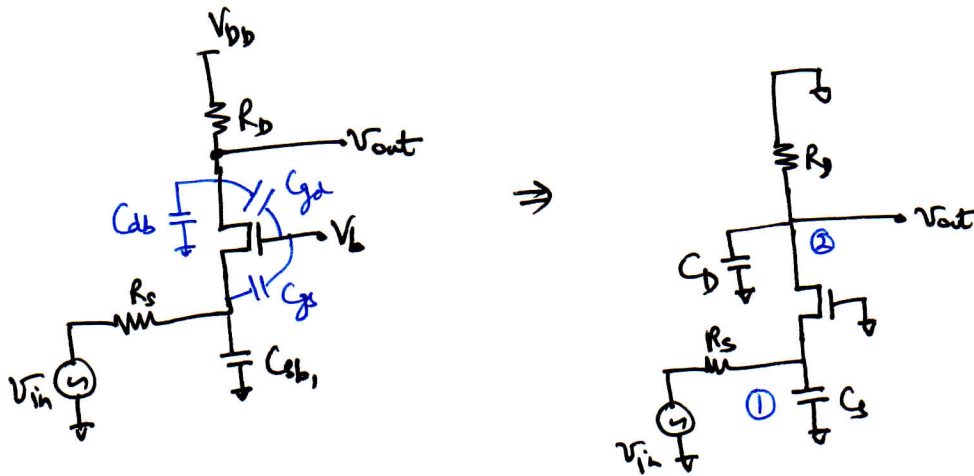(5)

In a CG, input and output nodes are 'isolated' if $\lambda=0$.



@ node ①

$$C_S = C_{GS1} + C_{GB1}$$

+ Since the nodes are isolated $\Rightarrow$ no Miller Cap
 $\Rightarrow$ no zeros in the frequency response


$$\Rightarrow \omega_{p1} = \omega_{in} = \frac{1}{(R_S \parallel \frac{1}{g_m + g_{mb}}) \cdot C_S}$$

@ node ②

$$C_D = C_{GD1} + C_{GB1}$$

$$\Rightarrow \omega_{p2} = \omega_{out} = \frac{1}{R_D C_D}$$
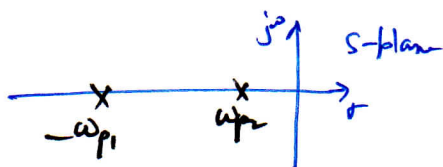
$$\Rightarrow \frac{V_{out}}{V_{in}}(\omega) = \frac{(g_m + g_{mb}) R_D}{1 + (g_m + g_{mb}) R_S} \cdot \frac{1}{(1 + s/\omega_{p1})(1 + s/\omega_{p2})}$$



(6)

⇒ No Miller multiplication of Capacitor

↳ potentially wide-band

↳ low impedance input may load the driving stage

↳ good for current input (i.e. transimpedance) amplifiers


As derived earlier

$$Z_{in} = \frac{Z_L}{(g_m + g_{mb})R_o} + \frac{1}{(g_m + g_{mb})}$$

$$\text{where } Z_L = \left(R_D \parallel \frac{1}{sC_D} \right)$$

Cascode Amplifier Frequency Response:

⑦

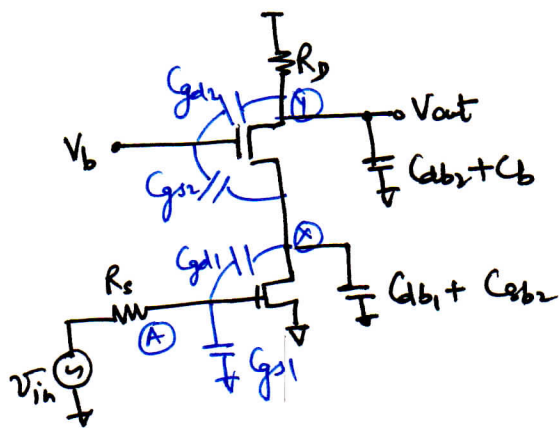

* Miller effect of C_{gd1} is determined by the gain from (A) to (X)

→ Assuming low value of R_D , this gain

$$\text{is } -g_{m1} \times \frac{1}{g_{m1} + g_{m2}} \quad (\text{assuming } \delta \approx 0)$$

$$\approx -\frac{g_{m1}}{g_{m2}} \approx -1$$

* Assume M_1 & M_2 to be identical

→ C_{gd1} is multiplied by 2x, instead of $|A_v|$

→ Miller effect is less significant in cascode amplifiers than in a CS stage. (normal CS)

$$\rightarrow \omega_{pA} = \frac{1}{R_s \left[C_{gs1} + \left(1 + \frac{g_{m1}}{g_{m2} + g_{mb2}} \right) C_{gd1} \right]}$$

* pole due to node (X)


$$C_X = 2C_{gd1} + C_{db1} + C_{cb2} + C_{gs2}$$

$$\rightarrow \omega_{pX} = \frac{g_{m2} + g_{mb2}}{2C_{gd1} + C_{db1} + C_{cb2} + C_{gs2}}$$

* Output pole: $\rightarrow$ third pole

$$\omega_{py} = \frac{1}{R_D (C_{db2} + C_L + C_{gd2})}$$

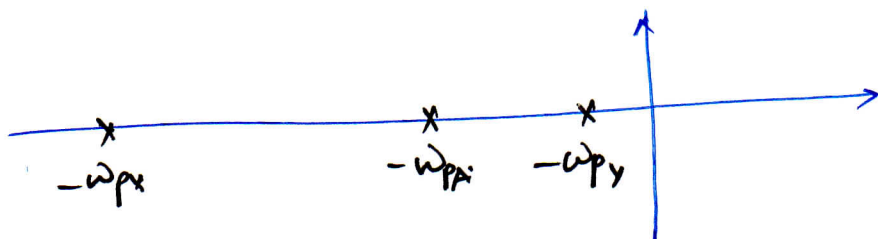* Must choose ω_{px} to be farther away from the other two
 $\hookrightarrow$ important for stability



* What if R_D is replaced by a cascode current source load?
 $\hookrightarrow$ higher DC gain $\rightarrow A_{DC} \propto (g_{m1} r_{on}^2) \parallel (g_{m2} r_{p2})$.

$\Rightarrow$ Impedance at node $\textcircled{x}$ reaches higher value (Derive this) yourself

$\hookrightarrow$ pole at node $\textcircled{x}$ can be quite lower than

$$\frac{(g_{m2} + g_{m2b})}{C_x}$$


$\hookrightarrow$ But in practice this pole doesn't degrade stability much.

$\Rightarrow$ But always be mindful of such scenarios!!

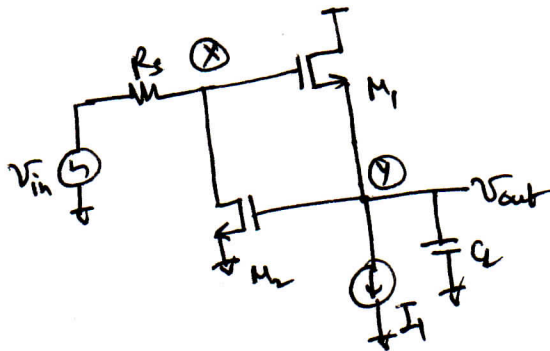Exercise !

⑧


- ① find the transfer function of the circuit (Assume $\lambda \Rightarrow 0, \gamma \Rightarrow 0$)



Ans:
$$\frac{V_{out}(s)}{V_{in}} = \frac{g_{m1} + C_{xy}s}{R_s s^2 + [C_y + g_{m1} R_s C_x + (1 + g_{m2} R_s) C_{xy}]s + g_{m1} (1 + g_{m2} R_s)}$$

$$C_{xy} = C_{gs1} + C_{gd2}$$

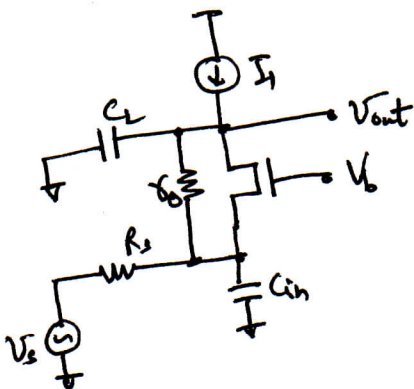- ② find $\frac{V_{out}(s)}{V_{in}}$ & Z_{in} for the circuit ($\lambda \neq 0$)



Ans:
$$\frac{V_{out}(s)}{V_{in}} = \frac{1 + g_{m2} R_s}{(r_o C_L C_{in} s^2 + [r_o C_L + C_{in} R_s + (1 + g_{m2} R_s) C_L R_s]s + 1)}$$

$$Z_{in} = \frac{1}{g_{m1} + g_{m2}} + \frac{1}{s C_L} \frac{1}{(g_{m1} + g_{m2}) r_o}$$